

ham *radio* magazine

**build this
compact
75-meter
monoband
transceiver**



hr

focus
on
communications
technology

stable LO's for microwave receivers • 10-80 meter homebrew receiver • adding digital frequency readouts to transceivers • scanner for CB-to-10 meter conversions • external receiver product detector • build a handy RF probe • plus W6MGI, W1JR, W6SAI, W9JUV, and KØRYW

ICOM HF Receiver

IC-R71A



The World Class World Receiver

ICOM introduces the IC-R71A 100kHz to 30MHz superior-grade general coverage HF receiver with innovative features including keyboard frequency entry and wireless remote control (optional).

This easy-to-use and versatile receiver is ideal for anyone wanting to listen in to worldwide communications. With 32 programmable memory channels, SSB/AM/RTTY/CW/FM (opt.), dual VFO's, scanning, selectable AGC and noise blanker, the IC-R71A's versatility is unmatched by any other commercial grade unit in its price range.



Keyboard Entry. ICOM introduces a unique feature to shortwave receivers...direct keyboard entry for simplified operation. Precise frequencies can be easily selected by pushing the digit keys in sequence of frequency. The frequency will be automatically entered without changing the main tuning control.

Superior Receiver Performance. Passband tuning, wide dynamic range (100dB), a deep IF notch filter, adjustable AGC (Automatic Gain Control) and a noise blanker provide easy-to-adjust clear reception even in the presence of strong interference or high noise levels. A preamplifier allows improved reception of weak signals.

32 Tunable Memories. Thirty-two tunable memories, more than any other general coverage receiver on the market, offer instant recall of your favorite frequencies. Each memory stores frequency, VFO and operating mode, and is

backed by an internal lithium memory battery.

Options. FM, RC-11 wireless remote controller, synthesized voice frequency readout, IC-CK70 DC adapter for 12 volt operation, MB-12 mobile mounting bracket, two CW filters, FL32-500Hz and FL63-250Hz, and high-grade 455kHz crystal filter, FL44A.




 **ICOM**

First in Communications


With SMART PATCH You are in CONTROL

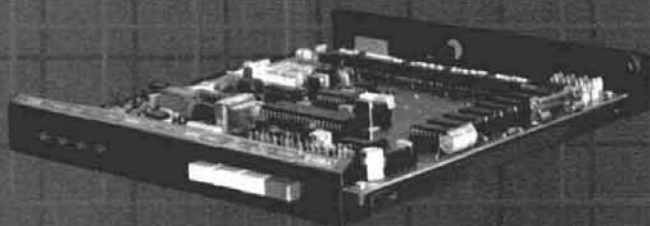With CES 510SA Simplex Autopatch, there's no waiting for VOX circuits to drop. Simply key your transmitter to take control.



SMART PATCH is all you need to turn your base station into a personal autopatch. SMART PATCH uses the only operating system that gives the mobile complete control. Full break-in capability allows the mobile user to actually interrupt the telephone party. SMART PATCH does not interfere with the normal use of your base station. SMART PATCH works well with any FM transceiver and provides switch selectable tone or rotary dialing, toll restrict, programmable control codes, CW ID and much more.

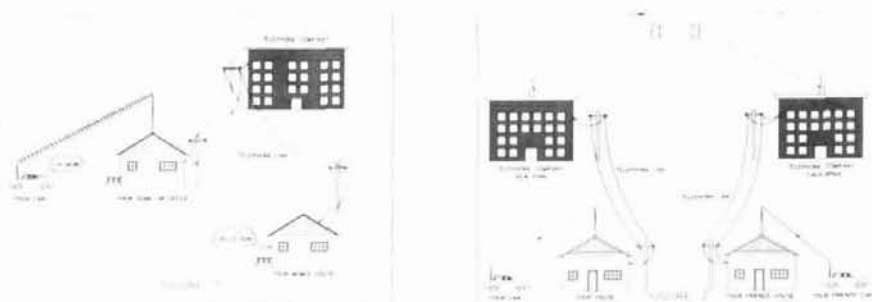**To Take CONTROL with Smart Patch
— Call 800-327-9956 Ext. 101 today.**



Communications Electronics Specialties, Inc.
P.O. Box 2930, Winter Park, Florida 32790
Telephone: (305) 645-0474 Or call toll-free (800)327-9956

How To Use SMART PATCH

Placing a call is simple. Send your access code from your mobile (example: *73). This brings up the Patch and you will hear dial tone transmitted from your base station. Since SMART PATCH is checking about once per second to see if you want to dial, all you have to do is key your transmitter, then dial the phone number. You will now hear the phone ring and someone answer. Since the enhanced control system of SMART PATCH is constantly checking to see if you wish to talk, you need to simply key your transmitter and then talk. That's right, you simply key your transmitter to interrupt the phone line. The base station automatically stops transmitting after you key your mic. SMART PATCH does not require any special tone equipment to control your base station. It samples very high frequency noise present at your receiver's discriminator to determine if a mobile is present. No words or syllables are ever lost.

SMART PATCH Is All You Need To Automatically Patch Your Base Station To Your Phone Line.

Use SMART PATCH for:

- Mobile (or remote base) to phone line via Simplex base. (see fig 1.)
- Mobile to Mobile via interconnected base stations for extended range. (see fig. 2.)
- Telephone line to mobile (or remote base).
- SMART PATCH uses SIMPLEX BASE STATION EQUIPMENT. Use your ordinary base station. SMART PATCH does this without interfering with the normal use of your radio.

WARRANTY?

YES, 180 days of warranty protection. You simply can't go wrong. An FCC type accepted coupler is available for SMART PATCH.

What To Look For In A Phone Patch

The best way to decide what patch is right for you is to first decide what a patch should do. A patch should:

- Give complete control to the mobile, allowing full break in operation.
- Not interfere with the normal operation of your base station. It should not require you to connect and disconnect cables (or flip switches!) every time you wish to use your radio as a normal base station.
- Not depend on volume or squelch settings of your radio. It should work the same regardless of what you do with these controls.
- You should be able to hear your base station speaker with the patch installed. Remember, you have a base station because there are mobiles. ONE OF THEM MIGHT NEED HELP.
- The patch should have standard features at no extra cost. These should include programmable toll restrict (dip switches), tone or rotary dialing, programmable patch and activity timers, and front panel indicators of channel and patch status.

**ONLY SMART PATCH
HAS ALL OF THE
ABOVE.**

Now Mobile Operators Can Enjoy An Affordable Personal Phone Patch. . .

- Without an expensive repeater.
- Using any FM transceiver as a base station.
- The secret is a SIMPLEX autopatch, The SMART PATCH.

SMART PATCH Is Easy To Install

To install SMART PATCH, connect the multicolored computer style ribbon cable to mic audio, receiver discriminator, PTT, and power. A modular phone cord is provided for connection to your phone system. Sound simple? . . . IT IS!

KENWOOD


...pacesetter in Amateur radio

Up Front and Center!

TR-7950/7930

The exceptional front-end selectivity and sensitivity, coupled with Kenwood's excellent audio section, gives you lots to hear! Compact design makes this transceiver at home in the shack or on the go!

- Large, easy-to-read backlit LCD readout. Indicates receive/transmit frequency, frequency offset, sub-tone selection, memory status. An LED readout indicates S & RF units, REVERSE, CENTER TUNING, PRIORITY, and ON AIR.
- Programmable scanning, with center-stop tuning. Microprocessor technology allows you to scan the entire 2 meter band, or just a small portion of it. Scanning stops on the center frequency during band scan—a Kenwood exclusive!

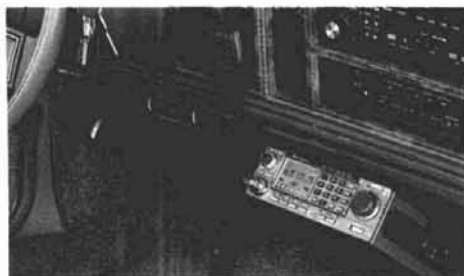

- 21 Multi-function memory channels. The TR-7950/7930 "remembers" frequency offset, and optional subtone channels. Memories 1-15 are for simplex and "normal" repeater operation. Memory pairs 16/17 and 18/19 are for "odd-ball" splits. Memories "A" and "B" store upper and lower band scan limits. The radio "beeps" when memory channel 1 is selected.
- Extended frequency coverage. Covers 142,000-148,995 MHz in 5-kHz steps. Repeater offsets are automatically selected in accordance with the ARRL 2 meter band plan. The front panel "OS" key may be used to allow manual changes in offset.
- Multi-function keyboard. The 16-key DTMF pad can also be used for direct frequency entry, sub-tone selection, memory address and scan programming. The keyboard is illuminated for night time use.



TR-7950 optional accessories:

- TU-79 three frequency tone unit
- PS-430 power supply
- KPS-12 fixed-station power supply for the TR-7950
- KPS-7A fixed-station power supply for the TR-7930
- SP-40 mobile speaker
- SP-50 mobile speaker
- MC-55 mobile microphone
- MC-46 16-key autopatch UP/DOWN microphone
- SWT-1 2 m. 100 W antenna tuner
- SW-100A/B power meters
- PG-3A noise filter

More TR-7950/7930 information is available from authorized Kenwood dealers.

KENWOOD

TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut Street
Compton, California 90220

Model TR-7950 (45 watts) shown. TR-7930 is identical, but with 25 watts output.
Complete service manuals are available for all Trio-Kenwood transceivers and most accessories.
Specifications and prices are subject to change without notice or obligation.

ham radio

magazine

NOVEMBER 1985

volume 18, number 11

T. H. Tenney, Jr., W1NLB
publisher

Rich Rosen, K2RR
editor-in-chief
and associate publisher

Dorothy Rosa, KA1LBO
assistant editor

Joseph J. Schroeder, W9JUV
Alfred Wilson, W6NIF
associate editors
Susan Shorrock
editorial production

editorial review board

Peter Bertini, K1ZJH
Forrest Gehrke, K2BT
Michael Gruchalla, P. E.
Bob Lewis, W2EBS
Mason Logan, K4MT
Ed Wetherhold, W3NQN

publishing staff

J. Craig Clark, Jr., N1ACH
assistant publisher

Rally Dennis, KA1JWF
director of advertising sales

Dorothy Sargent, KA1ZK
advertising production manager

Susan Shorrock
circulation manager

Therese Bourgault
circulation

ham radio magazine is published monthly by
Communications Technology, Inc.
Greenville, New Hampshire 03048-0498
Telephone: 603-878-1441

subscription rates

United States:

one year, \$19.95; two years, \$32.95; three years, \$44.95

Canada and other countries (via surface mail):

one year, \$22.95; two years, \$41.00; three years, \$58.00

Europe, Japan, Africa (via Air Forwarding Service): one year, \$28.00

All subscription orders payable in U.S. funds, via international
postal money order or check drawn on U.S. bank

international subscription agents: page 138

Microfilm copies are available from
University Microfilms, International
Ann Arbor, Michigan 48106
Order publication number 3076

Cassette tapes of selected articles from ham radio
are available to the blind and physically handicapped
from Recorded Periodicals,
919 Walnut Street, Philadelphia, Pennsylvania 19107

Copyright 1985 by Communications Technology, Inc.
Title registered at U.S. Patent Office

Second-class postage paid
at Greenville, New Hampshire 03048-0498
and at additional mailing offices
ISSN 0148-5989

Send change of address to ham radio
Greenville, New Hampshire 03048-0498



contents

- 13 a compact 75-meter
monoband transceiver
Rick Littlefield, K1BQT
- 29 high stability local oscillators
for microwave receivers
and other applications
Cornell Drentea, WB3JZO
- 40 10 through 80-meter
homebrew receiver
Robert Thompson, N1BFV
- 54 VHF/UHF world
Joe Reisert, W1JR
- 67 ham radio techniques
Bill Orr, W6SAI
- 75 practically speaking
Joe Carr, K4IPV
- 83 digital frequency readout
using the Commodore 64
Clifford J. Bader, W3NNL
- 98 a scanner for CB to 10-meter
conversions
Robert K. Baker, W2FMY,
and Gary Bischoff, KB2GA
- 107 external product detector
improves receiver performance
Alan Nusbaum, W6GB
- 115 build a handy RF probe
Keats A. Pullen, Jr., W3QOM
- 140 the Guerri report
Ernie Guerri, W6MGI
- 142 advertisers index
and reader service
- 136 ham mart
129 new products
- 8 comments
6 presstop
- 92 DX forecaster
5 reflections
- 138 flea market

MFJ TUNERS

This may be the world's most popular 3 KW roller inductor tuner because it's small, compact, reliable, matches virtually everything and gives you SWR/Wattmeter, antenna switch, dummy load and balun — all at a great price!

Meet "Versa Tuner V". It has all the features you asked for, including the new smaller size to match new smaller rigs—only 10 3/4" W x 4 1/2" H x 14 7/8" D.

Matches coax, balanced lines, random wires—1.8 to 30 MHz, 3 KW PEP—the power rating you won't outgrow (250pf-6KV caps).

Roller inductor with a 3-digit turns counter plus a spinner knob for precise inductance control to get that SWR down to minimum every time.

Built-in 300 watt, 50 ohm dummy load, built-in 4:1 ferrite balun.



MFJ-989 \$329.95

Accurate meter reads SWR plus forward and reflected power in 2 ranges (200 and 2000 watts). Meter light requires 12 VDC. Optional AC adapter, MFJ-1312 is available for \$9.95.

6 position antenna switch (2 coax lines, through tuner or direct, random/balanced line or dummy load). SO-239 connectors, ceramic feed-throughs, binding post grounds.

Deluxe aluminum low-profile cabinet with sub-chassis for RFI protection, black finish, black front panel with raised letters, tilt bail.

MFJ's Fastest Selling TUNER

MFJ-941D \$99.95



MFJ's fastest selling tuner packs in plenty of new features. New styling! Brushed aluminum front. All metal cabinet. New SWR/Wattmeter! More accurate. Switch selectable 300/30 watt ranges. Read forward/reflected power.

New antenna switch! Front panel mounted. Select 2 coax lines, direct or through tuner, random wire/balanced line or tuner bypass for dummy load.

New airwound inductor! Larger more efficient 12 position airwound inductor gives lower losses and more watts out. Run up to 300 RF power output.

Matches everything from 2.8 to 30 MHz! dipoles, inverted vee, random wires, verticals, mobile whips, beams, balanced and coax lines.

Built-in 4:2 balun for balanced lines. 1000 V capacitor spacing. Black. 11 x 3 x 7 inches. Works with all solid state or tube rigs. Easy to use anywhere.

MFJ's 1.5 KW VERSA TUNER III

MFJ-962 \$229.95



Run up to 1.5 KW PEP and match any feedline continuously from 1.8 to 30 MHz: coax, balanced line or random wire.

Built-in SWR/Wattmeter has 2000 and 200 watt ranges, forward and reflected power. 2% meter movement. 6 position antenna switch handles 2 coax lines (direct or through tuner), wire and balanced lines. 4:1 balun 250 pf 6 KV variable capacitors. 12 position inductors. Ceramic rotary switch. All metal black cabinet and panel gives RFI protection, rigid construction and sleek styling. Flip stand tilts tuner for easy viewing. 5 x 14 x 14 in.

MFJ's Best VERSA TUNER

MFJ-949C \$149.95



MFJ's best 300 watt tuner is now even better! The MFJ-949C all-in-one Deluxe Versa Tuner II gives you a tuner, cross-needle SWR/Wattmeter, dummy load, antenna switch and balun in a new compact cabinet. You get quality conveniences and a clutter-free shack at a super price.

A new cross-needle SWR/Wattmeter gives you SWR, forward and reflected power—all at a single glance. SWR is automatically computed with no controls to set. Has 30 and 300 watt scale on easy-to-read 2 color lighted meter (needs 12 V).

A handsome new black brushed aluminum cabinet matches all the new rigs. Its compact size (10 x 3 x 7 inches) takes only a little room.

You can run full transceiver power output—up to 300 watts RF output—and match coax, balanced lines or random wires from 1.8 thru 30 MHz. Use it to tune out SWR on dipoles, vees, long wires, verticals, whips, beams and quads.

A 300 watt 50 ohm dummy load gives you quick tune ups and a versatile six position antenna switch lets you select 2 coax lines (direct or thru tuner), random wire or balanced line and dummy load.

A large efficient airwound inductor—3 inches in diameter—gives you plenty of matching range and less losses for more watts out. 100 volt tuning capacitors and heavy duty switches gives you safe arc-free operation. A 4:1 balun is built-in to match balanced lines.

Order your convenience package now and enjoy.

2 KW COAX SWITCHES

MFJ-1702 \$19.95



MFJ-1702, \$19.95. 2 positions. 60 dB isolation at 450 MHz. Less than .2 dB loss. SWR below 1:1.2.

MFJ-1701, \$29.95.

6 positions. White markable surface for antenna positions.

\$29.95 MFJ-1701



MFJ's Smallest VERSA TUNER

MFJ-901B \$59.95



MFJ's smallest 200 watt Versa Tuner matches coax, random wires and balanced lines continuously from 1.8 thru 30 MHz. Works with all solid state and tube rigs. Very popular for use between transceiver and final amplifier for proper matching. Efficient airwound inductor gives more watts out. 4:1 balun for balanced lines. 5 x 2 x 6 inches. Rugged black all aluminum cabinet.

MFJ's Random Wire TUNER

MFJ-16010 \$39.95



MFJ's ultra compact 200 watt random wire tuner lets you operate all bands anywhere with any transceiver using a random wire. Great for apartment, motel, camping operation. Tunes 1.8-30 MHz. 2 x 3 x 4 inches.

MFJ's Mobile TUNER

MFJ-945C \$79.95



Designed for mobile operation! Small, compact. Takes just a tiny bit of room in your car. SWR/dual range wattmeter makes tuning fast and easy. Careful placement of controls and meter makes antenna tuning safer while in motion.

Extends your antenna bandwidth so you can operate anywhere in a band with low SWR. No need to go outside and readjust your mobile whip. Low SWR also gives you maximum power out of your solid state rig—runs cooler for longer life.

Handles up to 300 watts PEP RF output. Has efficient airwound inductor, 1000 volt capacitor spacing and rugged aluminum cabinet. 8x2x6 inches. Mobile mounting bracket available for \$5.00.

ORDER ANY PRODUCT FROM MFJ AND TRY IT-NO OBLIGATION. IF NOT SATISFIED, RETURN WITHIN 30 DAYS FOR PROMPT REFUND (less shipping).

• One year unconditional guarantee • Made in USA • Add \$5.00 each shipping/handling • Call or write for free catalog, over 100 products.

MFJ

MFJ ENTERPRISES, INC.
Box 494, Mississippi State, MS 39762

TO ORDER OR FOR YOUR NEAREST DEALER, CALL TOLL-FREE

800-647-1800

Call 601-323-5869 in Miss. and outside continental USA Telex 53-4590 MFJ STKV

VISA
MasterCard

REFLECTIONS

muchas gracias

Yesterday, September 20, a massive earthquake struck Mexico City. Early reports from the networks and wire services told of massive damage in Mexico City, with 25 per cent of the downtown area totally destroyed, and thousands of deaths and injuries. Ships have been reported missing and a tsunami wave has severely damaged part of the Mexican coastline. All modes of communications — save one — are down and authorities have no idea of when service might be restored.

The one mode that's still functioning is Amateur Radio. I've spent quite a while listening to the emergency traffic being passed on a number of frequencies; I'm quite impressed with how effectively and efficiently health and welfare traffic is being passed. But there's a personal sense of urgency to my listening this time: my youngest brother is in Mexico City, and my family and I have no way of knowing if he's all right.

Yes, the State Department has a hotline that we can call for information. But the volume of calls received has shut the system down. We've contacted the Red Cross, but they're too busy passing more important medical traffic.

So how do I — or others — use Amateur Radio to find out about the safety of relatives and friends? I'm afraid I really don't know. I usually have the world at my fingertips with just the flip of a switch and the twist of a dial. But right now I feel just about totally helpless in trying to get the information I want.

Propagation into the Mexico City area isn't favorable at this time, and I'm reluctant to jump into a pile-up and add to the confusion. But that's about the only way I'll be able to get a message to the Mexican stations. . . .

There's got to be a better way! Would somebody please tell me what it is?

Craig Clark, N1ACH
Assistant Publisher

Craig's initial feeling of helplessness is completely understandable. The circumstances — a natural disaster that, within 60 seconds, killed thousands, injured many, and caused catastrophic damage to buildings and other structures — is something one doesn't deal with on a daily basis. So it's hard to pull from your experience and function immediately.

Several things are reasonably certain: all conventional power and most telephone service is gone. Few reliable means of communicating with the outside world are available. This is where Radio Amateurs come in — and what a service they provide! Just after the Mexico City earthquake, several stations were on the air. One in particular that I heard was XE1VIC, manned by Vic and Sergio, who did a yeoman's job in passing health and welfare information, medical emergency traffic, and high-level government phone patches.*

With this in mind, what can *you* do to find out about the safety of a relative or friend known to be in a particular area when disaster strikes?

LISTEN CAREFULLY. If there's any activity from the devastated area, someone as competent as XE1VIC is likely to be on the air. If you don't hear such a station, continue listening. Chances are good that other Amateurs, in your country will have information and be discussing it.

IF YOU DON'T HEAR, ASK. Once again, someone will probably know something.

THINK. For the distances involved, time of day, and propagation, one particular band will be optimum. Try it. XE1VIC was 59+ into New Hampshire on 80 meters for hours.

LISTEN FOR INSTRUCTIONS. The control station will make it very clear as to how he wishes to proceed. Many stations will be attempting to contact him. Though it may seem like contest operation at times, remember that a disaster has occurred, and discipline is essential.

BE BRIEF. Once you've gotten the traffic handler's attention, give the information required — nothing more, nothing less. Decide beforehand how you might be able to help.

ACCEPT THE RESPONSE GIVEN. Once he contacted the requested relative or friend, XE1VIC kept his side of the conversation short and sweet. Most of the time the news was very good, and in every case he was extremely reassuring. Remember that many other stations are concerned about their loved ones, too.

OTHERS WILL HELP PASS YOUR MESSAGE. In this case, stations in the Houston area acted in this capacity.

Every emergency, of course, is different. These are just a few suggestions that have been applied in the past and appear to work.

Rich Rosen, K2RR
Editor-in-Chief

Note: Craig's brother returned home safely on September 23.

*XE1VIC was just one of many Mexican stations that should be commended. In addition, the list of U.S. and international stations that contributed to the success of this traffic handling situation in a calm and controlled manner is long, and one we should be quite proud of — proving once again how Radio Amateurs rise to the occasion and provide a real service.

presstop de W9JUV

AMATEUR RADIO'S RESPONSE FOLLOWING MEXICO CITY'S DISASTROUS EARTHQUAKE was, in short, simply overwhelming! Almost before the first major tremors ended, a number of Mexico City stations were on and handling emergency traffic with the U.S. As the hours wore on and the disaster's magnitude became apparent, the activity multiplied—but even after health and welfare input began, and despite a variety of message handling techniques, turnaround was generally quite fast. W9JUV's first two Friday afternoon inquiries came back "We're all OK!" from XELUSA in under five minutes! Amateur Radio's media exposure was also fantastic due to the complete breakdown in commercial communications, which left the Amateur Service as the media's only source of earthquake news for a number of hours.

Media Abuse Of Amateur Radio Was Also Extensive, unfortunately. Not only was there the usual "XE1XX, I have Newt Newshawk of NNUT-TV in the shack to ask you some questions," but all of the networks and news services invaded the Amateur bands for their coordination and logistical efforts! Heard on 20 meters Sunday were equipment requests, personnel assignments, even arguments about overtime and the special menu needs of a network anchor! To its credit, NBC's Mexico City station did take health and welfare traffic and made phone calls when not otherwise occupied; inquiries to the others triggered responses that they were too busy on network business to make casual contacts! The FCC is very much interested in this media incursion, and would appreciate receiving specific reports and tapes on it.

One Glaring Weakness Of Amateur Radio Was Quickly Apparent—anxious friends and relatives of persons living in or visiting Mexico City had no idea of how to locate hams willing to relay messages. Though churches, community centers, the Red Cross, and even some Amateur Radio dealers were often able to make referrals, what's badly needed—before another such catastrophe strikes—is a well advertised, accessible conduit through which the public can reach Amateur Radio operators able to communicate with loved ones abroad.

Despite Such Problems, However, Amateur Radio Has Never Served People Better or made a deeper, more favorable impression on the public than it has during Mexico City's agony. "Well done!" to all involved, both those actively participating and the many "stand-bys."

STATE AND LOCAL REGULATIONS MAY NOT PRECLUDE AMATEUR COMMUNICATIONS, the FCC declared in its September 16 decision on PRB-1! Responding to the ARRL's July, 1984, request for a Declaratory Ruling limiting local limitations on Amateur operations and stations, the FCC affirmed "a strong federal interest in promoting Amateur communications" and cited Amateur Radio's value in "providing emergency communications" and "a reservoir of trained operators, technicians and electronic experts," as well as furthering international goodwill. In summary, they said: "State and local regulations that operate to preclude Amateur communications in their communities are in direct conflict with federal objectives and must be preempted."

Though They Did Not Specify Any Minimum Antenna Height, the Commission further stated, "...local regulations which involve placement, screening, or height of antennas based on health, safety, or aesthetic considerations...must be crafted to accommodate reasonably Amateur communications (with) minimum practicable regulation..."

Though The Lack Of A Specified Height Will Cause Some Amateurs Problems, the FCC's action is certainly going to help the vast majority. Also not covered are Amateurs who've signed restrictive covenants, since those are private contracts entered into voluntarily.

Congratulations To The Commissioners And FCC Staff for a courageous decision, since their favorable ruling for Amateur antennas and operations will undoubtedly be cited by other services who'd also like to get out from under the yoke of local regulation.

POSSIBLE FEDERAL SANCTIONS AGAINST "ELECTRONIC EAVESDROPPING" are close to being introduced in the U.S. House of Representatives by Rep. Kastenmeyer. In his "Electronic Communications Privacy Act of 1985," Rep. Kastenmeyer proposes restricting the monitoring of any transmission by "wire, radio, electromagnetic, or photoelectric system..." with exceptions for communications "readily accessible to the public," stations for general public use, distress signals, police or fire, and Amateur or CB stations. Penalties for commercial violators could be \$25,000 and a year in prison, others \$5,000 and six months.

Though The Goal Is Almost Surely The Protection Of Cellular Radio, the effect on Amateurs and others with a general interest in radio communications could be serious.

APPLICANTS WHO FLUNK AN AMATEUR EXAM NEEDN'T WAIT 30 DAYS to retake the exam, the FCC decided September 16. In its decision to eliminate the waiting period entirely, the Commission agreed a delay had little benefit and dropping it could permit applicants who failed the first day of a two-day hamfest to review problem areas for a second-day try.

DPØSL WILL BE THE CALLSIGN FOR THE UPCOMING EUROPEAN STAFFED SPACEFLIGHT, now set for launch about October 30th on Space Shuttle Flight 61-A. They will listen on 437.125, 437.175, 437.225, 437.275, 437.325, and 437.375 MHz; transmit on 145.450, 145.475, 145.550, or 145.575 MHz. 145.575 down, 437.275 MHz up will be the normal pair.

Rumors Of 10 Or 15-Meter Operation Still Persist at presstime; an operating schedule for DPØSL has not yet been released.

You may not be able to solve the world's problems. But at least you can listen.



The Panasonic Command Series™. With double superheterodyne tuning, you'll hear the world loud and clear.

Now it's easy to listen in on the world's hot spots. With the Panasonic RF-B600 Command Series FM/LW/MW/SW receiver.

Its advanced microcomputer-controlled tuner lets you preset up to nine different frequencies. And reach them at the touch of a button. Or, press the appropriate buttons and tune in any desired frequency with direct-access digital tuning. It'll lock right in to every signal with a PLL quartz-synthesized tuner. Once tuned in, the Panasonic double superheterodyne system helps deliver a clean, consistent signal.

There's even built-in auto-tuning to let you scan the shortwave band automatically, as well as manually. All this means you can tune in Berlin, pick up Paris, or locate London in an instant. Without dialing all over the band.

Both the RF-B600 and the RF-B300 are packed with features and built to go anywhere.

The Panasonic Command Series offers something for everyone. With equipment sophisticated enough to impress the most avid enthusiast, and automatic features that get you where you want to be. Fast.

There's a whole world out there that's waiting to be heard. Tune in to it with the Panasonic Command Series.



Batteries not included.



comments practically speaking

Dear HR:

Joe Carr, K4IPV, is off to a fair start with his new column, "Practically Speaking." The first (September, page 67) was good reading. I have to disagree with him, however, when he says, "The first time to think about repairs is while you're unpacking the new rig."

Wrong.

The first time to think about repairs is *before* the rig is bought. The unpacking stage is too late.

Before plunking down several kilobucks for one of the so-called state-of-the-art transceivers being marketed these days, ham operators need to give serious, careful thought to the crucial question of servicing and maintaining the rig(s) under consideration. Is that aspect of ownership going to cost an arm, a leg and another part of the anatomy — to say nothing of the time spent without the rig while it is being repaired?

Are all those gongs, whistles, and bells *really* worth it? Does one truly need rigs that scan, memorize, and do all sorts of other gimmicks?

Two years ago two friends here returned from a national Amateur Radio convention, each with a new rig. One, who purchased the latest offering from Brand X had to return the rig to the factory once while it was still under warranty and twice since then. He is no slouch at troubleshooting or repair, but the complicated circuitry was more than he could handle. Labor, parts, and shipping charges thus far have totaled more than one-third the original cost of the transceiver, and he has been without it almost 60 days altogether.

My second friend brought home a shiny, new Brand Z transceiver. It was

almost a pure vanilla rig with no gong, whistles, or bells. It has sat in his shack and has worked, day in and day out. What few repairs have been needed were done quickly, easily and inexpensively. He said he decided on that rig because of the ease and simplicity of operation.

Practically speaking, which do you think was the more practical?

Fred Conavita, W5QJM
Austin, Texas

audio filter design

Dear HR:

Instead of transforming the normalized values of a five-branch Butterworth low-pass prototype design to get a five-branch high-pass as discussed in Stefan Niewiadomski's article, "Passive Audio Filter Design," part 2, October, 1985, a simpler procedure would be to use standard-value capacitor (SVC) filter tables to select an appropriate design. The fact that the SVC capacitor design values are exactly identical to the commercially available standard values simplifies construction. For example, a "near-Butterworth" 500-ohm design with a VSWR of 1.023 and a 3-dB cutoff frequency of 487 Hz (within 3 percent of the desired 500 Hz cutoff frequency) is available with standard values of $C_{1,5} = 0.82 \mu\text{F}$ and $C_3 = 0.33 \mu\text{F}$. $L_{2,4} = 96.2 \text{ mH}$. The 20-dB and 40-dB attenuation frequencies are 330 and 214 Hz. Some SVC filter tables appear in *The ARRL 1985 Handbook*, (pages 2-40 through 2-44) and a more complete selection will appear in the next edition of the *Radio Handbook*, edited by Bill Orr, and to be published soon by Howard W. Sams and Co., Inc. The SVC filter tables were also published in the record of the IEEE 1985 International Symposium on Electromagnetic Compatibility held in Wakefield, Massachusetts from August 20-22. *ham radio* readers should therefore understand that the preferred procedure for designing simple passive LC filters, such as generally required by the Radio Amateur, is to use SVC filter tables. The procedure explained by Niewiadomski should be used only when there is a special requirement for

a specific response type and a precise cutoff frequency.

Ed Wetherhold, W3NQN
Annapolis, Maryland

J-pole or Zepp?

Dear HR:

K1WWT is right, (see "J-pole or Zepp," Comments, *ham radio*, February, 1985, page 8). The J-pole antenna described in KD8JB's earlier *ham radio* article* is a Zepp antenna.

The Zepp antenna, named for the Zeppelin airship, on which it was originally used, is not a 3/4-wave antenna operating against a 1/4-wave counterpoise as KD8JB mentioned in the reply comments.

The classical Zepp antenna, now more than 75 years old, is a full-wave current-fed antenna with a 1/4-wave section folded over on itself. This leads to a 1/2-wave end-fed radiator with 1/4-wave matching transformer. The antenna at first was a balloon antenna

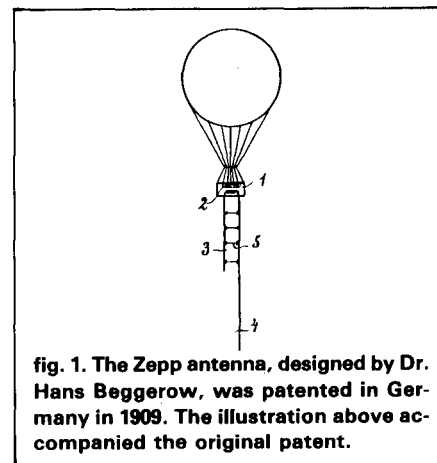


fig. 1. The Zepp antenna, designed by Dr. Hans Beggerow, was patented in Germany in 1909. The illustration above accompanied the original patent.

(fig. 1) and looked like an inverted J-pole dangling from the airship. In the beginning the matching transformer and the radiator hung in a straight line. Later on the matching transformer was set at right angles to the radiator. This low-voltage input feed arrangement was a remarkable improvement over the dangerous practice of using a high-voltage feed in the presence of the oxyhydrogen-gas with which the balloons were filled.

Alois Krischke, DJØTR/OE8AK
Munich, West Germany

*See "All-metal, 2-meter J-pole Antenna," *ham radio*, July, 1984, page 42.

L U X O R 9 9 0 0

THE
INTELLIGENT
SATELLITE
TELEVISION
SYSTEM

THE LUXOR 9900 KNOWS

Where all the satellites are

Up to 36 satellite locations can be programmed for instant recall. The antenna controller is integrated into the satellite receiver. The hand-held remote control activates a 3-speed actuator action which precisely locates the satellite and fine tunes the antenna position for maximum signal reception.

Where all the channels are

Every channel on every satellite is individually factory programmed prior to delivery. All audio and video information is ready for recall automatically. As new channels are added they can be added to the program. The 9900 is ready to receive individual channel selection information for up to 864 separate selections.

All about stereo Hi-Fi sound

5 audio modes, factory programmed to individual transponders, deliver the right sound system automatically when a channel is selected. Dozens of audio subcarriers can be added to the program for audio only hi-fi enjoyment (including Dolby® Noise Reduction) in addition to television.

**ALL YOU NEED TO KNOW IS
WHAT SHOW YOU WANT TO WATCH**

NOW LUXOR HAS UNIFIED SATELLITE, VIDEO, AUDIO AND COMPUTER TECHNOLOGY IN A SINGLE INTEGRATED HOME SATELLITE TV SYSTEM


So advanced it's as easy to operate as an ordinary TV



The front panel LED display tells you what satellite you're on, what channel you're watching, what sound system you're receiving and a signal bar graph indicates signal strength. All functions are controlled from the hand-held wireless remote.


The sky is alive with the sound of music

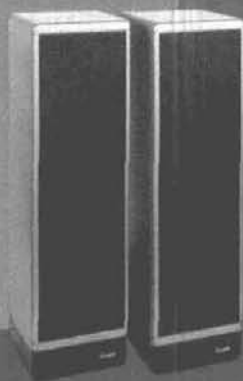Luxor loudspeakers bring new life to TV audio, mono or stereo, and much more. Satellite audio sub-carriers broadcast a wide range of music for audio only. These optional high quality 6-speaker sets (3 per side) are available in passive or active models with sound power up to 40 W per channel. They are specially magnetic shielded for close location to your TV set.



Here is the best of Scandinavian design and high technology. Because Luxor is a leading European manufacturer of satellite products, TV's, audio hi-fi systems, and computers, the company is able to combine these technologies in the advanced 9900 series. After all, Luxor has been a leader in radio, television and electronic technology since 1923.

Simple, clear and color-coded

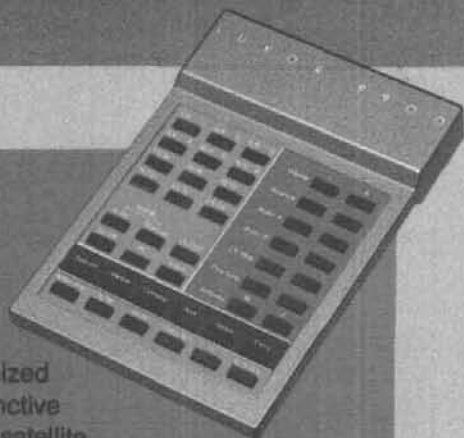

The Luxor hand-held remote is clearly organized to make life easy. Distinctive color sections present satellite and channel selection functions, tuning functions and switching functions. For most viewing however, video and audio delivery will be automatic. When a channel is selected, the exclusive Luxor Micro-Step™ Tuning System (LMS) automatically seeks out the right signal within that channel's frequency. The receiver automatically compensates for any form of frequency drift due to climate or transponder variances.

An internal TI filter can be assigned to individual channels to minimize terrestrial interference.

And a discrete parental lock-out can eliminate one or more individual channels on a single satellite, as desired.

That's it. Advanced Luxor technology has produced a system so simple to operate, yet complete enough to satisfy the most fanatic videophile and audiophile. For the technician, the Luxor 9900 even has its own diagnostic system built-in and ready at the touch of a button.

The perfect companion



The Luxor Model 9995 Block Satellite Receiver is designed and built to function as an add-on receiver to Luxor 9900 multiple TV's installations. This low cost manually operated receiver offers independent channel selection for TV's located throughout the house. The 9995 can also be used as a stand-alone receiver for both C-Band and Ku-Band reception.

LUXOR HAS ADVANCED THE STATE-OF-THE-ART TO THE POINT OF ELEGANT SIMPLICITY FOR THE CONSUMER AND THE TECHNICIAN

Each electronic innovation is incorporated to aid ease of operation, assure high performance reliability, and maintain outstanding quality of both picture and sound.



9900 Block Receiver

Control Functions

- + Integrated satellite receiver and antenna controller.
- C-band (4 GHz) and Ku-band (12 GHz) capable. Remote control switchable.
- Satellite direct access.
- Transponder direct access.
- + Built-in A/B switch.
- + "Normal" button return to factory pre-set values.
- Built-in polarotor drive.
- Built-in RF modulator.
- Non-volatile memory unaffected by power outages.
- Remote sensor interface.

Programs

- + Factory programmed for individual transponders on each satellite.
- + Automatic correct audio system factory programmed for each satellite and each transponder.
- + Program capacity up to 864 individual selections, audio video matched and fine tuned.
- + Self-diagnostic microprocessor.
- + LED display of satellite, channel, audio system and signal strength

Video Functions

- + Luxor Micro-Step™ tuning system (LMS).
- Baseband audio and video output for VCR or monitor.
- Baseband input for other video sources.
- Built-in polarity control.
- + Built-in programmable TI filter.
- Raw video (unfiltered, unclamped) for descrambler connection.


Audio Functions

- + Audio subcarrier frequency read-out.
- Wide/Narrow Bandwidth selection.
- + Remote audio volume control.
- + Remote stereo balance control.
- + Remote Dolby® on/off
- + 5 audio modes—2 mono, 2 matrix, and discrete stereo. Automatic multiplex selection.
- Built-in stereo processor.
- + Direct loudspeaker drive.



9902 Remote Sensor

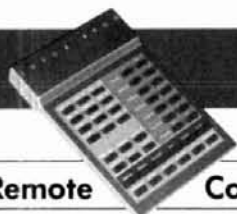- Controls satellite system from any room.
- Low-cost add-on for other TVs.
- Comes complete with hand-held IR remote control.



9901 Remote Control

- + Full-function, color-coded IR wireless remote control.
- + Remote ON/OFF
- + Discrete parental lock-out for individual channels.
- + Remote mute.
- + Volume control.
- + Stereo balance.
- Channel UP/Down.
- + Video fine tune.
- + Audio fine tune
- Antenna fine tune.
- Satellite selection.
- Channel selection.
- + Divided into 4 easy-to-read segments: Satellite selection, channel selection, tuning functions, switching functions.



9904 Actuator Interface

- + 36V power supply to antenna drive.
- + Surge protected.
- + Voltage spikes protected.
- + Design coordinated with 9900.
- + Can be wall-mounted out of sight.



9906/9907 Stereo Loudspeakers

- + Passive or active models.
- + Up to 40 W per channel.
- + 3 elements per side; tweeter, mid-range and woofer.
- + Magnetic shielded.
- + Automatic ON/OFF.
- + LED indicators; standby and active.
- + Complete with line cable feed.



9995 Block Satellite Receiver

- + Add-on "slave" to 9900 multiple TV's installations.
- + Can function as a stand-alone block receiver; C-band and Ku-band reception.
- + Manually operated channel selection.
- + Video fine tune. AFC defeat.
- + Built-in V/H switch.
- + Built-in antenna switch for satellite or local reception.
- + Preprogrammed audio frequencies 6.2 and 6.8 MHz.
- + Audio frequency selection 5.0 to 8.0 MHz.
- + Wide/narrow audio bandwidth selection.
- + Raw video output (unclamped, unfiltered) for descrambler connection.
- + External TI filter input.
- + Skew control.
- + Polarotor One control output.
- + Denotes new features available only on 9900 series products.



Luxor High-Performance Microwave Block Downconverters

Designed and constructed for continuous reliable performance, each Luxor unit is individually inspected and tested against all specification requirements. The Block Downconverter (30 dB gain min.) is used in conjunction with an LNA. The LNB Block Downconverter (60 dB gain min.) is an LNA and a Block Downconverter in one compact package. Each unit is weather-tight, rust-proof and fully warranted.

Luxor Sales And Technical Services
Throughout America

1-(800)245-9995

Canada: Evolution Technology (416) 335 4422
Mexico: Klan SA 52 83 789 015

LUXOR®

Luxor (North America) Corp.
600 108th Ave. N.E., Bellevue, WA 98004



a compact 75-meter monoband transceiver

Modular design
yields 30 watts PEP
and high performance

This article describes a compact monoband SSB transceiver that employs broadband techniques, IC building blocks, and an FET power chain. A detailed block diagram that shows all module interconnections is shown in **fig. 1**. As an extension of an earlier receiver project, the design provides all of the basic features required for convenient operation.¹ The receiver section offers excellent sensitivity and selectivity, audio-derived AGC, an S-meter, headphone or speaker operation, and above-average audio quality. The transmitter has amplified ALC and delivers 30 watts PEP to a 50-ohm load. The completed package is about the size of a 2-meter FM transceiver, measuring 2 × 5 × 6 inches (5 × 12.7 × 15.25 cm) and weighing about 2 pounds (1 kg).

circuit description


The transceiver employs a single conversion frequency plan with a 9-MHz IF and a 5.0-MHz VFO. Receiver preselection is provided by a two-section bandpass filter (see **fig. 2**). Additional HF rejection is obtained from the transmitter's low-pass filter. Receiver mixer U1 is an active DBM which has been biased for maximum gain. Mixer output is fed to crystal sideband filter FL1 through a simple diode switching network.

IF stage U2, shared by the transmitter, provides 45 dB of gain with an AGC range of about 70 dB. Gain for the entire receiver is controlled via U2's AGC line. Automatic control is audio-derived from the output of audio amplifier U4. Manual control is provided by a

voltage divider circuit. During the receive cycle, the two control voltages are gated onto the AGC line through diodes. The output of IF amplifier U2 is simultaneously fed to product detector U3 and transmit mixer U7. U3, an active DBM product detector, provides audio detection and additional system gain.


Since gain is controlled exclusively through IF amplifier U2, audio amplifier U4 operates at full gain (see **fig. 3**). U4 provides 400 mW of output — more than enough to drive the transceiver's small built-in speaker. Attenuation is provided for speaker protection and for headphone operation.

AGC voltage is sampled from the output of U4, detected, and fed to DC amplifier Q1. The RC time constant of Q1 is switched to provide slow release time during receive, and fast release time during transmit. Q2 provides additional amplification of the control signal, sets the AGC threshold for U2, and drives meter M1. M1 functions as an S-meter during receive and as an ALC indicator during transmit. The entire receiver section operates from a 12-volt source with an average current drain of only 50 mA on receive.

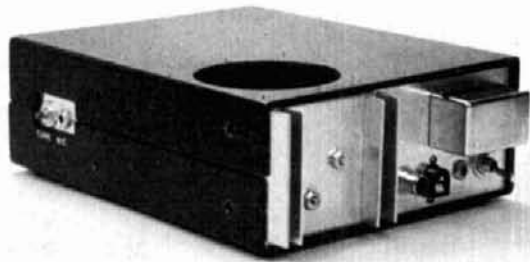

A small heatsink is sufficient for intermittent SSB operation, but area should be increased for CW operation. Mounting FL1 on rear panel saves internal space.




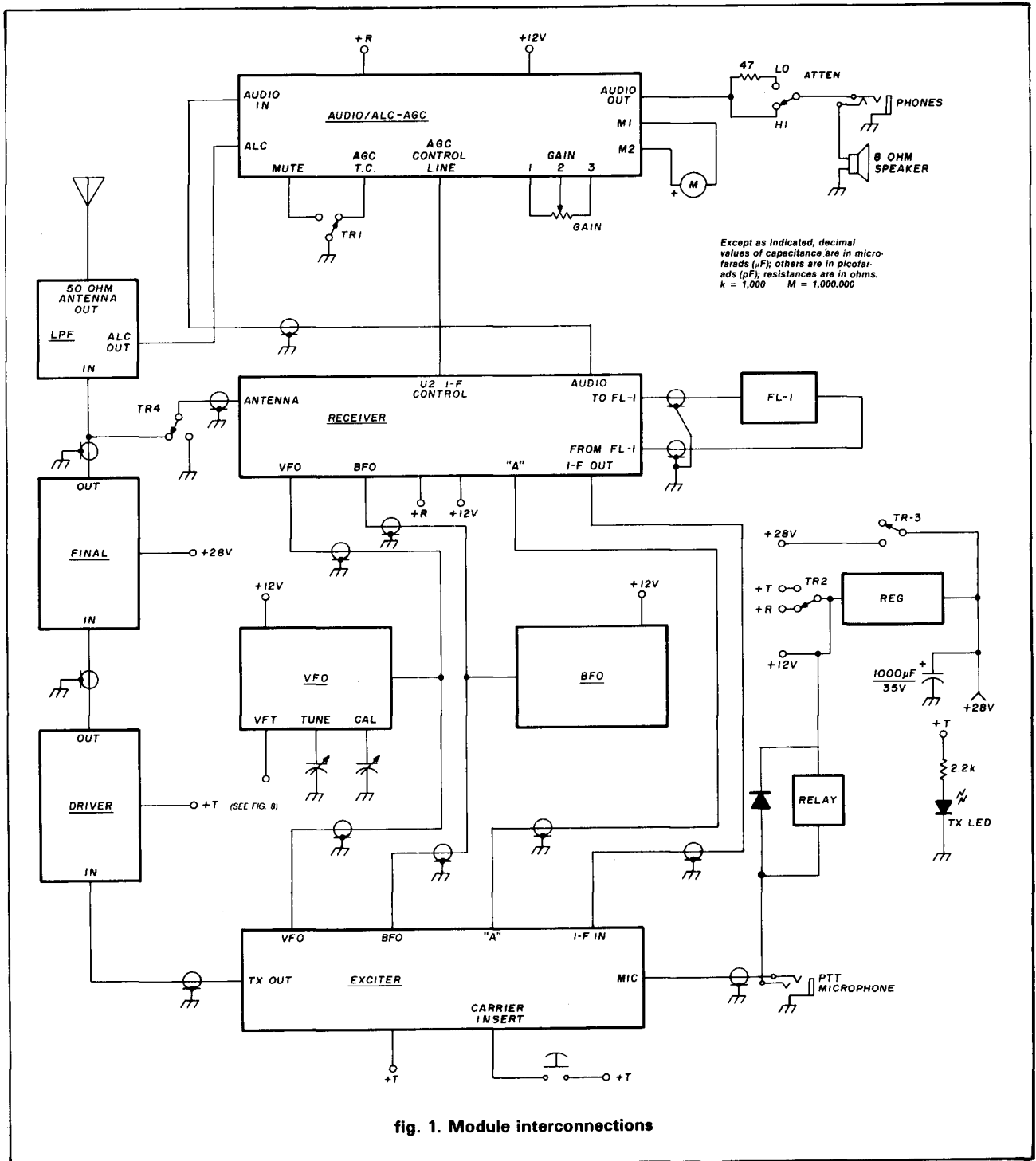
By Rick Littlefield, K1BQT, Box 114 Barrington, New Hampshire 03825



Low-Z microphone amplifier U5 is a standard op-amp circuit which develops the necessary audio voltage to drive balanced modulator U6 (see fig. 4). Like all other mixing devices in the transceiver, U6 is an active DBM. Provisions are made to unbalance the device when carrier is needed for RF chain or antenna tuner adjustment. The output of U6 is fed through a diode switching network to sideband filter FL1 and

IF amplifier U2. As noted earlier, ALC voltage is applied to U2 during transmit to maintain high transmitter output without driving the RF chain into saturation.

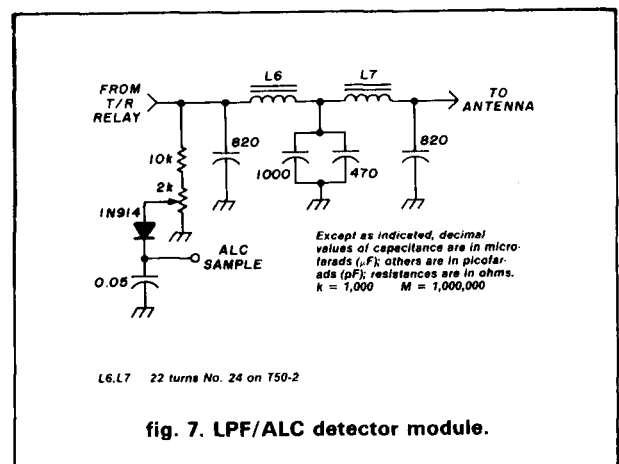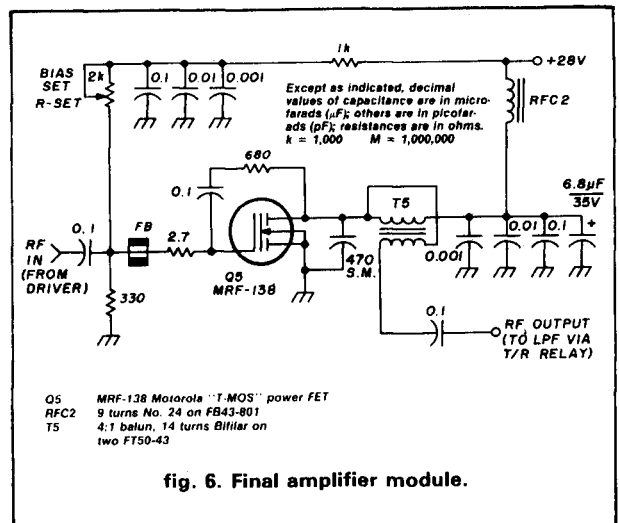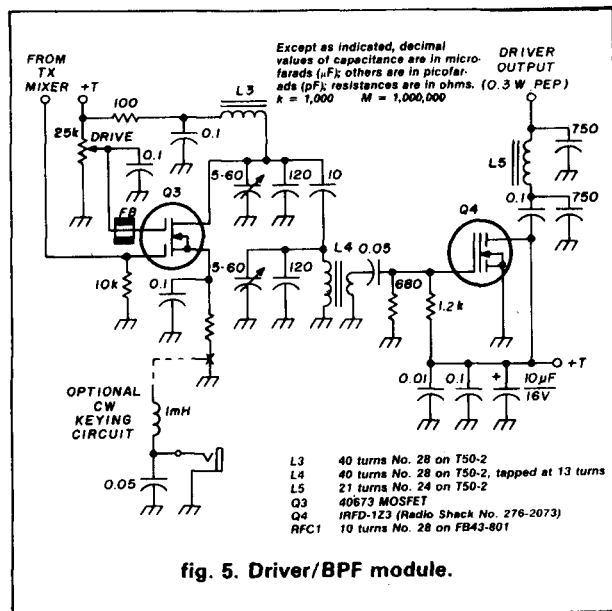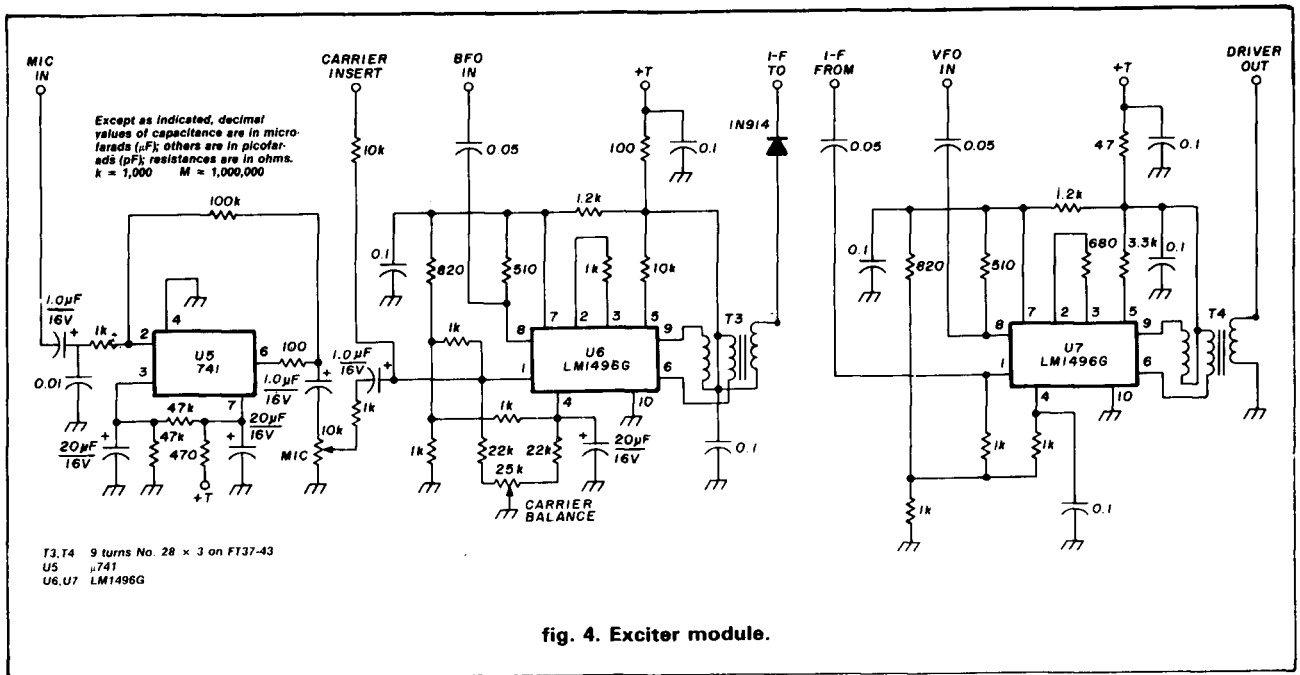Transmit mixer U7 combines the IF signal from U2 with VFO drive to produce 75 meter output (a CW-only design would substitute BFO drive for the IF signal). The output of U7 is buffered and amplified by



than 100 mV of injection. Consequently, drive demands on the VFO and BFO are minimal. VFO Q6 is a popular Hartley JFET circuit which is buffered by source follower Q7 (see fig. 8). An optional VFT control aids fine tuning. BFO Q8 is a simple unbuffered crystal oscillator (see fig. 9). If the transceiver is modified for 20 or 15-meter operation, the BFO output should be carefully matched to its load and filtered for harmonic content.

The PA is the only stage requiring a 28-volt source. An on-board monolithic voltage regulator reduces supply voltage to the other stages. The compact 28-volt

ICOM 25-1300MHz Plus!

IC-R7000



ICOM's commercial quality scanning receiver...Top quality at a gem of a price.

ICOM introduces the IC-R7000 advanced technology 25-2000MHz* continuous coverage communications receiver. With 99 owner programmable memories, the IC-R7000 covers low band, aircraft, marine, business, FM broadcast, amateur radio, emergency services, government and television bands.

Keyboard Entry. For simplified operation and quick

tuning, the IC-R7000 features direct keyboard entry. Precise frequencies can be selected by pushing the digit keys in sequence of the frequency or by turning the main tuning knob.

99 Memories. The IC-R7000 has 99 memories available to store your favorite frequencies, including the operating mode. Memory channels may be called up by simply pressing the Memory switch, then rotating the memory channel knob, or by direct keyboard entry.

Scanning. A sophisticated scanning system provides instant access to most used frequencies. By depressing the Auto-M switch, the

IC-R7000 automatically memorizes frequencies in use while the unit is in the scan mode. This allows you to recall frequencies that were in use.

Other Outstanding Features:

- FM wide/FM narrow/AM/upper and lower SSB modes
- Six tuning speeds: 0.1, 1.0, 5, 10, 12.5 or 25KHz
- Dual color fluorescent display with memory channel readout and dimmer switch
- Compact Size: 4-3/8"H x 11 1/4"W x 10 7/8"D
- Dial lock, noise blanker, combined S-meter and center meter

- Optional RC-12 infrared remote controller
- Optional voice synthesizer. When recording, the voice synthesizer automatically announces the scanned signal frequency.

*Specifications guaranteed from 25-1300MHz. No additional module required for coverage to approximately 2.0GHz.

See the IC-R7000 receiver at your local authorized ICOM dealer. Also available is the IC-R71A 0.1-30MHz general coverage receiver.

ALL THIS AT A PRICE YOU'LL APPRECIATE.



First in Communications


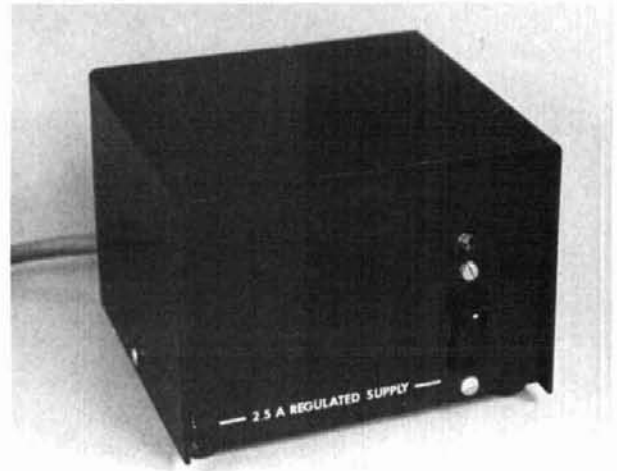
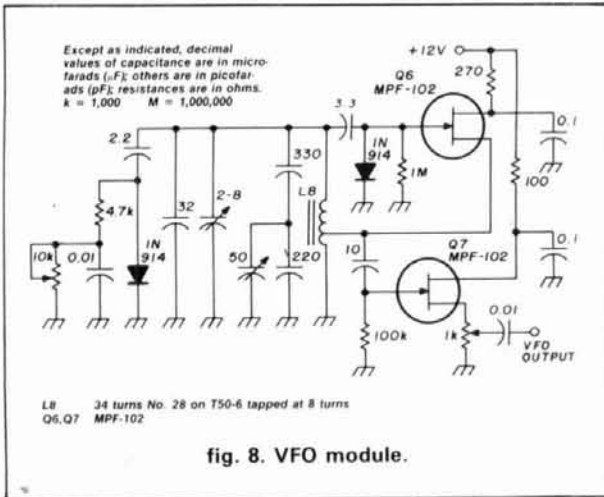
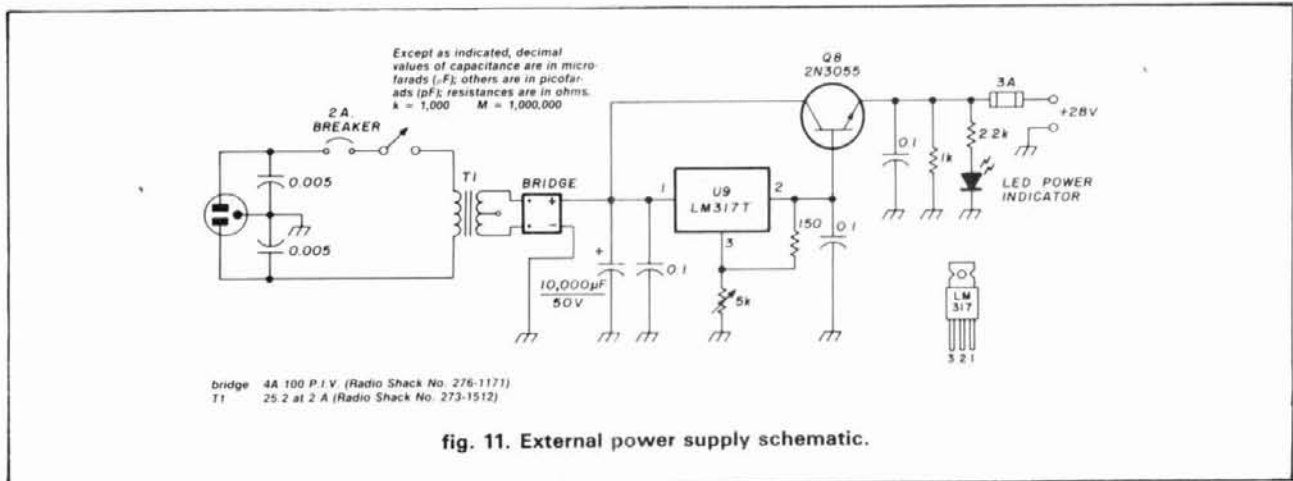
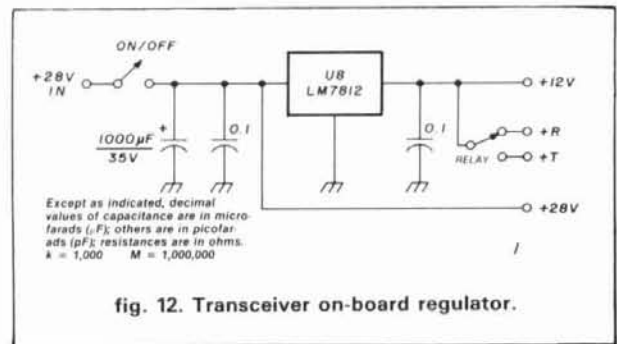


fig. 10. The transceiver's compact power supply measures only $4 \times 3 \times 3$ inches ($10 \times 7.6 \times 7.6$ cm). The design is simple, and can be built entirely from off-the-shelf Radio Shack components.

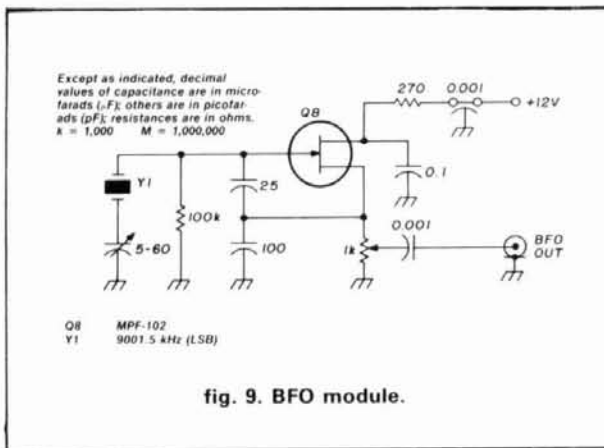

external power supply and schematic shown in figs. 10 and 11, respectively, was built from off-the-shelf Radio Shack components. The output of transformer T1 is bridge rectified, filtered, and regulated by pass transistor Q1. Adjustable regulator U1 drives the base of Q1 to set output voltage and to provide additional

electronic filtering. An on-board regulator is also incorporated in the transceiver (fig. 12).

construction

The boards for this project were laid out in modular strips to facilitate modification during the design pro-

L1 38 turns No. 28 on T50-2, 3 turn link
 L2 28 turns No. 28 on T50-2, tap at 18
 T1 No. 28 x 3 on FT37-43
 T2 10.7 MHz 10 mm IF transformer
 U1,U3 LM1496G
 U2 MC1350P


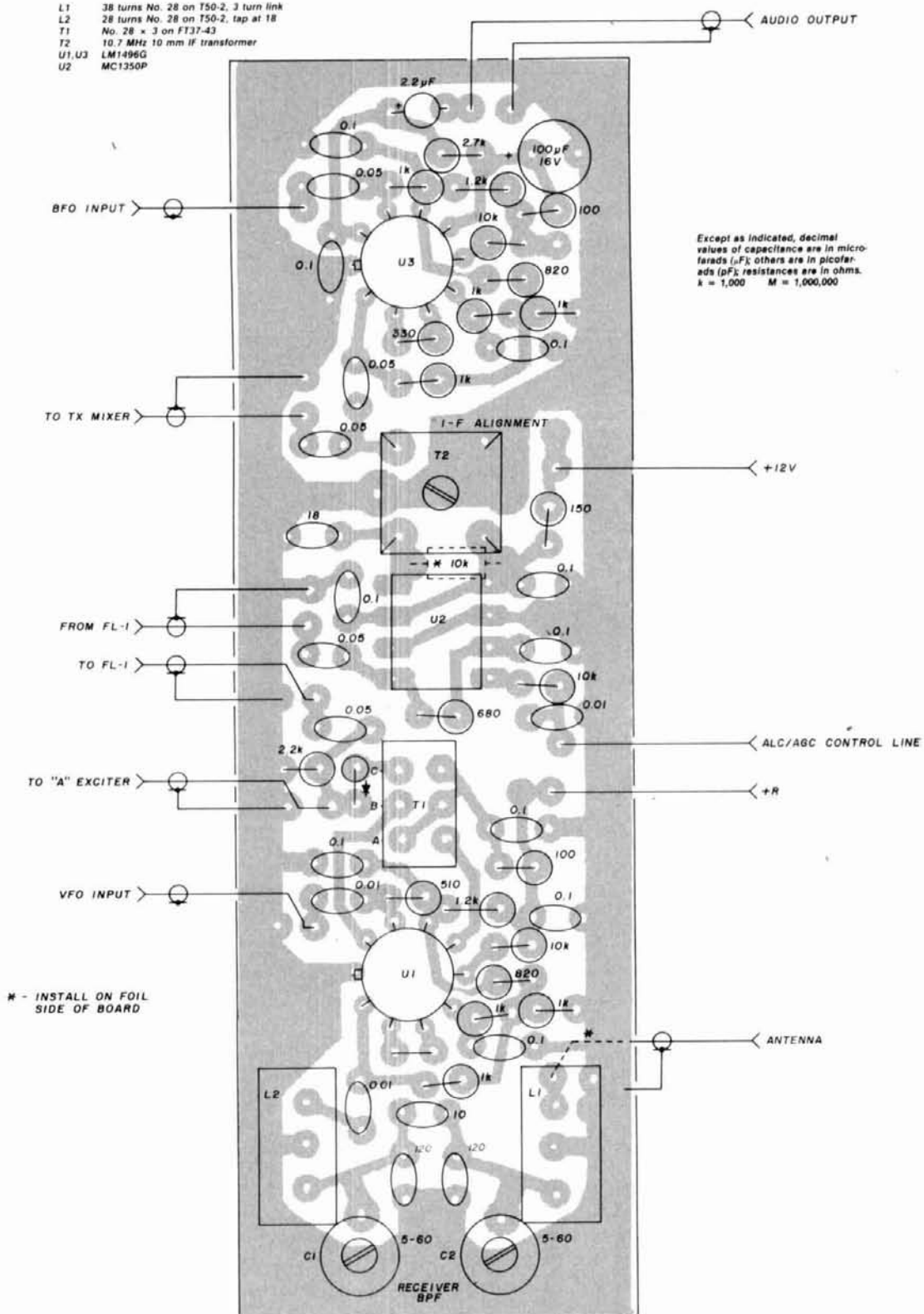
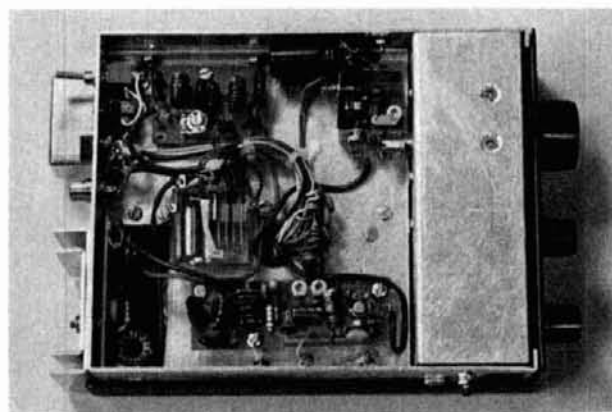


fig. 13. Receiver module.

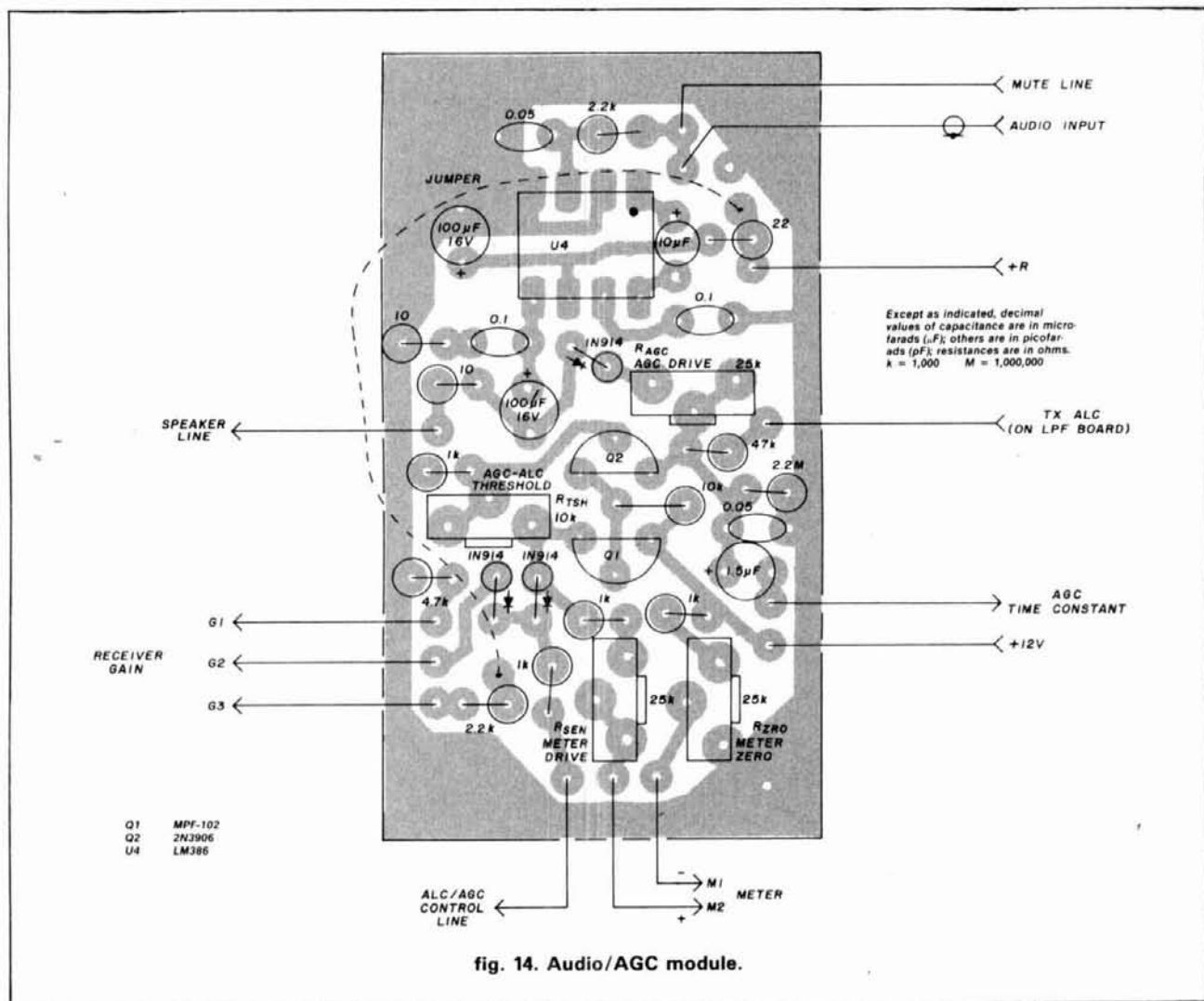

Bottom view shows BFO, driver, and low-pass filter modules. Voltage regulator is mounted on the side of the case. A 4PDT relay for T-R switching simplifies circuit design and reduces receiver power consumption.

cess. To make the job of interstage wiring easier, the exciter and receiver strips were later joined together.*

Figures 13 (receiver module), 14 (audio/AGC module), 15 (exciter module), 16 (driver/bandpass filter), 17 (MRF-138 final amplifier module), 18 (low-pass filter board), 19 (VFO module), and fig. 20 (BFO module) show the printed circuit board patterns and component layouts.

Board assembly is routine, but a few specific points deserve mention. The boards were designed around miniature parts. Substituting 1/2-watt resistors, high-voltage capacitors, and other large components can quickly result in overcrowding. Since the parts density is quite high, double-checking parts placement against the schematic or a layout is also recommended.

Use care when winding toroidal transformers and chokes. Most FT (ferrite) cores have rough edges that can easily abrade the insulation from enamel covered

*A complete kit containing all parts, etched pre-drilled circuit boards, punched, painted enclosure, and assembly manual is available from Radiokit, Box 411, Greenville, NH 03048

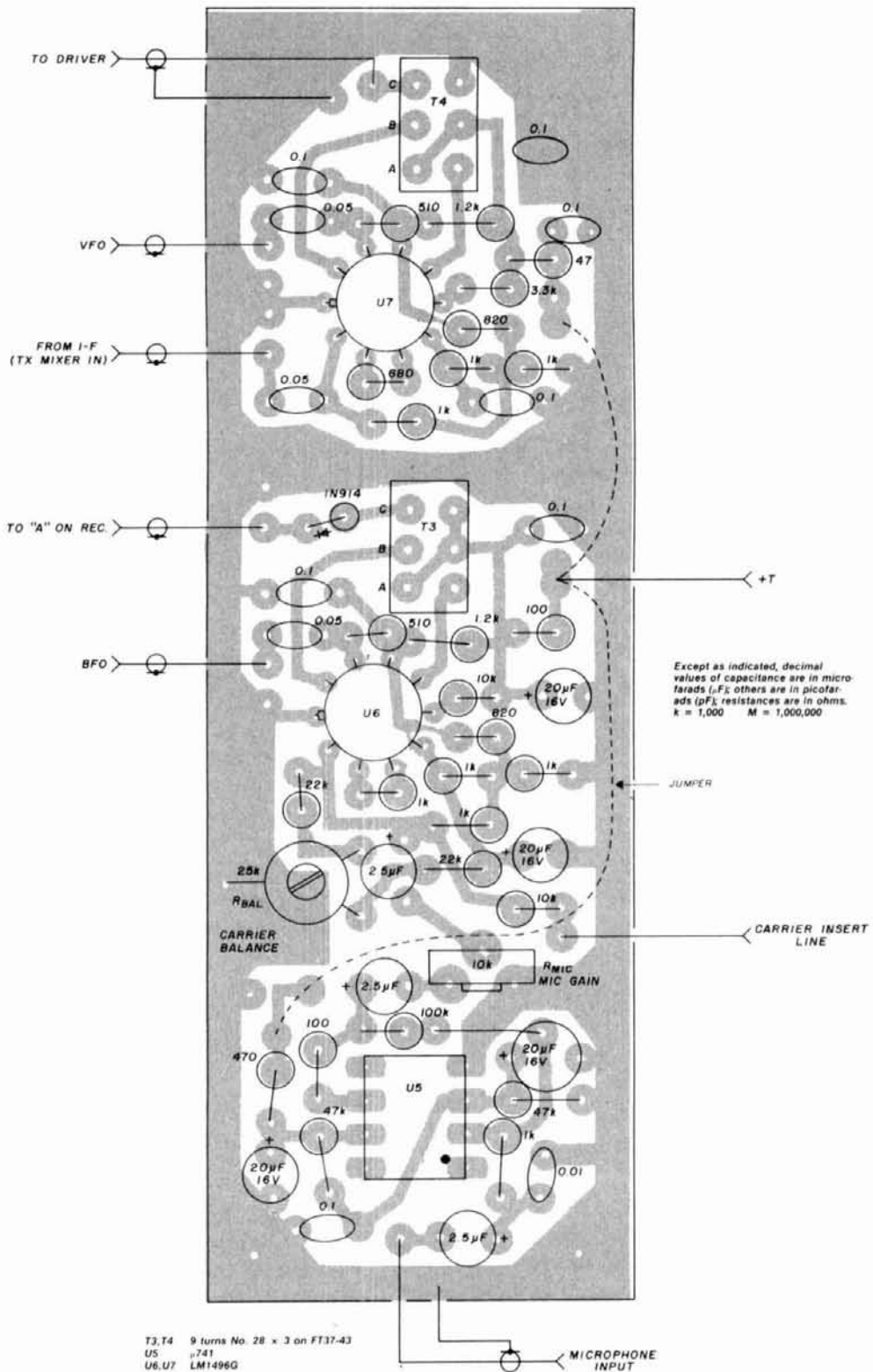


fig. 15. Exciter module.

State
of the art



by

K.V.G.

9 MHz CRYSTAL FILTERS

MODEL	Applic- ation	Band- width	Poles	Price
XF-9A	SSB	2.4 kHz	5	\$53.15
XF-9B	SSB	2.4 kHz	8	72.05
XF-9B-01	LSB	2.4 kHz	8	95.90
XF-9B-02	USB	2.4 kHz	8	95.90
XF-9B-10	SSB	2.4 kHz	10	125.65
XF-9C	AM	3.75 kHz	8	77.40
XF-9D	AM	5.0 kHz	8	77.40
XF-9E	FM	12.0 kHz	8	77.40
XF-9M	CW	500 Hz	4	54.10
XF-9NB	CW	500 Hz	8	95.90
XF-9P	CW	250 Hz	8	131.20
XF910	IF noise	15 kHz	2	17.15

10.7 MHz CRYSTAL FILTERS

XF107-A	NBFM	12 kHz	8	\$67.30
XF107-B	NBFM	15 kHz	8	67.30
XF107-C	WBFM	30 kHz	8	67.30
XF107-D	WBFM	36 kHz	8	67.30
XF107-E	Pix/Data	40 kHz	8	67.30
XM107-SQ4	FM	14 kHz	4	30.15

Export inquiries invited.

Shipping \$3.75

MICROWAVE MODULES VHF & UHF EQUIPMENTS

Use your existing HF or 2M rig on other VHF or UHF bands.

LOW NOISE RECEIVE CONVERTERS

1691 MHz		MMk1691-137	\$249.95
1296 MHz GaAsFET		MMk1296-144G	149.95
432/435		MMc432-28(S)	74.95
439-ATV		MMc439-Ch x	89.95
220 MHz		MMc220-28	74.95
144 MHz		MMc144-28	59.95

Options: Low NF (2.0 dB max., 1.25 dB max.), other bands & IF's available

LINEAR TRANSVERTERS

1296 MHz	1.8 W output, 2M in	MM1296-144-G	\$299.95
432/435	10 W output, 10M in	MM1432-28(S)	269.95
144 MHz	10 W output, 10M in	MM144-28	179.95

Other bands & IFs available.

LINEAR POWER AMPLIFIERS

1296 MHz	20 W output	UP1296-20-L	439.95
432/435	100 W output	MML432-100	369.95
	50 W output	MML432-50	199.95
	30 W output	MML432-30-LS	209.95
144 MHz	200 W output	MML144-200-S	374.95
	100 W output	MML144-100-LS	239.95
	50 W output	MML144-50-S	149.95
	30 W output	MML144-30-LS	109.95

All models include VOX T/R switching.
"L" models 1 or 3W drive, others 10W drive.

Shipping: FOB Concord, Mass.

ANTENNAS

420-450 MHz MULTIBEAMS

28 Element	70/MBM28 12 dBd	\$49.95	\$39.95
48 Element	70/MBM48 15.7 dBd	75.75	59.95
88 Element	70/MBM88 18.5 dBd	105.50	89.95

144-148 MHz J-SLOTS

10 + 10 Twist	10XY/2M	11.3 dBd	69.95
---------------	---------	----------	-------

UHF LOOP YAGIS

1250-1350 MHz	29 loops	1296-LY 20 dBd	\$49.95
1650-1750 MHz	29 loops	1691-LY 20 dBd	59.95

Order Loop-Yagi connector extra:


Type N \$14.95, SMA \$5.95

Send 44¢ (2 stamps) for full details of all your VHF & UHF equipment and KVG crystal product requirements.



si

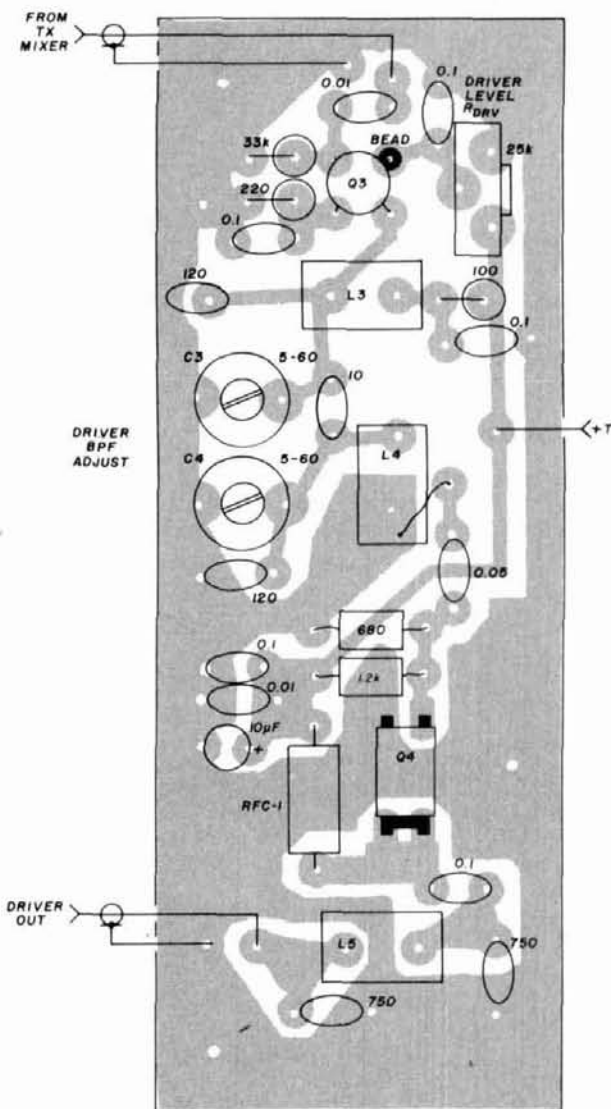(617) 263-2145
SPECTRUM
INTERNATIONAL, INC.
Post Office Box 1084
Concord, MA 01742, U.S.A.





Except as indicated, decimal values of capacitance are in microfarads (μ F); others are in picofarads (pF); resistances are in ohms. $k = 1,000$ $M = 1,000,000$

L3	40 turns No. 28 on T50-2
L4	40 turns No. 28 on T50-2, tap at 13
L5	21 turns No. 24 on T50-2
Q3	40673
Q4	IRFD-123
RFC-1	10 turns No. 28 on FB43-801

fig. 16. Driver/bandpass filter.

wire. Prepare all FT cores in advance by smoothing the corners and applying two coats of clear nail polish ("T" cores are usually epoxy coated and require no preparation). Since most toroid devices have delicate leads that are easily broken, they should be mounted last and glued securely to the board with Ambroid™ cement. †

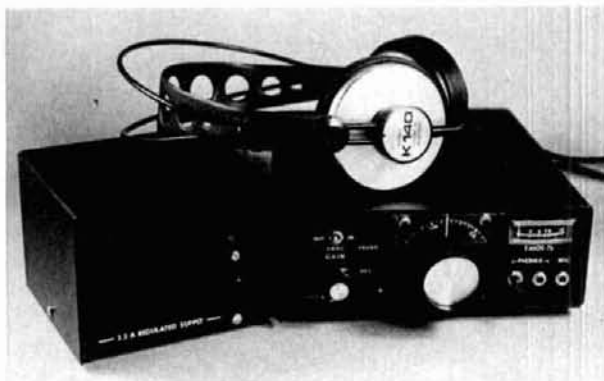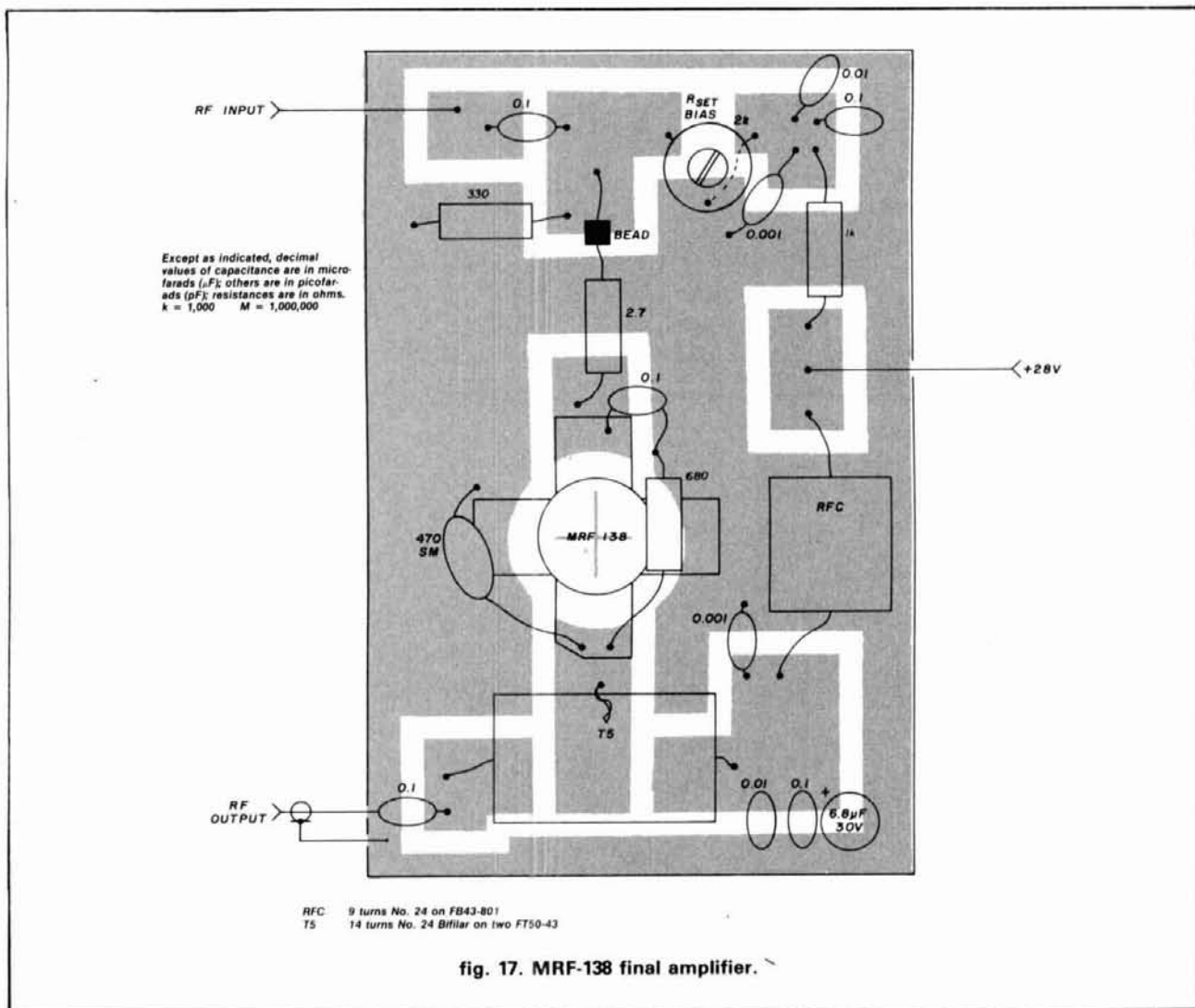†T2, a 10.7 MHz 10 mm green-core transformer, is available from Morning Distributing Co., P.O. Box 717, Hialeah, Florida 33011.



The transceiver can be packaged to suit the builder. The larger cabinet shown here provides more panel space and room for a larger speaker.

Because the VFO circuit is vulnerable to thermal and mechanical instability, its construction requires special attention. These hints should be followed to insure satisfactory performance:

- Use NPO capacitors in the tank circuit wherever possible — the thermal characteristics of silver mica capacitors are often unpredictable.
- To immobilize VFO inductor windings, dip or paint the coil in clear nail polish and sandwich it to the board between fiber washers with a non-inductive screw.
- To insure smooth tuning, the main VFO variable should be a ball-bearing design with either a built-in or external reduction drive.
- The calibration trimmer should be a miniature air-variable (ceramic trimmers drift).
- When installing the VFO module, make all leads connecting external VFO components as short and rigid as possible.
- To avoid thermal instability, locate the VFO away from heat-generating stages such as the PA and the voltage regulator.

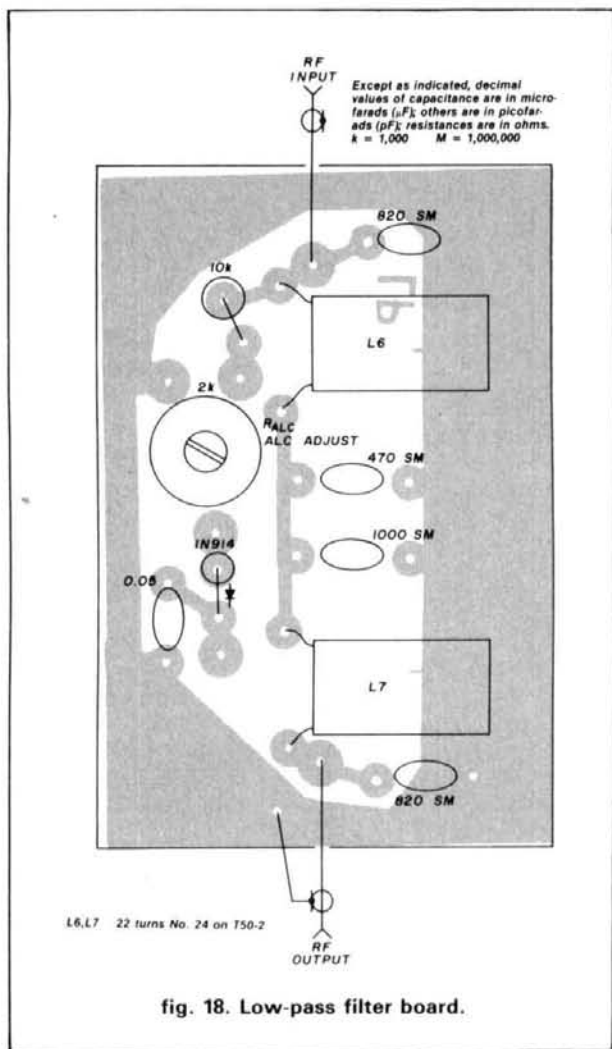


fig. 18. Low-pass filter board.

- Shield the VFO compartment against strong RF fields.
- Locate the transceiver's T-R relay away from the VFO compartment. If located too close, the relay's magnetic field will produce an unwelcome frequency shift.

The only other stage requiring special care during construction is the final amplifier. To prevent the possibility of VHF parasitics, strip-line construction is used and components are soldered directly to the top of the board. To insure strong solder connections, each lead should have a short 90-degree bend at its end in order to make flat contact with the board's surface. The transistor should be mounted first. The MRF-138 is an unprotected MOS device, and I recommend using a grounded iron and wrist-strap to prevent static build-up during installation. Once the module is completed, the circuitry will protect the device.

The transceiver cabinet is a bi-level design fabricated in a custom sheet-metal shop. While this packaging


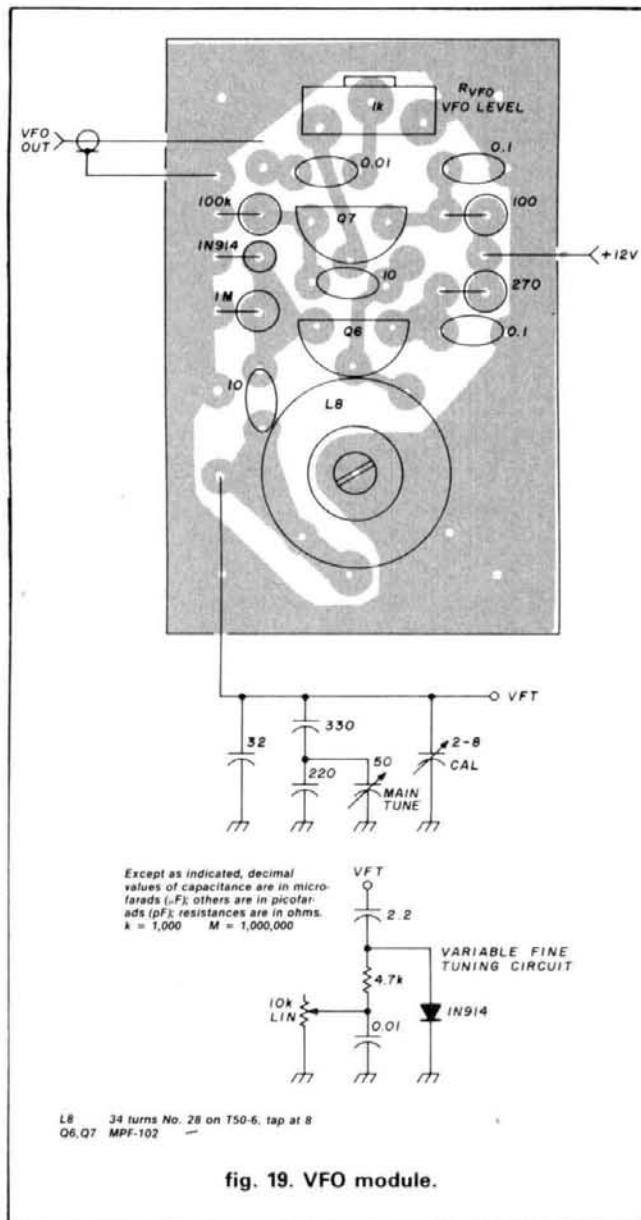


fig. 19. VFO module.

contributes to the appearance and small size of the finished unit, much simpler cabinetry is perfectly acceptable as long as a few basic conditions are met. First, all recommendations to insure VFO stability should be observed. Second, the PA module should be mounted to the inside of the back panel with a suitable external heatsink provided on the opposite side. Additional heatsink area is required for extended phone, RTTY, or CW operation. Finally, the VFO and BFO should be fully shielded.

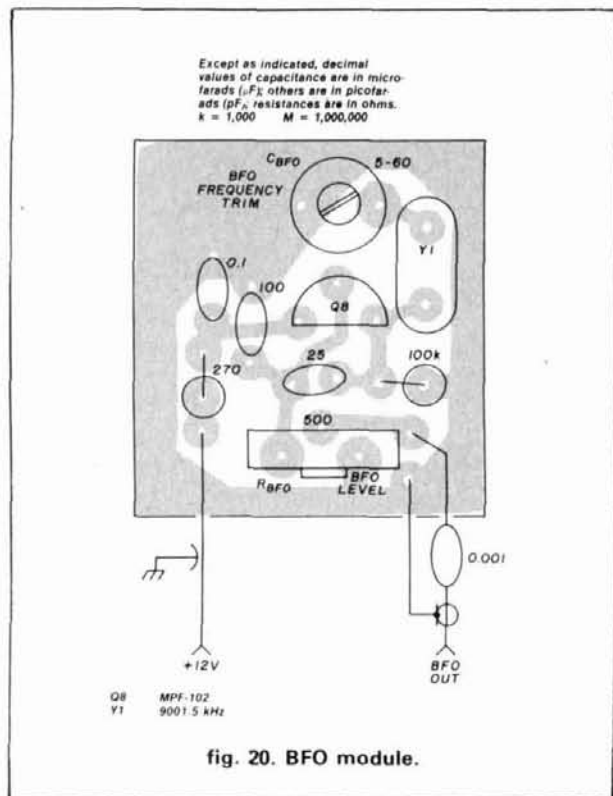In any modular project, interstage wiring can become a nightmare if the wire is prone to breakage or is difficult to handle. Selecting only highly flexible small-diameter wire and shielded cable keeps interstage harnesses small and manageable. I have found that lavalier microphone cable is smaller and much



easier to handle than RG-174 miniature coax. Mounting boards on 1/4-inch standoffs also contributes to a neat layout, since this provides space for interstage wiring to pass underneath. Once the modules are mounted and interstage wiring is completed, testing and alignment can begin. Power distribution and T-R switching should be thoroughly checked first, since an error here could damage components.

alignment

Fixed capacitor values in the VFO tank may require some substitution to establish the desired operating range (5000 kHz to 5200 kHz for 4000 to 3800 kHz operation). Once this range is established, a tuning dial can be calibrated. A frequency counter facilitates the calibration process. Once the VFO dial is calibrated, receiver alignment can proceed. Use fig. 21 to locate the calibration and alignment controls.

- Connect the receive and transmit mixers to the VFO, and adjust R_{VFO} for 100 mV RMS output.
- Connect the product detector and balanced modulator to the BFO, and adjust C_{BFO} for an operating frequency of 9001.5 kHz. Adjust R_{BFO} for an output of 100 mV RMS.
- Set the receiver AGC threshold by adjusting R_{TSH} for 5 volts as measured at TP1. Zero the S-meter via R_{ZRO} .
- Set the receiver gain fully clockwise for maximum

gain and adjust IF transformer T2 for a peak in background noise.

- Connect a 50-ohm antenna and tune the VFO to 3900 kHz. Peak bandpass filter trimmers C1 and C2 for maximum sensitivity.

The receiver should now be fully functional. Check AGC action by tuning in an extremely strong SSB signal. If the audio cracks and distorts at full gain, the AGC is under-controlling IF stage U2. Increase AGC gain via R_{AGC} to eliminate this condition. If the audio "pumps" on voice peaks or motorboats with no signal, the opposite conditions exist and AGC gain should be decreased. Meter sensitivity control R_{SEN} should be adjusted so that extremely strong signals register in the upper 10 percent of the scale.

To prepare for transmitter alignment, disconnect the 28-volt supply line from the final amplifier board. Terminate the output of the driver with a 47-ohm resistor and connect a scope across the termination. Microphone gain R_{MIC} should be set fully off, and pre-driver gain R_{DRV} set to the middle of its range (maximum gain). Tune the VFO to 3900 kHz.

- Key the transmitter and activate the carrier insert switch. Adjust IF transformer T2 and bandpass filter trimmers C3 and C4 for maximum output.

- Key the transmitter and adjust R_{BAL} for minimum carrier output. A receiver tuned to the output frequency may provide a better null indication.

- Connect a 500-ohm dynamic microphone and advance R_{MIC} to 75 percent. Speak into the microphone and watch the scope for signs of instability ("grass" or parasitic oscillations on the waveform). The pattern may show flat-topping on voice peaks, since the ALC is not yet functional.

If instability or parasitics are observed, find their source before going on. Check the RF amplifiers in isolation, and check IF amplifier U2 (reducing the value of the 10-kilohm resistor across the primary of T1 should tame unstable operation in U2). If operation is normal through the driver stage, alignment can continue.

- Connect the 28-volt supply line to the final amplifier board through an ammeter. Short the amplifier's input terminal to ground. Key the transmitter, and adjust R_{SET} for an idling current of 250 mA. Note that this adjustment is sensitive to changes in supply voltage. If the power supply voltage is changed significantly at a later date, the bias should be re-set.
- Remove the driver termination, unshort the input to the PA, and hook up the driver. Connect a 50-ohm dummy load to the output of the transceiver. Place a single turn pick-up loop through balun T5, and connect it to the scope. The driver low-pass filter and bandpass responses are shown in figs. 22A, B.



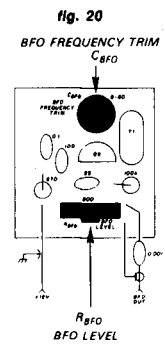
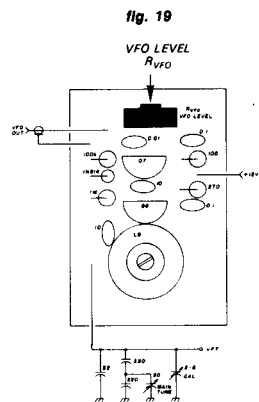
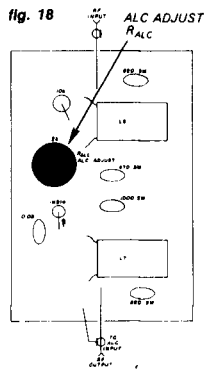
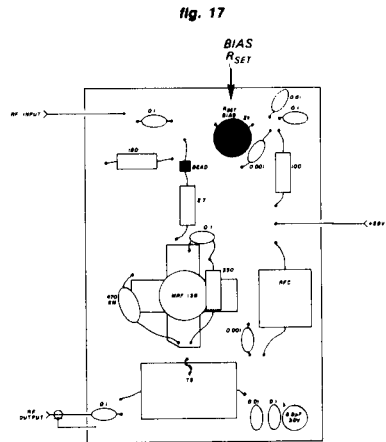
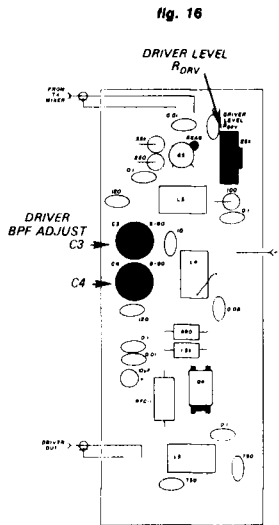
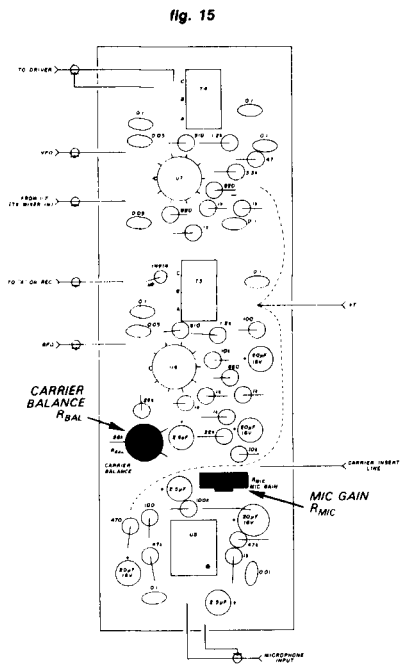
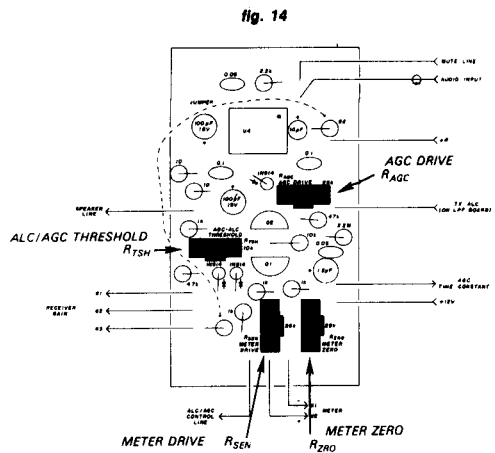
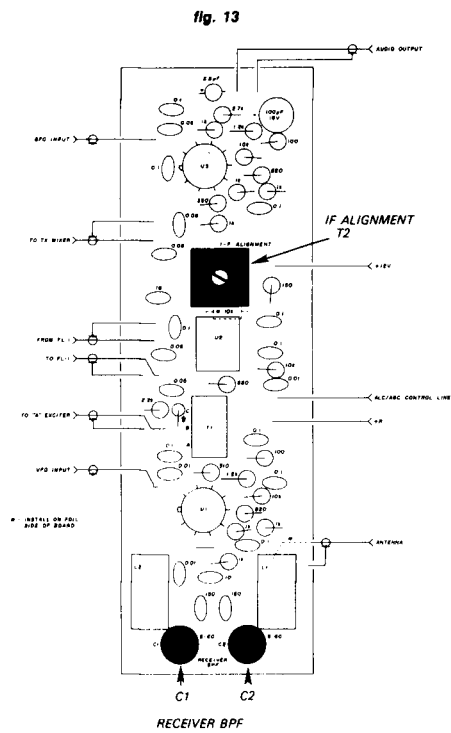


fig. 21. Calibration and alignment controls.

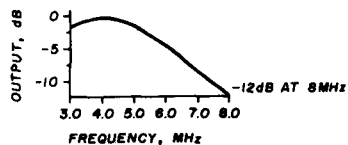

(A)

fig. 22A. Driver low-pass filter response.

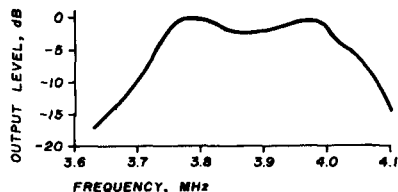

(B)

fig. 22B. Driver bandpass filter response.

- Key the transmitter and speak loudly into the microphone, adjusting R_{ALC} for maximum transmitter output. The scope pattern should show flat-topping on voice peaks. If saturation does not occur, increase microphone gain until it does. If the final cannot be saturated, system gain is low and a problem exists (check the AGC threshold voltage at TP1 first; if set above 5 volts, transmitter gain is reduced).

- To set ALC level, close-talk the microphone and adjust R_{ALC} to the point where flat-topping just disappears. The ALC meter should deflect past mid-scale on voice peaks and a power meter should indicate an average output of 10-15 watts.

This completes transceiver alignment.

performance

The transceiver was tested to see if performance approximated industry standards and met FCC regulations for spectral purity. Receiver noise floor was measured at -120 dBm. Selectivity reflected the published specifications of filter FL1. AGC held a 60 dB change in signal strength to a 3 dB change in audio output. AGC attack was a bit slow, resulting in some audible "cracking" on extremely strong signals. This condition is not uncommon in simple audio-derived systems. Overall receiver audio quality was judged excellent when compared against a popular imported multi-band transceiver. Tests for receiver intermodulation distortion were not conducted.

At 30 watts PEP output, transmitter IMD was measured at -30 dB. Second and third harmonics were -47 dB and -55 dB, respectively. Saturation occurred at 35 watts PEP. Transmit audio reports were generally excellent, but microphone selection was an important factor. Low-Z broadcast dynamics produced the best overall quality, but an inexpensive mobile microphone provided a bit more "punch" under difficult band conditions. The MRF-138 final amplifier survived open and shorted port conditions without damage, indicating acceptable immunity to high SWR.

operation

The transceiver's small size makes it a natural for traveling, or for use as a second station at home. Mine resides in a corner of the family room on a small writing desk, close to the wood stove, kitchen, and other comforts of home. On-air performance has been very gratifying. Using an inverted-V antenna at 50 feet, I have worked all U.S. call areas, operated contests, controlled nets, and elbowed my way through evening QRM with excellent regularity. In evaluating the transceiver's effectiveness, it is important to remember that dropping transmitter output from 100 watts to 30 watts reduces the received signal less than 1 S-unit. Under most band conditions, this is not significant.

conclusion

My goal was to design and build a simple mono-band SSB transceiver that would be compact, easy to replicate, and powerful enough to provide reliable communication on 75 meters. Off-the-shelf components and contemporary design techniques were employed wherever possible to make the job easier. The transceiver described in this article is my third, and carries with it the experience of the first two. With minor modifications, the design should be transferable to other bands. I hope this article will encourage others to take the plunge and build — there's no magic involved, and the enjoyment that comes from operating a homebrew rig is fantastic.

references

1. Rick Littlefield, K1BQT, "Compact SSB Receiver," *ham radio*, November, 1983, page 10.
2. Hayward and DeMaw, *Solid State Design For The Radio Amateur*, ARRL, Newington, Connecticut, 1977.
3. DeMaw, "Go Class B or C with Power MOSFETs," *QST*, March, 1983, page 25.
4. T. C. McNulty, "Power MOSFETs — What the Designer Needs to Know," *Electronic Products*, February 7, 1984, pages 133-137.
5. Helge O. Granberg, "Power MOSFETs versus Bipolar Transistors," *Application Note 860*, Motorola Semiconductor Products, Phoenix, Arizona, 1982.
6. F. Perkins, WB5IPM, "Action Machine for 20," *73*, January, 1983, page 12.
7. G. Woodward, W1RN, editor, *The Radio Amateur's Handbook*, 62nd edition, ARRL, Newington, Connecticut 1985.

ham radio

PACKET RADIO . . .

. . . THE FASTEST GROWING PART OF AMATEUR RADIO TODAY

is already providing high speed, error free, communications on many amateur bands for qso's, data transmission, emergency traffic, dx'ing, traffic nets, mailboxes, endless experimentation, and soon... satellite operation.

networks continue to grow, as does the number of hams who enjoy this new and exciting mode. The increasingly popular **PACKETERM IPT** is contributing to phenomenal growth in amateur packet radio by providing a full function packet terminal in a compact, portable unit...



ALL YOU NEED FOR PACKET OPERATION IS A **PACKETERMtm IPT AND YOUR RIG !**

Designed for true portability, the IPT is equally at home in your ham shack or (with its optional carrying case) trekking in the country for battery powered hilltopping!

A single cable connects to your transceiver....that's all there is to it!

Use it with your base station, mobile, or with your HT on that hilltop!!!

- FEATURES:**
- * * 9 inch portable terminal and full function tnc combined
 - * * 66 commands available - the most widely used, field proven programming .
 - * * Built-in LSI modem ; 300 or 1200 baud, 200 or 1 kHz audio shift
 - * * stores setup parameters with power off - uses lithium battery
 - * * custom "beacon" text -- your call, qth, etc. in permanent memory
 - * * 74 key, full travel keyboard with 14 function keys for commands, calls, etc.
 - * * printer port - RS232C serial
 - * * optional printer, carrying case, and dc adaptor (13.8 VDC)

 **Packeterm**

Box 835, Amherst, NH 03031
(603)-673-6630

PRICES:	IPT COMPLETE	\$995
	PRINTER	\$349
	DC ADAPTOR	\$125
	TNC (BOARD ONLY)	\$275

high stability local oscillators for microwave receivers and other applications

Phase-locked approach offers greater stability

This article describes a reliable phase-locked loop originally designed for the first conversion of a radio astronomy microwave receiver¹ applicable for general microwave receiver use and to other HF, VHF, and UHF phase-locked applications as well.² Its design evolved from one of my earlier efforts incorporated in a fully synthesized, general coverage HF transceiver as shown in fig. 1.

Local oscillators used for conventional microwave (TVRO) such receivers are usually open loop and are installed outdoors as part of the first converter, known as the "head end" and located at the feed point of a parabolic dish antenna. They normally exhibit gross frequency instability (typically ± 1.5 MHz) due to their free running characteristics, which are affected by ambient temperature changes as well.

The two types of open-loop local oscillators most commonly used for this application are the free running tuned cavity and the crystal controlled multiplier type. This article deals with the second approach, which allows an already-clean multiplier chain to lock on a much more stable reference frequency strategically located away from the elements. Consequently, the unit can be used under varying temperature conditions and will follow a remote reference source kept indoors for good stability.


The synthesizer uses a simple version of a type-one crystal-controlled phase-locked-loop operating at 88 MHz.³ Its output is divided by a fixed modulus divider

involving emitter-coupled-logic (ECL) and transistor-transistor-logic (TTL) circuits. The division number N is fixed at 88 and followed by an exclusive OR digital phase detector that closes the loop through a simple low-pass filter as shown in fig. 2.

In order to obtain the desired microwave frequency, the output of the oscillator running at exactly 88 MHz is used to drive a times-12 multiplier such as described by Paul Shuch, N6TX.⁴ Other multiplications are possible for even higher frequencies. The reference frequency can be supplied to the synthesizer from the back end of the receiver via fiber optics or coaxial cable communication links (depending on the distance; digital line drivers may be required in the latter). With this approach, a remotely located temperature-compensated crystal oscillator (TCXO) that acts as a time base will maintain the short and long term frequency stability of the 88-MHz crystal oscillator through the phase-locked technique. The stability of the multiplier chain in the microwave receiver will thereby also be favorably affected. High initial stability and spectral purity would be required to compensate for the magnifying effect of the multiplier. My circuit used a 4-MHz TCXO manufactured by McCoy Electronics for the reference oscillator. This part guarantees $\pm 5 \times 10^{-7}$ (± 0.5 PPM or ± 2 Hz at 4 MHz) Hertz per year.² This represents an ultimate stability for the remotely located L-band local oscillator of ± 6 Hertz, respectively.

The circuit design of the synthesizer is simple (although making one work is another story) as shown in fig. 3. A highly stable 88-MHz (0.001 percent) fifth overtone crystal was chosen to guarantee initial start-up almost on frequency before locking occurs. It is

By Cornell Drentea, WB3JZO, 7140 Colorado Avenue North, Brooklyn Park, Minnesota 55429

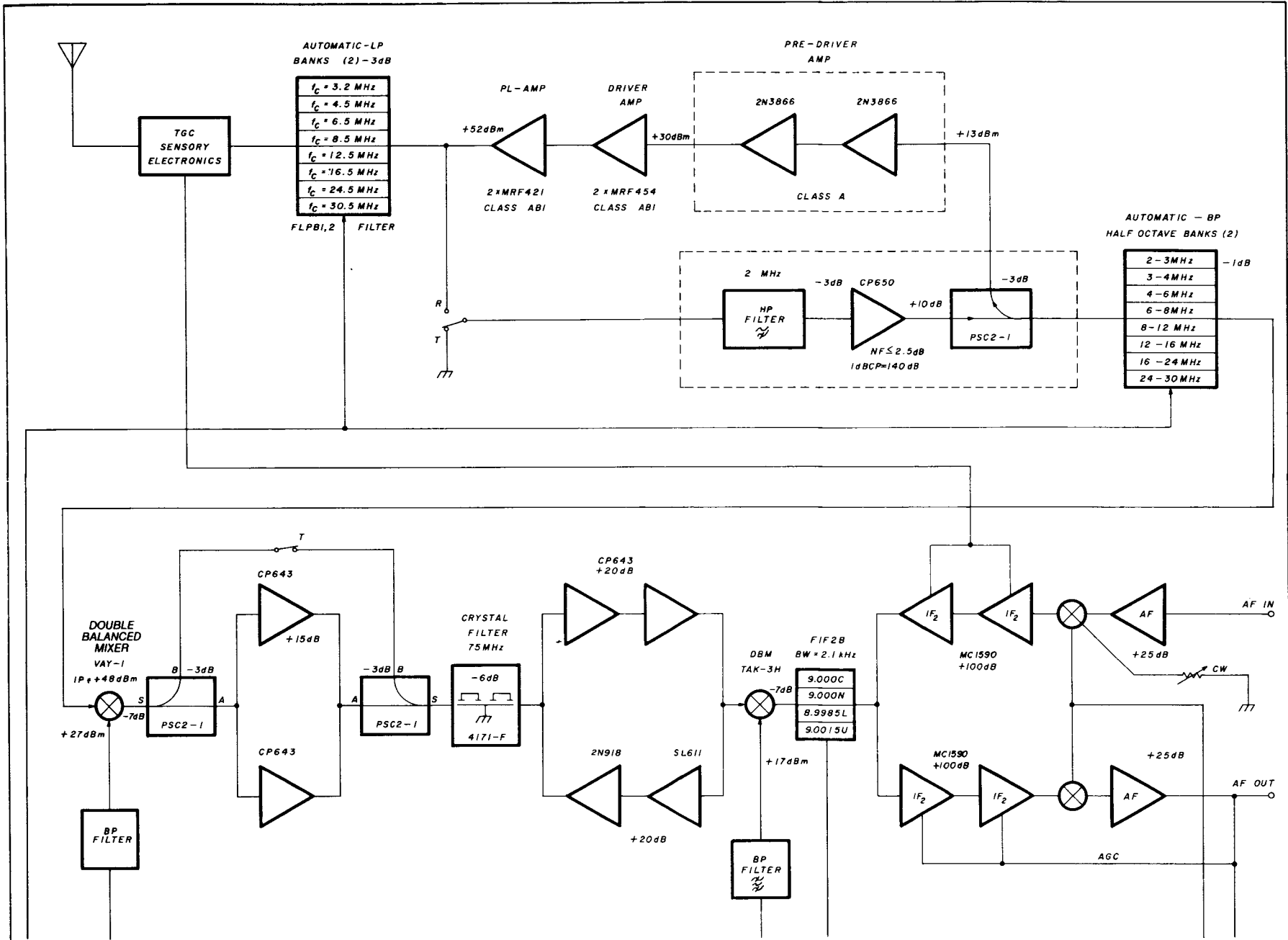

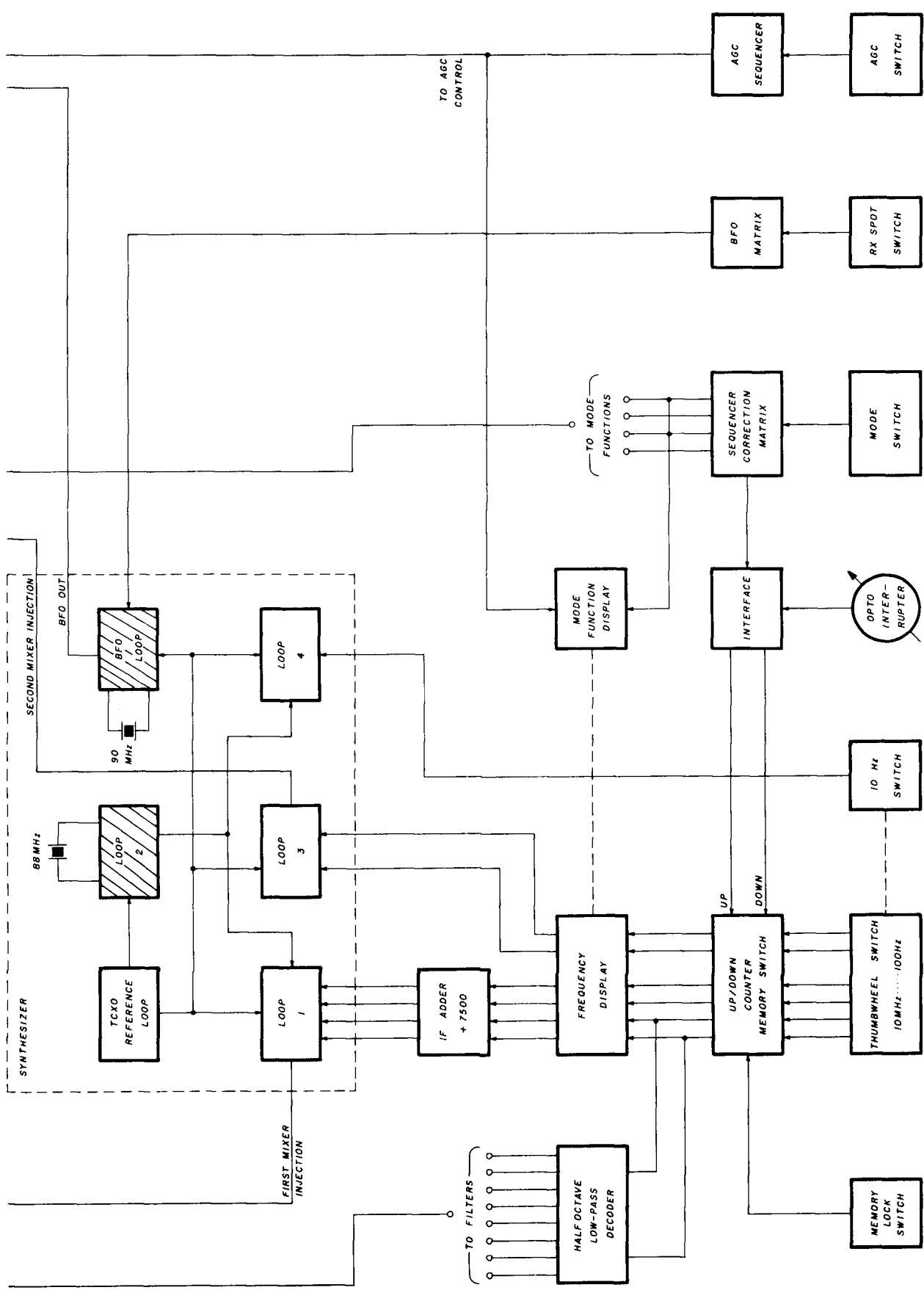


fig. 1. Application of fixed VHF phase-locked-loops in a fully-synthesized HF transceiver. The VHF loop described here is used twice (88 MHz and 90 MHz for the BFO) in order to ensure full synthesis for the entire radio.


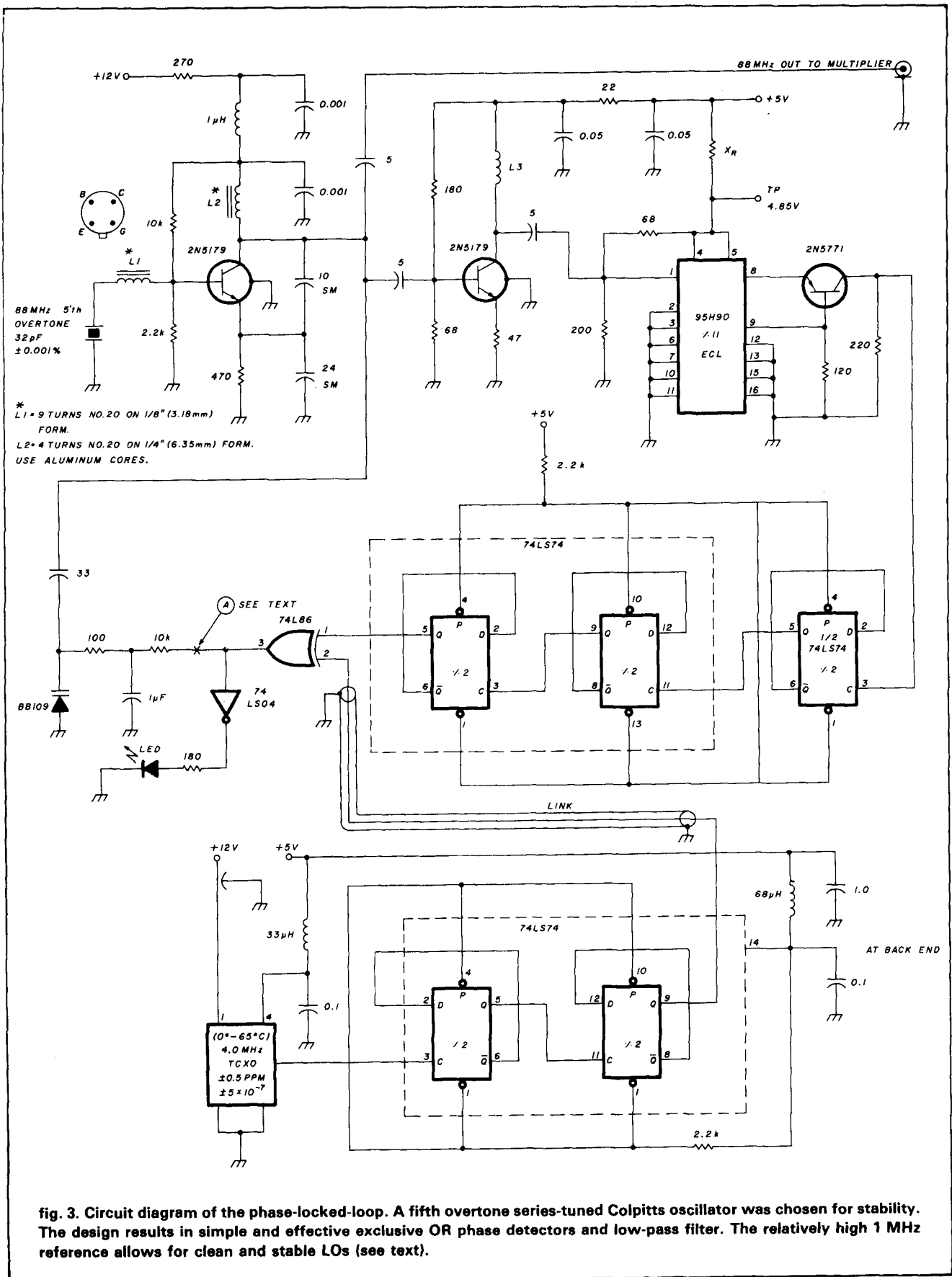


fig. 3. Circuit diagram of the phase-locked-loop. A fifth overtone series-tuned Colpitts oscillator was chosen for stability. The design results in simple and effective exclusive OR phase detectors and low-pass filter. The relatively high 1 MHz reference allows for clean and stable LOs (see text).

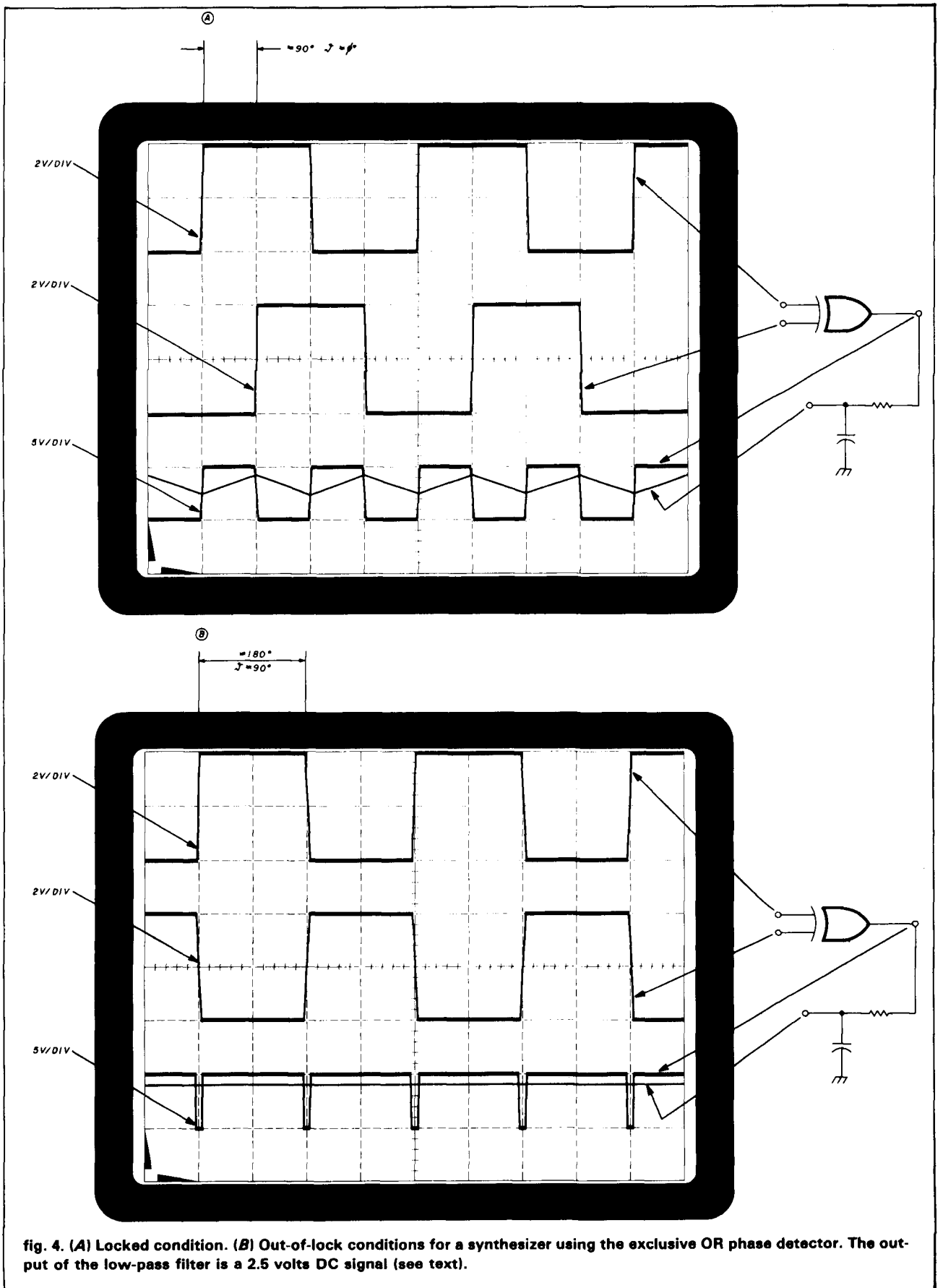

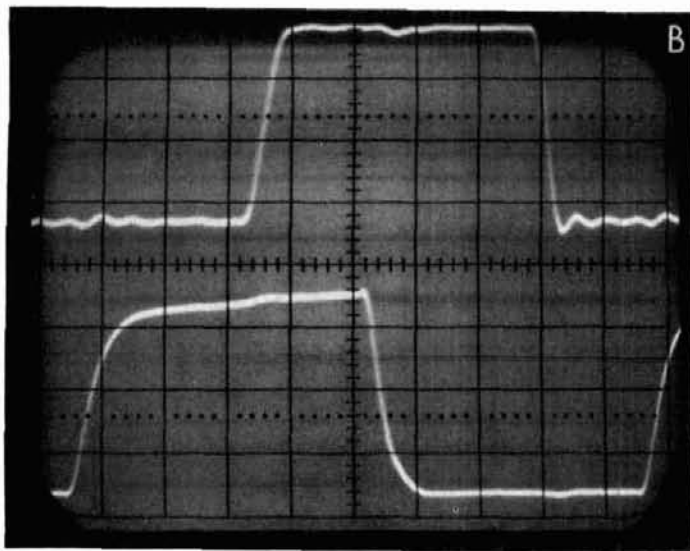
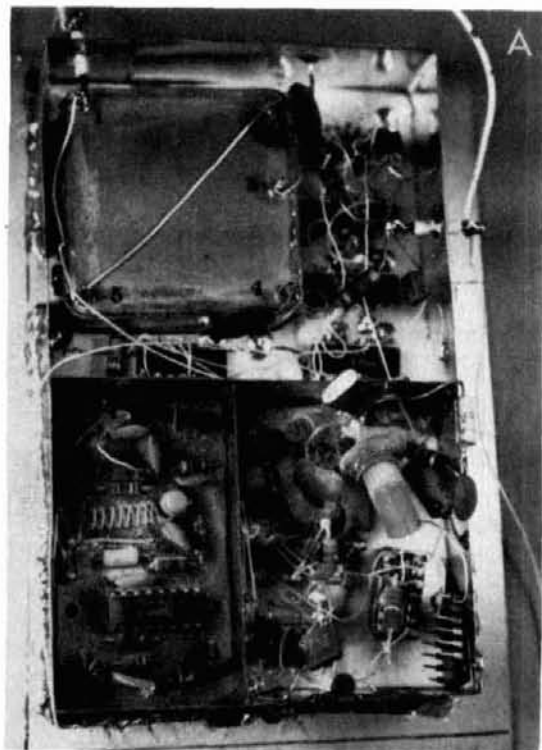


fig. 5. (A) The synthesizer circuit was frozen to -78 degrees F with cooling spray. (B) After calibration the phase-locked-loop remained locked over the entire temperature range. The divided 1 MHz square wave shown at the top follows the reference frequency at the bottom by -90 degrees, which represents a 0-degree phase error (see text).

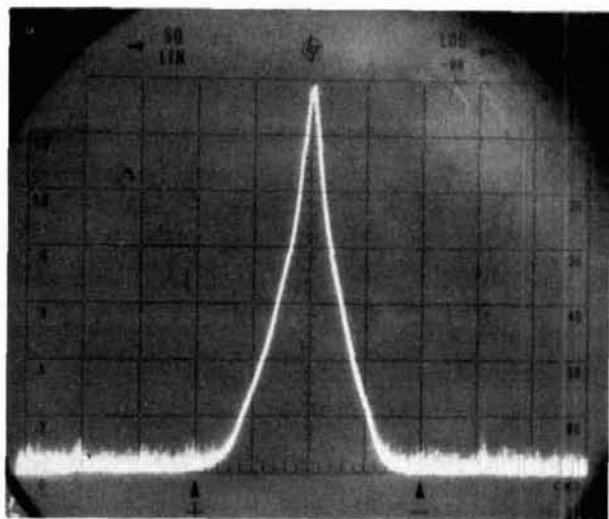


fig. 6. Spectrum analyzer tests performance of the phase-locked-loop.

by approximately 90 degrees (delay is introduced by the additional circuitry) which corresponds to a zero phase error.³ The secret of the entire circuit is L1 and L2, which are calculated to resonate the Colpitts oscillator on the fifth overtone of the crystal. Additional "tweaking" may be required to bring the circuit into resonance due to local stray elements. High Q aluminum cores were used in my prototype for best results.

adjustments

With the loop line disconnected at A (see fig. 3),

inject a 2.5 VDC level at the 10 kilohm resistor (which is part of the low-pass filter. The best way to do this is to use a couple of batteries in series through a 10-kilohm linear potentiometer voltage divider to insure a pure DC voltage. With the circuit board heated to 80-degrees F (a 100-watt lamp on top of the circuit will do well), adjust L1 and L2 for resonance at the fifth overtone of the crystal as measured on a frequency counter. Observe the position of the cores. Cool the circuit to -78 degrees F with a dry cooling spray. Adjust L1 and L2 again for resonance. (The circuit should still work at this temperature; according to calculations, the transistor junctions will reach only about -40 degrees F.) To accomplish this, selected parts have been used in the prototype. Again, observe the new position of the cores.

Wait until the circuit returns to room temperature and readjust L1 and L2 midway between the two positions. Remove the 2.5 VDC voltage from the low-pass filter and reconnect the loop back at A.

The circuit should now lock every time power is turned on and lock should be maintained over the entire temperature range. This can be verified through repeating the above procedures with the loop closed.

Figures 5A and B show the "brassboard" of the synthesizer and how phase locking was maintained under freezing conditions. For convenience a lock indicator was incorporated in the design as shown in fig. 3.

An out-of-lock condition would be indicated by the blinking LED, should recalibration become necessary.

NEWEST RIGS, BEST BEAMS, AWESOME ACCESSORIES.

New rigs and old favorites, plus the best essential accessories for the amateur.

3621 FANNIN ST.
HOUSTON, TX. 77004-3913
CALL FOR ORDERS
1-713-520-7300 OR
1-713-520-0550

ALL ITEMS ARE GUARANTEED OR SALES PRICE REFUNDED.

EQUIPMENT

Kenwood	Call for prices on all Kenwood
New Kantronics UTU-XT	319.00
Yaesu 2700 RH	529.00
Icom IC735	749.00
Four lot price IC-735	2800.00
Kenwood TS940S, contesters delight	Call
Ten-Tec 2510 Satellite	489.00
Icom R7000 25-2000 MHz	Call
Alpha (ETO)	List - 15%
Icom 271A, 27A	Call
Icom IC3200	489.95

SERVICES

Alignment, any late model rig	50.00
Flat fee Collins rebuild	Call

ACCESSORIES

Heil HC3/HC4/HC5	Stock
Heil BM10 Boom Mike headset	53.95
Heil HCS Control Box/Interface	89.95
CES 510 Smart Patch	349.00
FLUKE 77 auto-ranging digital multimeter	115.00
Shure 444D Mic	54.95
Bird 43 Wattmeter	Call
Bird Elements, H/59.00; A-E/48.00; Special	In Stock
Ameco Pre-Amps	10% Off
Daiwa CN620B, 20-200, 2000W	109.95
Collins 500Hz Filter, F455J05, new	95.00
Sanyo AA Nicads, tabs	2.50
2, 4, 5, 6, 8 pin mic plugs	4.00
Fox Tango	- 10%
Tenna Hitch	
By D.C. Sales, Fits Class 1, 2 Hitches. Adapts existing hitch on your car/truck to any HF antenna. 3/8 x 24 thread. No holes, complete unit	29.95
Daiwa CN630 140-450 20/200 watt	129.00

KEYS

Benchner & Vibroplex	Less 10%
Vibroplex Carrying Case	\$20.00 w/key purchase
MFJ Super Keyboard #496	199.95

TUBES

GE6146B	11.95
Eimac 3-500Z	109.95
GE Industrial Tubes	Call
GE 12BY7A	6.00
GE 6JS6C	11.95
Collins & Drake Replacement Tubes	Stock

BOOKS

Hayden, Computer Programs for Amateur Radio	16.95
We also stock SAMS, TAB, ARRL, RSGB, Radio Pubs & Ameco books	Call
CALRAD 65-287 SWR, Relative Power Meter	32.95
3-150Mhz, KW +	

PACKET?PICKIT!

AEA PK64	199.00
AEA PK80	Soon

KANTRONICS PACKET	199.00
CP100 vs. CP1 Worth the difference?	
Yes!!!	Call
ICOM 271A Great Packet Radio	Call



ANTENNAS

ARX 2B, V2S, 2MVCV-5, ISOPOLE	44.95
A4	289.95
402CD	279.95
New Cushcraft LAC-3 Lighting Arrestor	7.95
215WB New, 15EL, 2MBeam	79.95
AOP-1, Complete Oscar Antenna	149.95
Butternut, HF6V, 80-10 Vertical	125.00
HF2V, 80 & 40 Vertical	125.00
Butterfly Antenna	169.95
HF4B, previous HF3B	169.95
Hustler G7-144	119.95
Barker & Williamson All Band Dipoles	Less 10%
Ham4 Rotator, T2X, CD45-2	Call
KLM HF World Class Series Antennas	Call Don
Cushcraft's 40-2cd, hottest selling 40 meter beam road band, easy assembly	279.95

OTHER ANTENNAS

Larsen Kuldock	17.00
Valor 75-10M complete mobil antenna	
AB-5	79.95
Avanti ASP151 3G, thru glass 2M	33.00
Anteco 2M, 5/8, Mag. Mount, Comp.	25.00
Stoner (McKay-Dymek) DA100D Receiving Antenna	190.00
Philly Stran	Call

SURPLUS

2.5A/1000PIV Epoxy diode	29¢ Each or 19.00/100
.0015/10KV	1.95
3N201	.95
4 Inch ferrite rod	1.95
Sanyo AAA Nicad w/tabs	2.50—each
Close out on rigs and accessories? All the time	Call
Close out Curtis Memory M480	\$50.00—each
24Pin IC Sockets	.25
365pF two gang cap	1.95

BELDEN

9913 low loss, solid center, foil/braid shield	45¢/ft.
8214 RG8Foam	43¢/ft.
8237 RG8	40¢/ft.
8267 RG213	52¢/ft.
8000 14Ga stranded copper ant. wire	13¢/ft.
8448 8 conductor rotor cable	31¢/ft.
9405 Heavy duty, 2-16 Ga. 6-18 Ga	52¢/ft.
9258 RG8x	19¢/ft.
8403 Mic Cable, 3 condctr & shield	80¢/ft.
100 Feet 8214 w/ends installed	45.00
8669 7/16" tinned copper braid	1.10/ft.
International Wire RG214, non-mil, good cable	70/ft.

AMPHENOL

831SP-PL259 Silverplate	1.25
UG176 reducer RG8X	.30
831J Double Female UHF	2.00

82-61 N Male	3.00
82-97 N Female Bulkhead	3.00
New 82-202-1006 N-Male fits 9913	5.00

ROHN

1/4" E.H.S. Guy cable, Rohn US, 1000 ft	250.00
3/16" E.H.S. cable	210.00
1/4" Guy Cable, 6100#7 x 7 strand, import	15¢/ft.
3/16" Guy Cable, 3700#7 x 7 strand, import	12¢/ft.
3/8 x 6 E&J Turnbuckle	7.95
3/16" Wire Rope Clips	.40
1/4" wire clips	.50
Porcelain 500D Guy Insulator (3/16)	1.69
Porcelain 502 Guy Insulators (1/4)	2.99

USED EQUIPMENT

All equipment, used, clean, with 90 day warranty and 30 day trial. Six months full trade against new equipment. Sales price refunded if not satisfied.

POLICIES

Minimum order \$10.00. Mastercharge, VISA, or C.O.D. All prices FOB Houston, except as noted. Prices subject to change without notice. Items subject to prior sale. Call anytime to check the status of your order. Texas residents add sales tax. D'ats all, folks.

SPECIAL TELEPHONE OFFER

Call our numbers and when you place your order, we'll deduct a dollar off it. And don't be shy. Ask tough questions. Our guys are more than order takers—they know the radios and the equipment.

DON'S CORNER

Those devoted to Yaesu fans out there—the FT101E certainly had a lot of supporters—should be pleased to know that Yaesu is just about to come roaring back into the marketplace. This means new products, stronger advertising and maybe—just maybe—a price promotion or two. Yaesu started to get serious about computer control of rigs with their ultra-boxes—so you might expect to see some more tricks with computer control. Now—when will these guys get wise enough to have the code written for the big 4 machines in amateur radio—Radio Shack, Commodore, Apple, and IBM. Contact Madison for the latest in Yaesu all the time. Another idea—how about a dual banded hand-held. Two meters and 430 for openers. Certainly the technology is available... and the market is ready. First one to market with this product will move a lot of radios.

73&Good DX

DON

MADISON

Electronics Supply

3621 FANNIN
HOUSTON, TEXAS 77004

1-713-520-7300 OR 1-713-520-0550


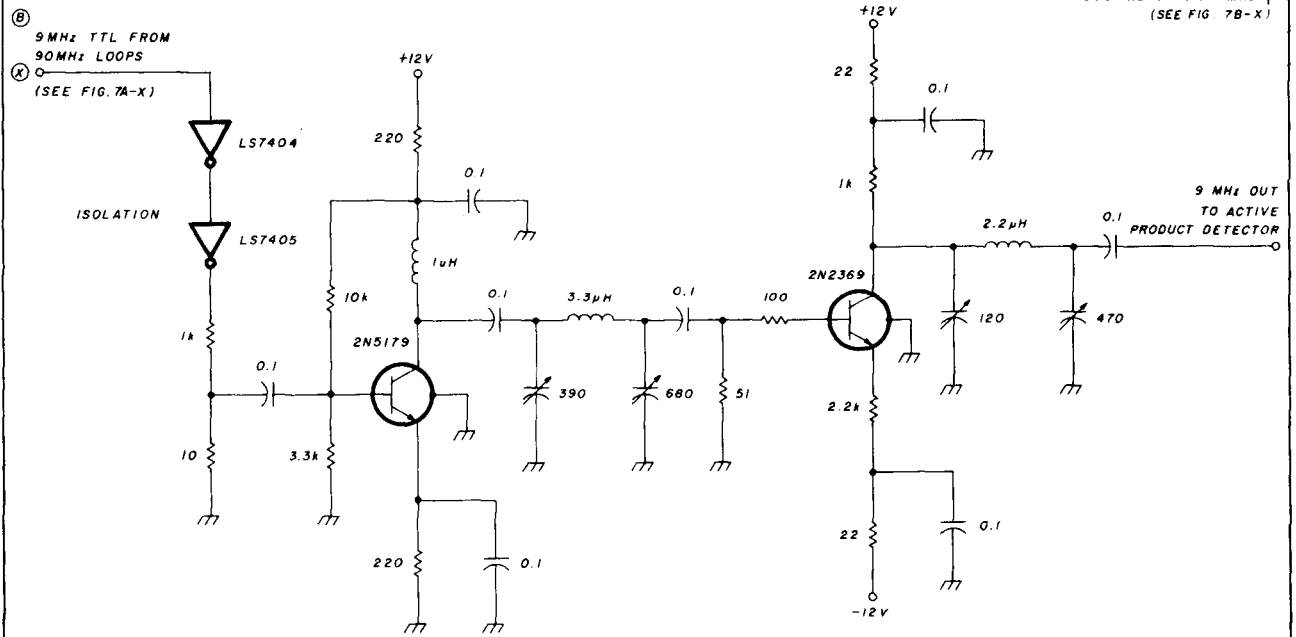


fig. 7. (A) Block diagram of an elegant 9 MHz BFO as used in a fully synthesized HF transceiver. The signal is derived from a dual 90 MHz phase-locked-loop similar to the one presented here (see text). (B) Signal processing for the 9 MHz BFO. The 90 MHz derived signal is conditioned before it is applied to the active mixer product-detector/modulator.

AMATEUR TELEVISION

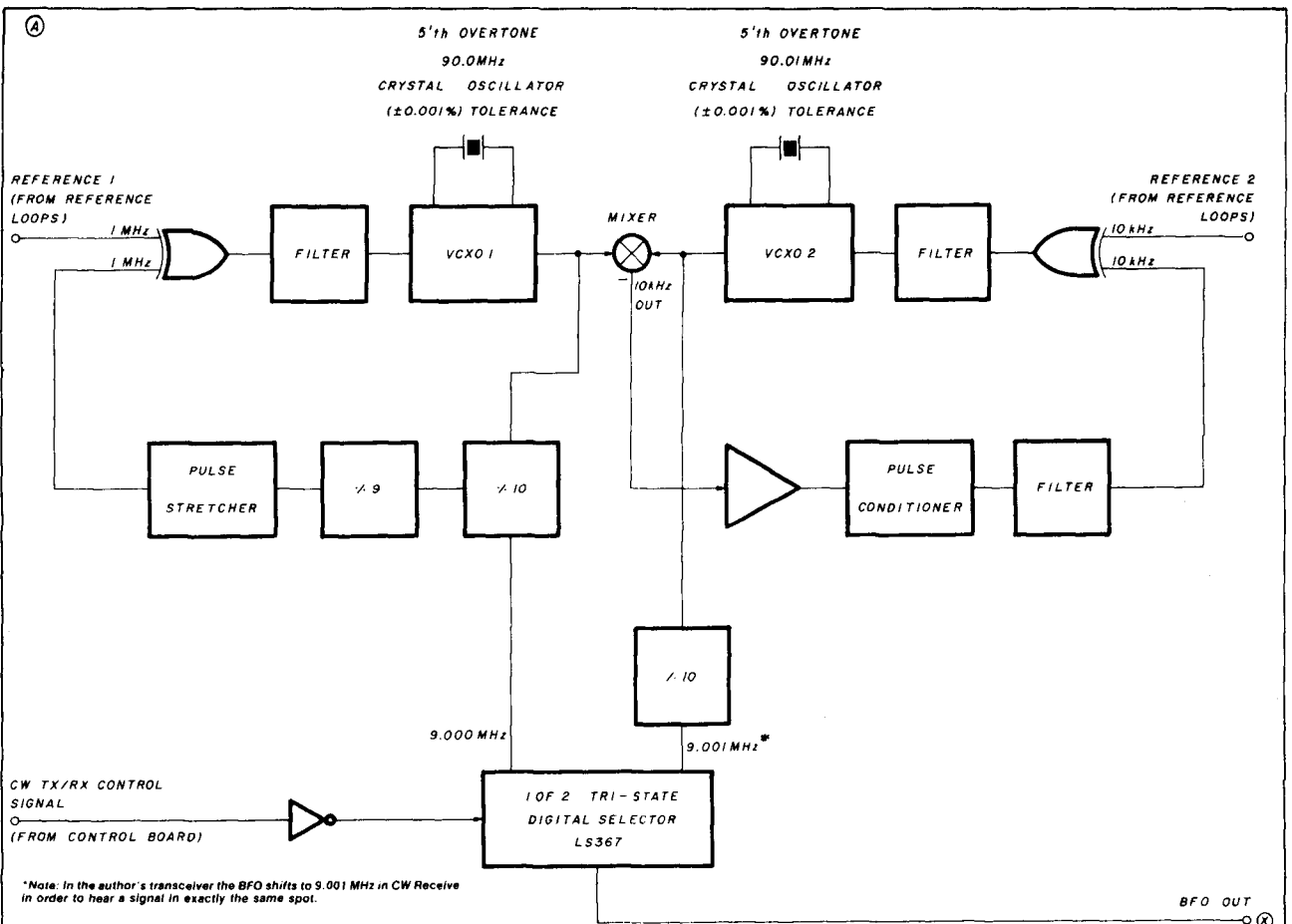NEW 70 CM ATV TRANSCEIVER ALL YOU NEED IN ONE BOX



\$299 delivered
TC70-1

- **FULL COLOR, SOUND, & LIVE ACTION** just like broadcast TV. Get on this exciting amateur video mode at our affordable ready to go price.
- **WHAT IS REQUIRED FOR A COMPLETE OPERATING SYSTEM?** The TC70-1s downconverter outputs to any TV on ch 3 for receiving. Connect a good 70 cm antenna and low loss coax. Plug in any composite video source you want to transmit: Camera, VCR, computer, etc. Plug in any low Z dynamic mic or use color camera mic for Standard 4.5 MHz TV sound. Connect to 13.8 vdc for base, mobile, or portable. See chapt. 20 1985 ARRL Handbook. That's it!
- **WHAT CAN YOU DO WITH THE TC70-1 ATV TRANCEIVER?** Show the shack, projects, computer program listings, home video tapes, repeat Space Shuttle audio and video if you have a TVRO, repeat SSTV or RTTY, Weather Radar, do public service events such as parades, marathons, races, CAP searches and rescues... the list goes on. DX depends on antennas and terrain, typically 1 to 40 miles. We have video compensated RF linear amps for 20 (\$119) or 50 (\$189) watts pep for greater DX.
- **FEATURES:** Small 7x7x2.5". Push to Look (PTL) T/R switching. GaAsFet downconverter tunes whole 420-450 MHz band. Two switch selected video & audio inputs... RCA phone jacks and 10 pin color camera jack. Xmit video monitor output. Over 1 watt pep RF output on one or two (add \$15) selected crystal controlled frequencies. 439.25, 434.0, or 426.25 MHz.

CALL OR WRITE FOR OUR CATALOG for more info or who is on in your area. We stock antennas, modules, and everything you need on ATV.

TERMS: Visa, MC, or cash only UPS CODs by phone or mail. Checks must clear bank before shipment. Price includes UPS surface shipping in cont. USA, others add 3%. Transmitting equipment sold only to licensed Tech class or higher amateurs, verifiable in 1985 call book or copy of new license.


(818) 447-4565 m-f 8am-6pm pst.

P.C. ELECTRONICS
Tom W6ORG Maryann WB6YSS


2522 Paxson Lane
Arcadia CA 91006

✓ 111

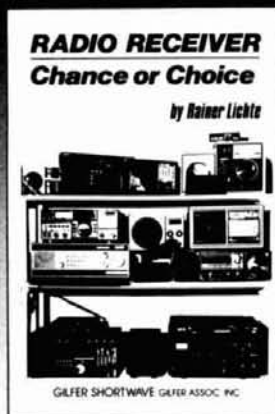HOW DO RECEIVERS REALLY PERFORM? READ THIS BOOK.



\$18.50
+ \$1.50 shipping
Available Sept.
Visa/Mastercards
accepted

You owe it to yourself to be informed. This comprehensive new book explores the receiver world through real-life tests conducted by internationally renowned radio engineer, Rainer Lichte. Read scores of no-axe-to-grind reviews about such famous brands as Panasonic, Sony, Yaesu, Kenwood, Drake, Eska, Hitachi, Grundig, Phillips, JVC, Zenith, Dymek, ITT, Bearcat - both old and new models, including ICOM R71A, Sony 2010, and Yaesu 8800. Explains the mysteries of technical specs, too. A must book.

GILFER SHORTWAVE

52 PARK AVE. • PARK RIDGE, NJ 07656 • Ph 201/391-7887

✓ 112

If the circuit is to be used at room temperature, such as in an HF or VHF/UHF receiver, no indicator should be required. Other status reporting features are possible and can be remotely monitored at the back end of the microwave receiver.

This synthesizer represents an effort of several weeks of design and "brassboarding." It began with the use of a 54S124 dual VCXO integrated circuit that was intended to work at 85 MHz, but was not successful for my application because of the crystal frequency restrictions and the limited upper frequency range for this device.

The new design will work to about 140 MHz (1680-MHz LO output when used with the N6TX multiplier, and beyond with other multipliers). Its limitations are the fabrication of crystals at VHF frequencies and the rather small size of L1 and L2 at the higher frequencies.

This design represents a practical approach to clean and stable local oscillators. Phase and amplitude noise have been measured to be at least -70 dB/Hz at ± 100 Hz from the desired carrier (see fig. 6). Discrete spurious components were better than -60 dB, while the wide band noise was at least -70 dB measured with a 10-kHz bandwidth.

These specifications depend on the application of sound RF design techniques and may vary according to the circuit components selected. Although a synthesizer layout is not provided in this article, compartmentalization of modules in a true "synthesizer fashion" is highly recommended.

As suggested at the beginning of this article, other than microwave applications of this synthesizer are possible. Among them are beat frequency oscillators (BFO) and fixed oscillators used in multi-loop fully synthesized HF and VHF/UHF receivers and transceivers, as shown in fig. 1. Figure 7A shows the block diagram of a 9-MHz BFO application as used in my HF transceiver. Figure 7B shows the circuit details of the digital to analog portion of the BFO which provides the proper injection to an active product detector/modulator in my transceiver. Many other applications are possible.

references


1. Cornell Drentea, WB3JZO, "New Trends in Communications Technologies: Radio Astronomy and the Search for Extraterrestrial Intelligence," *ham radio*, March, 1985, page 10.
2. Cornell Drentea, WB3JZO, *Radio Communications Receivers*, TAB, 1982, pages 158, 165, 168, and 181.
3. E. Roland Best, *Phase-locked Loops, Theory, Design, and Applications*, McGraw-Hill, New York, 1984, pages 70, 74, and 156-164.
4. Paul H. Shuch, N6TX, "Compact and Clean L-band Local Oscillators," *ham radio*, December, 1979, page 40.
5. Herbert L. Kraus, Charles W. Bostian, Fredrick H. Rabb, *Solid State Radio Engineering*, John Wiley & Sons, 1980, page 159.
6. Marion D. Kitchens, Jr., K4GOK, "VHF Prescaler for Digital Frequency Counters," *ham radio*, February, 1976, page 32.
7. Ulrich L. Rohde, DJ2LR, *Digital PLL Frequency Synthesizers, Theory and Design*, Prentice-Hall, 1983, page 209.
8. *VHF 300-MHz Prescaler, Application Note*, Fairchild, 1979.

ham radio

MUST LIQUIDATE At Far Below Dealer Cost! TOTAL Personal Computer System



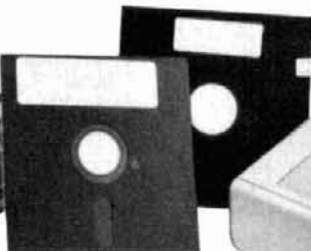**Factory Reconditioned with
Factory Warranty!**



**Carries easily
as a suitcase!
Plugs into 115V outlet**

GREAT GIFT IDEA!

**Sorry, we're not permitted to PRINT the famous brand-name.
BUT, we CAN "tell all" if you call us TOLL FREE: 1-800-328-0609!**

THE COMPUTER

Snap-on computer keyboard! 64K RAM, 20K ROM. Full-size typewriter keyboard. Upper and lower case letters, numerals, symbols, reverse characters. 2 cursor control keys, 4 function keys, programmable to 8. Music synthesizer with 3 independent voices, each with 9 octave range. Input/output ports accommodate . . . user, serial, ROM cartridge, joysticks, external monitor, phone modem.

Built-in disk drive! Intelligent high speed unit with 5 1/4" floppy disk recorder, 170K formatted data storage; 35 tracks, 16K ROM. Uses single sided, single density disk. Serial interface. Second serial port to chain second drive or printer.

Built-in color monitor! Displays 40 columns x 25 lines of text on 5" screen. High resolution, 320 x 200 pixels. 16 background, character colors.

Built-in ROM cartridge port! Insert ROM program cartridge. Multitude of subjects available in stores across the nation!

Original List Price **\$995.00**
Liquidation Priced At Only **\$388**

Item H-763-63631-00 Ship, handling: \$20.00

THE PRINTER

Print method: Bi-directional impact dot matrix.
Character matrix: 6 x 7 dot matrix.
Characters: Upper and lower case letters, numerals and symbols. All PET graphic characters.
Graphics: 7 vertical dots — maximum 480 columns. Dot addressable.
Character codes: CBM ASCII code.

Print speed: 60 characters per second.
Maximum columns: 80 columns.
Character spacing: 10 characters per inch.
Line feed spacing: 6 lines per inch in character mode or 8 lines per inch selectable. 9 lines per inch in graphics mode.

Line feed speed: 5 lines per second in character mode. 7.5 lines per second in graphics mode.
Paper feed: Friction feed.
Paper width: 4.5" to 8.5" width.
Multiple copies: Original plus maximum of two copies.
Dimensions: 13"W x 8"D x 3 1/4"H. Wt.: 6 1/2 lbs. Power: 120V AC, 60 Hz.

Original List Price: **\$200.00**
Liquidation Priced At **\$118**

Item H-763-63681-00 Ship, handling: \$7.00

THE SOFTWARE

"Easy Script" One of the most powerful word processors at any price! Cut re-typing, create documents from standard paragraphs, do personalized letters, see and change a document before it is printed. Instruction manual has extensive training section that simplifies use . . . even for someone who has never used a computer or word processor before!

"The Manager" A sophisticated database manager for business or home use. Business uses: accounts payable/receivable, inventory, appointments, task manager. Home uses: mailing lists, home inventory, recipes, collection organizer, investment tracking, checkbook balancing. School uses: research article index, gradebook.

Original List Price: **\$73.98**
Liquidation Price **\$24**

Item H-763-64011-03 Ship, handling: \$3.00

**BUY INDIVIDUAL UNITS OR
GET THIS ULTRA-FAMOUS
SYSTEM AT ONE LOW
PACKAGE PRICE!**

**TOTAL Personal Computer System
available at FAR BELOW dealer cost!**

Original List Price **\$1,293.00**

TOTAL PACKAGE PRICE **\$488**

Item H-763-64011-02 Ship, handling: \$24.00

Compatible with above Computer System (Not included in package price.)

JOYSTICKS (Set of 2)

Mfr. List: **\$59.90** pr. **\$18** pr.
Liquidation Price **\$18** pr.

Item H-763-63622-01 S/H: \$6.00 pr.

64K MODEM (Factory Reconditioned w/Warranty)

Mfr. List: **\$124.95** **\$19**
Liquidation Price **\$19**

Item H-763-63646-01 S/H: \$4.00



Credit card members can order by phone,
24 hours a day, 7 days a week.

Toll-Free: 1-800-328-0609

Your check is welcome!
No delays when you pay by check!

C.O.M.B. CO.®

Authorized Liquidator

14605 28TH AVENUE NORTH
MINNEAPOLIS, MINNESOTA 55441-3397

SEND ME THE ITEMS I HAVE LISTED BELOW

Price subject to change after 60 days. Sales outside continental U.S. are subject to special conditions. Please call or write to inquire.

Item No.	#	Item	Price	S/H
TOTAL				


C.O.M.B. CO.® Item H-763
14605 28th Ave. N./Minneapolis, MN 55441-3397

Send the items indicated at left. (Minnesota residents add 6% sales tax. Please allow 3-4 weeks delivery. Sorry, no C.O.D.)

My check or money order is enclosed. (No delays in processing orders paid by check, thanks to TeleCheck.)

Charge: MasterCard® VISA
Acct. No. _____ Exp. _____
PLEASE PRINT CLEARLY

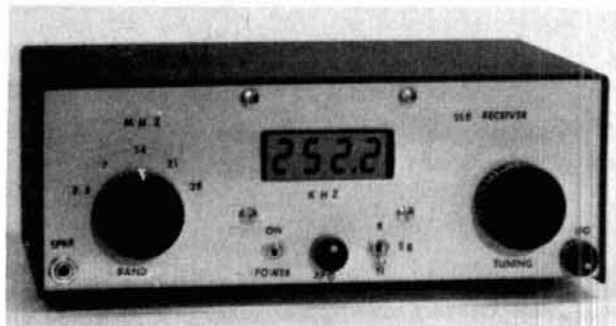Name _____
Address _____
City _____
State _____ ZIP _____
Phone _____
Sign here _____



10 through 80-meter homebrew receiver

Even the beginner
can build and understand
these circuits

If you're looking for a ham band receiver that combines good performance with simplicity of construction and low cost, read on — because this article is for you. This receiver covers the 80, 40, 20, 15, and 10 meter bands and can easily be modified to include the WARC bands or other shortwave segments between 3 and 30 MHz.

This project evolved in response to discussions with other hams about the deplorable decrease in the number of new Amateurs. Traditionally, a large part of our newcomers have come from the ranks of high school students; at one time, young people interested in the electronics almost inevitably gravitated to Amateur Radio because it was easy to get into, with little technical knowledge and only a small investment required. In recent years, the computer hobby with its inexpensive, easily accessible hardware — has provided similar easy entry.

Many hams have expressed the opinion that entry-level equipment has become too expensive and that construction articles now seem to deal with equipment that is complex, expensive to build, and requires a great deal of technical sophistication to construct. This started me to thinking about what it would take to build a receiver for the main ham bands that would provide good performance, yet be simple and inexpensive to build.

the VFO is important

In the 1950's and 60's most receivers used oscillators that switched coils for each band. In later years, however, multiple conversion schemes used crystal oscillators to establish each band and one non-switched oscillator as the variable frequency element to tune within each band. Many receivers now use frequency synthesized oscillators. These latter two concepts, while improving stability, unfortunately increase cost and complexity by a substantial amount.

Recalling more recent commercial rigs, such as the Atlas series, that used switched coil oscillators, I wondered how difficult it would be to design and construct a VFO that had acceptable stability for SSB reception (see fig. 1). After deciding it was worth a try, I chose 9 MHz as the IF because of the wide availability of good, inexpensive crystal filters at this frequency. For maximum utility I wanted coverage of both the CW and SSB portions of each band. The VFO covers 500 kHz on 80 through 15 meters and over 1 MHz on 10 meters. As we will see later, these ranges can be easily changed to suit the user's preference.

The choices for the IF and band ranges determine the VFO frequencies as follows:

band meters	VFO frequency MHz
80	12.5-13.0
40	16.0-16.5
20	5.0- 5.5
15	12.0-12.5
10	19.0-20.0

Varactor diode tuning of the VFO was chosen because it helps eliminate hard-to-find mechanical

By Robert Thompson, N1BFV, 4 Owens Brook
Circle, Simsbury, Connecticut 06070

variable capacitors as well as the mechanical linkage they require. It also allows size reduction by eliminating the bulk of a variable capacitor and allows significant reduction in the overall mechanical complexity of the VFO unit. One disadvantage of varactors, however, is that they require a tuning voltage as close to pure DC as possible. I therefore decided to use a 9-volt alkaline battery on the prototype. This led to thoughts of running an entire receiver on batteries, in the interest of even greater simplicity.

Since the VFO frequencies for 80 and 15 meters are close, one coil was used for both (see table 1). The VFO coils could have been switched electrically with diodes, but doing so would have taken about 30 mA

of additional current from the main battery supply. A rotary switch was chosen for current economy.

board construction

The VFO, the frequency counter, the BFO, the bandpass filter, and the IF unit are all constructed in a similar fashion. With the method used here you can actually build any unit in the same or less time than it takes to design and etch a printed circuit board. (One main advantage of etched boards, however, is saving time on successive boards — but since I seldom build more than one of any particular project, PC boards are not time-effective for me.)

I use epoxy material punched with holes on a 0.1-


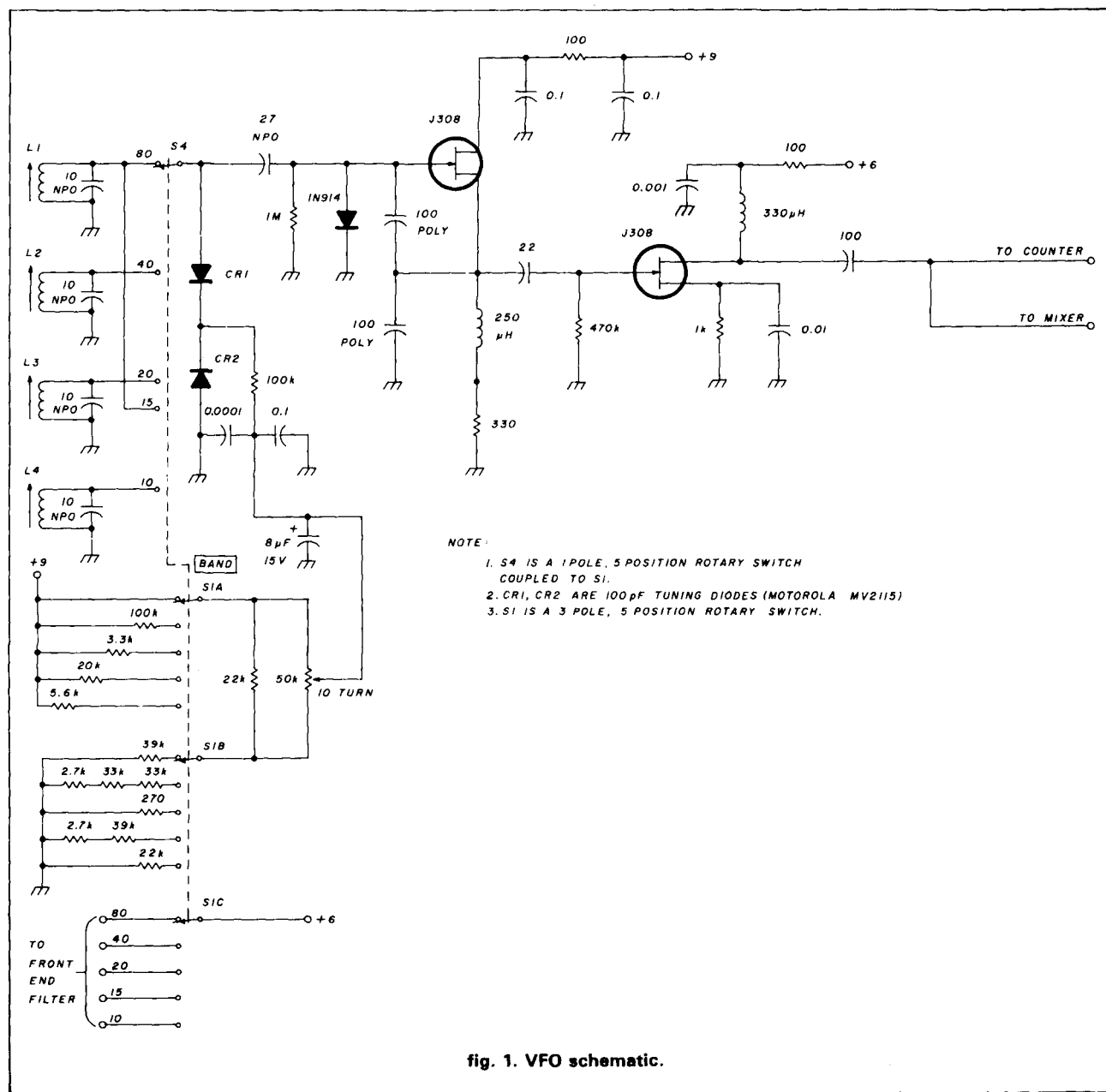


fig. 1. VFO schematic.

table 1. VFO coil data.

coil number	band	turns on 1/4" form*	frequency range (MHz)	wire No.
L1	80	21	12.5-13.0	26
L2	40	15	16.0-16.5	26
L3	20	48	5.0-5.5	32
L1	15		12.0-12.5	
L4	10	10	19.0-20.0	22

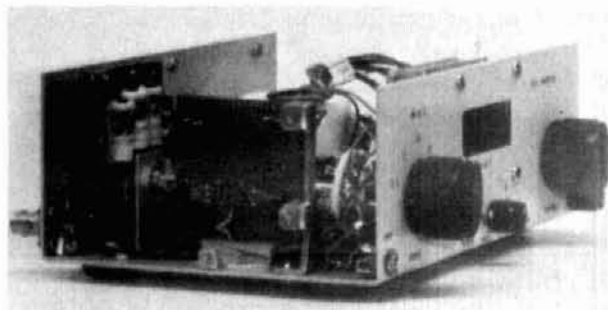*Coil forms Millen 69043 used but any good 1/4-inch (0.635 cm) ceramic form should be suitable.



Left side view shows bandswitch and ganged VFO switch. Vertical board in center is BFO; VFO board and coils are mounted vertically against rear panel.

inch grid and clad with copper on one side, widely available from mail order suppliers.* Insulated circular pads for IC pins and other components are cut with a pad cutter tool,* either by hand or with the tool in a drill.

For the VFO I disassembled a single-pole, six-position rotary switch and mounted a 3-inch (7.6 cm) square piece of the epoxy material between the switch wafer itself and the switch index mechanism. Three holes were drilled in the material: one for the switch shaft and two that coincide with the wafer mounting screws on the switch itself. (You may have to obtain mounting screws a little longer than those that come with the switch to allow for the 1/16 inch (0.16 cm) thickness of the copper clad board.)

Next cut appropriate pads for the coils and the VFO circuitry. Use T-44 push-in pins,* for terminals such as transistor connections and all input and output connections. The four coils are mounted on the front (non copper-clad) side of the board by passing their leads through and soldering to the pads on the other side which directly connect to the switch. The coil bodies are then covered with clear Silicone II, an adhesive that bonds them firmly to the board and prevents any movement of either the coil bodies or the windings on the coils. This is extremely important in that it is a significant factor in the frequency stability of the VFO. All wiring on the VFO should be direct and rigid, especially the jumper on the switch for the 80-meter position. Sound VHF wiring practices should be followed.

VFO adjustment

After wiring is completed, a test jig should be assembled as indicated to determine the values of the series voltage-dropping resistors necessary to have the tuning control, a 10 turn, 50 kilohm potentiometer, cover the desired range of frequencies (see fig. 2).

VFO adjustment proceeds as follows:

- Connect a frequency counter to the VFO output.


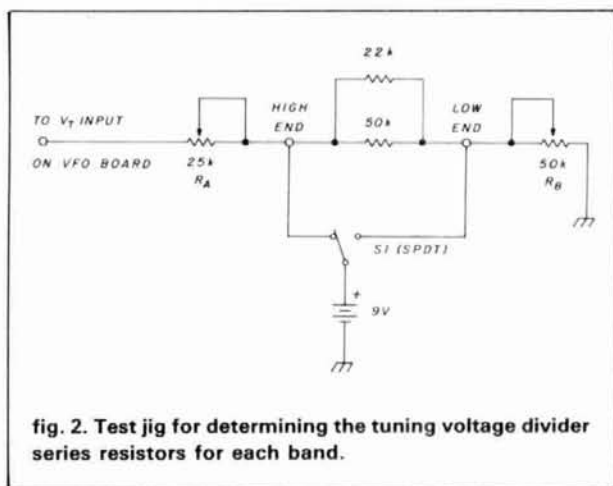


fig. 2. Test jig for determining the tuning voltage divider series resistors for each band.

- Set the VFO to the 10 meter position.
- Set S1 on the test jig to the HI position (at end of potentiometer R_A).
- Adjust R_A so that the VFO frequency is about 10 kHz above the upper limit wanted — for example, on 80 meters set R_A so that the VFO output is 13.010 MHz.
- Put S1 in the LO position at the end of R_B .
- Adjust R_B until the VFO output is about 10 kHz below the lower limit wanted — for example, on 80 meters set R_B so that the VFO output is 12.49 MHz.
- Put S1 back to the HI position and recheck the frequency. Since these settings interact it may be necessary to repeat the procedure. Measure the values of R_A and R_B and use fixed resistors of those values on the bandswitch.
- Repeat this procedure for the remaining band positions on the VFO. It may be necessary to adjust the coil slugs to obtain the required range. On 40 meters it may be necessary to place an approximately 68 kilohm resistor in series with the 9-volt source and R_A . Because it's unlikely that your unit will require the

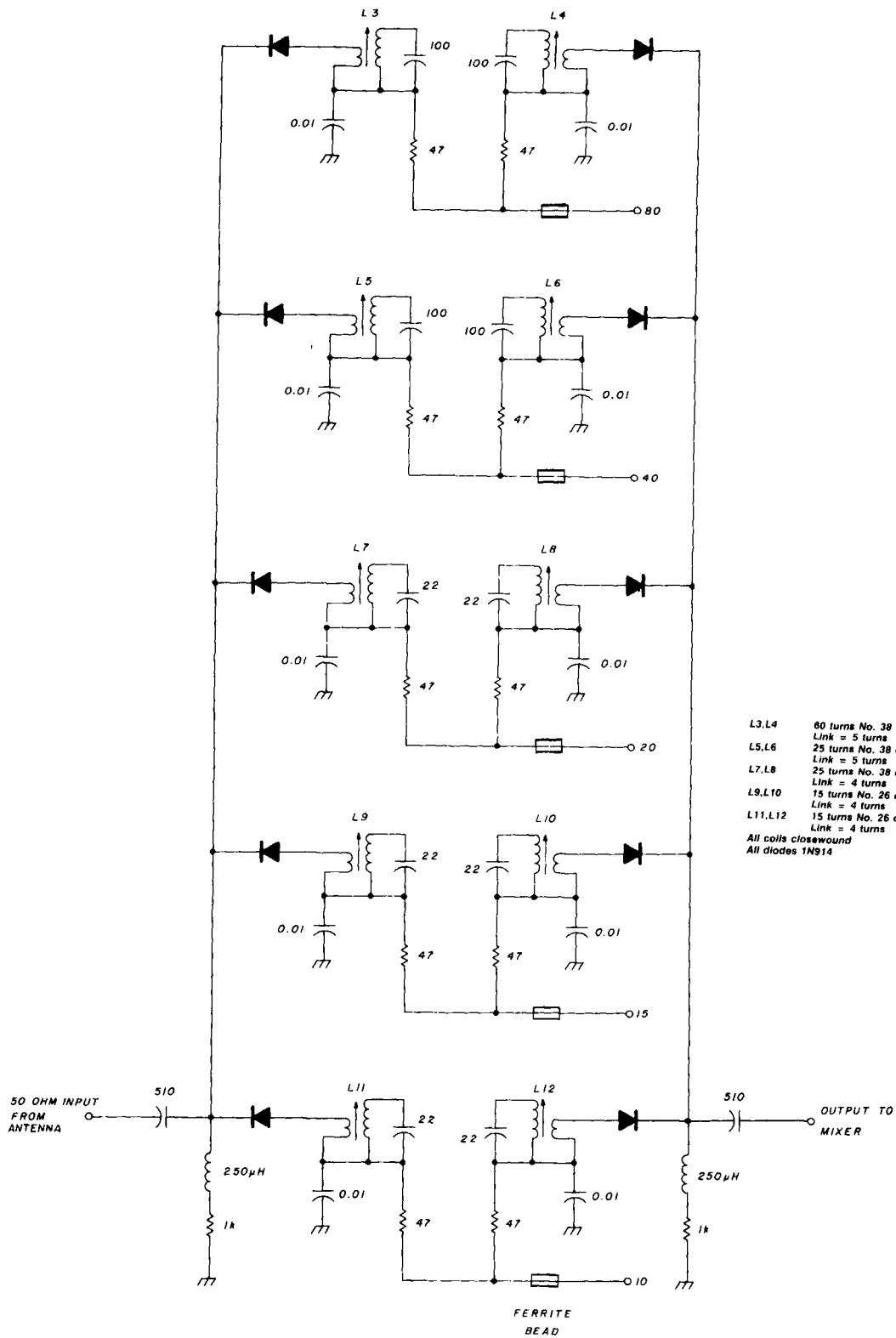*All items marked with an asterisk are manufactured by Vector, Inc.



- L3,L4 60 turns No. 38 on 1/4-inch diameter
Link = 5 turns
 - L5,L6 25 turns No. 38 on 1/4-inch diameter
Link = 5 turns
 - L7,L8 25 turns No. 38 on 1/4-inch diameter
Link = 4 turns
 - L9,L10 15 turns No. 26 on 1/4-inch diameter
Link = 4 turns
 - L11,L12 15 turns No. 26 on 1/4-inch diameter
Link = 4 turns
- All coils closewound
All diodes 1N914

fig. 3. Bandpass filter schematic.

same values of series resistors as mine because of differences that will occur in many components, I advise going through the procedure. I also recommend using alkaline batteries for both 6 and 9-volt supplies. Because of other connections to the 9-volt supply, six AA cells are used; the 6-volt supply consists of four D cells.

bandpass filters

These components are enclosed in a separate unit made entirely of copper-clad punched board. The two coils for each band are placed next to each other on 1/4-inch (0.635 cm) centers. Six volts applied to a band terminal forward biases the respective diodes and allows signals from the antenna to pass through the resonant circuit. The use of diodes, while drawing additional current, significantly reduces the mechanical problems associated with rotary switches.


Adjustment proceeds in the following order:

- Connect an antenna to the input and a receiver to the output.
- Set the receiver to 80 meters.
- Apply 6 volts DC to the 80-meter terminal.
- Set the receiver frequency 1/4 of the way up from the bottom of the band, at approximately 3.625 MHz.
- Adjust one of the 80-meter bandpass coils for maximum received signal (or noise).
- Move the receiver to a frequency 1/4 of the way down from the top end of the band, at approximately 3.875 MHz.
- Adjust the other 80-meter bandpass coil for maximum response.
- Repeat as necessary to compensate for interaction.
- Do the same for the remaining four bands.

These settings will establish filter response across the entire bands. If you're primarily interested in either SSB or CW, the coils can be peaked accordingly. If you don't have a receiver or cannot borrow one, it's possible to peak the bandpass filters with the receiver itself, once completed.

BFO

This unit is constructed on a separate board but could be placed on the IF board. Using an available crystal filter translated to a USB BFO frequency of 9.000 MHz and an LSB BFO frequency of 9.0030 MHz (see **fig. 3**). Normal (i.e., non-inverted) sideband in this receiver uses the 9.000 MHz BFO crystal, so no readout offset is necessary. In the reverse sideband position the readout will be off by 3 kHz. The BFO circuit uses series resonant crystals. L1 and L2 are 10.7 MHz IF transformer primary windings (4 μ H) with the

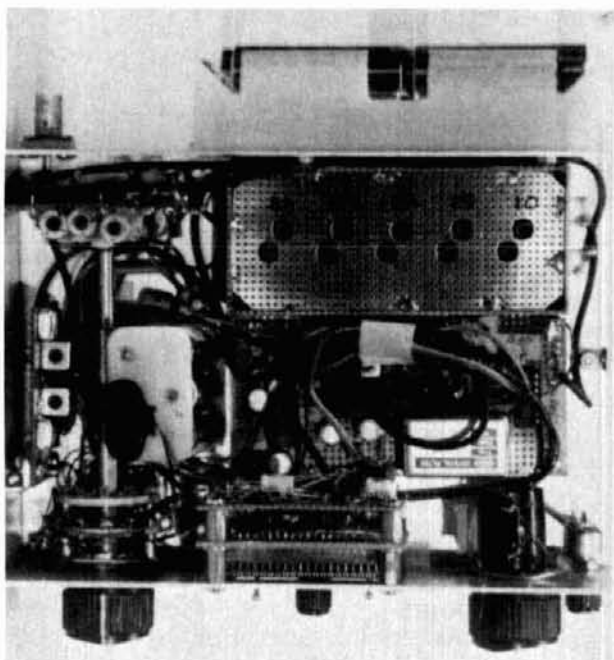

Top view shows bandpass filter (top left), IF strip (top center); VFO board (bottom left), BFO board (bottom center); and counter boards (right center). 6-volt battery pack is mounted at rear.

resonating capacitor removed. The 260 and 220 pF capacitors are polystyrene and the 100 pF capacitors are silver mica. To adjust, connect a counter to the output and apply 6 volts DC to the BFO oscillator desired. Adjust the corresponding series inductance for the correct output frequency.

IF board

This board contains the double-balanced mixer, crystal filter, IF amplifier, and audio stages (see **fig. 4**). The only adjustment here is to peak the slug in T1 for maximum signal. T1 is also a 10.7 MHz IF transformer with an external capacitor to bring it down to 9.0 MHz. RF derived AGC is internally generated in the Plessey SL6700 IC. U4 is a Texas Instruments TL442 double-balanced mixer. Connection of pins 3 and 12 result in a 500-ohm output impedance to match the crystal filter. If your filter has a different input impedance you may have to design an appropriate matching network. Application of 9 volts to the mixer is necessary to achieve adequate gain. U6 is an audio preamp and U7 provides up to a quarter watt of audio output to an 8-ohm speaker or headphones. The SL6700 has a maximum voltage rating of 7 volts.

frequency counter

This unit uses LCD and CMOS components because both draw little current and also because we need to count frequencies up to 20 MHz (see **fig. 5**). The least

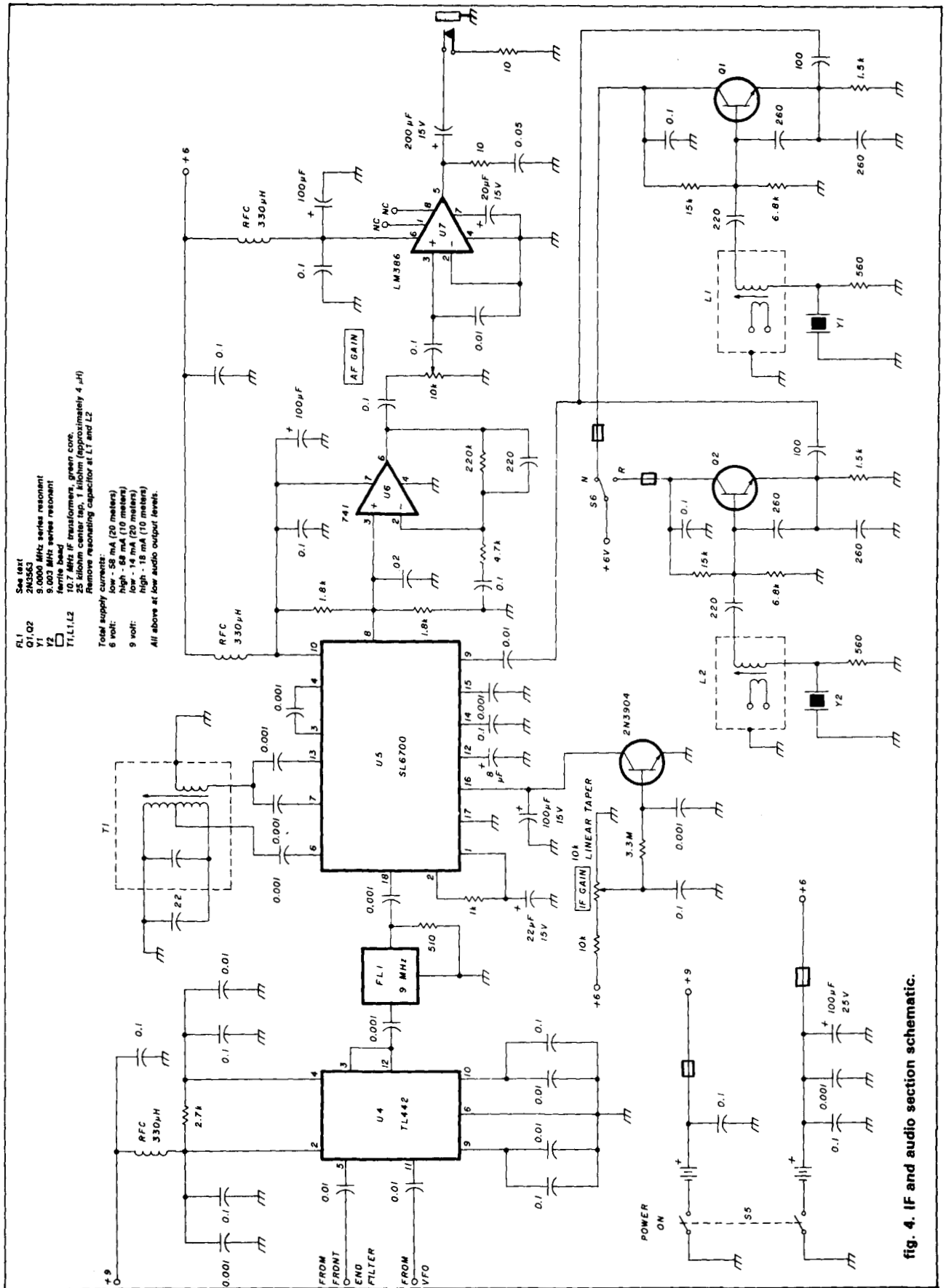


fig. 4. IF and audio section schematic.

Electronic Enclosures
Off Shelf O.E.M.

U.S. POWER CONVERTING CO./RELCO
Torrance, CA (213) 316-9984 * Canada (519) 696-2616

REGULATED POWER SUPPLIES

Magnetically Regulated Available from 5V to over 1000V with current range from 50 to over 100A.

Designed to supply large peak current demands.

Electronically Regulated Voltage range is 0 to 50V with a current range of up to 20A. Ideal for critical laboratory or service applications requiring tight regulation with low hum and noise.

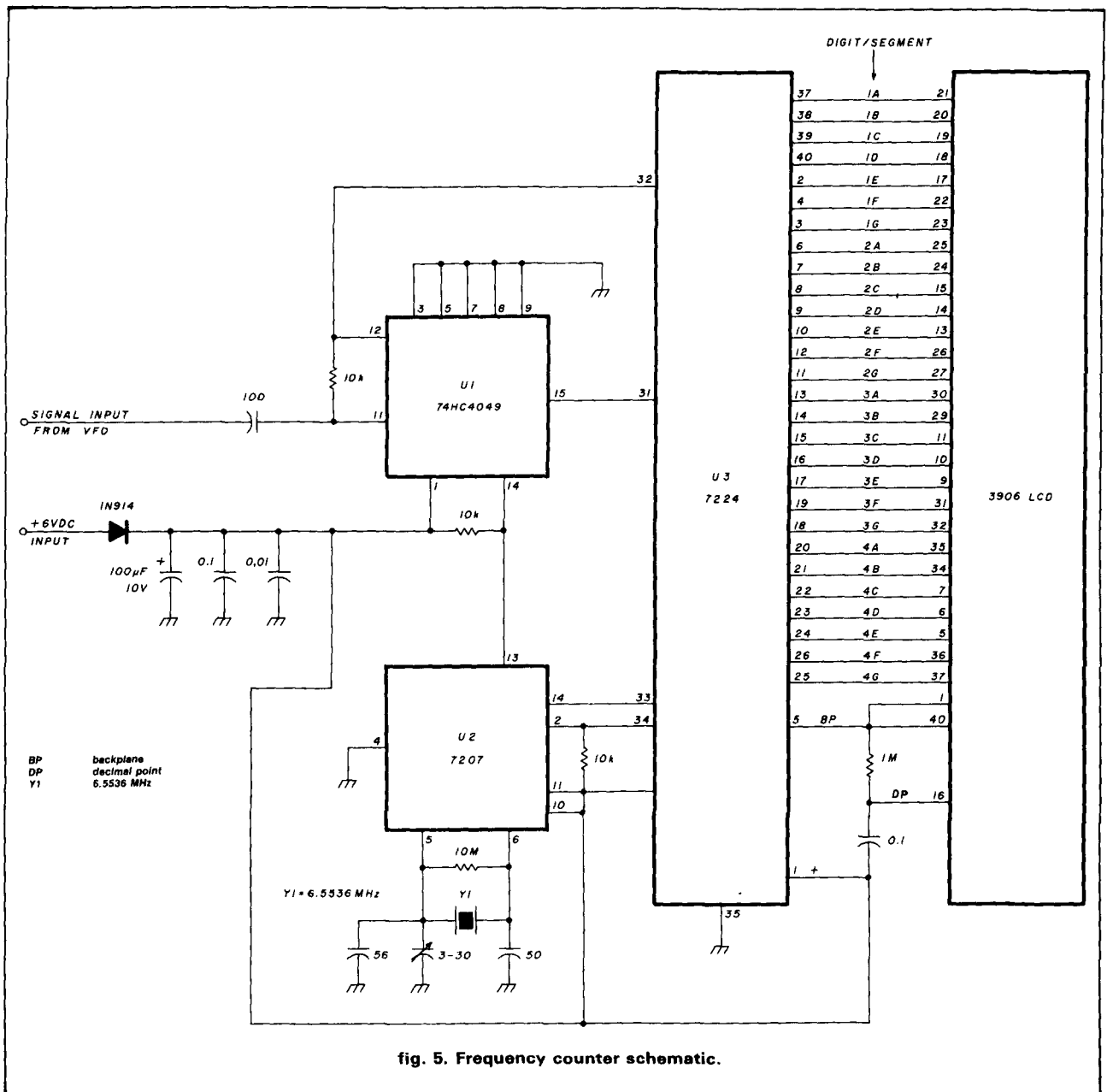


fig. 5. Frequency counter schematic.

significant digit reads out in hundreds of Hertz because of a 10 millisecond gate provided by U2 and its associated crystal. This, and the counter chip, U3, are Intersil ICs. (It's important to note that Intersil also manufactures a 7207 A. It's only through the use of the 7207 — without the "A" — and the specified crystal frequency that the 10 millisecond gate time can be obtained, so be careful when ordering.)

Note that U1 is a high-speed version of the CMOS type 4049. Because the latter type will not function up to 20 MHz, the 74HC4049 is used instead.

The liquid crystal display is a Hamlin type 3906. It's a little tricky to identify pin 1; to do so just hold the display in front of you and move it so that light reflects

off its face. You'll notice the outlines of the 8s that are the digits. Look for the three decimal points between the 8s. Rotate the display if necessary so that the decimal points are at the bottom. The left end pin on the top row is pin 1. These both connect to the display backplane (see table 2).

The counter is constructed on two pieces of perforated board 2-1/2 inches (6.35 cm) square, separated from each other and the receiver front panel by 1/2 inch (1.27 cm) threaded metal standoffs at each corner. The socket for the 7224 IC is a low profile type and is nested inside the socket strips for the LCD. These strips are merely the halves of a 40-pin IC socket separated by cutting it lengthwise with a hacksaw.

PICK A COMPUTER INTERFACE TO MATCH YOUR NEEDS

**COMPUTER PATCH™
MODEL CP-1**



MICROPATCH™ MODEL MP-1



COMPUTER PATCH MODEL CP-100



COMPUTER PATCH™ MODEL CP-1

The AEA Model CP-1 Computer Patch has earned a solid reputation for being the best overall interface value on the market today. We at AEA have now reaffirmed what our competitors already know; for the money, the CP-1 cannot be beat! That is why we have chosen to leave the popular CP-1 in our product line and to introduce new computer interface/terminal units with differing features and performance at different prices.

MICROPATCH™ MODEL MP-1

The new AEA model MP-1 Micropatch represents the best features and performance available for under \$140.00. Featuring true dual-channel filtering of Mark and Space tones with an AM detector and Automatic Threshold Correction (ATC) circuit, the MP-1 is in a totally different performance class than competitive units that often have only a single channel filter or no filtering at all.

The MP-1 also offers a high performance CW capability. With respect to the CP-1, overall performance is nearly as good; but the CP-1 offers a few more advanced features such as variable shift tuning, RS-232 option, and a more advanced tuning indicator.

COMPUTER PATCH MODEL CP-100

The new CP-100 Computer Patch offers all the following exciting features in addition to the CP-1 features:


- 170, 425, 850 Hz Calibrated Shifts for Transmit and Receive
- 75 to 1000 Hz Variable Receive Shift Range
- Normal and Reverse FSK Outputs
- Input AGC
- Direct Coupled Automatic Threshold Control
- Front Panel Squelch
- Discriminator Style Tuning Indicator
- Current Loop Option
- Built-in Monitor Speaker
- Baud Rate Switch
- Improved AM Detector

 **VHF
COMMUNICATIONS**

915 North Main Street
Jamestown, New York 14701 (716)664-6345



**Brings you the
Breakthrough!**

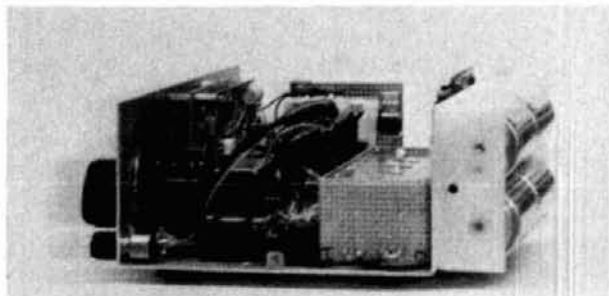

Right side view shows tuning pot and IF gain pot.

table 2. 3906 and 7224 designations.

3906 pins				7224 pins			
20	1B	1A	21	20	4A	4B	21
19	1C	1F	22	19	3F	4C	22
18	1D	1G	23	18	3G	4D	23
17	1E	2B	24	17	3E	4E	24
16	DP *	2A	25	16	3D	4G	25
15	2C	2F	26	15	3C	4F	26
14	2D	2G	27	14	3B	1/2	27
						digit	
13	2E		28	13	3A	CO	28
12		3B	29	12	2F	LZ1	29
11	3C	3A	30	11	2G	LZO	30
10	3D	3F	31	10	2E	C	31
						inhibit	
9	3E	3G	32	9	2D	count	32
						in	
8	4DP		33	8	2C	RST	33
7	4C	4B	34	7	2B	ST	34
6	4D	4A	35	6	2A	ground	35
5	4E	4F	36	5	BP	OSC	36
4		4G	37	4	1F	1A	37
3			38	3	1G	1B	38
2			39	2	1E	1C	39
1	BP	BP	40	1	+	1D	40

*Use this decimal point

These two sockets are mounted on unclad perfboard. The rear board is copper clad and contains the signal processing and gating ICs, U1, and U2. Because of the relatively high frequencies involved, this board *must* be copper clad.

Upon completion of the counter wiring connect a clip lead between pin 29 on U3 and ground. For test purposes this will cause all digits to appear as zeros with no signal input. Connect the 6 volts to the counter; application of voltage greater than 6.5 to U3 could destroy the IC. The purpose of the 1N914 in the counter is to reduce the 6 volts slightly. Four zeros should appear on the display with a decimal point between the least significant zero and the next one.

To calibrate the counter, run a short length of RG-174/U coax from the output of the BFO to the counter input. Connect an external frequency counter to the same point. Adjust the 30 pF trimmer capacitor at U2 until the last four digits of the two counters are

the same. Remove the clip lead from the 7224. Leading zeros will now be blanked on the display.

general construction notes

The receiver is built in an aluminum enclosure available from Radio Shack (see table 3). A slightly larger box would have allowed placement of the batteries inside. The band switch is a three-pole, six-position rotary mounted on the front panel. A coupling joins the end of its shaft to the VFO switch shaft. The 9-volt battery pack is attached to the chassis bottom with self-adhesive Velcro strips from Radio Shack. This sturdy arrangement allows easy removal for battery replacement. Four D cells in a holder mounted on the outside rear wall of the receiver supply 6 volts. A jack on the front panel provides audio for external speaker or headphones. All circuits and functional modules are extensively decoupled with ferrite beads and capacitive bypassing. The receiver has no birdies and the decoupling is probably a significant factor. Small diameter RG-174/U coax is used for all signal interconnections as well as to and from the volume control. The only totally shielded unit is the bandpass filter unit. The IF gain control carries DC and does not require shielding.


changes

Few designs remain unchanged for long. Were I to build this one again, I would consider making some

table 3. Parts and source list.

part	source
Hamlin 3906 LCD, MV2115 diodes, 74HC4049, J308, 741, LM386, 10.7 MHz IF transformers, Vector board	Circuit Specialists PO Box 3047 Scottsdale, Arizona 85267
Intersil 7224 counter IC	Jameco Electronics 1355 Shoreway Road Belmont, California 94002
6.5536 MHz crystal	Digi-Key Corp. 701 Brooks Avenue South Thief River Falls, Minnesota 56701
Intersil ICM7207 IC	Advanced Computer Products PO Box 17329 Irvine, California 92713-7329
Texas Instruments TL442 IC	Radiokit PO Box 411 Greenville, New Hampshire 03048
Plessey SL6700 IC	Circuit Board Specialists PO Box 969 Pueblo, Colorado 81002
BFO crystals	JAN Crystals 2400 Crystal Drive PO Box 06017 Fort Myers, Florida 33906-6017
Enclosure, battery holders, miscellaneous parts	Radio Shack

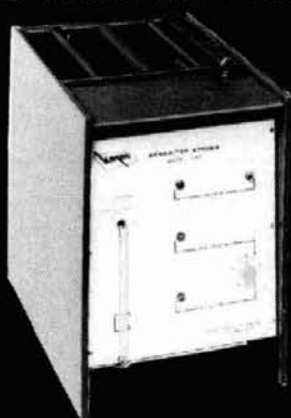QUALITY ETCHED PC BOARDS IN LESS THAN 5 MINUTES.



Convenient economical, high quality production of 12" x 12" panels is obtained using Kepro's Bench-Top Spray Etcher, only \$765. Kepro-the one stop source for all your Prototype and Short Run PCB needs.

kepro



Kepro Circuit Systems, Inc.

Write for full line catalog or call
1-800-325-3878 • 1-314-343-1630 (Missouri)

630 Axminister Drive • Fenton, MO 63026-2992

116

changes. First, this receiver is designed with VFO frequencies chosen so that, for conventional SSB practices, a 9 MHz USB filter and one BFO oscillator and crystal would probably be adequate for most users. Given the current drawn from the D cells, the batteries will probably last their shelf life; it may be possible to change to C cells to save weight and volume. Perhaps the two sets of batteries could be changed to one set of eight C cells with a voltage regulator for the 9 volts and a direct tap for the 6 volts. One change I would definitely make would be separate 80 and 15 meter VFO coils. This would make it much easier to set the required frequency range on both bands.

Other than the 10 pF NPO capacitors across each VFO coil, no further temperature compensation was done since stability at that point was adequate for my purposes. VFO stability could be further enhanced, especially at the higher VFO frequencies. I would also build the VFO in a separate, shielded enclosure, because there is a slight frequency shift when the receiver cover is removed. This small portable receiver meets all my original goals: simplicity, low cost, and good performance. These are exactly the characteristics which make this receiver ideal for newcomer and old-timer alike.

I'll be happy to respond to any questions accompanied by an SASE. (Send to Author's address — Ed.).

ham radio

ICOM
SPECIAL
IC-745
\$789.00

MA. ★

TEL-COM ★

Electronic Communications

Authorized Dealers For

KENWOOD &  ICOM

Also displaying the popular accessories needed to complete a HAM STATION . . .

ARRL PUBLICATIONS • AEA PRODUCTS • AMPHENOL
• ALPHA DELTA • ASTRON • AUSTIN ANTENNAS • AVANTI
• BELDEN • BENCHER • B & W • DAIWA • HAM-KEY
• HUSTLER • KLM • LARSEN • MIRAGE • ROHN
• TELEX/HY-GAIN • VIBROPLEX • WELZ • ETC.

KENWOOD
SPECIAL
NEW
TS-940S
with automatic
tuner
\$1765.00

OPEN SIX DAYS A WEEK

117

Telephone 617/486-3400, 3040

675 Great Rd., (Rte. 119) Littleton, MA 01460
1 1/4 miles from Rte. 495 (Exit 31) toward Groton, Mass.

Please enter my gift subscriptions
to HAM RADIO Magazine as follows:

FIRST SUBSCRIPTION \$19.95

TWO OR MORE SUBSCRIPTIONS \$16.95 EA. SAVE \$3.00
(you can also renew your own subscription at this low rate)

FIRST	Name _____ Call _____
	Address _____
	City _____ State _____ Zip _____
	<input type="checkbox"/> new <input type="checkbox"/> renewal

SECOND	Name _____ Call _____
	Address _____
	City _____ State _____ Zip _____
	<input type="checkbox"/> new <input type="checkbox"/> renewal

THIRD	Name _____ Call _____
	Address _____
	City _____ State _____ Zip _____
	<input type="checkbox"/> new <input type="checkbox"/> renewal

- Start or Renew my own HR subscription.
- Enclosed is a check or money order for \$ _____ for
_____ subscriptions. (use separate envelope)
- VISA MasterCard Bill me later
- Acct. # _____
- Expires _____ MC Bank # _____
- My Name _____ Call _____
- Address _____
- City _____ State _____ Zip _____

Prices U.S. only. Inquire about foreign rates.

Please
enter my
subscription



NO POSTAGE
NECESSARY
IF MAILED
IN THE
UNITED STATES

BUSINESS REPLY CARD

First Class Permit No. 1 Greenville, NH

Postage Will Be Paid By Addressee

**ham
radio**

Greenville, NH 03048



'Tis best to give as well as receive.

(especially before our January price increase!)

One Year/12 issues

\$ 19⁹⁵ SAVE*
OVER 10%


First Gift
OR

\$ 16⁹⁵ SAVE*
25%

**FOR TWO OR MORE SUBSCRIPTIONS OR EXTENSIONS
INCLUDING YOUR OWN**

*One-year subscriptions will be \$22.95 after January 1, 1986.

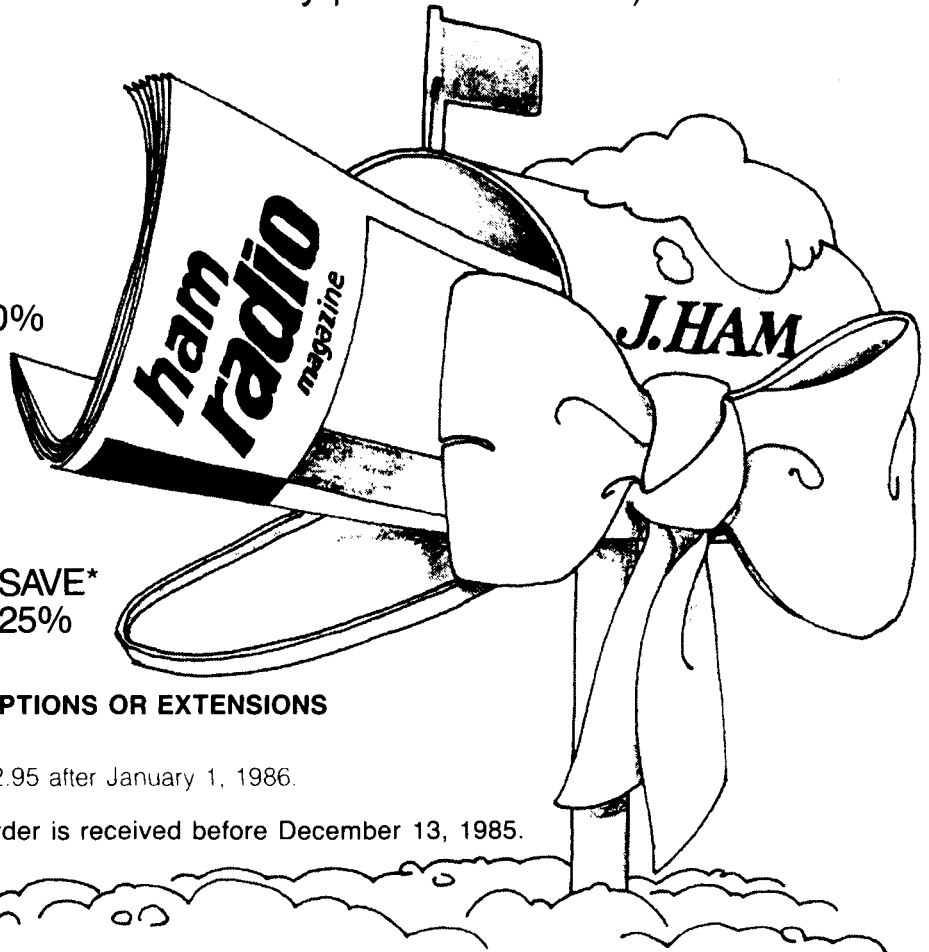A gift card will be sent if your order is received before December 13, 1985.



Giving Ham Radio is both fun and thoughtful.

And at the receiving end of a Ham Radio gift subscription, it's remembered all year long as a token of your friendship.

We have a super busy year planned for 1986, just take a look at a sampling of what your special Amateur friends(s) will see in their 12 big gift issues next year: The very latest in state-of-the-art projects and technical discussions, our Annual Antenna issue

in May and our Receiver issue in November, computers, monthly columns by Orr, Stonehocker, Reiser, and Guerri plus much, much more.

There's no time like the present to give the gift of HAM RADIO Magazine to that "hard to buy for" ham friend. While you're at it, why not treat yourself to another year of HR and save \$3 off our regular rate and \$6 off our new rate.

**Please use handy
bind-in card.**

**ham
radio**
magazine

Greenville, NH 03048

Prices US only

high dynamic range on 2 meters

In last November's VHF/UHF World column¹ we discussed high dynamic-range (HDR) with emphasis on circuitry for the 6-meter band. Judging from the correspondence I've received and the quantity of parts ordered from Proto Parts,* the interest in this subject is quite high. There were also plenty of inquiries for information about a companion 2-meter down-converter.

Further work has been conducted since reference 1 was published. Much of this new work, which primarily dealt with antenna pattern improvements, local oscillator phase noise studies and problems with the IF or receiver, was presented at the Dayton Hamvention.²

*Proto-Parts (formerly Proto Fab), 74 Wedgemere Drive, Lowell, Massachusetts 01852.

Since time is precious, I'll keep this month's column short and to the point, concentrating almost entirely on the design of a 2-meter HDR receiver down-converter as shown in block form in fig. 1. The material in reference 1 will not be repeated except as required. Further information on this very interesting subject will be published as time permits.

preamplifiers

Let's start by assuming that you've read references 1 and 2. Let's go directly to the preamplifier stage. Common semiconductor devices used on 2-meter preamplifiers include bipolar transistors, JFETs, dual-gate MOS FETs and GaAs FETs. All of these can attain excellent noise figures (less than 2 dB) and more than sufficient gain (12 to 30 dB!).

High gain is not too compatible with high dynamic range since the higher

the gain, the more likelihood of compression, overload, and IMD (inter-modulation distortion). Furthermore, overdriving the mixer, which results in a lower dynamic range, can result from too much gain in the stage preceding the mixer.¹

The HDR transformer-coupled lossless feedback preamplifier described in reference 1 can be used as shown to cover the entire frequency range from 1.5 to 200 MHz with almost no loss of dynamic range and only a slight increase (0.5 to 1.0 dB) in noise figure at the higher end of this frequency range. Hence this circuit is highly recommended for a 2-meter HDR preamplifier. However, it requires proper input and output filtering similar to the scheme shown on the 6-meter converter to prevent responding to the entire HF/VHF spectrum! (More on this shortly.)


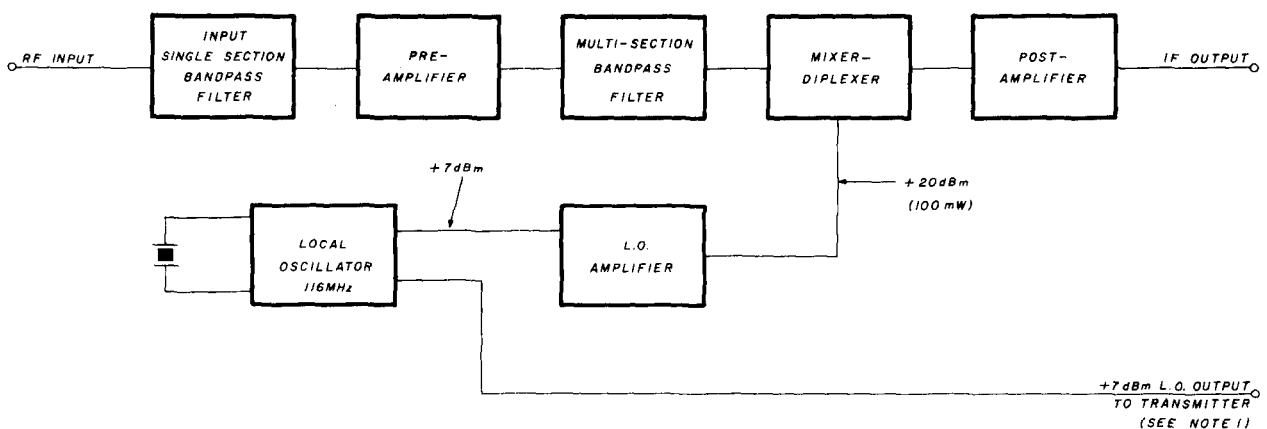
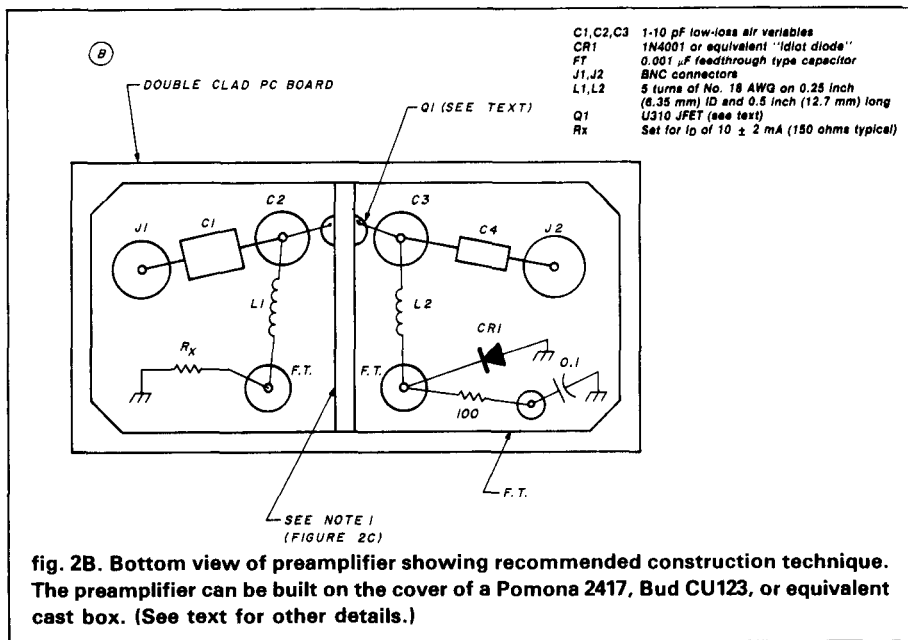


fig. 1. Overall block diagram of a 2-meter HDR receive-type down converter. Note 1: If the transmitter LO port is unused, terminate it with a 50-ohm load.

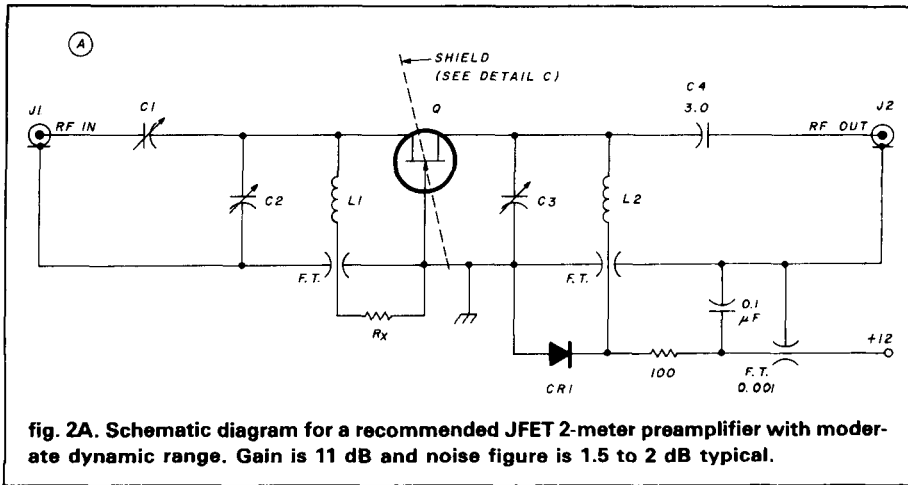

Dual-gate MOSFETs — and GaAs FETs as well — are not recommended for HDR since they have too much gain. Both are excellent for very low noise figures. The output compression point for GaAs FETS is poor for HDR (+6 to +8 dBm or 4 to 6.3 milliwatts).³ If you use them they should have built-in bypass relays so they can be switched out of the circuit if there are strong signals present that limit the dynamic range.

One of my favorite quick-and-dirty preamplifiers uses a JFET. I particularly like the U310, a low-cost, readily avail-


able JFET. *Caution: don't use the J310, a plastic TO-92 version of this device, above 100 MHz. The plastic package has too much internal inductance in the gate lead and the device will be potentially unstable at 2 meters and above.*



The U310 can deliver good performance from 50-450 MHz with a typical gain of 11 to 13 dB, a reasonable noise figure (1.5 to 3 dB), and very good dynamic range. The typical output compression point is not as high as the HDR lossless feedback circuit and is typically in the range of +10 to +14

dBm (10 to 25 milliwatts), which is more than sufficient for most applications.

A JFET preamplifier offers another advantage in that it has some "built-in" selectivity from its associated matching circuits so it can be operated without additional input or output filtering. Two of these amplifier circuits in cascade will usually have more than adequate selectivity to do the job as is. The circuit I use has been around many years and was discussed in reference 4. The recommended circuit and values for 2 meters are shown in fig. 2.

If you don't want to build all the extra filtering associated with the bipolar lossless feedback circuit and can sacrifice a small amount of dynamic range, you can use the JFET circuit shown in fig. 2. If only a single stage is used, the overall noise figure of the converter will be approximately 4 dB, hardly a problem for most types of operation. This sure beats many commercial transceivers that usually have a 7-10 dB or higher noise figure along with poor dynamic range and phase noise to boot! Two JFET preamplifier stages can be cascaded for moderate

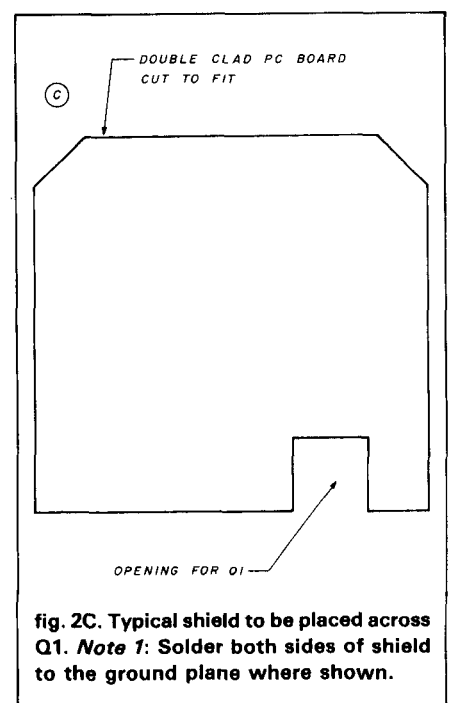

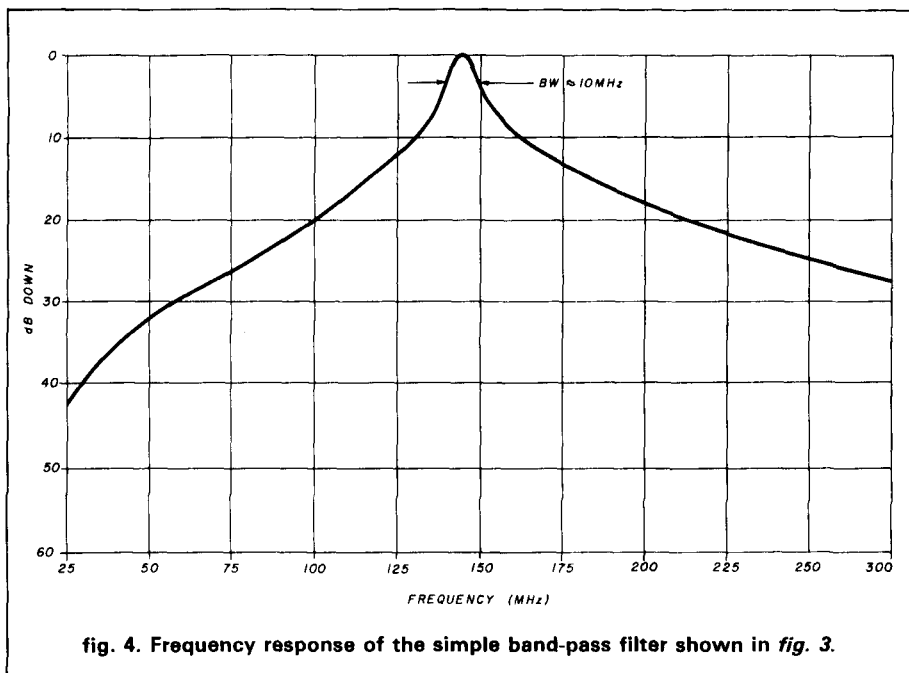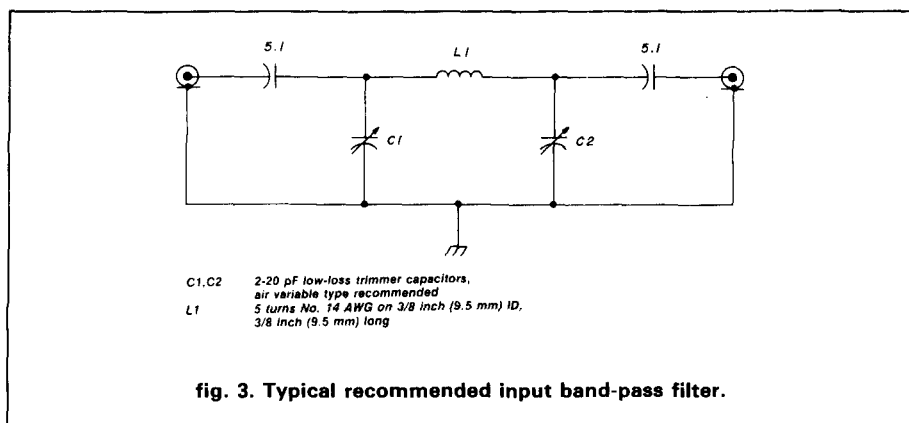

noise figure (1.5-2 dB) with a commensurate loss in dynamic range.

input filters

If the HDR lossless feedback preamplifier is used, input and output filtering are required. A simple single section bandpass should be used on the input for reasons discussed in reference 1. Typically speaking, the capacitance-coupled circuit in reference 1 has a sort of high-pass type of bandpass response,⁵ so it is not as effective with all the many types of high power RF emitters that are active on both sides of the 2-meter band.

Figure 3 shows an interesting filter topology.⁶ At first glance it looks like a Pi-network. It has one more component than the usual filter, a second tuning capacitor.

The advantage of this filter topology is that it has a symmetrical response about the center frequency with only a moderate loss, 0.3 to 0.5 dB typical. As shown in fig. 4, the half-power bandwidth is 10 MHz, while the 10 dB and 20 dB down bandwidths are about 30 and 110 MHz, respectively.

band-pass filters

Again, if a broadband preamplifier

is used, additional filtering will be required just ahead of the mixer as discussed in reference 1. A recommended three-section band-pass filter is shown in fig. 5. A plot of its filter characteristics is shown in fig. 6. It has a fairly symmetrical passband shape and only a moderate loss — 1.3 to 1.5 dB. Typical half-power bandwidth is 10 MHz, and the 10 and 30 dB down bandwidths are typically 15 and 33 MHz, respectively.

The loss in this band-pass filter will not degrade noise figure significantly if it is preceded by at least 9 to 10 dB of preamplifier gain. This filter should provide more than adequate selectivity for a high performance 2-meter receiving converter.

mixers

Various types of mixers were discussed in reference 1. The double balanced mixer (DBM) is highly recommended. The MiniCircuits Labs TAK-1H or equivalent is highly recommended for 2 meters. Other mixers, shown in table 1 of reference 1, are also acceptable. The lower drive DBMs such as the SRA-1 will reduce dynamic range but still may be more than sufficient for most applications.

The DBM circuit in reference 1 is very wideband and already covers frequencies through 500 MHz so it will not be duplicated here. *Don't leave out the diplexer; it's very necessary.* Also, since the 2-meter band is much higher in frequency, the use of a 14-MHz IF is discouraged since it won't offer sufficient image rejection without extensive filtering.

local oscillator

A Colpitts series-mode oscillator similar to the one discussed in references 1 and 7 is highly recommended. Since the typical IF for a 2-meter converter is 28-30 MHz, a 116-MHz local oscillator is recommended. *Don't use a 58-MHz oscillator with a frequency doubler; it will make breakthrough from TV and FM stations a potential problem. Don't be "penny wise and pound foolish." Remember — this is*

THE LAST WORD IN PERFORMANCE

**Superb audio quality • Virtually
no phase noise • 16-pole crystal
filter • Variable bandwidth
— PBT • Continuous tuning
audio filter plus notch filter •
Dual noise blanker •
Built-in memory keyer •
Low noise RF preamp •
Dual speed QSK • Five
function meter • Fully
AMTOR compatible •
No power “fold-back” into high
SWR • All solid-
state broad
band design •
Built-in
speech processor •
American
made, full
one year
warranty**



Corsair II
HF TRANSCEIVER

See your dealer or write

TEN-TEC, INC.
SEVIERVILLE, TENNESSEE 37862

CALL TOLL FREE FOR QUOTES

TNT RADIO SALES INC.

1-800-328-0250

1-612-535-5050

(IN MINNESOTA - COLLECT)

**EXPLOSION
OF
VALUES!**

ICOM KENWOOD
KANTRONICS
TELEX HY-GAIN
MIRAGE
HUSTLER
AEA
KLM
SANTEC
ROHN
KDK
MFJ
NYE VIKING
AMERITRON
WELZ
BENCHER
LARSEN BUTTERNUT

CALL NOW!

1-800-328-0250

FOR ABSOLUTE
**LOWEST PRICE
BUSTERS!**

**INVENTORY REDUCTION
PRICED TO GO!**

We must make room for your trade-ins. Check now for lowest prices on previously owned bench-tested equipment!

NEW! ICOM R7000 RCVR

Covers continuous 25 mhz to 2 ghz!
99 memories—scans—etc., etc.
Loaded with features. Available November, 1985.

VISA/MASTER CARD
FREE SHIPPING
ON MOST RIGS FOR CASH!



S.A.S.E. FOR OUR
"BENCH-TESTED"
USED EQUIPMENT LISTING

MON-FRI 9 AM - 6 PM CENTRAL TIME
SATURDAY 9 AM - 5 PM

4124 West Broadway, Robbinsdale, MN 55422 (Mpls./St. Paul)

118

Nano Fast Coax Protection

We have the right Impulse Suppressor to keep your system up and operational.

Over 36 Models From DC to 2.5 GHz.
50, 75, 93 and 300 Ohms
Bulkhead Mountability
20,000 Amp capability
Throughput Energy in μ J.
0.1 dB loss • 1.1 to 1 VSWR

Protectors

- GaAs Fet Front End
- Cellular Transmit
- DC Injector/Pickoff for Tower Top Preamp
- Cable TV
- Closed Circuit TV • NEMP
- Marine
- Military
- Coaxial Data (TwinAx)
- Power Supplies-120VAC.
- Power Line • Microwave
- Telephone Line
- Voltage Breakdown Tester

SHOULDN'T YOU HAVE A

POLYPHASER IMPULSE SUPPRESSOR ON YOUR LINE?

Phone: (702) 782-2511
RCA TELEX:
272718 POLYPHASER

PolyPhaser Corporation

1425 Industrial Way
P.O. Box 1237
Gardnerville, NV 89410

TOWERS by ALUMA

HIGHEST QUALITY ALUMINUM

- TELESCOPING (CRANK-UP)
- GUYED (STACK-UP)
- TILT-OVER MODELS

Easy to install. Low Prices.
Crank-ups to 100 ft.

EXCELLENT FOR AMATEUR COMMUNICATIONS



Mobile Trailer Type



Mobile Truck Type

Over 36 types aluminum and steel towers made—specials designed and made—write for details

SPECIAL Four Section 50 Ft. Van Mounted Crank-Up Alum Tower



Fixed Base

ALUMA TOWER CO.

BOX 2806HR
VERO BEACH, FLA. 32960-2806
(305) 567-3423 TELEX 80-3405

40' Alum. Crank-Up Model T-140


Mobile Trailer Type

Mobile Truck Type

SPECIAL Four Section 50 Ft. Van Mounted Crank-Up Alum Tower

Fixed Base

120

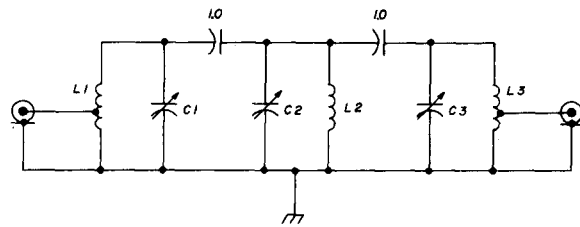

C1,C2,C3 2-20 pF trimmer capacitors
 L1,L3 4 turns No. 20 AWG 0.25 inch (6.35 mm) ID
 and 0.5 inch (12.7 mm) long. Tap
 is placed 1 turn up from ground end
 L2 Same as L1 without tap

fig. 5. Typical recommended three-section 2-meter band-pass filter.

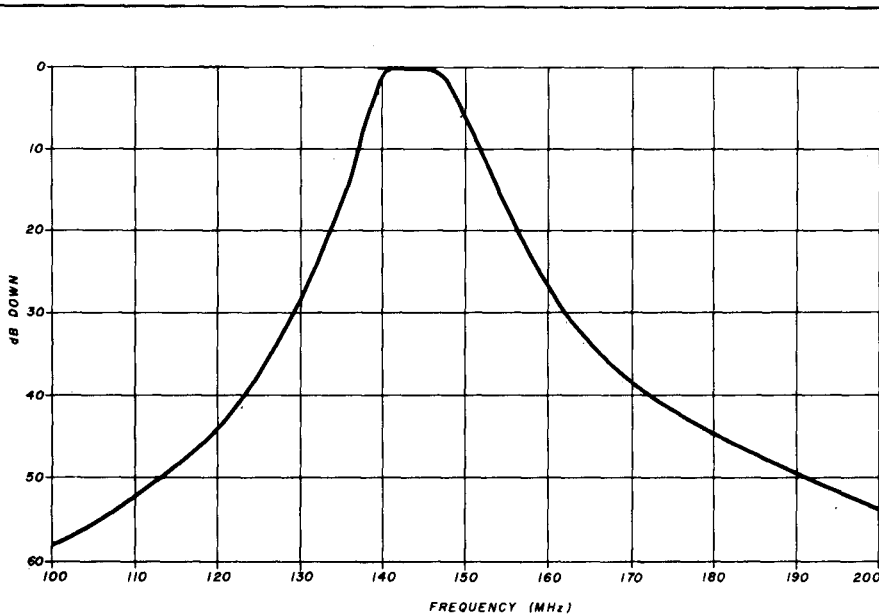


fig. 6. Plot of the frequency response of the three-section 2-meter band-pass filter shown in fig. 5.

a high-performance HDR receiving converter!

Since the frequency of the oscillator is much higher than in the 6-meter converter, the tuned components had to be modified. The final oscillator circuit and a suitable power amplifier are shown in figs. 7 and 8. It will provide the necessary 100 milliwatts of power. (More on this later.) Again, a low-level output is provided for a transmitting up-converter.^a

postamplifiers

The low-noise postamplifier using the lossless feedback circuit describ-

ed in reference 1 is recommended without changes, so it won't be duplicated here. Note how the modular approach discussed in references 1 and 7 has paid off. If you have the mixer and post-amplifier from the 6-meter converter, all you have to do is to change the local oscillator and front end, and away you go on 2 meters.

construction tips

Once again, the modular approach is recommended, with each separate circuit packaged in a shielded box. The circuits can be built above a double-

clad printed circuit type of material as described in reference 1. The boards can be attached to the cover of the boxes with the connectors. This method provides excellent grounding, and the components can be soldered directly to the board where grounding is required.

The three-section band-pass filter must be carefully laid out so that mutual coupling will not cause pass-band ripple. This can be accomplished if the individual coils are all wound in the same direction and placed at least 1/2 inch (12.7 mm) apart.

The U310 preamplifier circuit, if used, should be carefully laid out with shielding in mind. First a hole should be drilled near one side of the center of the circuit through the PC board. Its diameter should be 0.191 inches (4.85 mm), the diameter of a No. 11 drill. Next, place the U310 in the hole upside down and quickly solder the gate lead to ground as well as the tab on the U310 can. This provides additional input to output isolation. Next place a shield with a notch for the transistor leads across the JFET to isolate the input and output circuits as shown in fig. 2.

Leads in the oscillator should be kept short, especially those going to the crystal and its associated components. Also, it's wise to place the oscillator in a box separate from the LO amplifier so that any heat generated by the amplifier will not affect the stability of the oscillator. This has a secondary benefit: if the oscillator is separate, it can be used directly with a standard (+5 dBm or 7 milliwatt) DBM until you upgrade to the high-level DBM.

tune-up

First connect all the modules together as a full converter per fig. 1. Then connect an appropriate 2-meter antenna to the input of the converter. If the oscillator is functioning, noise and possibly signals will be heard.

The local oscillator should be tuned for maximum output as indicated on an RF power meter. *Don't detune the oscillator for frequency "netting"; this*

**SIMPLEX / DUPLEX
AUTOPATCH**



NOVAX I
NOVAX II

**IT'S NOT JUST ANOTHER
AUTOPATCH**

NOVAX
MOBILE CONNECTION

YOUR OWN PRIVATE AUTOPATCH

NOVAX interfaces your standard 2 meter, 220, 450, etc. base station and telephone, using a high speed scan switching technique so that you can make and receive calls automatically from your automobile or with your HT. Easy installation. Use it as half duplex, using two transceivers, interface HF or other audio sources, remote switch emergency alert etc. etc.

FEATURES	NOVAX I	NOVAX II
• 1 touch Call Reception timer	YES	YES
• Up to 45 sec. in busy time	YES	YES
• Single digit Access Control	YES	NO
• DTMF (Touch Tone) phone connection	YES	YES
• 4 digit Access Control (Programmable)	NO	YES
• 1st Receiver	NO	YES
• LED Signal Displays	NO	YES
• Mounts standard alarm, scan, etc.	5" x 6" x 2"	10" x 6" x 1 1/2"
• Directly interfaces with Radios	NO	YES
• Rotator Dial System (with remote features)	NO	YES (Optional) \$39.95
• 20 mg Back Inverse autopatch	YES	YES
• Price	\$199.95 (NOVAX I) \$249.95 (NOVAX II)	\$299.95 (NOVAX II) \$349.95 (NOVAX II with Rotator)

NOVAX I, NOVAX II, NOVAX II with Rotator, NOVAX II with Rotator and Scan, NOVAX II with Rotator and Scan, NOVAX II with Rotator and Scan

© 1988, 1989, 1990 NOVAX I, NOVAX II, NOVAX II with Rotator, NOVAX II with Rotator and Scan, NOVAX II with Rotator and Scan

LIBRENT DEVELOPMENT CORPORATION, 4000 W. 15th St., Westborough, N.Y. 13860, or Phone 515-755-5116

✓ 122

**SYNTHESIZED
SIGNAL GENERATOR**



MADE IN USA

MODEL
SG-100F
\$429.95
delivered

- Covers 100 MHz to 199.999 MHz in 1 kHz steps with thumbwheel dial
- Accuracy +/- 1 part per 10 million at all frequencies
- Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate
- External FM input accepts tones or voice
- Spurs and noise at least 60 dB below carrier
- Output adjustable from 5-500 mV at 50 Ohms
- Operates on 12 Vdc @ 1/2 Amp
- Available for immediate delivery • \$429.95 delivered
- Add-on accessories available to extend freq range, add infinite resolution, AM, and a precision 120 dB attenuator
- Call or write for details • Phone in your order for fast COD shipment.

✓ 123

VANGUARD LABS
196-23 Jamaica Ave., Hollis, NY 11423
Phone: (718) 468-2720 Mon. thru Thu.

**DRAKE R-4/T-4X
OWNERS AVOID
OBSCOLESCENCE**

PLUG-IN SOLID STATE TUBES!
Get state-of-the-art performance.
Most types available

**INSTALL KITS TO UPGRADE
PERFORMANCE!**

- BASIC Improvement
- Audio Bandpass Filter
- Audio IC Amplifier


TUBES \$23 PPD KITS \$25 PPD

OVERSEAS AIR \$7

SARTORI ASSOCIATES, W5DA
BOX 832085
RICHARDSON, TX 75083
214-494-3093

✓ 124

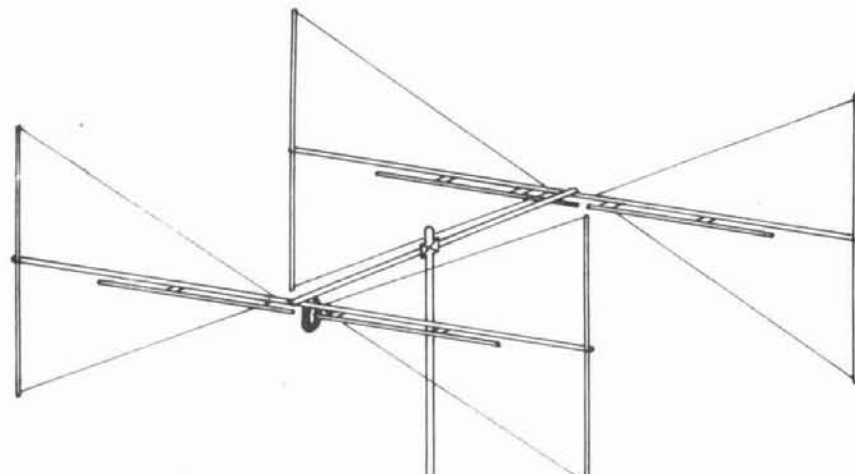Introducing the BUTTERFLY™ Beam from Butternut!




**The HF4B Compact, 2-element
Beam for 20-15-12-10 meters**

Compact Size
The HF4B's 12 1/2-foot elements and 6-foot boom are ideal for home-station use and for weekend retreats, condos, apartments and other places where oversized beams are prohibited. Its light weight (17 pounds) means it can be turned with a tv rotator, yet it is robustly constructed in the best tradition of our world-famous Butternut verticals.

Performance
The HF4B BUTTERFLY™ has not sacrificed performance for compactness. Its unique design with fanned elements and L-C circuits avoids use of power-robbing traps yet provided high-efficiency operating on all bands. The BUTTERFLY™ outperforms anything in its class.

The HF4B offers an SWR of 1.5:1 or less at resonance. Its 2:1 bandwidth is 200 kHz on 20 meters, 450 kHz on 15, 1.7 MHz on 10, and across the entire 12 meter band. And it will handle the legal power limits both CW & SSB. Gain is at least 3 dB on 20, 4.5 dB on 15 and 5 dB on 10 & 12 meters. Front-to-back is up to 18 dB on 10, 12 and 20m, and up to 15 dB on 15m.

See your authorized
Butternut dealer

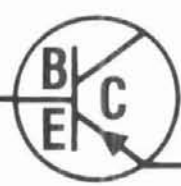


BUTTERNUT ELECTRONICS CO.
405 East Market Street
Lockhart, Texas 78644

Please send all reader inquiries direct.

Turn a few hours work into years of fun with Amateur Television.

Convert any TV receiver to a fast scan ATV monitor with the Communication Concepts ATV-2 converter. It allows you to monitor 430MHz ATV signals using channel 2, 3, or 4 on a standard TV set, without modification to the set. The circuit uses durable microstrip design for stability and simplicity. The combination of a dual RF stage, the microstrip design, and the hot-carrier diode double-balanced mixer reduces UHF TV intermod problems. An additional feature not found on other ATV downconverters

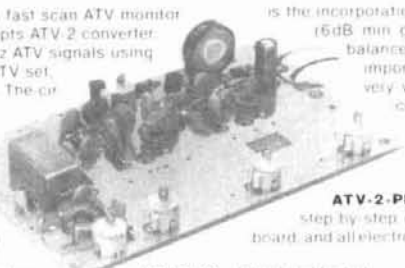is the incorporation of a *post amplifier* stage (6dB min gain) following the double-balanced mixer. This is especially important and most noticeable on very weak signal reception. The converter requires an external 12 volt DC regulated power supply at 50 milliamps.




ATV-2-PK Kit includes detailed step-by-step instructions, printed circuit board, and all electronic components as shown
\$44.95
\$59.95

ATV-2-W Wired and tested

VISA **CCI Communication Concepts Inc.** **MasterCard**

2648 North Aragon Ave. • Dayton, Ohio 45420 • (513) 296-1411

✓ 125

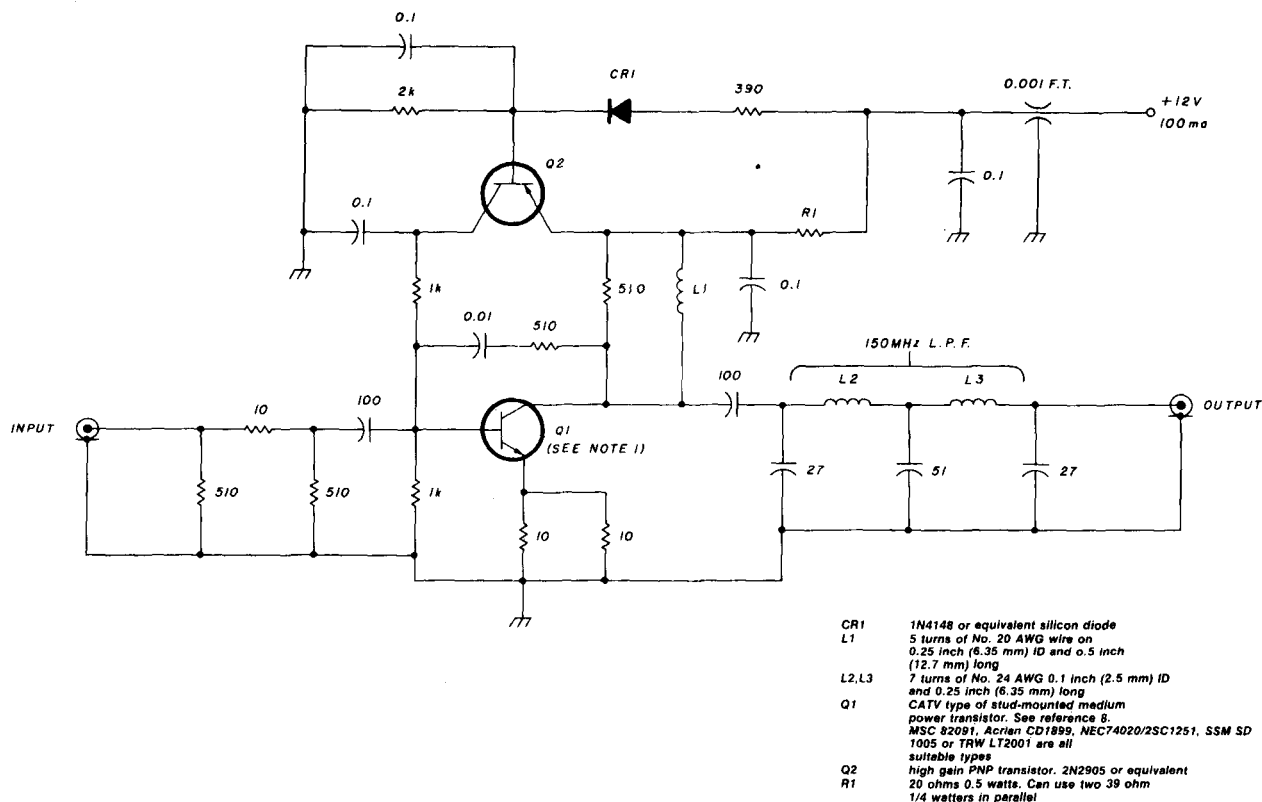

- CR1 1N4148 or equivalent silicon diode
- L1 5 turns of No. 20 AWG wire on 0.25 inch (6.35 mm) ID and 0.5 inch (12.7 mm) long
- L2,L3 7 turns of No. 24 AWG 0.1 inch (2.5 mm) ID and 0.25 inch (6.35 mm) long
- Q1 CATV type of stud-mounted medium power transistor. See reference 6. MSC 82091, Acrlon CD1899, NEC74020/2SC1251, SSM SD 1005 or TRW LT2001 are all suitable types
- Q2 high gain PNP transistor. 2N2905 or equivalent
- R1 20 ohms 0.5 watts. Can use two 39 ohm 1/4 watts in parallel

fig. 8. Recommended local oscillator amplifier for use with high-level DBM. Note 1: Bolt Q1 stud to cover of box to provide better heatsinking.

about anyone who's working into your area, if your antenna gain is sufficient.

In the presence of strong signals, you will immediately notice the improved performance. Now you'll see why I've previously stressed that the IF will ultimately be the limiting device! If you used the modular approach, the circuits can be swapped at will as you step up in performance. Also, should you ever suffer a failure, repair or bypassing is easily accomplished. It may even be smart to incorporate a bypass switching arrangement to switch out the IF postamplifier when high level signals are present.

summary

This month's column again stressed improved performance that is within the means and skill level of most Amateurs. Those who have tried these approaches have been pleasantly sur-

prised. It's nice to know that you're keeping up with the state-of-the-art! When good gear is used, contacts are more enjoyable and the weak ones are easier to work.

references

1. Joe Reisert, W1JR, "VHF/UHF World: High Dynamic Range Receivers," *ham radio*, November, 1984, page 97.
2. Joe Reisert, W1JR, "High Dynamic Range," 1985 Dayton Hamvention, April 27, 1985. (Copies are available from WA8OGS, for a nominal fee.)
3. Joe Reisert, W1JR, "VHF/UHF World: Low-Noise GaAs FET Technology," *ham radio*, December, 1984, page 99.
4. Joe Reisert, W1JR, "VHF/UHF World: Improving Meteor Scatter Communications," *ham radio*, June, 1984, page 82.
5. Joe Reisert, W1JR, "VHF/UHF World: The VHF/UHF Primer — An Introduction to Filters," *ham radio*, August, 1984, page 112.
6. M. Martin, DJ7VY, "A New Type of Preamplifier for 145 MHz and 435 MHz Receivers," *VHF Communications*, Spring Issue, 1978.
7. Joe Reisert, W1JR, "VHF/UHF World: VHF/UHF Receivers," *ham radio*, March, 1984, page 42.
8. Joe Reisert, W1JR, "VHF/UHF World: VHF/UHF Exciters," *ham radio*, April, 1984, page 84.

important VHF/UHF events

- November 2: Peak of Taurids Meteor Shower predicted at 0930 UTC
 - November 2-3: ARRL International EME Contest
 - November 3: Peak of Casseopids Meteor Shower predicted at 0930 UTC
 - November 12: EME Perigee
 - November 17: Peak of Leonids Meteor Shower predicted at 0300 UTC
 - November 23-23: ARRL International EME Contest
 - December 2: 7-11 PM Local, 2-meter SWOT Contest (contact K5JS for details)
 - December 11: EME Perigee
 - December 13: Peak of Geminids Meteor Shower predicted at 0650 UTC
 - December 21: Peak of Ursids Meteor Shower predicted at 2200 UTC
 - December 21: ± 1 month, winter peak of sporadic-E propagation
- ham radio**

Kantronics out "SMARTS" the competition

Presenting three intelligent, versatile, compatible terminal units.

"SMART" means an internal microprocessor is used to improve performance and add versatility. The "Smart" Kantronics TU's can transmit and receive CW/RTTY/ASCII/AMTOR or Packet when combined with your computer and transceiver.

Any computer with a serial RS232 or TTL port can connect directly to a Kantronics TU. A simple terminal program, like one used with a telephone modem, is the only additional program required. Kantronics currently offers Pac-term and UTU Terminal Programs for IBM, Kaypro, Commodore 64, VIC 20, and TRS-80 Models III, IV, and IVP. Disk version \$19.95. Cartridge \$24.95.

UTU The Universal Terminal unit (UTU) is the original "Smart" amateur TU. CW, RTTY, ASCII, and AMTOR can all be worked with this single unit. Switched capacitance filters and LED display tuning make using the UTU easy for even the Novice. 12 Vdc 300mv power supply required. Suggested retail \$199.95.

UTU-XT The UTU-XT is an enhanced version of the UTU. Programmable baud rates, tone frequencies, and tone shifts give special versatility. Automatic Gain Control and Threshold Correction circuits greatly enhance sensitivity and selectivity. A RTTY signal detect circuit mutes copy with no carrier, and the CW filter center frequency and bandwidth are programmable. Power supply is provided. Suggested retail \$359.95.



Packet Communicator Kantronics joined the Packet Radio revolution with the Packet Communicator. The unit is an AX.25/Vancouver compatible TNC with features not found in other units, including Direct TTL connection for easy hookup to the VIC-20 and Commodore 64. With our onboard modem you can select either Bell 202 or 103 tones for VHF/UHF or HF work. Power supply is provided. Suggested retail \$219.00.

For more information contact your local
Kantronics dealer or write:

Kantronics

1202 E. 23rd Street (913) 842-7745
Lawrence, Kansas 66046



ALINCO ELECTRONICS

The new name to look for in Amateur gear and the name to watch for innovation.

RF Power Amplifiers



ELH-730D
List \$156.95



ELH-230D
List \$89.95

* GaAsFet RX Preamp

Power Supplies



EP-3030 List \$208.00



EP-660 List \$69.00

Model	ELH-230D	ELH-260D	ELH-730D
Frequency Range	144-148MHz	144-148MHz	430-450MHz
Modes	All Mode (FM SSB CW)	All Mode (FM SSB CW)	All Mode (FM SSB CW)
Input Power	1W-3W	1W-3W	3W
Output Power	30W	50W	30W
Power Source	DC13.8V/4.5A	DC13.8V/10A	DC13.8V/7A
RX-PRE-AMP (About)	10dB	10dB	15dB
Input & Output Impedance	50Ω	50Ω	50Ω
Dimension (m/m) (W x H x D)	3.6" x 1.6" x 6.5"	3.6" x 1.6" x 8.5"	3.6" x 1.6" x 7.75"
N/W (About g)	18 oz.	24 oz.	23.5 oz.

	(With Two Meters)	(With Dual Meter)	(With Two Meters)
Model	EP-3030	EP-660	EP-5500
Output Voltage	About 10V-15V D.C. (With Voltage Adjuster on rear side)	About 10V-15V D.C. (With Voltage Adjuster on rear side)	About 10V-15V D.C. (With Voltage Adjuster on rear side)
Output Current	25A D.C. (Continuous) 30A D.C. (Max.) (50% Duty Cycle)	5.5A D.C. (Continuous) 6.5A D.C. (Max.)	50A D.C. (Continuous) 55A D.C. (Max.)
Ripple Voltage	Under 30mV (P-P) (Rated)	Under 30mV (P-P) (Rated)	Under 30mV (P-P) (Rated)
Power Consumption	770VA (Rated)	180VA (Rated)	1300VA (Rated)
Circuit Protection System	Automatic Current Limiting System shuts down in excess of 30 amps	Automatic Current Limiting System shuts down in excess of 6 amps	Automatic Current Limiting System shuts down in excess of 55 amps
Dimension (L x W x H)	13" x 9 1/2" x 6"	9" x 4 1/2" x 4"	18 1/2" x 12 1/2" x 7.5"
Weight	10 lbs.	8 1/2 lbs.	44 lbs.

many others from 6-55 amps

Watch for the introduction of our new 2 meter hand held available soon! Contact Alinco for your nearest dealer

Alinco Electronics Corp. P.O. Box 70007 Reno, NV 89570 (702) 359-1414

CASH IN on your old Channel Elements



For the past fifteen years, ICM has been replacing original crystals in elements sent to us by our customers. Our crystals carry an unusual guarantee . . . they are guaranteed FOREVER when used in the equipment for which they were designed.


Upon receipt, elements are tested, repaired, and parts replaced if required to assure they are working properly. The crystal is installed and checked for trimability. The output is checked to see that it meets original specs. Elements that are actively modulated are tested under load conditions. The element is subjected to temp vs frequency tests and compensated using computer controlled test chambers. After compensation, all tests are repeated to insure proper operation of the element.

Please call or write for more information




International Crystal Manufacturing Co., Inc.

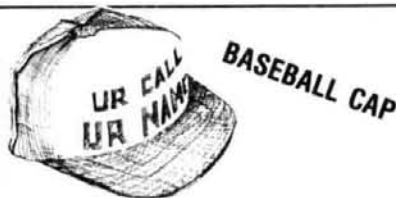Box 26330 Oklahoma City, OK 73126-0330
(405) 236-3741 Telex 747-147



How about an attractive **BASEBALL** style cap that has name and call on it. It gives a jaunty air when worn at Hamfests and it is a great help for friends who have never met to spot names and calls for easy recognition. Great for birthdays, anniversaries, special days, whatever occasion. Hats come in the following colors: **GOLD, BLUE, RED, KELLY GREEN.** Please send call and name (maximum 6 letters per line).

UFBC-81 **\$6.00**

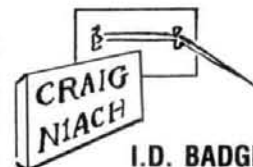

I.D. BADGES

No ham should be without an I.D. badge. It's just the thing for club meetings, conventions, and get-togethers, and you have a wide choice of colors. Have your name and call engraved in either standard or script type on one of these plastic laminated I.D. badges. Available in the following color combinations (badge/lettering): white/red, woodgrain/white, blue/white, white/black, yellow/blue, red/white, green/white, metallic gold/black, metallic silver/black.

UID Engraved I.D. Badge **\$2.50**

Please Enclose \$1.00 to cover shipping and handling

ham radio **BOOKSTORE**
GREENVILLE, NH 03048

PACKET EVOLUTION

From
\$219.95
Suggested Amateur Net

ANOTHER BREAKTHROUGH FROM AEA

Packet + RTTY = Pakratt™ PK-64.

If you've read about packet, or are already into it, you know how exciting it is. With the hot new Pakratt PK-64 we've just brought a new dimension to packet. The Pakratt PK-64 is a complete, fully assembled and tested packet radio controller which, together with a Commodore 64 or 128 computer, can convert your shack into a packet operations center. And we've included a new version of our advanced MBA-TOR™ software to make it the first packet controller with AMTOR, Baudot, ASCII and Morse. But an even more exciting part of the Pakratt controller is its great price.

Incredibly Simple To Set Up

Just plug the Pakratt controller into the C-64's game cartridge slot, add a mic connector for connecting to your particular

transceiver, and you're set. If you're anxious to try it out, our new "quickstart" manual section can get you on the air in under ½ hour.

Simply Powerful

The versatile Pakratt controller shows messages and connect status simultaneously on your Commodore with a unique split-screen display. And it lets you



PK-64 shown with HF modem option. Computer not included.

send letter-perfect text from the text editor software while monitoring incoming messages. The 20K byte QSO buffer stores more than 20 video screens of text! Disk commands let you save

specific operating parameters for quick set-up for emergency services, clubs, and multiple frequency use. And the Pakratt controller's standard, TAPR style modem gives you 300 and 1200 baud operation with great HF/VHF performance.

We can't possibly list all of the important features of Pakratt here. But the absolutely best part of the Pakratt PK-64 is that it's at your dealer now. So stop reading, run down to your local dealer, and check Pakratt out. Because the real challenge will be to find one after the other hams see it.

Pakratt PK-64. Packet Power from AEA. At amateur radio dealers everywhere.



Advanced Electronic Applications, Inc.
P.O. Box C-2160
Lynnwood, WA 98036-0918
(206) 775-7373
Telex: 6972496 AEA INTL UW

The Problem Solver...

The RF Wattmeter Model 81000-A from Coaxial Dynamics, Inc. does more than provide accurate rf measurements. Testing of transmission lines, antennas, connectors, filters and related components can reveal unknown problems and assure optimum equipment performance.

The 81000-AK Watkit features this easy-to-read RF Wattmeter (pictured here), with its optional carrying case and an array of elements and accessories. Coaxial Dynamics elements can be purchased separately for use in other manufacturer's Wattmeters. For more information on the 81000-A Wattmeter or any of the complete line of Coaxial Dynamics RF products and OEM components please contact Coaxial Dynamics, Inc.



COAXIAL DYNAMICS, INC.

15210 Industrial Parkway, Cleveland, OH 44135 • (216) 267-2233
Outside Ohio, WATS: (800) Coaxial, Telex: 980-630

✓ 129

DIRECTION FINDING?

- ★ Interference Location
- ★ Stuck Microphones
- ★ Cable TV Leaks
- ★ Security Monitoring



- ★ VHF and UHF Coverage
- ★ Computer Interface
- ★ Speech Synthesizer
- ★ 12 VDC Operation

New Technology (patent pending) converts any VHF or UHF FM receiver into an advanced Doppler shift radio direction finder. Simply plug into receiver's antenna and external speaker jacks. Uses four omnidirectional antennas. Low noise, high sensitivity for weak signal detection. Call or write for full details and prices.

DOPPLER SYSTEMS, INC. 5540 E. Charter Oak, (602) 998-1151
Scottsdale, AZ 85254

✓ 130

CUSTOM COMMUNICATION CONSOLES

Personal, Commercial, Industrial & Governmental Applications

Any shape & size to fill a corner or a room. Special design features & services are:

- Replaceable front panel, for equipment changes.
- Precisely cut front panel holes by computerized equipment.
- Computer aided design for: Floor plan lay-out, & console design.
- Design assistance, on-site analysis & installation are available.

Constructed from plastic laminated birch plywood & black anodized aluminum extrusions.

Contact: Larry Kushner, WA6BKC/4, President
BCS, Inc., 5817 SW 21 Street, Hollywood, FL 33023 (305) 989-2371

✓ 134

POPULAR PA 19 Wideband Preamp

- Over 8,000 sold
- 0.5 - 200 MHz
- 19 dB gain
- 50 Ω in/output
- For receivers, counters, transmitter amp stages
- Built, tested & ready-to-go

ONLY \$9.95 + \$1 shipping

NEW POCKET SIZED 500 MHz Freq. Counter

- Fits in your shirt pocket
- Uses 1 9-volt battery
- 4 digit LED readout, 6 digit resolution
- 1 MHz - 500 MHz



• Great addition to shack and toolbox
ONLY \$49.95 + \$2 shipping

✓ 132

DIGITREX

1005 BLOOMER
ROCHESTER, MI 48063

WEST COAST DISTRIBUTOR

R. LUKASZEWICZ

20610 ALAMINOS DRIVE SAUGUS, CA 91350
(805) 252-6021

ham radio TECHNIQUES

Bill Over
W6SAI

the mystery of the tapered element

I received an interesting letter in the mail the other day. It seemed some of the DXers were having a lively discussion on the effects of taper on the elements of a Yagi beam antenna. Recently published information on tapered elements seemed to indicate that a severely tapered element could actually be longer than a half-wavelength yet still be resonant.¹

The letter writer concluded that it was reasonable to see that a "thick" element is shorter than a "thin" element, but it was beyond the realm of possibility that a tapered element could be longer than either a "thin" or "thick" element.

My friendly inquirer closed his letter by saying that a "longer-than-normal resonant element of the tapered variety contradicts the laws of Nature. Say it isn't so!"

the background

This was an interesting letter. Is it possible to have a tapered element physically longer than a half-wavelength at a given frequency, yet resonant at that frequency? A little insight into basic antenna theory might provide the answer. To quote the *ARRL Antenna Handbook*:²

The shortest length of wire that will resonate to a given frequency is one just long enough to permit an electric charge to travel from one end to the other and then back again in the time

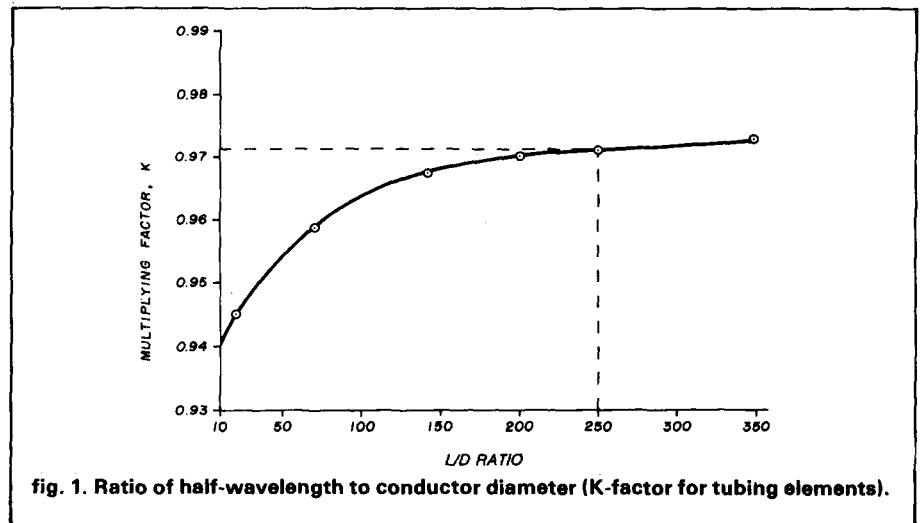


fig. 1. Ratio of half-wavelength to conductor diameter (K-factor for tubing elements).

of one RF cycle. If the speed at which the charge travels is equal to the velocity of light, 300,000,000 meters per second, the distance it will cover in one cycle will be equal to this velocity divided by the frequency in cycles per second, or

$$\lambda = \frac{300,000,000}{f(\text{Hz})}$$

in which λ is the wavelength in meters. Since the charge traverses the wire twice, the length of wire needed to permit the charge to travel a distance λ in one cycle is $\lambda/2$, or one-half wavelength.

Since the speed of light is a universal constant, either the frequency can be adjusted to a given wire length, or the wire length can be adjusted to a given frequency. Finally, by changing from the metric system to the English system and dividing the formula by


two, the familiar and useful formula for a half-wavelength in space is:

$$L = \frac{492}{f(\text{MHz})}$$

where L is length in feet of a half-wavelength for a frequency, f , in MHz.

The final step is to take into account the ratio of length to diameter of the conductor. The smaller the ratio, the shorter the antenna will be for a given electrical length. This is illustrated for tubing elements in the graph fig. 1.

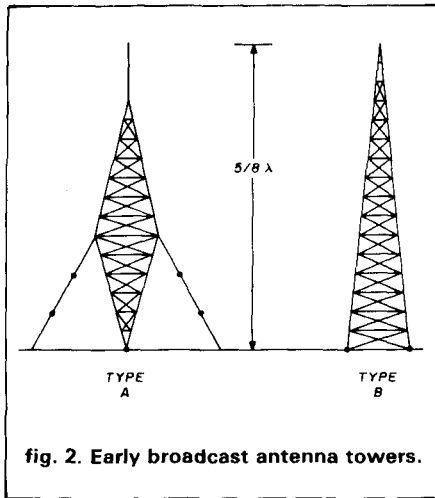A length-to-diameter ratio of about 4,000 to 1 is appropriate for a wire antenna in the HF range. A length-to-diameter ratio of, say 250 to 1 could apply to a resonant element made of aluminum tubing. The tubing element would be about 97 percent as long as a wire element for the same frequency. It is possible, then for a "thick" element to be quite a bit shorter than a



“thin” wire element, or than the free-space dimension of a radio wave of a given frequency. No argument so far, is there?

what the broadcasters found out in 1934

In 1924 Stuart Ballantine showed that, for a given amount of radiated power, the field strength at the horizon would be greatest when the vertical antenna (over a good ground) was 0.64 wavelength high.³ This was the concept behind the popular 5/8-wavelength vertical antenna.

This was of immense benefit to broadcast stations because it allowed them to have a signal about 40 percent greater than that provided by a 1/4-wave vertical antenna fed the same power. During the period between 1925 and 1930, many broadcast stations in America and Europe switched over to the new antenna design.

In attempts to obtain this optimum situation the broadcaster had to erect a tower more than twice as high as had been used previously. Two types of tower designs were available, as shown in fig. 2. The type A installation consisted essentially of two towers placed base-to-base and held in a vertical position by four or more guy wires. The type B design was more conventional, with the four tower legs mounted on base insulators. No guy wires were required.

After using these towers for some months it became apparent that the

results achieved were not consistent with theory. The promised gain failed to materialize, and the unwanted, high angle radiation was not appreciably reduced. In May, 1934, extensive tests were run on the radiation pattern of WABC (in Wayne, New Jersey), using an airplane to provide vertical pattern plots. The results were discouraging (fig. 3).

The next step was to measure the current distribution along the tower. In the case of the type A design, the 5/8 wavelength tower should have the current distribution shown by curve A of fig. 4. But the measured current actually resembled curve B! The current distribution did not resemble the sinusoidal curve predicted by theory, nor was there a current reversal approximately a 1/2-wavelength from the top end of the antenna! The top portion of the antenna carried very little current and the bottom portion of the antenna nearest the ground carried most of the current.



H.E. Gihring and G.H. Brown of the RCA Victor Company ran tests on antenna models built to scale for a wavelength of 4 meters. The tests on the models duplicated the results found by measurement on the larger broadcast antennas.⁴ The clue was that the current distribution on the tower was *non-sinusoidal*, and the rules that applied to normal antennas with sinusoidal current distribution did not apply to towers of irregular cross section!

Armed with this information, tests were run on the type A tapered antenna tower at WCAU (in Philadelphia, Pennsylvania). This tower has an additional 100-foot shaft protruding out of the top. They found little current in the shaft and, again, no reversal of current at the half-wave point along the tower.

The final check was to build a 4-meter model antenna out of wire having a constant cross-section. They reported “substantial agreement” between theoretical and observed values.

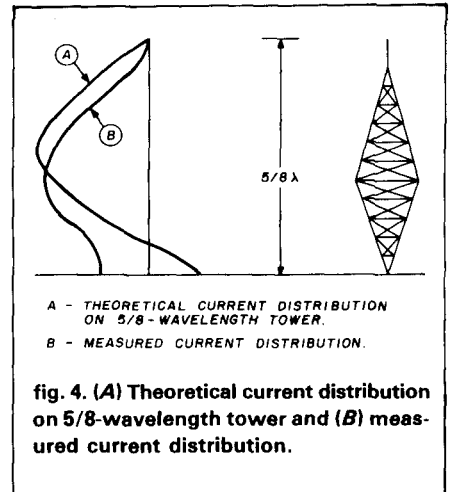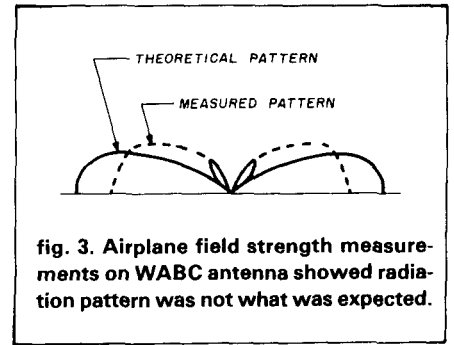problem defined how to solve it

Gihring and Brown had proved that it would be desirable to make the



cross-section of the 5/8-wave antenna constant if it were to obey the theoretical laws and deliver the anticipated power gain. They proved this in simple fashion. They made a wooden framework the same size as the maximum tower cross-section for the WCAU tower and dropped wires down to the corners of a square frame placed at the base of the tower (fig. 5). Voila! Even with as few as four wires, the current distribution on the tower approximated the desired sinusoidal waveform and the radiation pattern proved to be what was predicted for the 5/8-wave antenna height.

So there it was. By summer, 1935, broadcasters had started to shift away from self-supporting towers in favor of uniform cross-section, guyed towers. And these are the tower designs that are in use today by the majority of broadcast stations around the world.

the taper effect

Although they had a different goal

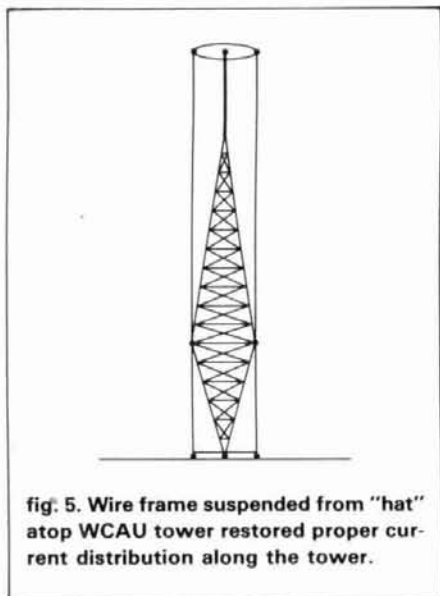


fig. 5. Wire frame suspended from "hat" atop WCAU tower restored proper current distribution along the tower.

in mind, Gihring and Brown had defined and described the so-called "taper effect" — that is, that normal assumptions about antenna length do not apply when the antenna element is not uniform in cross-section throughout its length. The antenna can be "thick" or "thin" and all is well, but when it's tapered, all sorts of strange things seem to happen!

the discoveries of W3MWC and W6KPC

While the tapered tower effect was well-known in the broadcast industry, it remained unknown to the Amateur fraternity in general. The taper problem did not apply to VHF beam antennas, it seems, because most of them were made of a single section of tubing for each element and no taper was present. Even conventional 6, 10, and 20 meter beams had little, if any, taper. For experimenters who built HF beams with tapered elements, the puzzling results and poor beam performance could not be linked to the conventional element dimensions in use.

As far as I know, the first discussion of element taper in Amateur literature was presented by my good friend Frank Clement, W6KPC.⁵ Frank found that his 14 MHz driven element ended up 17 feet 2 inches (5.23 meters) long because of the extreme taper. (Note

that the element is longer than the conventional electrical half-wavelength.)

There the matter rested until 1967, when Jim Berger, W3MWC, attempted to build a 3-element, 40-meter beam with tapered elements. In a letter to *QST*,⁶ Jim noted that he had to lengthen his elements to make the antenna work properly. The tapered driven element ended up 71 feet (23.6 meters) long (again, much longer than the conventional electrical half-wavelength.)

W2PV defines and solves the problem

Aided by data from W6KPC, I derived a simple chart that provided a correction factor for a tapered element, based upon the maximum and minimum diameters of the element. It proved to be practical, and a few beams with tapered elements were designed from my data with good results. However, I had no mathematical proof that my supposition was correct.

I pushed the matter to the back of my mind until the late Jim Lawson, W2PV, published a mathematical explanation of element taper in his monumental series of articles in *ham radio*.⁷ The computer program he suggested was quickly compared against my heuristic (cut-and-try) data and I was pleased to find excellent agreement. A variation of the original program has since been published in *ham radio*.^{8,9}

and the answer is

Yes, it is entirely possible for a "half-wave" element to be longer than predicted by conventional formulas *if* the element in question has a nonsinusoidal current distribution along it. One of the most common examples (there are others) is the simple tapered element having a non-uniform diameter along its length. But the means are now at hand to predict this aberration and to compensate for it.

the 80-meter Yagi at OH1RY

Build an 80-meter Yagi antenna?

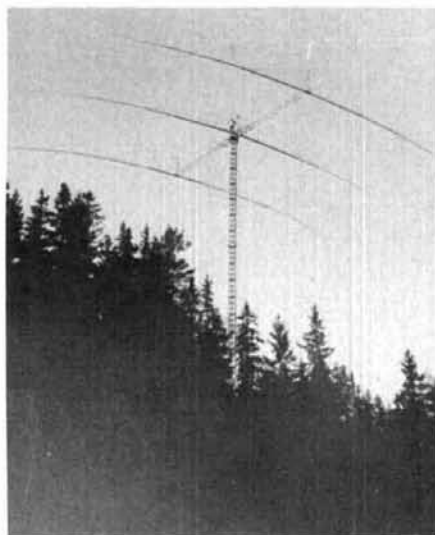


fig. 6. The 80-meter Yagi of Peter, OH1RY. If you look closely, you can see Peter standing atop the center of the beam.

Impossible. But Peter Kolehmainen, OH1RY did it! The antenna is shown in **figs. 6 and 7**. This monster is atop a 92-foot (30.6 meter) high tower placed on the crest of a 60-foot (18 meter) hill, making the beam about 150 feet (46 meters) above the surrounding territory. The boom length (including the tip guying supports) is 72 feet (22 meters) long. The antenna itself weighs about a half-ton (454 kg).

Element taper? The element is 6 inches (15.24 cm) in diameter at the boom, tapering to 1/2-inch (1.27 cm) diameter at the tips! As you can imagine, this provides some bizarre element lengths. The driven element is 135.5 feet (41 meters) long for resonance at 3.8 MHz. The first photo shows Peter squatting on the driven element, which is hinge-mounted to heavy insulating plates bolted to the side of the boom. The weight of the element is supported by the small "mast" and guy wire assembly behind him (I wonder where the photographer was standing when this picture was taken?)

If you look at the photo of the beam, you'll see Peter standing atop the antenna, dwarfed in size by the monster he has created!

Does the antenna work? Just listen for OH1RY and judge for yourself!

ISOPOLE™ "BREAKTHROUGH" BENEFITS

THE IDEAL OMNIDIRECTIONAL PACKET ANTENNA

- Greatest Simplex Range for Price
- Maximum Decoupling Minimizes Computer Hash
- No Feedline Radiation to Lock Up Computer

PERFORMANCE

- Low Vertical Radiation Angle
- No Feedline Radiation
- Wideband Matching Network
- Efficient Design
- Omnidirectional Pattern

DEPENDABILITY

- High Quality Materials
- Weatherproof Design
- Rugged Construction
- Advanced Engineering

PRICE & CONVENIENCE

- \$49.95 Suggested Retail
- Easily Installed
- Compact & Lightweight
- UPS Shippable
- Inexpensive TV Mast Support (not included)

ISOPOLE™ is available for 144 MHz, 220 MHz, 440 MHz. Ask for our spec sheet and radiation pattern plots, or visit your favorite AEA dealer for more information.

(Prices and specifications subject to change without notice or obligation)

AEA

Advanced Electronics Applications, Inc.
P.O. Box C-2160
Lynnwood, WA 98036
(206) 775-7373
TELEX: 6972496
AEA INTL UW

AEA BRINGS YOU THE
BREAKTHROUGH



fig. 7. Peter, OH1RY, atop the driven element of his 80-meter Yagi. Center of element is 6 inches (15.24 cm) in diameter!

good reading from Canada

Our neighbor to the north, Yuri Blanarovich, VE3BMV, is the editor of a publication that all Amateurs (especially DXers) should be aware of. A first-class production *Radiosporting* covers all aspects of contest and DX operating — antennas, equipment, station operation, stories of DXpeditions — the works! I enjoy every issue of this publication. If you're interested in it, contact Yuri at Box 65, Don Mills, Ontario, Canada M3C 2R6. (I wish somebody would explain the British and Canadian postal code system!)

references

1. Bill Orr, W6SAI, and Stu Cowan, W2LX, *Beam Antenna Handbook*. Available from Ham Radio's Bookstore, Greenville, New Hampshire 03048.

2. *The ARRL Antenna Book*, 14th edition, 1982, ARRL, Newington, Connecticut. (Available from Ham Radio's Bookstore, Greenville, New Hampshire 03048.)

3. S. Ballantine, "On the Optimum Transmitting Wavelength for a Vertical Antenna Over Perfect Earth," *Proceedings of the IRE*, December, 1924, pages 833-839.

4. H. Gihring and G. Brown, "General Considerations of Tower Antennas for Broadcast Use," *Proceedings of the IRE*, April, 1935, pages 311-356.

5. Frank Clement, W6KPC, "The Driven Beast," *QST*, May, 1958, pages 11-17.

6. Jim Berger, W3MWC, "Technical Correspondence," *QST*, February, 1968, page 55.

7. James H. Lawson, W2PV, "Yagi Antenna Design," *ham radio*, January, February, May, June, July, September, October, November, and December, 1980.

Special offer: All nine issues are available from Ham Radio's Bookstore for \$9.95 postpaid (U.S. only). All foreign orders FOB Greenville, NH 03048.

8. Alan Hoffmaster, WA3EKL, "Designing Yagis with the Commodore 64," *ham radio*, June, 1985, page 59.

9. Walter J. Schulz, Jr., K3OQF, "Key to 3-element Yagi Design," *ham radio*, March, 1984, page 48.

ham radio

RECEIVE OSCAR 10 TELEMETRY



Complete Kit

\$134.95

plus \$3.00
shipping and
handling

PSK DEMODULATOR—

decodes satellite's housekeeping status reports, environmental data collected and plain text bulletins

INPUT—

audio output of SSB receiver or cassette player.

OUTPUT—

RS232 compatible serial bit stream at 1200 baud.


1985-86
CATALOG
50¢



RADIO KIT
BOX 411H
Greenville, NH
03048
(603) 878-1033
telex 887697

131

Take it with you.

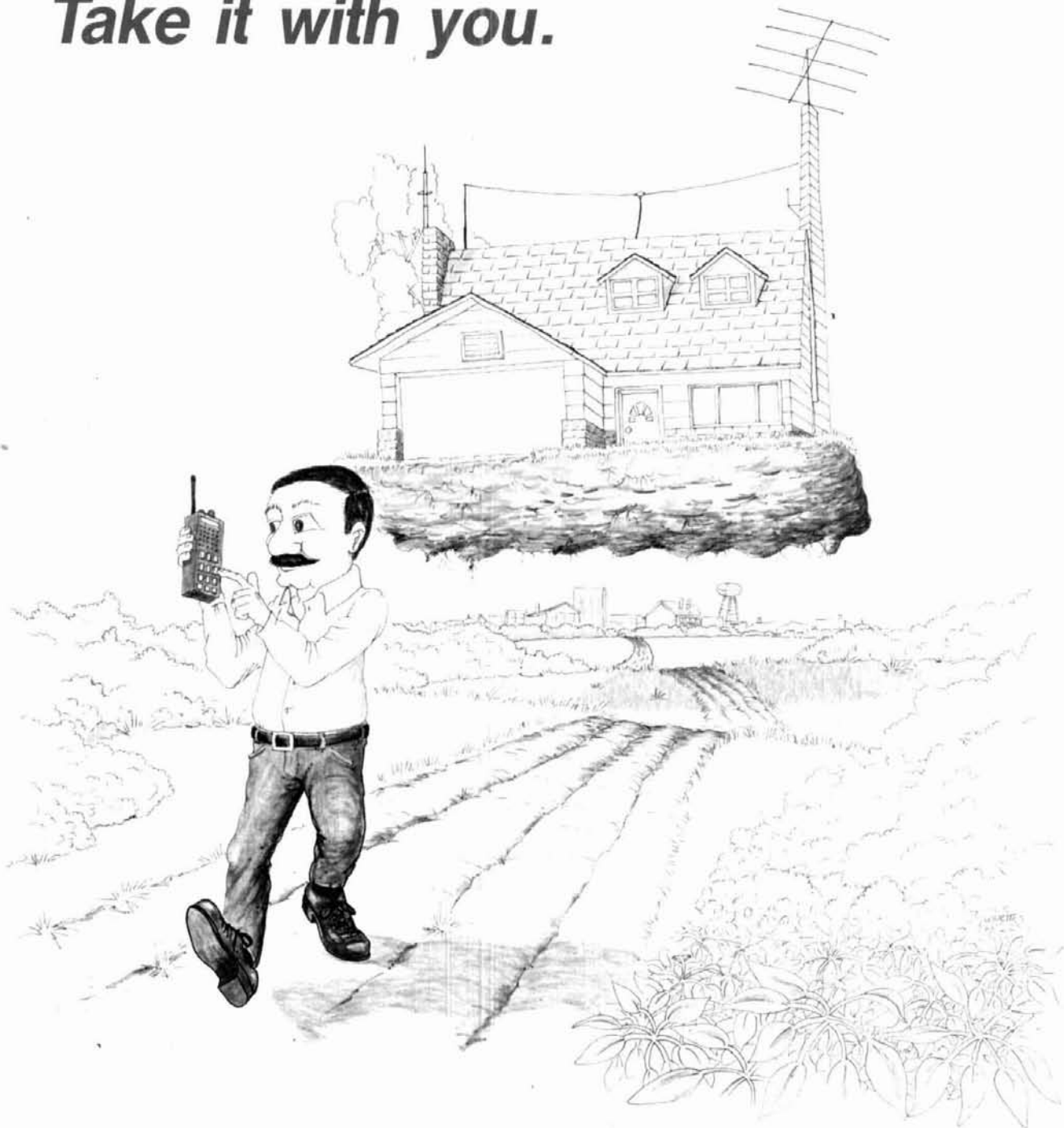

ShackMaster™ puts your home station in the palm of your hand. Whether portable, mobile, around the yard or around town you'll be linked through your handheld to your high performance equipment at home. Even call home from any Touch-Tone phone and operate.

Scan the bands, change modes, select antennas, turn gear on and off – all from your Touch-Tone keypad. Check into nets, work skeds, ragchew and DX without being tied down to the shack.

Exchange electronic mailbox messages with your family – like "I'll be late", or "All is OK". Or talk with your family directly through *ShackPatch™*, with you in remote control of your home station. Report traffic accidents or disabled motorists through your home phone while mobile or portable with *PersonalPatch™*.

All the power of your home station (and more) really can follow you anywhere... to find out more about ShackMaster™ just write, send us your QSL, or call and talk with us at 408-749-8330.

acc

advanced
computer
controls, inc.

10816 Northridge Square • Cupertino, CA 95014

(408) 749-8330

THOUSANDS OF SATISFIED
CUSTOMERS WORLDWIDE



HAM RADIO OUTLET

ALL MAJOR BRANDS IN STOCK

KENWOOD HAND-HELDS



TR-2600A Deserves its well-earned reputation as the leading HT

TH-21AT/41AT
"COMPACT"
Only 2 1/4" W. 4 7/2" H. 1 1/4" D.
Outstanding performers in an ideal package size



CALL FOR PRICE

TOLL-FREE PHONE

INCLUDING ALASKA AND HAWAII



MA-40 40' TUBULAR H.D. MAST

Regular \$745

SALE \$549

MA-550 55' TUBULAR H.D. MAST

Regular \$1245

SALE \$899

•Why You Should Buy•

1. Will handle 10 Sq. Ft. 50 mph
2. Pleases neighbors with tubular streamlined look
3. In stock for quick delivery
4. Other models at great prices



FREE SHIPMENT

MOST ITEMS. U.P.S. SURFACE.



SIMPLEX-REPEATER-SATELLITE



IC-271H
2 METERS • 100 WATTS
• ALL-MODE

IC-471H

430-450MHz • 75 WATTS
• ALL-MODE



CALL FOR YOUR SPECIAL PRICE



ICOM IC-27A

SUPER-COMPACT
2 METER MOBILE



ALSO *IC-27H HIGH POWER VERSION
AND IC-37A, 220MHz
IC-47A, 70CM **SAVE!**

CALL FOR LOW, LOW PRICE



TOWER
SALE



W-51 \$899
51' CRANK-UP 9 SQ'



ELH 23D 2 MTR
30 W

CALL FOR PRICE

THE VERY BEST DEAL ON EVERY COUNT!



YAESU

FT-757GX



FT-2700H

NEW!
2M/70CM
TRANSCIVER



FT-726R



FT-209RH

CALL FOR GREAT PRICES

KENWOOD TS-940S

TOP-OF-THE-LINE HF TRANSCEIVER

PAY REGULAR PRICE ~~\$1799.95~~



CALL FOR
YOUR LOW,
LOW PRICE

Free UPS Surface

THOUSANDS OF SATISFIED
CUSTOMERS WORLDWIDE



HAM RADIO OUTLET

ALL MAJOR BRANDS IN STOCK

ICOM IC-R71A

SUPERIOR GRADE
GENERAL COVERAGE
RECEIVER



Regular \$799
SALE! \$629.95
\$599.95

TOLL-FREE PHONE

INCLUDING ALASKA AND HAWAII

ICOM HAND-HELDS



IC-02AT IC-2AT IC-3AT
IC-04AT IC-4AT

AT GREAT LOW
LOW PRICES

FREE SHIPMENT
MOST ITEMS U.P.S. SURFACE.

ICOM IC-735

THE LATEST IN ICOM'S LONG LINE
OF HF TRANCEIVERS



CALL FOR LOW, LOW PRICE

ICOM IC-37A



220 MHz's BEST BUY!
REGULAR \$449

SALE! \$299.95
LIMITED QUANTITIES
THIS PRICE.

ICOM LATEST EDITION

IC-3200A DUAL BANDER
COVERS BOTH 2 METERS
and 70CM



CALL FOR
LOW,
LOW
PRICE

6 STORE BUYING POWER!



PERSONALIZED SERVICE

BOB FERRERO W8RU
President
JIM HAFFERTY N8RJ
VP So. Calif. Div. Anaheim
Managers
GEORGE, WB8DSV Burlingame
DON, N8UPE Oakland
BOB, K7RHH Phoenix
GLENN, K8NA San Diego
AL, N8YTA Van Nuys
and other active amateurs to serve you

800-854-6046

TOLL FREE PHONE INCLUDING ALASKA AND HAWAII
CALIF. AND ARIZONA CUSTOMERS CALL OR VISIT NEAREST STORE
PHONE HOURS: 9:30 AM TO 5:30 PM PACIFIC TIME.
STORE HOURS: 10 AM to 5:30 PM Mon. through Sat.

FREE SHIPMENT
MOST ITEMS U.P.S. SURFACE



ANAHEIM, CA 92801
2620 W. La Palma,
(714) 761-3033, (213) 860-2040,
Between Disneyland & Knotts Berry Farm.

BURLINGAME, CA 94010
990 Howard Ave.,
(415) 342-5757,

5 miles south on 101 from San Fran. Airport. ✓ 136

OAKLAND, CA 94609
2811 Telegraph Ave.,
(415) 451-5757,
Highway 24 Downtown. Left 27th off-ramp.

PHOENIX, AZ 85015
1702 W. Camelback Road,
(602) 242-3515,
East of Highway 17.

SAN DIEGO, CA 92123
5375 Kearny Villa Road,
(619) 560-4900,
Highway 163 and Clairemont Mesa Blvd.

VAN NUYS, CA 91401
6265 Sepulveda Blvd.,
(818) 988-2212
San Diego Freeway at Victory Boulevard

AEA • ALLIANCE • ALPHA • AMECO • B & W • CALLBOOK • CENTURIAN • COLLINS • JSC • J. W. MILLER • KANTRONICS • SIGNAL ONE • STONER • TEMPO • TEN TEC
AMPHENOL • ANIKTER MARK • ANTENNA • COLUMBIA • CURTIS • CUSHCRAFT • KENWOOD • KLM • LARSEN • LUNAR • ME 7Z • THISTAD • TRI-EX • VAN GORDON • VOICOM
SPECIALISTS • ARR • ASTRON • BASH • DAIWA • DRAKE • DIX EDGE • E/MAC • MFJ • MICRO LOG • MINI PRODUCTS • VIBROPLEX • WEST • YAESU and more
BEUDEN • BENCHER • BIRD • BUTTERNUT • GILFER • HAL • MUSTLER • HY GAIN • ICOM • MIRAGE • NVE • PALOMAR • REHN • SHURE •


Prices, specifications, descriptions subject to change without notice. Calif. and Arizona residents please add sales tax.

THE MOST AFFORDABLE REPEATER

ALSO HAS THE MOST IMPRESSIVE PERFORMANCE FEATURES

(AND GIVES THEM TO YOU AS STANDARD EQUIPMENT!)

Band	Kit	Wired
10M,6M, 2M,220	\$680	\$880
440	\$780	\$980


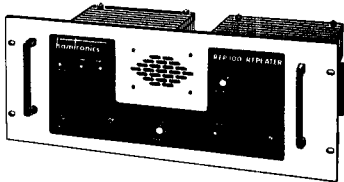


FEATURES:

- SENSITIVITY SECOND TO NONE: 0.15 uV (VHF), 0.2 uV (UHF) TYP.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE XTAL FILTER & CERAMIC FILTER FOR > 100 dB AT ± 12KHZ. HELICAL RESONATOR FRONT ENDS TO FIGHT DESENSE & INTERMOD.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMITTERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY TUNE TRANSMITTER; UP TO 20 WATTS OUT (UP TO 50W WITH OPTIONAL PA).

HIGH QUALITY XMTR & RCVR MODULES FOR REPEATERS, LINKS, TELEMTRY, ETC.

- **R144/R220 FM RCVRs** for 2M or 220 MHz. 0.15uV sens., 8 pole xtal filter & ceramic filter in l-f, helical resonator front end for receiver selectivity, > 100dB at ± 12kHz, best available today. Flutter-proof squelch. AFC tracks drifting xmtrs. Xtal oven avail. Kit only \$138.
- **R451 FM RCVR** Same but for uhf. Tuned line front end, 0.3 uV sens. Kit only \$138.
- **R76 FM RCVR** for 10M, 6M, 2M, or 220. As above, but w/o AFC or hel. res. Kits only \$118. Also avail w/4 pole filter, only \$98/kit.
- **R110 VHF AM RECEIVER** kit for VHF aircraft or ham bands or Space Shuttle. Only \$98.
- **T51 VHF FM EXCITER** for 10M, 6M, 2M, or 220 MHz. 2 Watts continuous, up to 3W intermittent. \$68/kit.
- **T451 UHF FM EXCITER** 2 to 3Watts. Kit only \$78. Xtal oven avail.
- **VHF & UHF LINEAR AMPLIFIERS.** For either FM or SSB. Power levels from 10 to 45 Watts to go with exciter & xmtrg converters. Several models. Kits from \$78.

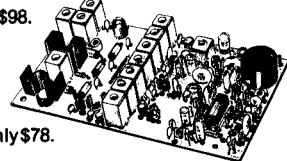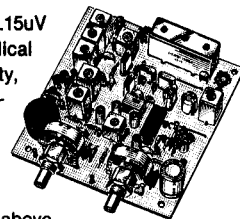

NOW—FCC TYPE-ACCEPTED TRANSMITTERS & RECEIVERS AVAILABLE FOR HIGH-BAND & UHF. CALL FOR DETAILS.

RECEIVING CONVERTERS

Models to cover every practical rf & lf range to listen to SSB, FM, ATV, etc. NF = 2dB or less.



Antenna Input Range	Receiver Output
28-32	144-148
50-52	28-30
50-54	144-148
144-146	28-30
145-147	28-30
144-144.4	27-27.4
146-148	28-30
144-148	50-54
220-222	28-30
220-224	144-148
222-226	144-148
220-224	50-54
222-224	28-30

VHF MODELS

Kit with Case	\$49
Less Case	\$39
Wired	\$69

UHF MODELS

Kit with Case	\$59	432-434	28-30
Less Case	\$49	435-437	28-30
Wired	\$75	432-436	144-148
		432-436	50-54
		438.25	61.25

SCANNER CONVERTERS Copy 808 MHz band on any scanner. Wired/tested ONLY \$88.

TRANSMIT CONVERTERS

For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 Watts output vhf, 1 Watt uhf.

For VHF,
Model XV2
Kit \$79
Wired \$149
(Specify band)

Exciter Input Range	Antenna Output
28-30	144-146
28-29	145-146
28-30	50-52
27-27.4	144-144.4
28-30	220-222*
50-54	220-224
144-146	50-52
50-54	144-148
144-146	28-30


For UHF,
Model XV4
Kit \$99
Wired \$169

28-30	432-434
28-30	435-437
50-54	432-436
61.25	438.25
144-148	432-436*

*Add \$20 for 2M Input

VHF & UHF LINEAR AMPLIFIERS. Use with above. Power levels from 10 to 45 Watts. Several models, kits from \$78.

LOW-NOISE PREAMPS

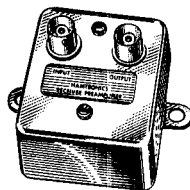

Hamtronics Breaks the Price Barrier!



No Need to Pay \$80 to \$125 for a GaAs FET Preamp.


FEATURES:

- Very Low Noise: 0.7 dB VHF, 0.8 dB UHF
- High Gain: 18 to 28 dB, Depending on Freq.
- Wide Dynamic Range for Overload Resistance
- Latest Dual-gate GaAs FET, Very Stable

MODEL	TUNES RANGE	PRICE
LNG-28	26-30 MHz	\$49
LNG-50	46-56 MHz	\$49
LNG-144	137-150 MHz	\$49
LNG-160	150-172 MHz	\$49
LNG-220	210-230 MHz	\$49
LNG-432	400-470 MHz	\$49
LNG-800	800-960 MHz	\$49

HELICAL RESONATOR PREAMPS

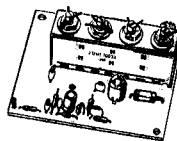Low-noise preamps with helical resonators reduce intermod and cross-band interference in critical applications. 12 dB gain.



Model	Tuning Range	Price
HRA-144	143-150 MHz	\$49
HRA-220	213-233 MHz	\$49
HRA-432	420-450 MHz	\$59
HRA-()	150-174 MHz	\$54
HRA-()	450-470 MHz	\$64

ACCESSORIES

- **MO-202 FSK DATA MODULATOR.** Run up to 1200 baud digital or packet radio signals through any FM transmitter. Automatically keys transmitter and provides handshakes. 1200/2200 Hz tones. Kit only \$45.
- **DE-202 FSK DATA DEMODULATOR.** Use with any FM receiver to detect packet radio or other digital data in "202" modem format. Provides audio conditioning and handshakes. Kit only \$38.
- **COR-2 KIT** With audio mixer, local speaker amplifier, tail & time-out timers. Only \$38.
- **COR-3 KIT** as above, but with "courtesy beep". Only \$58.
- **CWID KITS** 158 bits, easily field programmable, clean audio. Kit only \$68.
- **A16 RF TIGHT BOX** Deep drawn alum. case with tight cover and no seams. 7 x 8 x 2 inches. Designed especially for repeaters. \$20.
- **DTMF DECODER/CONTROLLER KITS.** Control 2 separate on/off functions with touchtones®, e.g., repeater and autopatch. Use with main or aux. receiver or with Autopatch. Only \$90
- **AUTOPATCH KITS.** Provide repeater autopatch, reverse patch, phone line remote control of repeater, secondary control via repeater receiver. Many other features. Only \$90. Requires DTMF Module.
- **SIMPLEX AUTOPATCH.** Use with your FM transceiver. System includes DTMF & Autopatch modules above and new Timing module to provide simplex autopatch and reverse autopatch. Complete patch system only \$200/kit. Call or write for details.

- SEND \$1.00 for 40 page CATALOG (Send \$2.00 or 4 IRC's for overseas mailing)
- Order by phone or mail • Add \$3 S & H per order (Electronic answering service evenings & weekends)
- Use VISA, MASTERCARD, Check, or UPS COD.

hamtronics, inc.

65-E MOUL ROAD • HILTON NY 14468

Phone: 716-392-9430

Hamtronics® is a registered trademark

tracking the hideous intermittent: part 1 — mechanical intermittents

Repair problems are never fun, especially since they take us off the air more times than not.


Probably the nastiest, meanest, and most contemptible of all repair problems are the intermittents. These come and go, usually occurring when it's least convenient. They almost never occur when you're ready to troubleshoot; you stand there, instrument probes in hand and brain engaged, only to find the darn set working properly. You turn your back, set the probes down, and — *zot!* — the trouble reappears momentarily and then disappears again.

Although I'm the first to admit that finding intermittents sometimes falls into the unholy realms of sorcery and witchcraft, certain things can be done to enhance the probability of success.

There's no such thing as a universal procedure for locating intermittents because different kinds of equipment have somewhat different requirements. To keep things simple, we'll limit the scope of this discussion to troubleshooting a high-frequency SSB transceiver with receive problems.

where to look

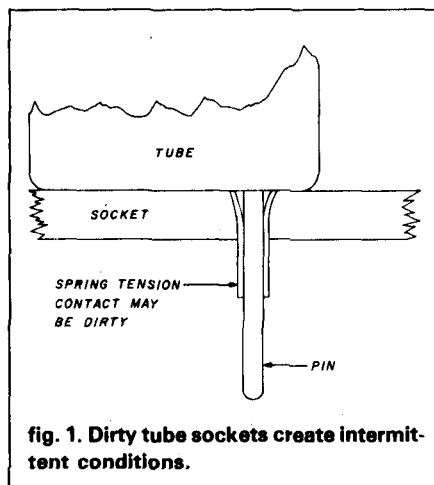One thing you can do is educate yourself about the kinds of parts and faults most likely to create intermittent symptoms. Very high on the list are switches and relays. Because these de-



VICES are mechanical, they're subject to wear and tear. You'll find dirty internal electrical contacts, poor spring tension, and other faults causing intermittent symptoms. In many cases, a session with a pencil eraser on the contacts or a squirt of contact cleaner (for example, *Blue Stuff*) will work wonders. In other cases, however, only replacement will solve the problem.

Another potential sore spot is potentiometers. These components are variable resistors in which a shaft-operated wiper electrode rubs against a wire-wound or carbon resistance element. If either the element or electrical contact on the wiper gets dirty, then operation can become intermittent. Unless the dirt has physically damaged the resistance element (as sometimes happens, especially on carbon elements), a simple squirt of contact cleaner will solve the problem. Be especially aware of potentiometers

that normally pass direct current (DC) through the wiper connection. I recall a 1963/64 car radio model in which cost-conscious engineers eliminated a coupling capacitor from the volume control and audio preamplifier circuit, thereby making the volume control resistance part of the preamp transistor's bias network. Passing the DC bias through the control generated a massive warranty problem for the manufacturer as those volume controls were chewed up by the truckload!

The printed circuit board (PCB) is another common source of intermittent problems. Two forms of the problem are common: poor solder joints and damage, sometimes hidden, to the board. Both types of fault are especially aggravated in hot parts of the equipment: near power transistors, rectifiers, vacuum tubes, power resistors (2 watts and above), lamps and so forth. These areas sometimes can be identified by discoloration of the PCB. (We'll discuss PCB problems in a moment.)

In vacuum tube equipment, the tube socket can produce intermittent problems. If the tube pins or the socket contact (fig. 1) lose tension, then an intermittent connection results. These faults can be repaired in most cases. If dirt is the problem, remove the tube and gently clean its pins with a dime-store ink eraser, spray the pins with a clear contact cleaner, and reinsert the tube into the socket. Next, pull the tube out of the socket and then reinsert it four or five times in a row. This action will clean the socket. Wait a hal-

PACKET RADIO GOES PORTABLE

GLB ELECTRONICS

presents

THE FIRST CONTROLLER DESIGNED FOR PORTABLE AND SOLAR-POWERED STATIONS

- LOW 25 mA Current drain.
- Designed for portable or solar-powered stations.
- Miniature size—Lightweight
- Rugged all metal, shielded enclosure.
- On-board Lithium Battery RAM backup.
- On-board watchdog for reliability.
- Standard DB-25 Connectors.
- Output signal indicates "Connected" Status.
- Does not require squelched audio.
- Comes with 8K of RAM.
- Remote Command Mode for Unattended operation.
- Hardware command lockout for security.
- Commands compatible with our Model PK1.
- Retains all other features of the Model PK1.
- Extra I/O lines for special applications.

Power requirement:

9 to 15 Volts DC @ 25 mA typical

Dimensions:

4.6 X 5.90 X 1.0 inches

Total Weight:

12 ozs.


PK1L—Wired and Tested

List— \$239.95

Amateur net— \$209.95

AVAILABLE OCTOBER 15, 1985

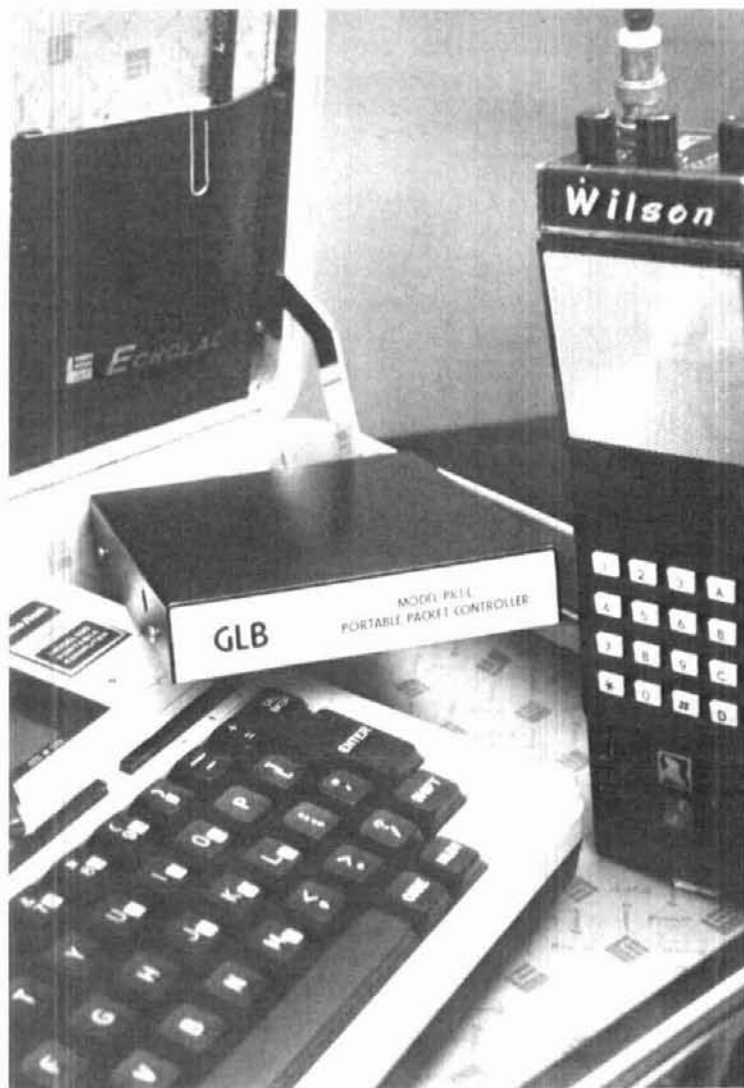*Call or write GLB for
options or Information.*



GLB ELECTRONICS, INC.

151 Commerce Pkwy.,
Buffalo, NY 14224
716-675-6740 9 to 4

hour or so for the cleaner to dry, then turn the rig on to evaluate the results. If the intermittent remains, re-tension the socket contacts with either a tiny screwdriver tip or other sharp-pointed tool.

Components can be the source of some maddening intermittents. Unfortunately, some component problems tend to heal themselves the instant a probe is attached (especially semiconductors). Be especially wary of plastic packaged transistors, tubular (non-mylar) capacitors, and resistors. These components account for a large portion of the problems.

Shielded IF and RF transformers (fig. 2A) are frequent sources of intermittent faults. The coil wire attaches to the lugs on the base, and these sometimes break (see fig. 2B). In some cases, a careful worker can repair these transformers; it's merely a matter of resoldering — you'd be surprised how many escape the factory unsoldered!

finding the intermittent

The first step, crucial to quick success, is observation. Define in your mind what the rig is doing wrong, what functions are affected, and whether it happens on both receive and transmit. Narrowing down the possibilities allows you to restrict your efforts to a certain few stages, once you determine which stages may or may not be affected. For example, if the problem happens on SSB but not CW, or on receive but not on transmit, we can then infer that the problem is probably not in a stage that is common to both affected modes. Deciding which stages are likely candidates depends on understanding your transceiver; do a block diagram analysis and read any circuit descriptions provided by the manufacturer.

Some intermittents occur under vibration, touching, or thumping. A certain number of such problems are due to bad switches and potentiometers. A little *light* tapping with an insulated probe, a little jiggling, or visual inspection will often locate the source of the problem.

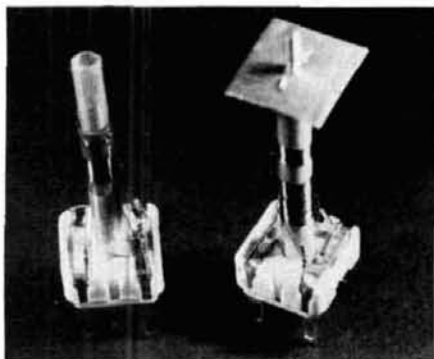


fig. 2A. RF/IF transformers.



fig. 2B. Another cause of intermittency is traceable to broken coil lead/base LUG connections.

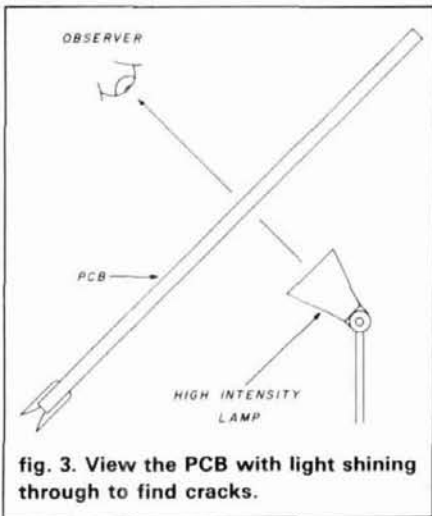


fig. 3. View the PCB with light shining through to find cracks.

Most mechanical faults are due to either bad PCB joints or bad components mounted on the PCB. Unfortunately, many of these problems fail to yield to the tapping method because any vibration at all, anywhere on the board, will produce the fault. Two approaches helpful in this regard don't require formal troubleshooting: visual inspection and shotgun solder touch-up.

Visual inspection involves examining every joint on the PCB with a 10X or so magnifying glass under adequate light. Examine the board two ways: first with the light shining on the soldered side, then with the light shining *through* the PCB from the component side (fig. 3). In the latter case, subsurface cracks in the PCB material can break a joint or track. Even if the joint or track appears normal it should be reworked.

Visual examination takes a certain amount of practice; one needs to develop a "small eye," that is, the ability to see defects where others would see a "normal" joint.

I usually inspect PCBs with a bottle of fingernail polish or a grease pencil handy. Especially on large boards, each apparent anomaly is marked so that I can find it easily later on. This habit is especially useful when using a magnifier because the glass will distort your perception of space.

Shotgun soldering is especially useful when the area of the intermittent is known, when the PCB is small, or when nothing else seems to work. I can recall another mobile radio receiver problem in which the VHF front-ends PCB had a high "bad joint" intermittent rate, but were difficult to remove and replace. In that case, the more elegant "visual inspection" method was not cost effective, so we pulled the PCBs, soldered every joint, and tinned every track. Rarely did this method fail on that particular problem.

At this point let me digress a little bit to answer the purists who would criticize this approach. I admit that the elegant method is to find the single bad joint or broken track and repair only that. Unfortunately, this approach can be time-consuming and may even be impossible. While the purist "super-tech" is messing around trying to analyze which joint is bad, I'm going to fix the rig! Commercially, the shotgun approach is more profitable — and to Amateurs it means getting back on the air sooner.

Next month: Tracking down thermal intermittents.

ham radio



When DISASTER Strikes YOU May be the Animals' Only Hope

The World Society for the Protection of Animals (WSPA), a nonprofit organization with offices around the globe, takes action to help animals in crisis, responding in times of fire, flood, earthquake, volcanic eruption, oil spills, and civil unrest.

To assure the quickest response to these disasters, WSPA needs the help of ham radio operators in the United States and abroad who can relay critical information to and from international trouble spots.

WSPA is the only organization officially recognized by the United Nations as a consultant on animal disaster issues. We urgently need you and your radio. To register as an animal-emergency operator, simply fill out the coupon and mail it to WSPA, Western Hemisphere Regional Office, 29 Perkins St., POB 190, Boston, MA 02130. We'll be depending on you when animals are in jeopardy.

THIS HAM OPERATES FOR ANIMALS!

NAME _____
 ADDRESS _____
 PHONE _____
 CALL _____
 EQUIPMENT AVAILABLE _____

ENGINEERING CONSULTING INTRODUCES

'REMOTE A PAD'[®] MODEL RAP-1

2 FOUR DIGIT DTMF DECODERS, PLUS 16 DIGIT KEYPAD CONTROL

TUNE THE WORLD FROM YOUR HANDHELD VHF/UHF RADIO

- Audio tones from any source are converted to solid state switches which control any 16 digit keypad of a radio or other device.
- Some examples you can control include the Pro-Search[®] Rotator (rotate beam remotely), ICOM IC-701 or ICOM IC-211 when using the RM-2 controller, ICOM 7950 & 7511 Azden PCS 4000, handhelds such as Yaesu FT-208 FT-708 ICOM IC 52AT and many more.
- Anything you can do manually with your 16 digit keypad the RAP-1 will do remotely using audio touch tones from any source.
- Two (four digit) programmable access codes are used to operate relays or other on/off functions.

Model RAP-1

\$149.95

'Remote A Pad'

Remote control interface board and DTMF decoder

- LED decoder status indicators and momentary push steady state decoder outputs are provided.
- 22 gold pin and edge connector, 16 pin dip socket and ribbon cable are supplied.
- All CMOS low power draw (30ma), SSI 201 Decoder.
- Uses eight wires (4 rows and 4 columns) in parallel with the existing keypad of the radio you wish to control remotely. Connect audio from any source 12 volts D.C. and you are in control!
- The dual 4 digit decoders will turn your links on and off using your programmable access code.
- Detailed interface diagrams and instructions included with purchase. Interface cable for Pro-Search[®] \$9.95 (plugs in to socket).

ICOM IC-22AT USER'S "AUDIO BLASTER" MODULE

- Module installs inside the radio in 10 minutes.
- Boosts audio to nearly 1 watt!
- Low power draw (4ma stand by)
- Complete step by step instructions included
- Corrects the LOW audio problem!
- Drive external speakers to full volume even signals with low deviation!



Model AB-1 **\$19.95**

Price includes postage and handling, U.S.A. CA res. add 6%

Send check or money order to
ENGINEERING CONSULTING
 583 CANDLEWOOD ST., BREA, CA 92621
 (714) 671-2009

TOUCHTONE™ DECODER KIT

- MODEL TTK -

\$22.95

4 DIGIT SEQUENCE DECODER

- SSI 201 DTMF Receiver
- Receive all 16 DTMF digits
- No additional filtering
- Output BCD or hex format
- Low power (29ma @ 12V)
- Kit includes 3.58Mhz crystal, 22 pin IC socket, resistor, capacitors, data sheet and schematics

4 DIGIT SEQUENCE DECODER

- Completely wired & tested
- User programmable
- LED status indicator
- Open collector output
- Control relays, mute audio
- Control link on/off
- Custom IC insures high reliability & small size!
- Fits inside most rigs runs on 12 VDC (35ma)
- Over 1500 different codes!

WIRED & TESTED - MODEL TSD -

\$59.95

- Makes excellent private call on busy repeaters!
- Use it to turn on audio or sound an alarm
- Momentary and latching outputs

MasterCard and Visa accepted, or send check/M.O. Cal. address add 6%, price includes shipping USA. Send to:

ENGINEERING CONSULTING
 583 CANDLEWOOD ST., BREA, CA 92621
 TEL: 714-671-2009

AMATEUR RADIO MAIL LISTS

Self-stick 1x3 labels

- *** NEWLY LICENSED HAMS ***
- *** ALL NEW UPGRADES ***
- *** UPDATED EACH WEEK ***

Total List = 462,728 (ZIP sorted)
 Price is 2.5 cents each (4-up Cheshire)

BUCKMASTER PUBLISHING
 Mineral, Virginia 23117
 703:894-5777

✓ 138

ENGINEERING CONSULTING INTRODUCES

TOUCHTONE™ DTMF to RS-232-C 300 BAUD INTERFACE

TOUCH TONES

RECEIVER → 'DECODE A PAD' → SERIAL PORT → COMPUTER

- Use your computer to decode DTMF touchtones.
- Receive all 16 digits as fast as they can be transmitted.
- Easily program your computer in BASIC to decode multi-digit "strings", display digits, sound alarms, observe secret codes, control relays, remote alarms.
- Simple to use, just provide +12 VDC and audio, hook two wires to the RS-232-C serial input on your computer, enter a simple BASIC program and begin to decode.
- Sample BASIC program and instructions included.
- LED Indicator

Model DAP-1

Wired and Tested **\$89.95**

Includes shipping USA. Cal. addresses add 6%.
 VISA and MasterCard accepted, or send check/M.O. to:

ENGINEERING CONSULTING
 583 CANDLEWOOD ST., BREA, CA 92621
 714/671-2009

"MULTI-BAND SLOPERS"

ALSO: DIPOLES & LIMITED-SPACE ANTENNAS

Outstanding performance of WINN antennas is well known! Now enjoy multiband BIG-SIGNAL reports! Automatic bandswitching! Very low SWR! Coax feed - 24w power - Compact - FULLY ASSEMBLED to your specified center frequency each band - EASY TO INSTALL - VERY low profile - Complete instructions - Your personal check accepted

4 BAND SLOPER - 160, 80, 40, 30, or 20M	60 ft long	\$ 48.95
3 160, 80, 40M	60 ft ..	\$ 43 ..
2 80, 40M	40 ft ..	\$ 35 ..
3 NO-TRAP DIPOLE - 160, 80, 40M	113 ft long	\$ 71 ..
2 80, 40M	85 ft ..	\$ 55 ..
9 BAND SPACE-SAVER DIPOLE - 160 thru 10M*	46 ft long	\$ 85.95

* Requires wide-range tuner (80, 40, 20, 15M without tuner)

SEND SASE for complete details of these and other unique antennas

WINN ANTENNAS 312-394-3414
 BOX 393-H MT. PROSPECT, IL 60056

✓ 139

Everything from Superman III to Super Bowl XX.


Movies. Sports. News. Entertainment specials.
Music videos.

Everything you always wanted to see on
television but were afraid you'd never get.

Over one hundred channels of spectacular
entertainment. Of crystal clear reception.
Throughout the house. 24 hours a day.
With no monthly fees. No cable TV.

Come see the entire line of Uniden
Satellite Television Systems. It's legal.
It's affordable. And it's a whole new
world of television. Right in your own
backyard.

uniden[®]
Satellite Television Systems

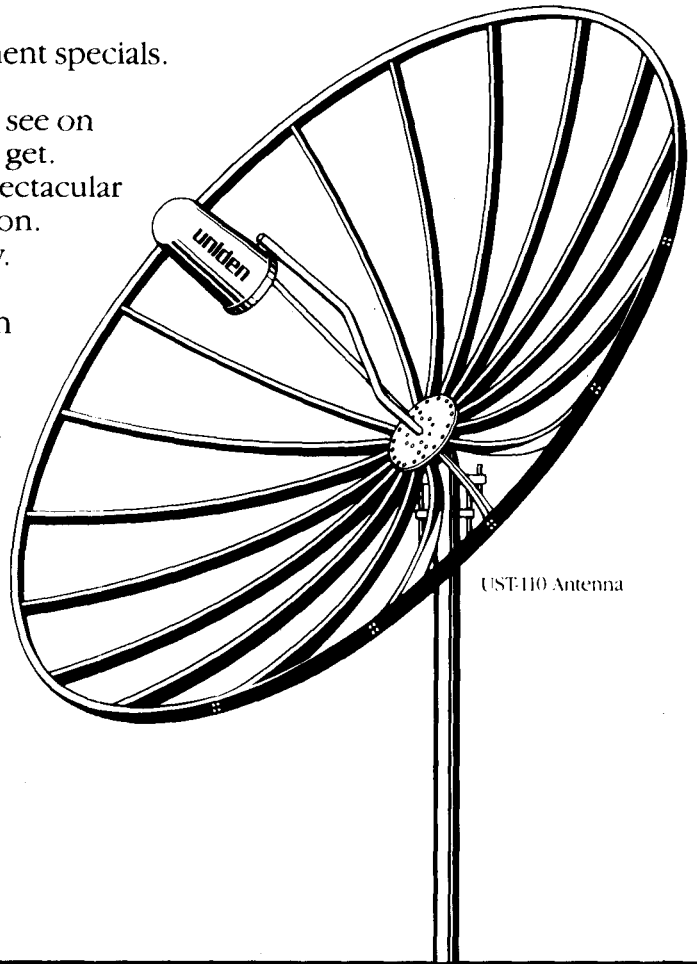

© Uniden Corporation of America 1985




2410 Ridge Road West
Rochester, New York 14626
716-225-6130
1-800-824-5014
Sales

17 Industrial Street
Rochester, New York 14614
716-454-3630
1-800-824-5014
Service

PUBLISHED BY:
THE AMERICAN RADIO
RELAY LEAGUE



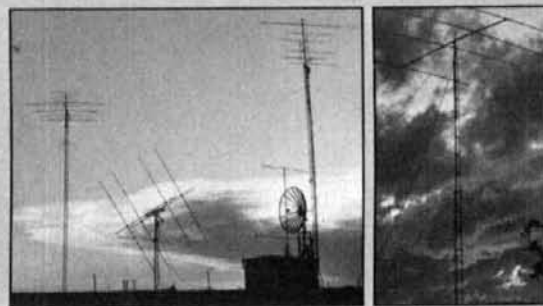THE ARRL 1986 HANDBOOK FOR THE RADIO AMATEUR



BIGGER AND BETTER THAN EVER!

The ARRL 1986 Handbook for the Radio Amateur takes over where the 1985 Edition left off. Each of the 40 chapters has had some revision, and there are more than 500 new or revised figures. The new edition will contain 1184 pages — way up from last year's count of 1024. Many key chapters with "hot" topics among today's radio amateurs have been completely revised and rewritten. In fact the new material represents 532 text pages.

An understanding of digital electronics is a must these days since such circuitry has so many practical applications in station control, frequency synthesis, telemetry, word processing and other information-handling systems. The Digital Basics chapter will help you to understand what is going on in everything from simple keyers to sophisticated microcomputers. Packet-radio enthusiasts will find the most up-to-date information available in the Digital Communications chapter. There are new sections on data interfacing and modems, 50 new and revised figures, plus an expanded bibliography and glossary.

The Special Modulation Techniques chapter has the latest on spread-spectrum. On the fun side, we've added a new section on remote control of model aircraft and vehicles.

On the practical side, you will find many of the 27 new projects described in October *QST*. There are new power amplifiers for 1.8, 50, 144 and 1296 MHz, plus preamplifiers and transverters for the VHF/UHF enthusiast. The new digital PEP Wattmeter - SWR Calculator will be one of the most popular projects.

We've only scratched the surface in describing what is the standard manual of RF communication. Over 5.7 million copies of *The Handbook* have been published in 63 editions since 1926. The new edition is must reading for today's radio amateur!

The *1986 Handbook* will be available in November. Paperbound prices are \$18.00 in the U.S., \$19.00 in Canada and elsewhere. Cloth prices are \$27.00 in the U.S. and \$29.00 elsewhere. Prices in U.S. funds. Foreign remittance should be in the form of an international money order or a check drawn on a bank account in the U.S.

NEW!
ICOM HF Transceiver

IC-735



Ultra Compact

The new ICOM IC-735 is what you've been asking for...the most compact and advanced full-featured HF transceiver with general coverage receiver on the market. Measuring only 3.7 inches high by 9.5 inches wide by 9 inches deep, the IC-735 is well suited for mobile, marine or base station operation.

More Standard Features

Dollar-for-dollar the IC-735 includes more standard features...FM built-in, an HM-12 scanning mic, FM, CW, LSB, USB, AM transmit and receive, 12 tunable memories and lithium memory backup, program scan, memory scan, switchable AGC, automatic SSB selection by band, RF speech processor, 12V operation, continuously adjustable output power up to 100 watts, 100% duty cycle and a deep tunable notch.

Superior Performance

It's a high performer on all the ham bands, and as a general coverage receiver, the IC-735 is exceptional. The IC-735 has a built-in receiver attenuator, preamp and noise blanker to enhance receiver performance. PLUS it has a 105dB dynamic range and a new low-noise phase locked loop for extremely quiet rock-solid reception.

Simplified Front Panel

The large LCD readout and conveniently located controls enable easy operation, even in the mobile environment. Controls which require rare adjustment are placed behind a hatch cover on the front panel of the radio. VOX control, mic gain and other seldom used controls are kept out of sight, but are immediately accessible.



Options. A new line of accessories is available, including the AT-150 electronic, automatic antenna tuner and the switching PS-55 power supply. The IC-735 is also compatible with most of ICOM's existing line of HF accessories.

See the IC-735 at your authorized ICOM dealer. For superior performance and innovative features at the right price look at the ultra compact IC-735.

 **ICOM**

First in Communications

Message Master™

Real-voice message system For any repeater or base

Now you can communicate vital information even when the station you are calling is not on the air — with Message Master. Message Master is a solid state voice recording system which can record messages just by listening to you speak, store messages in memory, and deliver messages on demand. If you can't be there to deliver your messages let Message Master deliver them for you - any messages in any language and in your own voice!

Message Master connects easily to any radio system for remote access: repeaters, base stations, even transceivers. It can even be connected to an autopatch device to exchange messages between your radio system and the telephone network.

Message Master is a multi-user system with mailbox style personalized message service for a hundred users. With 8 minutes of message storage it can store hundreds of messages simultaneously making it ideal for large, active repeater groups.

Would you like your callsign identifications, tail messages, and bulletin messages sent in real-voice? Message Master can send them too. Record several identification messages and it will even send a different ID each time. Almost like magic, Message Master knows when to send identifications and tail messages so it needs no special control signals from your base or repeater.

Call or write for further information before you make another wasted call.

Commercial users: Ask for a brochure on the Message Master Electronic Dispatcher with group and all call messaging.



- **Create messages just by talking.** Message Master's 'real-voice' technique saves YOUR VOICE in digital memory to deliver messages in your own voice, language and dialect.
- **Mailbox-style operation** gives individual message delivery service to 100 system users.
- **Easily added to any repeater or base station** for remote operation with only four connections.
- **Special features include** callsign identifications, tail messages, and bulletin messages.
- **Digital message storage** provides instant playback of stored messages.
- **Modular memory** meets your exact needs from 2 to 8 minutes of total message storage.

Serving all your repeater needs

- *Mark 4 Repeaters and Repeater Controllers are THE PERFORMANCE LEADERS with real voice, more autodial numbers, more synthesized voice and more features.*
- *Mark 3 Repeaters offer the winning combination of high performance and high value.*
- *LR-1 Repeaters boast superb RF circuitry at an economical price.*
- *MR-4 Receivers with 7 helical resonators are the only receivers to choose in harsh RF environments.*
- *PA-100 Amplifiers with rugged TMOS power FETs give you a continuous duty high power signal.*



COMING SOON: A 4-channel receiver voting system which operates on true signal-to-noise ratio to extend your coverage by linking to remote receivers.

**KENDECOM INC.
MICRO CONTROL SPECIALTIES**

23 Elm Park
Groveland, MA 01834
(617) 372-3442



digital frequency readout using the Commodore 64

A ÷ by 16 prescaler
designed for the Argosy I
can be adapted
to other transceivers

Although digital frequency readout is clearly a major advance in Amateur transceiver technology, many excellent rigs that offer most of the other advantages typical of state-of-the-art gear don't have digital readout. Yet it seems ridiculous to replace a good piece of equipment because of this one shortcoming. If you have such a rig, you might want to consider adding a digital frequency display as an accessory.

This can be done through the purchase or construction of a frequency counter, but such gadgets tie up both station space and dollars, and without special hookups can display only transmitted frequencies. Furthermore, when the station already contains a computer and monitor, it seems redundant to add yet another display with its associated batch of electronics.

I was doing a good job of break-in CW with a Ten-Tec Argosy and a Commodore 64 serving as a CW keyboard. With conditions becoming more and more difficult as the sunspot number fell, the need for sharp filters and "on-the-nose" schedules became too acute to be ignored, and the analog dial of the Argosy fell short of what was needed. Accordingly, I decided to make the computer display the required information.

Fortunately, the C64 contains an array of hardware timers that operate independently off the central processor and can be accessed through the user port. It

also contains a stable frequency reference in the form of the machine clock. The timers perform the comparison of unknown and reference frequencies. The mathematics necessary to display the operating frequency, formulated in BASIC, run in real time in order to provide a continuous readout. The system is easy to implement and debug, performs beautifully, and is readily adaptable to other popular transceivers.

timer

The timers are part of two 6526 Complex Interface Adapter (CIA) integrated circuits contained in the machine. One of the two ICs is dedicated primarily to the keyboard interface, but its timers are partly accessible through the user port. The second CIA is dedicated to the user port and the serial interface, and its functions are fully accessible.

The timers are 16-stage binary counters that can be preset to any count between 1 and 65,535. They count down from the preset value and deliver an output when the count passes zero. Thus, they can divide an input frequency by any integral number within their range. Furthermore, they can be cascaded by appropriate instructions to form a longer counter chain.

The signal counted can be either an external input or the machine clock. The latter runs at 1.022727 MHz and is derived from a master crystal oscillator that also generates the color subcarrier in a TV.

The counting rate is limited to about 500 kHz by the internal mechanics of the interface chip. It is therefore necessary to bring the frequency to be measured down into the range below 500 kHz. However, an aliasing effect permits moderate extension of the limit with appropriate modification of the programmed mathematics.

By Clifford J. Bader, W3NNL, 1209 Gateway Lane, West Chester, Pennsylvania 19380

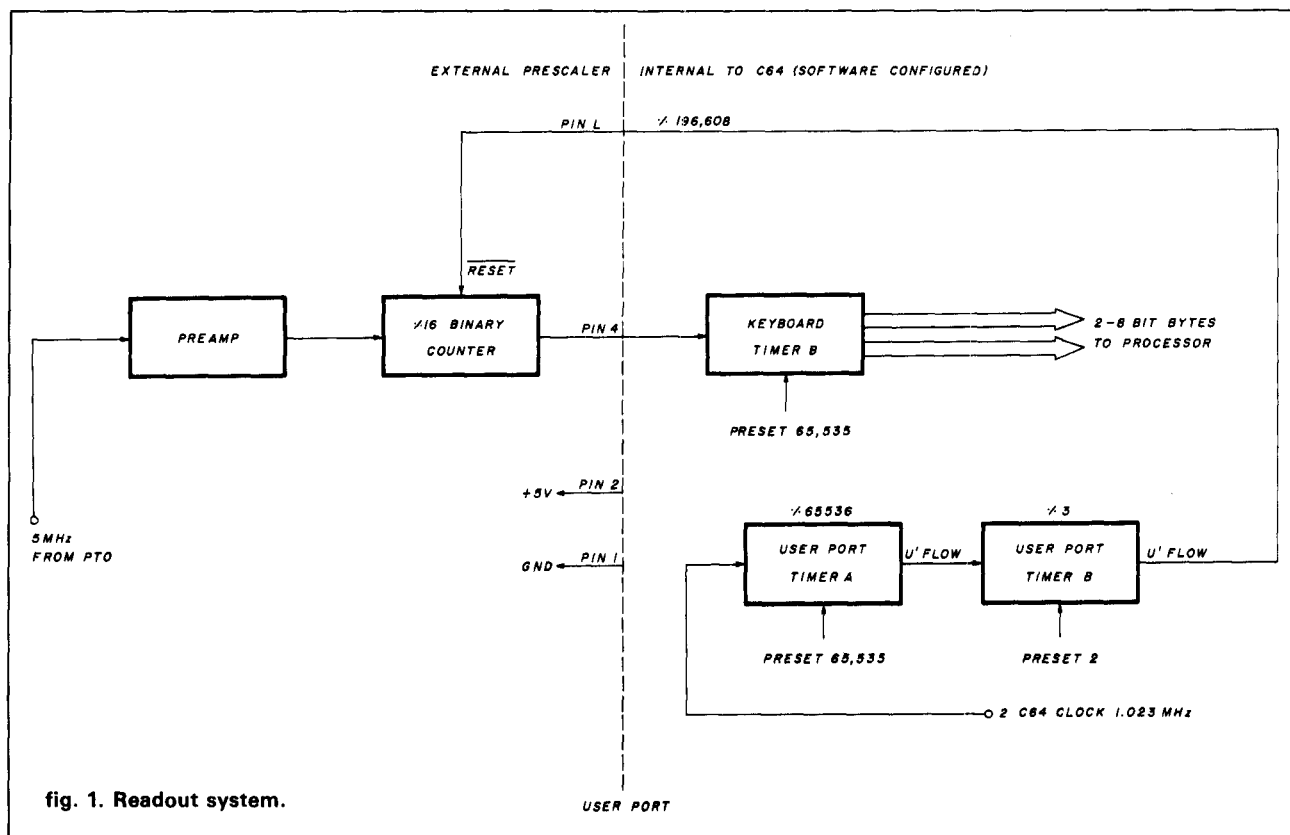


fig. 1. Readout system.

design considerations

A key requirement for digital frequency readout is precise gating of the counter that records the frequency to be measured. This would be difficult to do if the gating were done through software, since the machine cycle times for executing BASIC instructions are a significant fraction of the counting period required. Fortunately, the designers of the CIA arranged for direct access of the timer output through the user port, without intervention by the computer's processor; thus, one timer can be used to precisely gate another by the addition of simple external circuitry, and the result can be examined by the computer at its leisure.

In general, neither the transmitted nor the received frequencies are present as a steady-state signal (except in the case of a direct-conversion system), so an indirect method of determining the frequency must be used. Since most modern gear uses a master oscillator covering a fixed range, in conjunction with crystal-controlled heterodyning oscillators for the various bands, it is generally satisfactory to measure the master oscillator frequency and to apply appropriate corrections to the display. The stability of the heterodyning system is usually good enough to make the correction a con-

stant factor, and no significant error results from warm-up or temperature changes.

My Argosy oscillator operates in the 5-MHz region, as do the oscillators in many other transceivers. To get the frequency below the 500-kHz limit, the frequency to be measured must be reduced by a factor of better than 10. Translation through a mixer could be used, giving an output of 0 to 500 kHz as the oscillator covers 5 to 5.5 MHz, but an additional crystal oscillator would be needed and the mixer output circuit would have to be broadbanded over the range from DC to 500 kHz.

It's easier to use a frequency divider in the form of a simple integrated-circuit counter. For example, a four-stage binary counter divides by 16, giving an output frequency range of 312.5 kHz to 343.75 kHz as the input varies from 5 MHz to 5.5 MHz.

An obvious disadvantage of the divider is the loss of precision associated with the compressed frequency range. The precision can be regained, however, by lengthening the counting interval by an equivalent factor. Normally, achieving 100-Hz resolution — which is typical of most digital readout transceivers — would require counting for 0.01 second; with the divide-by-16 prescaler, the time must be lengthened to 0.16 second or more. Fortunately, a repetition rate of two or three

times per second is fast enough for a useful real-time readout, so the divider scheme is practical. It is easy to implement, requiring only the binary counter and a transistor buffer-driver to amplify the small amount of RF taken from the 5-MHz transceiver oscillator. Power can be taken from the computer's user port.

The computer program for performing the readout and display handles a number of functions. First, it arranges the timers for the task at hand. Then it starts the count cycle running and monitors for completion of the cycle. Next it obtains the resultant count and performs the mathematics necessary to deduce the oscillator frequency from the count. It applies the appropriate corrections for the band and mode in use, as input by the operator. Finally, it displays the resultant figure on the screen, and initiates a new cycle. Despite all this activity, the program is a short one, requiring fewer than 50 lines of typing and only a few seconds to load from tape or disk.

system implementation

The readout system is shown in fig. 1. Timer A of the user port divides the machine clock frequency by 65,536. When its count passes zero a pulse is delivered to user port timer B. The latter is preset to a count of 2; when it also indicates an underflow (at a clock count of $65,536 \times 3 = 196,608$), line PB7 (Pin L) of the user port switches from plus 5 volts to zero volts. This voltage transition gates off the external counter.

The counting interval is $196,608/1,022,727 = 0.192239$ second.

Counter B of the keyboard interface CIA counts the input pulses delivered from the external divide-by-16 prescaler through Pin 4 of the user port. It is preset to 65,535 at the start of each cycle and counts down until the external signal is gated off.

The schematic of the external prescaler is shown in fig. 2. The binary counter is a TTL 74197, which is capable of 70-MHz operation. There are numerous other possible choices, including some CMOS varieties; however, with the latter it may be necessary to run the prescaler at a higher voltage than 5 volts to achieve the 5 MHz counting speed. This would in turn lead to power supply and interfacing complications.

A cursory glance at the transistor buffer circuit suggests that it violates all the rules of stable biasing for amplifiers. So it does, but the objective is not linear reproduction of the signal, but rather the development of a square wave drive from a hundred millivolts or so of sinusoidal signal. Thus, it is permissible to operate the stages at a small degree of either saturation or cutoff. The resistor values shown keep the 2N2222s in such a state.

The coupling to the transceiver is through a simple capacitive pickoff and a 3-foot (0.9 meter) shielded cable to the prescaler. The loss in signal caused by the voltage-divider effect of the cable capacitance is made up by the two-stage amplifier in the prescaler.

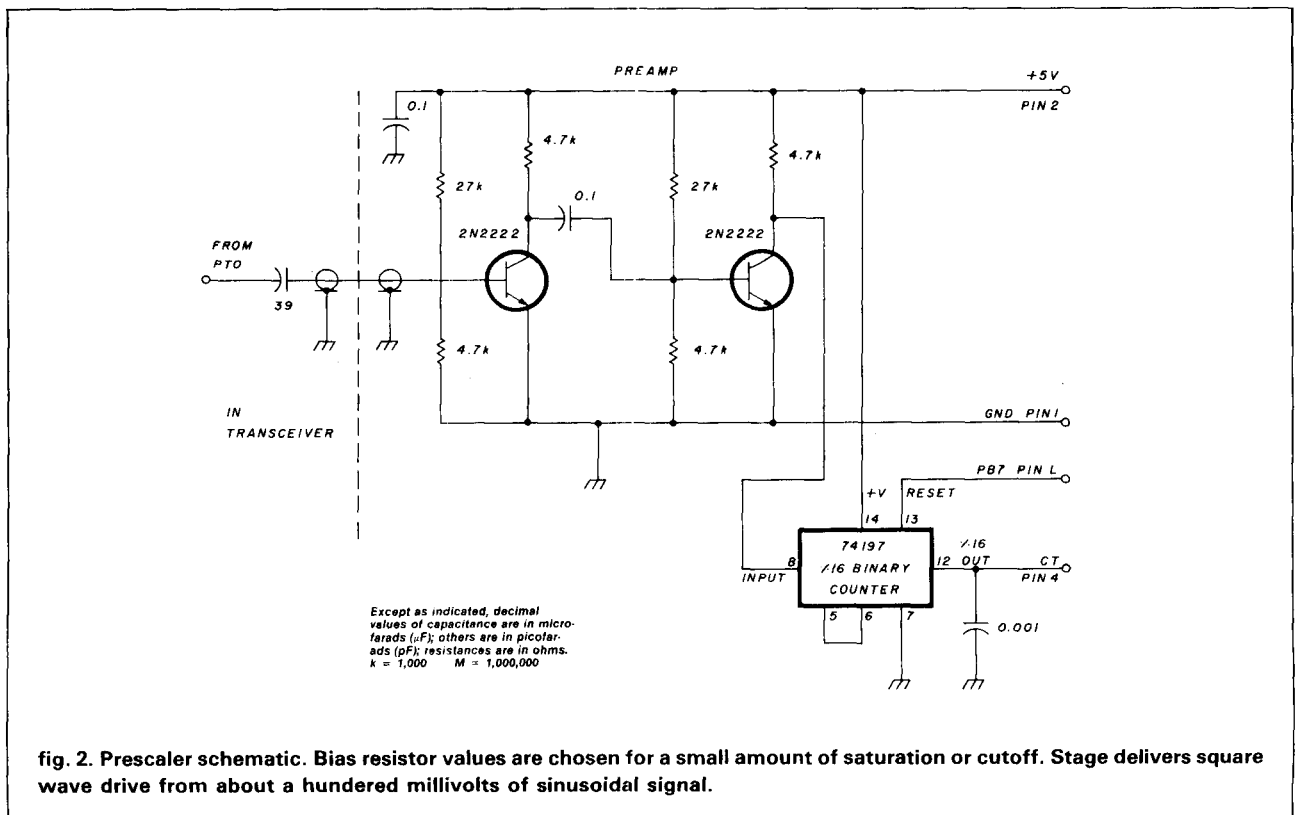


fig. 2. Prescaler schematic. Bias resistor values are chosen for a small amount of saturation or cutoff. Stage delivers square wave drive from about a hundred millivolts of sinusoidal signal.

The advantage of this approach is that it requires no active hardware inside the transceiver and produces no large-amplitude square waves near the transceiver's receiver circuitry.

In my Argosy, the 39 pF capacitor is connected to the output (rearmost) terminal of the PTO assembly and a shielded cable is run from there to one of the spare RCA jacks on the rear panel. Many transceivers have the VFO signal already available on the back panel and require no internal modification. In general, the pickoff point should be at the output of the VFO buffer, and the rig should be checked after connection of the prescaler to make sure that there is no loss of output.

The prescaler is located close to the user port and enclosed in a small aluminum box (fig. 3) to prevent radiation of harmonics of the scaled-down frequency every few hundred kilohertz throughout the spectrum. Such radiation is also suppressed by the 0.001- μ F capacitor from the prescaler output to ground, which slows down the edges of the square wave going into the port.

At W3NNL, the prescaler shares the user port with an MFJ-1228 CW/RTTY interface, and is piggybacked on the latter (fig. 4). There is only one port line (Pin L) in conflict, and a switch is provided to transfer it from frequency readout to the MFJ. I have also combined a CW keyboard program (not shown) with the frequency readout.

In the absence of such a piggyback scheme, it will be necessary to procure a connector with the required 0.156-inch (4-mm) contact spacing. These seem to turn up at hamfests only in much longer sizes than the 24-pin variety needed for the user port; however, the excess length is easily removed with a hacksaw.

computer program

The BASIC program shown in fig. 5 can be followed using the memory map presented in the C64 Programmer's Reference Guide. Lines 110 through 290 are concerned with acquiring the operator-specified band and mode, and defining the pre-established correction factors. The section from line 300 through 420 sets up the timers, runs the count cycle, and calculates the frequency. The remainder of the program is devoted to formatting and displaying the output and starting a new cycle.

The timer interface uses POKE and PEEK statements directed to the appropriate addresses. The count in timer B of the keyboard CIA is picked off in two eight-bit bytes, and the number of pulses is calculated and multiplied by a factor which yields the original input frequency to the prescaler. The low-edge oscillator frequency is subtracted from the input frequency, and the lower edge of the band in use is added. Finally, corrections unique to the individual transceiver are

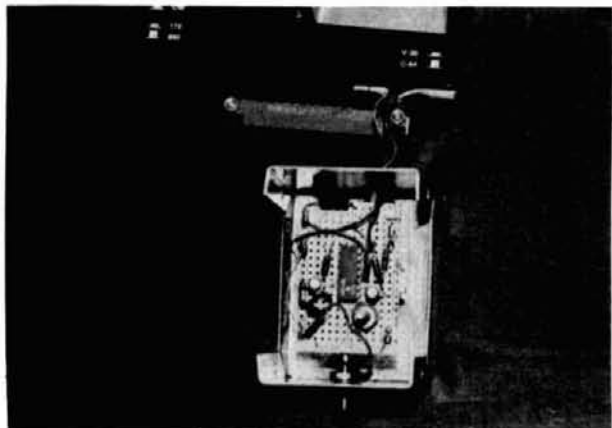


fig. 3. Prescaler is enclosed in a small aluminum box to prevent harmonic radiation.

either added or subtracted; these corrections take care of crystal-tolerance errors in the heterodyne frequencies, deliberately introduced offsets such as those used in the Argosy to avoid birdies, and shifts in the received and transmitted frequencies dependent on the mode of operation selected (CW or either sideband).

The correction consists of a term K representing the conversion-oscillator related effects, a factor D representing the offset between CW and normal sideband operation, and a multiple of D which is the shift incurred when the reverse sideband is selected. Of course, if only one mode is to be used, D may be omitted from the selection statements and from the frequency equation of line 400, and the mode select routines of lines 130-160 and 270-280 can be omitted. The value of K can be determined for the mode of interest.

Several tasks are associated with formatting and display. The screen is cleared and the "FREQ =" leader is printed, followed by the frequency, a wide space, and the mode entered. To avoid a string of meaningless extra digits after the decimal point, the computed frequency is rounded off to the nearest 0.1 kHz. To eliminate the visually unpleasant sensation produced by the C64's dutiful suppression of the decimal point and following zero on integral kilohertz readings, some jockeying is performed to tack the point and zero back on. Finally, compensation is made for the leading-zero suppression, which occurs when tuning from above 10 MHz, to below 10 MHz, and which would otherwise shift the display left and expose a spurious right-hand digit.

The above action is repeated every few hundred milliseconds, except that the screen is left uncleared after the first cycle. Clearing produces flicker and is unnecessary unless the format changes.

For the display to work properly, it is imperative that

PERFORMANCE

THAT IS OUT OF THIS WORLD...



\$389⁰⁰

**MODEL 2000 20MHz
DUAL TRACE**

\$549⁰⁰

**MODEL 3500 35MHz
DUAL TRACE DELAYED SWEEP**

...AT A DOWN TO EARTH PRICE

At last! Truly affordable test equipment with no compromise in design, and features you would expect to find only on oscilloscopes costing hundreds of dollars more! JDR Instruments presents two, new, high-performance models backed by a two year warranty and technical support which is only a phone call away. Perfect for the technician or advanced hobbyist, both models feature Dual Trace capability and a variety of operating and triggering modes, including CH-B Subtract and X-Y operation.

MODEL 2000 has a 20 MHz bandwidth and 20 calibrated sweeps ranging from .2s to .2 μ s. A convenient built-in component tester provides additional diagnostic power.




INCLUDES TWO HIGH QUALITY
1x, 10x TEST PROBES

MODEL 3500 features a 35 MHz bandwidth and exceptional 1mV/DIV sensitivity. Delayed sweep and variable holdoff allow stable viewing of complex waveforms.

ORDER TOLL FREE
800-538-5000
800-662-6279 (CA)

143

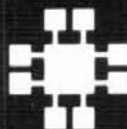

JDR INSTRUMENTS
1224 South Bascom Avenue
San Jose, California 95128 (408) 995-5430



ICOM

KENWOOD YAESU



Regular SALE
 IC-735 New, compact HF Transceiver Call
 IC-751 9-band Xcvr/1-30 MHz Rcvr \$1399.00 Call
 IC-745 9-band Xcvr/1-30 MHz Rcvr \$ 999.00 Call



IC-271 100w 2m FM/SSB/CW Xcvr .. \$899 Call
 IC-271 A 25w 2m FM/SSB/CW Xcvr. \$699.00 Call
 IC-471 A 10w 430-450 SSB/CW/FM Xcvr \$799.00 Call



IC-02AT Call
 IC-04AT Call
 IC-2AT Call
 IC-3AT Call
 IC-4AT Call

**IC-R71A
GENERAL
COVER RCVR**



Regular SALE
 TS-940S/AT \$1995.00 Call
 TS-930S/AT \$1799.00 Call
 TS-930A \$1599.00 Call



TS-711A TS-811A Call



TR-2600A Call
 TH-21A Call
 TH-21AT Call
 TH-41A Call
 TH-41AT Call

**R-2000
GENERAL
COVER**



Regular SALE
 FT-980 \$1659.00 Call
 FT-09G Call



FT-726R \$ 899.00 Call



FT-209RH Call
 FT-709RH Call
 FT-203RH Call
 FT-103R Call
 FT-703R Call

**FRG-8800
GENERAL
COVER RCVR**



**SALE!!
NEW RTTY/CW
COMPUTER
INTERFACES**



THIS MONTH'S SPECIAL

FREE PB-21
 with the purchase of a TH-21AT
 IC-04AT Yaesu FT-709R
 Call for special price



**MIRAGE
AMPLIFIER
SALE!**



**AMERITRON
AL-80**



JUN'S
ELECTRONICS
 800-882-1343
 INCLUDES ALASKA HAWAII
 Calif. Call Collect for Order

- AMATEUR ● TWO WAY ● MARINE
- CELLULAR MOBILE PHONE ● SCANNER
- ★ Free U.P.S. Cash Order (Most Item, Most Place)
- ★ Shoppers, call us last, save \$\$
- ★ SE HABLA ESPANOL

(213)390-8003 3919 Sepulveda Blvd. Culver City, CA 90230

**CADDELL
COIL CORP.**
 35 Main Street
 Poultney, VT 05764
 802-287-4055

BALUNS

Get POWER to your antenna! Our Baluns are already wound and ready for installation in your transmatch or you may enclose them in a weatherproof box and connect them directly at the antenna. They are designed for 3-30 MHz operation. (See ARRL Handbook pages 19-9 or 6-20 for construction details.)

- 100 Watt (4:1, 6:1, 9:1, or 1:1 Impedance - Select one) \$ 9.50
- Universal Transmatch 1 KW (4:1 Impedance) 13.50
- Universal Transmatch 2 KW (4:1 Impedance) 16.00
- Universal Transmatch 1 KW (6:1, 9:1 or 1:1 - select one) 15.00
- Universal Transmatch 2 KW (6:1, 9:1 or 1:1 - select one) 17.50

Please send large SASE for info

145



**AR-200 XL
MEDIUM DUTY ANTENNA ROTOR**

Select a Heading - Antenna Turns and Stops Automatically

\$99⁹⁵

SIDE BAND SQUELCH

- Fits inside most HF SSB transceivers
- Requires human voice to activate
- Ignores static, noise and heterodynes
- On/off switch only - no adjustments!
- Connects to audio leads and 9-12 VDC
- Fully assembled and tested \$99.95
- Complete with comprehensive manual
- Used worldwide in commercial and military transceivers



CMC COMMUNICATIONS
 5479 Jetport Tampa FL 33614 (813) 885-3996

146

**Crystal
Filters**

IMPROVE YOUR FT-980!

For super-selectivity replace your stock filters with a matched pair of genuine 8-pole Fox Tango units. All drop-in easily except replacement for ceramic. Complete instructions

SUPERIOR FT-980 FILTER REPLACEMENTS

- 2 1KHz (SSB) sub for XF-8 9HSM \$ 60 ea
- 2 1KHz (SSB) sub for CFM-455J1 ceramic \$100 ea
- 250 or 500Hz (CW) sub for XF-8 9HC \$ 60 ea
- 500Hz (CW) sub for XF455 8MCM \$ 75 ea

DISCOUNT: 10% off any 2 or more of above
 SHIPPING \$3 US, \$5 Air (US & Canada), \$10 Elsewhere
 Order by mail or phone • VISA/MC or COD accepted
 Ask About Our Filters For Many Other Rigs

FOX-TANGO Corp.

Box 15944, W. Palm Bch, FL 33416
 147 Telephone: (305) 683-9587



fig. 4. Prescaler mounted on MFJ interface.

the display portion of the program be typed *exactly* as specified, including all embedded punctuation marks.

correction factor determinations

When the program is first typed, **lines 180** through **280** should be omitted. The missing lines may be entered after determining the K and D factors as described below.

If the correct nominal low-edge oscillator frequency has been entered on **line 290**, the indicated frequency will be somewhere within 10 kilohertz or so of the true value when the program is run and WWV, CHU, or the crystal calibrator is tuned in. Before starting the correction factor procedure, the calibrator should be checked to make sure it is accurately tuned to the standard-frequency station.

To determine K for a given band, only one measurement is necessary. With the rig set in the normal sideband position for the band in use, the crystal calibrator should be tuned to zero beat. The frequency indicated by the display should be noted and subtracted from the actual frequency of the calibrator harmonic. The result is the value of K . This operation should be repeated for each band or bandswitch segment and the numbers recorded for entry into the program (don't forget the minus signs where applicable).

Next, the transceiver should be set for CW and the calibrator harmonic tuned for the proper CW pitch rather than for zero beat. The direction and magnitude of the change in indicated frequency should be noted. The change will normally be about 0.8 kHz. An accurate value can readily be determined if the rig has a sharp audio or crystal filter. If a separate receiver is available, a still more accurate measurement can be made by noting the display reading when the transceiver is placed in the transmit mode and zeroed in the external receiver with a known reference. The RIT or OFFSET control should be set to zero for this measurement.

The value of D obtained is positive if the indicated frequency decreases as compared to the zero beat setting, and negative if it increases. By way of example, in the program (**fig. 5**) at 10 MHz the indicated frequency with WWV at zero beat in the SSBN (normal sideband) mode was 10010.8 kHz, leading to a K of minus 10.8. With the WWV carrier peaked in the audio filter, the indicated frequency increased another 800 Hz to 10011.6 kHz, yielding -0.8 for D . The numerical value of D holds for all bands, but the sign changes as the rig implements CW on different sides of zero beat.

Finally, the opposite sideband should be selected and the zero-beat procedure followed. The correction determined should be divided by D to give the multiplier used in **line 280**. Again with reference to **fig. 5**, my display read 10014.2 in the reverse (USB) mode, or 3.4 kHz higher than SSBN. This is 4.25 times as large as the CW correction and in the same direction, so the multiplier in **line 280** becomes 4.25.

operation

The program asks for entries of the band in MHz and the mode (0 for CW, 1 for normal SSB, and 2 for reverse SSB). It then displays the frequency to the nearest 0.1 kHz and the mode in use. A flickering of the display between two adjacent tenths digits indicates that the frequency is approximately halfway between the two values.

The readout follows the incremental tuning on receive and shows the transmitted frequency when the key is pressed or the mike activated. If there is considerable RF in the station the readout may be erratic on transmit, but will work if the drive is decreased to reduce the spurious RF.

To change the band and/or mode in use, press the f1 key. This restores the prompts and starts the process again.

adaptation to other transceivers

As described, the program and hardware should work with the Ten-Tec Omni as well as the Argosy. However, a number of other transceivers use upper/lower sideband selection rather than normal/reverse for the band in use. In general, it's merely necessary to change the format, substituting LSB and USB for SSBN and SSBR. Proper choice of correction factor values and algebraic signs will then produce equivalent performance.

Of more concern is the VFO frequency and its relationship to output frequency. Both the Kenwood TS520S and the Yaesu FT101E use backward-tuning VFOs—that is, the low-band edge corresponds to maximum VFO frequency. This requires modification of the frequency equation of **line 420** to read:

★ QUALITY PARTS ★ DISCOUNT PRICES ★ FAST SHIPPING!

SEND FOR FREE FALL 1985 CATALOG... 48 PAGES!

ALL ELECTRONICS CORP.

EDGE CONNECTORS

ALL ARE 1.56" SPACING.

- 22/44 EDGE CONNECTOR**
PC style \$2.00 each
10 for \$18.00
- 22/44 EDGE CONNECTOR**
solder lug style \$2.50 each
- 28/56 EDGE CONNECTOR**
PC style \$2.50 each
10 for \$22.00
- 36/72 EDGE CONNECTOR**
PC style \$3.00 each
- 43/86 EDGE CONNECTOR**
PC style \$4.50 each

TRANSISTORS

- 2N705 4 for \$1.00
2N2222A 3 for \$1.00
PN2222A 4 for \$1.00
2N2904 3 for \$1.00
2N2904 3 for \$1.00
2N2905 3 for \$1.00
MJ2955 \$1.50
2N3055 \$1.00
PMD 10K40 \$1.00
TIP 121 75¢
TIP 125 75¢

"SPECIAL PRICE" TRANSISTOR

PN1569 TO-92 N.P.N. plastic transistor
100 for \$3.00
1000 for \$60.00
LARGE QUANTITIES AVAILABLE

TRANSFORMERS

- 120 volt primaries
- 5.6 volts @ 750 ma. \$3.00
6 volts @ 200 ma. \$1.25
12 v.c.t. @ 200 ma. \$2.00
18 volts @ 850 ma. \$3.50
18 volts @ 1 amp. \$4.50
24 v.c.t. @ 200 ma. \$2.50
24 v.c.t. @ 400 ma. \$3.00
28 v.c.t. @ 15 amps \$20.00
30 v.c.t. @ 2 amps \$5.00

WALL TRANSFORMERS

- all plug directly into 120 vac outlet
- 4 VDC @ 70 ma. \$2.00
6 VDC @ 500 ma. \$3.50
6 VDC @ 750 ma. \$6.50
9 VDC @ 500 ma. \$5.00
12.5 VDC @ 255 ma. \$4.50
24 VDC @ 250 ma. \$3.00
MULTI-VOLTAGE @ 500 ma. \$3.00
3, 4, 5, 6, 7, 9, or 12 VDC \$7.50

MINI-BOX

Pomona #2104

Heavy-duty black phenolic project box with cover and screws. 2 1/2" x 1 1/2" x 1 1/2"

\$1.00 EACH

SOUND AND VIDEO MODULATOR FOR T.I. COMPUTER

T.I. # UM1381-1. Designed for use with T.I. computers. Can be used with video sources. Built-in A/B switch. Channel 3 or 4 selection switch. Operate on 12 vdc. Hook-up diagram included.

\$10.00 EACH

SUB-MINIATURE D TYPE CONNECTORS

- DB-15 PLUG \$2.75
DB-15 SOCKET \$4.00
DB-15 HOOD \$1.50
DB-25 PLUG \$2.75
DB-25 SOCKET \$3.50
DB-25 HOOD \$1.25

PARALLEL PRINTER CONNECTORS

Solder style 36 pin used on parallel data cables.

MALE CONNECTOR \$5.50 each
FEMALE CONNECTOR \$5.50 each

I.D.C. CONNECTORS

Will press fit on standard ribbon cable

DB-25 PLUG \$6.25
DB-25 SOCKET \$8.75
36 PIN MALE \$5.50
36 PIN FEMALE \$5.50

Twist-LOCK CONNECTOR

Same as Switchcraft #12CL5M 5 conductor in-line plug and chassis mount jack. Twist-lock style.

\$2.50/SET

TI SWITCHING POWER SUPPLY

Compact, well-regulated switching power supply designed to power Texas Instruments computer equipment

INPUT 14 - 25 vac @ 1 amp
OUTPUT + 12 vdc @ 350 ma.
+ 5 vdc @ 1.2 amp
- 5 vdc @ 200 ma.

SIZE: 4 1/4" x 4 1/4" x 1 1/4" high

\$5.00 each

13.8 VDC REGULATED POWER SUPPLY

These are solid state, fully regulated 13.8 vdc power supplies. Both feature 100% solid state construction, fuse protection, and L.E.D. power indicator U.L. listed

2 amp constant, 4 amp surge \$18.00 each
3 amp constant, 5 amp surge \$25.00 each

D.C. CONVERTER

Designed to provide a steady + 5 vdc @ 240 ma. from a battery supply of 3.5 to 6.25 volts.

2 1/8" x 1 1/8" x 1 1/8"

\$1.50 each

8" P.A. SPEAKER

C.T.S. Model 8B3079
8 ohms coil
3.0 oz ferrite magnet
Typical response range 100 - 10,000 hz
Power rating 15 watts max
Drilled to mount line matching transformers

\$5.00 each
CASE OF 8 SPEAKERS \$32.00

LINE CORDS

- TWO WIRE**
- 6' 18/2 SPT-1 flat 3 for \$1.00
6' 18/2 SPT-2 flat
6' 18/2 SJT round \$1.25 each
- THREE WIRE**
- 6' 18/3 flat \$1.50 each
8' 18/3 round \$2.00 each
8' 16/3 round \$4.00 each

COMPUTER GRADE CAPACITORS

- 2,000 mfd. 200 VDC 1 1/4" DIA x 5" HIGH \$2.00
3,600 mfd. 40 VDC 1 1/4" DIA x 3 1/4" HIGH \$1.00
6,400 mfd. 60 VDC 1 1/4" DIA x 4 1/4" HIGH \$2.50
9,700 mfd. 50 VDC 1 1/4" DIA x 4 1/2" HIGH \$3.00
31,000 mfd. 15 VDC 1 1/4" DIA x 4" HIGH \$2.50
72,000 mfd. 15 VDC 2" DIA x 4 1/2" HIGH \$3.50
185,000 mfd. 6 VDC 2 1/2" DIA x 4 1/2" HIGH \$1.50

SLIM LINE COOLING FAN

Etri # 99XM182 low noise fan. Measures 3 1/2" square x 1" deep. 21 cfm. 23 db. 1700 rpm

SPECIAL PRICE \$12.50 each

2K 10 TURN MULTI-TURN POT SPECTROL #MOD 534-7161

\$5.00 EACH

SOLID STATE BUZZER

Star #SMB-06L
6 vdc
TTL compatible
\$1.00 each
10 for \$9.00

12Vdc or 24Vdc POWER SUPPLY

DELTRON MODEL QD12/15-1.7 Dual plus and minus 12Vdc open frame power supply. Can be used as 24Vdc @ 1.5 amp. INPUT: either 115 Vac or 230 Vac. Fully regulated computer grade supply. 7" x 4 3/4" x 2 3/4"

\$12.50 each 10 for \$110.00

"SPECIAL PRICE" DUAL L.E.D. DISPLAYS

.560 high, 7 segment L.E.D. read-outs. Mount in 24 pin DIP sockets...

MAN-6640 orange, c.c. 75¢ each
FND-5148 red, c.c. 75¢ each
DL-527 red, c.a. 75¢ each

CASSETTE MECHANISM

New stereo cassette mechanism includes record/playback and erase heads. 2-12VDC motors drive belts, pulleys. 3-12VDC solenoids pinch wheels and other mechanical parts. These parts, used on other current model decks, would cost several times our selling price if purchased separately. Build your own audio or data recorder or use for spare parts.

5 1/4" X 3 1/2" X 3 1/4"

\$7.50 EACH 2 FOR \$12.50

3 1/2" SPEAKER

8 ohm impedance, Full range speaker. 8 oz magnet 4" diagonal mounting centers.

\$2.50 each 10 for \$20.00

SPRING LEVER TERMINALS

Two color coded terminals on a sturdy 2 1/4" x 3 1/4" bakelite plate. Great for speaker enclosures or power supplies.

\$1.00 each 10 for \$9.00

MINIATURE TOGGLE SWITCHES ALL ARE RATED 5 AMPS @ 125 VAC

- S.P.D.T. (on-on)**
PC style non-threaded bushing. 75¢ each 10 for \$7.00
- S.R.D.T. (on-on)**
Solder lug terminals. \$1.00 each 10 for \$9.00
100 for \$80.00
- S.R.D.T. (on-off-on)**
Solder lug terminals. \$1.00 each 10 for \$9.00
100 for \$80.00
- S.R.D.T. (on-off-on)**
PC lugs threaded bushing. \$1.00 each 10 for \$7.00
- S.R.D.T. (on-on)**
PC lugs threaded bushing. \$1.00 each 10 for \$7.00
- D.R.D.T. (on-on)**
Solder lug terminals. \$2.00 each 10 for \$19.00
100 for \$160.00

STANDARD JUMBO DIFFUSED T 1 1/2"

- RED 10 for \$1.50
100 for \$13.00
- GREEN 10 for \$2.00
100 for \$17.00
- YELLOW 10 for \$2.00
100 for \$17.00

D.P.S.T. LIGHTED ROCKER SWITCH

115 vac lighted rocker, snap mounts in 3/4" x 1 1/4" hole. Orange lens. 16 amp contact.

\$1.50

FLASHER LED

5 volt operation red jumbo T 1 1/2" size. \$1.00 each

MINI-PUSH BUTTON

S.P.S.T. momentary normally open 1/4" bushing. Red button. 35¢ each 10 for \$3.00

BI-POLAR LED HOLDERS

Two piece holder for jumbo LED. 10 for 65¢ 100 for \$5.00

KEY ASSEMBLY

5 KEY \$1.00 each
contains 5 single-pole normally open switches. Measures 3/4" long.

CLEAR CLIP LITE LED HOLDER

Make LED a fancy indicator. Clear. 4 for \$1.00

6 KEY

\$1.25 each
contains 6 single-pole normally open switches. Measures 4 1/4" long.

METAL OXIDE VARISTOR

Popular GE # 130LA10A varistor. 1/4" diameter. \$1.25 each

ALL ELECTRONICS CORP.
LOS ANGELES, CA STORE
905 S. Vermont Ave
213 380 8000

VAN NUYS, CA STORE
6228 Sepulveda Blvd
818 997 1806

MAIL ORDERS TO
PO BOX 24006
Los Angeles, CA 90006

TW 51010161 ALL ELECTRONIC
LASYLK MBX 62987748

TOLL FREE ORDERS ONLY
1 800 826 5432
(ORDER ONLY)
(IN CALIFORNIA: 1-800-258-6666)

ALASKA, HAWAII, OR INFORMATION
(213) 380-8000 NOC.O.D.!

QUANTITIES LIMITED
MINIMUM ORDER \$10.00
USA: \$3.00 SHIPPING
FOREIGN ORDERS
INCLUDING SUFFICIENT SHIPPING
CALIF RES. ADD 6 1/2%



```

110 REM DIGITAL FREQUENCY READOUT BY W3NNL 3/85
120 PRINT CHR$(147)
130 INPUT "BRND MHZ":B:INPUT"MODE (0=CW, 1=SSBN, 2=SSBR)":M
140 IF M=0 THEN M#="CW"
150 IF M=1 THEN M#="SSBN"
160 IF M=2 THEN M#="SSBR"
170 REM K AND D FACTORS BELOW APPLY TO W3NNL AROOSY ONLY
180 IF B=3.5 THEN K=-.1:D=-.8
190 IF B=7 THEN K=-.4:D=-.8
200 IF B=10 THEN K=-.8:D=-.8
210 IF B=14 THEN K=-.4:D=.8
220 IF B=21 THEN K=-10.4:D=.8
230 IF B=28 THEN K=-11.3:D=.8
240 IF B=28.5 THEN K=-11.8:D=.8
250 IF B=29 THEN K=-11.6:D=.8
260 IF B=29.5 THEN K=-11.5:D=.8
270 IF M=1 THEN D=0
280 IF M=2 THEN D=4.25*D
290 E=5000:REM ARGUSY PTO FREQ KHZ AT LOW BANDEDGE
300 PRINT CHR$(147)
310 POKE56589,0
320 POKE56590,1
330 POKE56582,2:POKE56583,0:POKE56591,16
340 POKE56591,71
350 POKE56327,255:POKE56326,255
360 IF PEEK(56577)>127 THEN 360
370 H=PEEK(56327):L=PEEK(56326)
380 POKE56335,16
390 POKE56335,33
400 N=255*(255-N)+255-L
410 IF N<32768 THEN N=N+65536
420 F=.08322975*N-E+1000*B+K+D
430 PRINT CHR$(19):PRINT" FREQ = ";
440 F=10#F
450 IF F-INT(F)<.5 THEN 470
460 F=F+1
470 F=INT(F)/10
480 IF F<10000 AND F>9000 THEN 560
490 IF F-INT(F)<.001 THEN 520
500 PRINTF:PRINT CHR$(157);
510 PRINT".0":PRINT M# GOTO 530
520 PRINTF:PRINT M#
530 DET C# IF C#CHR$(133) THEN 120
540 IF PEEK(56577)<128 THEN 540
550 GOTO 360
560 PRINT CHR$(29);
570 GOTO 490

```

fig. 5. C-64 program for digital frequency readout.

$$420 F = E - .08322975 * N + 1000 * B + K + D$$

The TS520 VFO tunes from 5.5 to 4.9 MHz, so the value of E in line 290 becomes 5500. The FT101 VFO tunes from 9.2 to 8.7 MHz, so E for this rig is 9200.

Since $9200/16 = 575$, the FT101 pushes the computer past its upper frequency limit. This is where the previously mentioned aliasing effect comes to the rescue: the increasing rate at which pulses are missed causes the timer to slow down in exact proportion to the frequency excess. It turns out that correct results are obtained if the count is subtracted from $2 \times 65536 = 131,072$. Thus, line 410 should be changed to read: $410 N = 131072 - N$

Rigs that have provision for 160 meters require the insertion of a correction-factor line for that band in the block between lines 170 and 270. For the TS520, B should equal 1.8, and for the FT101, B should equal 1.5. Line 200 may of course be omitted for rigs which do not have a 10-MHz band.

Both the TS520 and FT101 have external access to the VFO. The TS520 VFO buffer is available through a 2:1 resistive divider at the VFO phone plug connector, and through direct connection at Pin 1 of the EXT VFO socket. The former connection is preferable if enough signal is obtained to drive the prescaler. The FT101 VFO is available at Pins 6 or 7 of the EXT VFO socket.

The program in fig. 5 will accommodate oscillator frequencies from about 2.7 to 8 MHz. Frequencies below 2.7 MHz can be handled if line 410 is omitted.

final comments

The most likely causes for failure of the system to operate are typing errors in the program or a problem in the prescaler. If the latter is running, it should be possible to hear harmonics at multiples of the divided-down frequency if the receiver antenna is brought near the circuit board. An analog DC voltmeter will read about 2.5 volts when connected to Pin 12 of the 74197. Some experimentation with preamplifier base resistor and input coupling capacitor values may be necessary if the VFO output is very low.


One very quickly becomes addicted to the circuit, to the extent that the rig is never on unless the computer is first fired up. It is satisfying to be able to set the display to 14000 kHz on a seemingly dead 20-meter band and have one of the beacon stations pop out right in the center of the audio passband.

acknowledgements

Thanks are due to Earle Lewis, W3JKX, Fritz Hauff, W3NZ, and Dick Briner, WB3GVU, for furnishing the Kenwood and Yaesu manuals. The photographs were taken by my son-in-law, Herb Hoppe, Jr.

ham radio

SATELLITE TELEVISION RECEIVER SEMIKIT

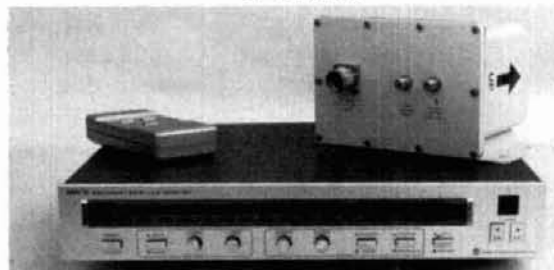

with dual conversion downconverter

FEATURES:


- Infrared remote control tuning
- AFC, SAW filter
- RF or video output
- Stereo output
- Polarator controls
- LED channel & tuning indicators

Install six factory assembled circuit boards to complete.

SEMIKIT	\$300.00
Completed downconverter add	100.00
Completed receiver and downconverter add	150.00

JAMES WALTER SATELLITE RECEIVER

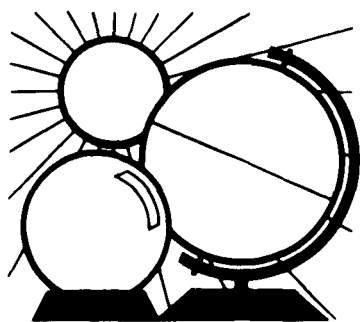2697 Nickel, San Pablo, CA 94806 149 Tel. 415-724-0587



DX FORECASTER

Garth Stonehocker, KØRYW

winter DX season

November through February constitutes the winter DX season. Because the D and E regions of the ionosphere receive less energy from the sun in the northern hemisphere during this time, less ionization occurs. Therefore, the daytime attenuation of radio signals is lower in winter than during the rest of the year.

Attenuation is a result of signal energy being absorbed by ions in the D region (35-50 miles or 60-80 km) above the earth. The amount of absorption is related to the zenith angle* to the sun from the points where your path crosses this D region. And on any propagation path, absorption increases with the number of transits of the D region and varies inversely with frequency. So in working DX, it pays to use the higher frequency bands to obtain more distance per hop (resulting in fewer transits) and less signal loss.

This is why we generally think of 6, 10, or 15 meters for DXing. But in winter, particularly near sunspot minimum, we have the opportunity to work DX on the lower frequency bands with lower signal loss, day or night, than at any other time of the year. But you can't *always* count on it; signals traveling a high latitude path may be poor for several days at a time. This is known as the winter anomaly.¹

Along with the lower signal attenuation, the QRN decreases as fewer local thunderstorms pass through your area and the large thunderstorm areas near

the equator move further south, requiring more than one hop to get to us. This decreases the noise some 6-8 dB, which is particularly noticeable on the 160, 80, and 40-meter bands.

Even though ion production in the D, E, and lower F regions is lower, ions are better able to diffuse and drift upward along the geomagnetic field lines into the F region. This layer is the major factor in defining the maximum usable frequency. In winter this maximum usable frequency rises rapidly as the sun rises each day, peaking just after noontime, then diminishing during the afternoon, evening, and through the night to a low value just before dawn the next day. The exception to this situation is for locations nearer to the equator, where the ionization continues to drift and diffuse up during the afternoon and evening to become the transequatorial maximums described in my October, 1983 column.² The maximum usable frequency peak reached each day and the depth of the predawn minimum frequency of the next morning are related to the solar flux of the day. The higher the flux that day, the higher the frequency peak and the lower the dip the next morning.

Another advantage during the winter season is that the geomagnetic field is least disturbed during November and December. This manifests as least variation of the magnitude and direction of the geomagnetic field lines in an hour's time. This translates into fewer periods of QSB during these months.

last-minute forecast

The first and second weeks of November are expected to favor the higher HF bands, 10 through 30 meters. The solar flux is expected to be higher at this time of the month and result in higher MUFs. If the geomagnetic field is also disturbed at this time then transequatorial propagation on southern paths should also be expected. More hours of darkness, less QRN, and stable signal conditions give an edge to the lower bands for east-west and northern DX contacts this time of year. The lower HF bands are expected to be best the last two weeks of the month. You can update this forecast daily by listening to the time and frequency radio station, WWV, on 2.5, 5, 10, 15, and 20 MHz at 18 minutes after each hour. When the solar flux, as announced, is below 75 and the geomagnetic A is less than 15 or K is less than 4 the lower bands should be best. If the geophysical indices are higher, consider using the higher HF bands instead.

The Taurids meteor showers will occur from October 26 to November 22, with a maximum count of ten per hour from the 3rd through the 10th of November. Lunar perigee is on the 12th, and a full moon falls on the 27th. A total (totality of 1 minute 59 seconds duration) eclipse of the sun is calculated to be visible on November 12th way down in the Antarctic regions. It starts south of Africa at 1209 UT and moves to the tip of South America, ending at 1612 UT. The bands open to Antarctica on the accompanying propagation chart should lower to 40 meters and then recover during the above time period on eclipse day. Try for a contact!

band-by-band summary

Ten, twelve, and fifteen meters, the day-only DX bands, will be open from morning to early evening almost every day, and to most areas of the world. The openings on the higher of these

*The Zenith angle is the angle measured from directly above an observer to the sun (0 degrees when the sun is directly overhead, 90 degrees when the sun is at the horizon).

ham radio

Reader Service

For literature or more information, locate the Reader Service number at the bottom of the ad, circle the appropriate number on this card, affix postage and send to us. We'll hustle your name and address to the companies you're interested in.

101 113 125 137 149 161 173 185 197 209 221 233 245 257 269 281 293 305 317 329 341
102 114 126 138 150 162 174 186 198 210 222 234 246 258 270 282 294 306 318 330 342
103 115 127 139 151 163 175 187 199 211 223 235 247 259 271 283 295 307 319 331 343
104 116 128 140 152 164 176 188 200 212 224 236 248 260 272 284 296 308 320 332 344
105 117 129 141 153 165 177 189 201 213 225 237 249 261 273 285 297 309 321 333 345
106 118 130 142 154 166 178 190 202 214 226 238 250 262 274 286 298 310 322 334 346
107 119 131 143 155 167 179 191 203 215 227 239 251 263 275 287 299 311 323 335 347
108 120 132 144 156 168 180 192 204 216 228 240 252 264 276 288 300 312 324 336 348
109 121 133 145 157 169 181 193 205 217 229 241 253 265 277 289 301 313 325 337 349
110 122 134 146 158 170 182 194 206 218 230 242 254 266 278 290 302 314 326 338 350
111 123 135 147 159 171 183 195 207 219 231 243 255 267 279 291 303 315 327 339
112 124 136 148 160 172 184 196 208 220 232 244 256 268 280 292 304 316 328 340

Limit 15 inquiries per request.


NAME _____ CALL _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Please use before December 31, 1985

November 1985

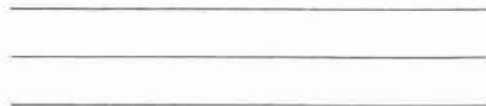

AFFIX POSTAGE
OR
POST OFFICE
WILL NOT
DELIVER

ham
radio
magazine

READER SERVICE CENTER
P.O. BOX 2558
WOBURN, MA 01888

ATTN: Reader Service Dept.

WESTERN USA

GART	PST	Directional Indicators							
		N	NE	E	SE	S	SW	W	NW
0000	4:00	30	40	20	10	10	10	10	20
0100	5:00	20	40	20	12	12*	10	10	20
0200	6:00	30	40	20	20*	12	12	12	20
0300	7:00	30	40	20	20	15	15	15	20
0400	8:00	30	40	20	20	15	20	20	30
0500	9:00	40	40	20	20	20	20	20	30
0600	10:00	40	40	20	20	20	20	20	30
0700	11:00	40	40	30	20	20	20	20	40
0800	12:00	40	40	30	20	20	20	20	40
0900	1:00	40	40	30	30	20	20	20	40
1000	2:00	40	40	30	30	20	20	20	40
1100	3:00	40	40	30	30	30	30	30	40
1200	4:00	40	40	30	30	30	30	30	40
1300	5:00	40	30	15	15	30	30	30	40
1400	6:00	40	20	12	12	20	30	30	40
1500	7:00	40	20	10	10	15	20	20	40
1600	8:00	40	20	10	10	12	20	20	40
1700	9:00	40	20	10	10	12	20	20	40
1800	10:00	40	30	10	10	12	15	20	40
1900	11:00	80	40	12	10	12	12	20	20
2000	12:00	80	40	15	10	12	12	15	20
2100	1:00	80	40	20	10	12	10	12	20
2200	2:00	80	40	20	10	12*	10	12	20
2300	3:00	80	80	20	10	10	10	10	20

MID USA

MST	Directional Indicators							
		N	NE	E	SE	S	SW	W
5:00	30	40	20	12	12	10	10	20
6:00	30	40	20	15	12	12	12	20
7:00	30	40	20	20	15	15	15	20
8:00	40	40	20	20	20	20	20	20
9:00	40	40	20	20	20	20	20	30
10:00	40	40	20	20	20	20	20	30
11:00	40	40	30	20	20	20	20	40
12:00	40	40	30	20	20	20	20	40
1:00	40	40	30	30	20	30	20	40
2:00	40	40	30	30	20	30	30	40
3:00	40	40	30	30	20	30	30	40
4:00	40	40	15	30	30	30	30	40
5:00	40	30	12	15	30	30	30	40
6:00	30	20	12	12	30	30	30	40
7:00	40	20	10	12	20	20	30	40
8:00	40	20	10	10	15	20	20	40
9:00	40	20	10	10	12	20	20	40
10:00	40	20	10	10	12	20	20	40
11:00	40	30	10	10	12	15	20	80
12:00	80	40	12	10	12	12	20	20
1:00	80	40	15	10	12	12	15	20
2:00	80	40	20	10	12	10	12	20
3:00	80	80	20	10	12	10	12	20
4:00	80	80	20	10	12	10	10	20

EASTERN USA

CST	EST	Directional Indicators							
		N	NE	E	SE	S	SW	W	NW
6:00	7:00	40	40	20	15	15	15	15	30
7:00	8:00	40	40	20	20	20*	20	20	30
8:00	9:00	40	40	20	20	20	20	20	40
9:00	10:00	40	40	20	20	20	20	20	40
10:00	11:00	40	40	20	20	20	20	20	40
11:00	12:00	40	40	30	20	20	20	20	40
12:00	1:00	40	40	30	20	20	20	20	40
1:00	2:00	40	40	30	20	20	20	20	40
2:00	3:00	40	40	30	20	20	20	20	40
3:00	4:00	40	40	30	30	30	30	30	40
4:00	5:00	40	30	12	30	30	30	30	40
5:00	6:00	30	20	12	15	30	30	30	40
6:00	7:00	30	20	10	15	20	20	20	40
7:00	8:00	40	20	10	12	20	20	20	40
8:00	9:00	40	20	10	12	15	20	20	40
9:00	10:00	40	20	10	10	12	30*	20	80*
10:00	11:00	40	20	10	10	12	20	20	80*
11:00	12:00	40	20	10	10	12	20	20	80
12:00	1:00	40	20	10	10	12	15	20	80
1:00	2:00	80	30	12	10	12	12	20	30
2:00	3:00	80	40	15	10	12	12	15	20
3:00	4:00	80	40	20	10	12	10	12	20
4:00	5:00	80	80	30	10	12	10	12	20
5:00	6:00	80	80	30	12	12	10	10	20

The italicized numbers signify the bands to try during the transition and early morning hours, while the standard type provides the MUF during "normal" hours.
 *Look at next higher band for possible openings.

ICOM R71-751-R7000* COMPUTER INTERFACE




MICROCOMPUTER ELECTRONICS CORPORATION NOW OFFERS THE M.E.C. 71α COMPUTER CONTROL INTERFACE THAT WILL CONTROL AND EXPAND THE CAPABILITY OF THE ICOM R71A.



MAIN MENU Control center for entire system. Showing: 24HR UTC time; radio freq. & mode; memory CH, freq, mode plus ID functions for your selection.



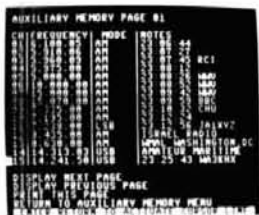32 CH RADIO MEMORY Showing freq to 10 Hz, mode, filter w/n. Load/change any memory, mode, filter direct from keyboard and print command.



AUXILIARY MEMORY Showing page 1 of 47 pages each having 15 memories. Freq, mode, UTC time and room for your notes. Auto log feature allows instant logging of receiver freq, mode, time.

- **Easy to use.** No computer knowledge needed, automatic program loading. No disk or tape required (except for aux memory storage).
- **Menu driven** to aid user at each step.
- **No radio modification necessary** (ICOM EX309 — not supplied — required).
- **AUTO LOG** Allows logging of radio freq, mode and time by press of a key.
- **UNLIMITED STORAGE** via computer disk or tape (store 705 CH per disk side). Let your imagination run wild.
- **Software update.** As new software is developed MEC will make it available to owner subscribers.

- **HARD COPY** via computer printer of all memory channels.
- **KEYBOARD** memory loading.

Price to be announced - CALL. Available Fall 85. Dealer inquiries invited.

EEB is the exclusive distributor for Microcomputer Electronics Corp.'s product worldwide. Address all inquiries to EEB.

EEB is an authorized ICOM dealer and service center. Buy with confidence.

GET ALL THE DETAILS. WRITE OR CALL EEB TODAY



- Prices & specs subject to change
- Shipping charges not included
- Returns subject to 20% restock charge
- Free catalog in USA; all others 3 IRC's

ORDER TOLL FREE 800-368-3270

Tech Info — VA orders 703-938-3350

ELECTRONIC EQUIPMENT BANK

516 Mill Street NE

Vienna, VA 22180 USA

bands will be shorter, occur closer to local noon, and provide paths mainly to the southern hemisphere with a possibility of transequatorial openings.

Twenty, thirty, and forty meters are both day and night bands. Twenty is the maximum usable band for DX in the northern directions these days during the daytime, then teams up with 30 meters to fill in through the night for the day-only bands. Forty meters becomes the main over-the-pole DX daytime band, with some hours covered by 30. This path may be affected by anomalous absorption during a few days of the month.

Eighty and one-sixty meters, the night-only DX bands, will exhibit short-skip propagation during daylight hours, then lengthen for DX at dusk. These bands follow the darkness path, opening to the east just before your sunset, swinging more to the north-south near midnight, and ending up in the Pacific areas during the hour or so before dawn. Eighty is the maximum usable band for some night hours now during sunspot minimum; consequently, signal strength and signal quality can be expected to improve. One-sixty may also be better. Remember the DX windows of 3790-3800, 1825-1830, and 1850-1855 kHz.

references

1. Garth Stonehocker, KØRYW, "DX Forecaster," *ham radio*, December, 1984, page 63.
2. Garth Stonehocker, KØRYW, "DX Forecaster," *ham radio*, October, 1983, page 92.

ham radio

✓ 150



GUS BROWNING, W4BPD's DX'ERS MAGAZINE

For over 17 years, Gus's DX'ERS MAGAZINE has brought thousands of DX'ERS worldwide, timely, pertinent information on when and where to find those elusive DX stations.

Gus's personable, chatty writing style and his years of DX operating experience makes the DX'ERS MAGAZINE a unique publication. One year \$14.00 USA, Canada & Mexico.

Gus also prints high quality QSLs and other related items.

Write today for a free sample of his QSLs and DX'ERS MAGAZINE.

Gus Browning, W4BPD • PO Drawer 405 • Cordova, SC 29039

✓ 151



Crystal Filters
for KENWOOD TS830, TS930, TS940

Our filters have received universal praise. As famous contributor VE3BMV wrote recently in Radiosporting's review: *Kenwood filters are great but 8-pole Fox Tango filters are better. I have put a pair in my 930 and the improvement is fantastic.*

FOX TANGO MATCHED-PAIR FILTER KITS

2.1KHz for SSB, 400Hz for CW	\$139.00
SSB and CW (4 filters) SPECIAL	\$250

Kits include detailed instructions and all needed parts. Specify bandwidths and Kenwood Model when ordering. FOX TANGO filters equal or exceed the claims of imitators. Why risk disappointment? Get the real thing!

SHIPPING: \$3 US, \$5 Air (US & Canada), \$10 Elsewhere
Order by mail or phone • VISA/MC or COD accepted
Ask About Our Filters For Many Other Rigs

FOX-TANGO Corp.
Box 15944, W. Palm Bch, FL 33416
Telephone: (305) 683-9587 ✓ 147

1986 CALLBOOKS



The "Flying Horse" has a great new look!

It's the biggest change in Callbook history! Now there are 3 new Callbooks for 1986.

The North American Callbook lists the amateurs in all countries in North America plus those in Hawaii and the U.S. possessions.

The International Callbook lists the calls, names, and address information for licensed amateurs in all countries outside North America. Coverage includes Europe, Asia, Africa, South America, and the Pacific area (exclusive of Hawaii and the U.S. possessions).

The Callbook Supplement is a whole new idea in Callbook updates. Published June 1, 1986, this Supplement will include all the activity for both the North American and International Callbooks for the preceding 6 months.

Publication date for the 1986 Callbooks is December 1, 1985. See your dealer or order now directly from the publisher.

- | | |
|---|---------|
| <input type="checkbox"/> North American Callbook
incl. shipping within USA | \$25.00 |
| incl. shipping to foreign countries | 27.60 |
| <input type="checkbox"/> International Callbook
incl. shipping within USA | \$24.00 |
| incl. shipping to foreign countries | 26.60 |
| <input type="checkbox"/> Callbook Supplement, published June 1st
incl. shipping within USA | \$13.00 |
| incl. shipping to foreign countries | 14.00 |

SPECIAL OFFER

- | | |
|---|---------|
| <input type="checkbox"/> Both N.A. & International Callbooks
incl. shipping within USA | \$45.00 |
| incl. shipping to foreign countries | 53.50 |

Illinois residents please add 6 1/4% sales tax.
All payments must be in U.S. funds.

RADIO AMATEUR
callbook INC.



Dept. F
925 Sherwood Dr., Box 247
Lake Bluff, IL 60044, USA

Tel: (312) 234-6600



SHORT CUT



A quarter-wave antenna is great for range. But it's too tall for most VHF handheld applications. So Larsen® has cut the quarter-wave down to size, without taking any shortcuts in design or construction.

The Larsen HQ (helical-quarter-wave) Kulduckie® antenna stands just slightly taller than a helical type, but measures up to almost full quarter-wave performance. The helical design below

gives it stability and keeps it short—nine to twelve inches. The flexible quarter-wave on top extends the range and allows it to bend 180°.

Larsen offers ten different VHF HQ series antennas in the 136 to 174 MHz range, to work with most popular handheld radios. So whether you're calling for help, or just shooting the breeze, you can be sure that Larsen Kulduckie antennas will never run short on performance.



Larsen Antennas
The Amateur's Professional™

See your favorite amateur dealer or write for a free amateur catalog.

IN USA: Larsen Electronics, Inc.
11611 N.E. 50th Ave.
P.O. Box 1799
Vancouver, WA 98668
206-573-2722

IN CANADA: Canadian Larsen Electronics, Ltd.
149 West 6th Ave.
Vancouver, B.C. V5Y 1K3
604-872-8517

LARSEN® KÜLROD® AND KÜLDUCKIE® ARE REGISTERED TRADEMARKS OF LARSEN ELECTRONICS, INC.

a scanner for CB to 10-meter conversions

Diode matrix replaces 40-position selector switch

There have been many articles on CB-to-10 meter conversion projects over the last few years, one of which was an excellent article by MacFarquhar and Grant¹ in which they described the steps necessary to convert a Citizens Band AM radio to an FM transceiver operating on 10 meters. In this article, we show how to replace their 40-position channel selector switch with some digital logic that adds the ability to scan up to 20 channels. In addition, we described a way to obtain a 100 kHz offset for repeater work without using a second crystal. All the other features of MacFarquhar and Grant's original modification are preserved.

If you already have a converted CB, enough information is provided here to build the scanner; if you're starting the project from scratch, the MacFarquhar and Grant article will be necessary.*

circuit description

Since the CB was designed for mobile operation, the converted radio must use a mobile power source or operate from a 13.8 volt DC power supply. Power supplies are available commercially at surplus stores, and many excellent articles on building your own have been published.

*Reprints are available from *ham radio*, Greenville, New Hampshire 03048, for \$3.00 each.

Rather than build a separate +5 volt supply for the scanner, we borrowed a few mA from the +5 volt supply in the CB. Low-power components were selected to minimize the load on the existing CB radio power supply.

The scanner and control circuit requires only six integrated circuits and can be built on a 3 × 3 inch (7.6 × 7.6 cm) card. A diode encoder is used to program the operating frequencies. This gives the advantage of being able to select any of ten frequencies and more importantly, gives one a choice of crystals (frequency) to use.

A schematic diagram of the scanner section is shown in fig. 1. U1 is a decade counter with a built-in binary to decimal decoder. The outputs feed the diode encoder and indicator LEDs. The input to U1 comes from oscillator U2 (in the scan mode) or flip-flop U3A (in the single step mode). The other half of U3 is used to offset the frequency by 10 kHz. The frequency of the original CB is controlled by a Phase Locked Loop integrated circuit, or PLL IC. The diode encoder converts the ten decimal outputs from U1 to four control inputs to the PLL. The four control inputs cause the PLL to change its output frequency and the receive/transmit frequency of the radio. U4A is used to monitor the squelch of the radio and stop the scan when a signal breaks the squelch.

A type 555 oscillator (U2) is used to provide a scan step to the counter. The 7555 is a CMOS version of the 555 timer; its operation is identical except that the 7555 draws much less current. Radio Shack carries a TLC-555 which is also low current.

By Robert K. Baker, W2FMY, 263 Washington Avenue, Saugerties, New York 12477, and Gary Bischoff KB2GA, 1358 Charles Hommel Road, Saugerties, New York 12477

The oscillator is cut off by grounding pin 4 or 5. Pin 5 is connected to S3, the SCAN/LOCK switch. Pin 4 is controlled by U4A, a comparator. When the radio receives a signal that breaks the squelch, the voltage at Q120 collector goes up, forcing the output of U4A low, stopping the oscillator. The other half of U4 is used to drive a "busy" light for visual indication when a signal is present.

The diodes at the input to the counter form an OR circuit so that inputs to either diode will step the counter. U3A is a debouncer for the STEP switch, which should be a push button or spring loaded toggle. U3A is used on an R-S flip-flop — even though it is a D-type device — by wiring the switch contacts directly into the Reset and Set inputs.

If S2 is closed, the output of U3B will be held in RESET state, forcing a logic zero to PLL control pin P0. Frequency coverage will be ten "even" frequencies — 29.50, 29.52 through 29.68 MHz. If S2 is open, U3B will be toggled by the end carry from the counter each time the counter counts ten pulses or wraps around. When the output of U3B is high, frequency coverage is shifted up 10 kHz to cover the "odd" frequencies of 29.51, 29.53 through 29.69. The circuit will alternately scan the even then odd channels while S2 is open. When the frequency is shifted up, the high level at U3 pin 9 turns Q11 on, lighting the +10 kHz LED.

The ten outputs from the CD4017 counter drive 10 LEDs in addition to feeding the encoder. Q1 through Q10 (and Q11) can be almost any general purpose NPN small signal transistor such as a 2N2222 or 2N3904. The 4.7 kilohm base resistors were chosen to provide about 1 mA of base current, which allows practically any transistor to be used. Note that there is only one dropping resistor (1K) used for the ten LEDs since only one LED is on at a time. The current for the LEDs comes from the 13.8 volt source.

A diode encoder is used to convert from a decimal number to the digital data required by the CB PLL chip to select different frequencies. **Figure 2** shows the encoder used with our selected output frequencies and crystal frequency.

Figure 3 shows a transmit offset circuit that can be added to obtain the -100 kHz offset required for repeater access. Two boards were built using the crystal switching scheme described by MacFarquhar and Grant. They worked fine, but the price of the 10.795 MHz crystal exceeded the price of the CB board. A simple circuit was therefore developed to make use of the existing counter U1 when working through a repeater. The circuit (**fig. 3**) consists of two cascaded timer circuits, where U5 is a one-shot enable for oscillator U6. When the microphone PTT switch is depressed, the voltage on the CB point 14 goes positive and

is inverted by Q13. The resulting negative shift at the collector of Q13 is coupled via the 470 pF capacitor to a diode gate and to the input of U5. The negative spike at pin 2 triggers U5, allowing oscillator U6 to send five pulses to the CD4017 clock input via the diode, which becomes the third leg of the existing OR circuit. When the PTT switch is released, the negative going level change at CB point 14 is coupled through the 0.01 microfarad capacitor to the input of U5 and another string of five pulses is sent to the 4017 counter. The circuit is disabled for simplex operation by grounding pin 4 of U5.

The pulse rate of U6 is about 240 microseconds. It is enabled for about 1 millisecond by U5. The time that U5 enables U6 must be set carefully. When the entire scanner is operating, the pulse width of U5 can be trimmed by selecting the proper value for R_X . Use a potentiometer or a decade box and lower the value of R_X until four pulses are output from U6. The pulses can be counted by using the PTT switch and observing the LEDs. Note the value at which the pulses change from five to four. Raise the value of R_X until six pulses are observed. Note this value and install a fixed resistor for R_X that is about halfway between these two values. If the 0.005 μ F capacitor is accurate R_X should be around 150 kilohm. A mylar capacitor should be used in this circuit.

frequency and crystal selection

The following explanation is provided to explain frequency control and how to use an available crystal. The CB Phase Locked Loop (PLL) was designed to operate in the range of 2.24 to 2.68 MHz. Attempting to operate the PLL outside this design range may require modification of the PLL lowpass filter.^{3,4}

The present ARRL 10-meter FM band plan covers the range of 29.50 to 29.70 MHz. The national calling frequency is 29.60 MHz (similar to 146.52 on 2 meters). Repeater outputs are on 29.62, 29.64, 29.66, and 29.68, with their inputs 100 kHz lower on 29.52 through 29.58. 29.50 is used as another simplex frequency. The CD4017 decade counter forms the heart of the scanner and gives us access to all ten frequencies. The ten additional frequencies are obtained by using a flip-flop to program the low order bit on the CB's PLL. The ten "odd" frequencies are presently all simplex frequencies.

To see how a crystal is chosen, we start at the required output frequency and work backward. If, for example, 29.6 MHz is the output frequency selected, the PLL VCO is mixed with a 10.695 MHz crystal oscillator to generate the transmit frequency. Our 29.6 MHz target requires that the VCO operates at 29.60 + 10.695 or 40.295 MHz. This in turn is mixed with the third harmonic of another crystal oscillator (Q105 on



HF Equipment	Regular	SALE
IC-735 HF transceiver/SW rcvr/mic	849.00	749 ⁹⁵
PS-55 External power supply	160.00	144 ⁹⁵
AT-150 Automatic antenna tuner	349.00	314 ⁹⁵
FL-32 500 Hz CW filter	59.50	
EX-243 Electronic keyer unit	50.00	
IC-745 9-band xcvr w/ 1-30 MHz rcvr	999.00	779 ⁹⁵
PS-35 Internal power supply	160.00	144 ⁹⁵
EX-241 Marker unit	20.00	
EX-242 FM unit	39.00	
EX-243 Electronic keyer unit	50.00	
FL-45 500 Hz CW filter (1st IF)	59.50	
FL-54 270 Hz CW filter (1st IF)	47.50	
FL-52A 500 Hz CW filter (2nd IF)	96.50	89 ⁹⁵
FL-53A 250 Hz CW filter (2nd IF)	96.50	89 ⁹⁵
FL-44A SSB filter (2nd IF)	159.00	144 ⁹⁵
HM-10 Scanning mobile microphone	39.50	
SM-6 Desk microphone	39.00	
HM-12 Extra hand microphone	39.50	
MB-12 Mobile mount	19.50	



IC-751 9-band xcvr/1-30 MHz rcvr	1399.00	1199
PS-35 Internal power supply	160.00	144 ⁹⁵
FL-32 500 Hz CW filter (1st IF)	59.50	
FL-63 250 Hz CW filter (1st IF)	48.50	
FL-52A 500 Hz CW filter (2nd IF)	96.50	89 ⁹⁵
FL-53A 250 Hz CW filter (2nd IF)	96.50	89 ⁹⁵
FL-33 AM filter	31.50	
FL-70 2.8 kHz wide SSB filter	46.50	
HM-12 Extra hand microphone	39.50	
SM-6 Desk microphone	39.00	
RC-10 External frequency controller	35.00	
MB-18 Mobile mount	19.50	

IC-720A 9-band xcvr • (CLOSEOUT) •	1349.00	749 ⁹⁵
PS-15 20A external power supply	149.00	134 ⁹⁵
FL-32 500 Hz CW filter	59.50	
FL-34 5.2 kHz AM filter	49.50	
BC-10A Memory back-up	8.50	
SM-5 8-pin electret desk mic	39.00	
MB-5 Mobile mount	19.50	

Other Accessories:	Regular	SALE
PS-15 20A external power supply	149.00	134 ⁹⁵
CF-1 Cooling fan for PS-15	45.00	
EX-144 Adaptor for CF-1/PS-15	6.50	
PS-30 Systems p/s w/cord, 6-pin plug	259.95	234 ⁹⁵
OPC Opt. cord, specify 2, 4 or 6-pin	5.50	
SP-3 External base station speaker	49.50	
SP-5 Remote speaker for mobiles	25.00	
CR-64 High stab. ref. xtal (745/751)	56.00	
PP-1 Speaker/patch (specify radio)	139.00	129 ⁹⁵
SM-8 Desk mic - two cables, Scan	69.95	
AT-100 100W 8-band auto. antenna tuner	349.00	314 ⁹⁵
AT-500 500W 9-band auto. antenna tuner	449.00	399 ⁹⁵
AH-1 5-band mobile antenna w/tuner	289.00	259 ⁹⁵
GC-4 World clock • (CLOSEOUT) •	99.95	79 ⁹⁵



HF linear amplifier	Regular	SALE
IC-2KL 160-15m solid state amp w/p/s	1795.00	1299
6-meter VHF Portable	Regular	SALE
IC-505 3/10W 6m SSB/CW portable	449.00	399 ⁹⁵
BP-10 Internal Nicad battery pack	79.50	
BP-15 AC charger	12.50	
EX-248 FM unit	49.50	
LC-10 Leather case	34.95	

VHF/UHF base multi-modes	Regular	SALE
IC-551D 80W 6-meter SSB/CW	699.00	599 ⁹⁵
EX-106 FM option	125.00	112 ⁹⁵
BC-10A Memory back-up	8.50	
SM-2 Electret desk microphone	39.00	
IC-271A 25W 2m FM/SSB/CW	699.00	569 ⁹⁵
AG-20 Internal preamplifier*	56.95	
IC-271H 100W 2m FM/SSB/CW	899.00	759 ⁹⁵
AG-25 Mast mounted preamplifier*	84.95	
IC-471A 25W 430-450 SSB/CW/FM xcvr	799.00	699 ⁹⁵
AG-1 Mast mounted preamplifier*	89.00	
IC-471H 75W 430-450 SSB/CW/FM	1099.00	969 ⁹⁵
AG-35 Mast mounted preamplifier*	84.95	

For a Limited time!
With the purchase of an IC-271A/H or IC-471A/H get the matching PREAMP* for only • \$1.00 Extra.

Accessories common to 271A/H and 471A/H	Regular	SALE
PS-25 Internal power supply for (A)	99.00	89 ⁹⁵
PS-35 Internal power supply for (H)	160.00	144 ⁹⁵
PS-15 External power supply	149.00	134 ⁹⁵
SM-6 Desk microphone	39.00	
EX-310 Voice synthesizer	39.95	
TS-32 CommSpec encode/decoder	59.95	
UT-15 Encoder/decoder interface	12.50	
UT-15S UT-15S w/TS-32 installed	79.95	

VHF/UHF mobile multi-modes	Regular	SALE
IC-290H 25W 2m SSB/FM, TTP mic	549.00	479 ⁹⁵
IC-490A 10W 430-440 SSB/FM/CW	649.00	579 ⁹⁵

VHF/UHF/1.2 GHz FM	Regular	SALE
IC-27A Compact 25W 2m FM w/TTP mic	369.00	299 ⁹⁵
IC-27H Compact 45W 2m FM w/TTP mic	409.00	359 ⁹⁵
IC-37A Compact 25W 220 FM, TTP mic	449.00	299 ⁹⁵
IC-47A Compact 25W 440 FM, TTP mic	469.00	399 ⁹⁵
PS-45 Compact 8A power supply	112.95	99 ⁹⁵
UT-16/EX-388 Voice synthesizer	29.95	
SP-10 Slim-line external speaker	29.95	
IC-3200A 25W 2m/440 FM w/TTP	549.00	489 ⁹⁵
UT-23 Voice synthesizer	29.95	
AH-32 2m/440 Dual Band antenna	32.95	
Larsen PO-K Roof mount	20.00	
Larsen PO-TLM Trunk-lip mount	20.18	
Larsen PO-MM Magnetic mount	19.63	
IC-1271A 10W 1.2 GHz SSB/CW Base	999.00	889 ⁹⁵
ATV-1200 ATV interface unit	TBA	
PS-25 Internal power supply	99.00	89 ⁹⁵
EX-310 Voice synthesizer	39.95	
UT-15S CTCSS encoder/decoder	79.95	
IC-120 1W 1.2 GHz FM Mobile	499.00	449 ⁹⁵
ML-12 1.2 GHz 10W amplifier	339.00	299 ⁹⁵

Repeaters	Regular	SALE
RP-3010 440 MHz, 10W FM, xtal cont.	999.00	899 ⁹⁵
RP-1210 1.2 GHz, 10W FM, 99 ch. synth	1199.00	1089
Duplexer 1210 1.2 GHz duplexer	1199.00	1089
Cabinet		249.00



Order Toll Free
Use your Credit Card!

Hand-held Transceivers	Regular	SALE
Deluxe models		
IC-02AT for 2m	349.00	289 ⁹⁵
IC-04AT for 440 MHz	379.00	289 ⁹⁵
Standard models	Regular	SALE
IC-2A for 2m	239.50	189 ⁹⁵
IC-2AT with TTP	269.50	199 ⁹⁵
IC-3AT 220 MHz, TTP	299.95	239 ⁹⁵
IC-4AT 440 MHz, TTP	299.95	239 ⁹⁵

Accessories for Deluxe models	Regular
BP-7 425mah/13.2V Nicad Pak - use BC-35	67.50
BP-8 800mah/8.4V Nicad Pak - use BC-35	62.50
BC-35 Drop in desk charger for all batteries	69.00
BC-60 6-position gang charger, all batts	SALE 359.95
BC-16U Wall charger for BP7/BP8	10.00
LC-11 Vinyl case	17.95
LC-14 Vinyl case for Dix using BP-7/8	17.95
LC-02AT Leather case for Dix models w/BP-7/8	39.95

Accessories for both models	Regular
BP-2 425mah/7.2V Nicad Pak - use BC35	39.50
BP-3 Extra Std. 250 mah/8.4V Nicad Pak	29.50
BP-4 Alkaline battery case	12.50
BP-5 425mah/10.8V Nicad Pak - use BC35	49.50
CA-2 Telescoping 2m antenna	10.00
CA-5 5/8-wave telescoping 2m antenna	18.95
FA-2 Extra 2m flexible antenna	10.00
CP-1 Cig. lighter plug/cord for BP3 or Dix	9.50
DC-1 DC operation pak for standard models	17.50
LC-2AT Leather case for standard models	34.95
RB-1 Vinyl waterproof radio bag	30.00
HH-SS Handheld shoulder strap	14.95
HM-9 Speaker microphone	34.50
HS10 Boom microphone/headset	19.50
HS-10SA Vox unit for HS-10 & Deluxe only	19.50
HS-10SB PTT unit for HS-10	19.50
ML-1 2m 2.3w in/10w out amplifier	SALE 79.95
SS-32M Commspec 32-tone encoder	29.95

Receivers	Regular	SALE
R-7000 25-2000 MHz, 117V AC	899.00	789 ⁹⁵
RC-12 Infrared remote controller	TBA	
R-71A 100 kHz-30 MHz, 117V AC	\$799.00	659 ⁹⁵
RC-11 Infrared remote controller	59.95	49 ⁹⁵
FL-32 500 Hz CW filter	59.50	
FL-63 250 Hz CW filter (1st IF)	48.50	
FL-44A SSB filter (2nd IF)	159.00	144 ⁹⁵
EX-257 FM unit	38.00	
EX-310 Voice synthesizer	39.95	
CR-64 High stability oscillator xtal	56.00	
SP-3 External speaker	49.50	
CK-70 (EX-299) 12V DC option	9.95	
MB-12 Mobile mount	19.50	



HOURS • Mon. thru Fri. 9-5:30; Sat. 9-3
Milwaukee WATS line: 1-800-558-0411 answered evenings until 8:00 pm Monday thru Thursday.
Please use WATS lines for Ordering
use Regular lines for other Info and Service dept.

Order Toll Free: 1-800-558-0411

In Wisconsin (outside Milwaukee Metro Area)
1-800-242-5195

AMATEUR ELECTRONIC SUPPLY [®] *Inc.*

4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200

AES BRANCH STORES

Associate Store


WICKLIFFE, Ohio 44092
28940 Euclid Avenue
Phone (216) 585-7388
Ohio WATS 1-800-362-0290
Outside Ohio 1-800-321-3594

ORLANDO, Fla. 32803
621 Commonwealth Ave.
Phone (305) 894-3238
Fla. WATS 1-800-432-9424
Outside Florida 1-800-327-1917

CLEARWATER, Fla. 33575
1898 Drew Street
Phone (813) 461-4267
No In-State WATS
No Nationwide WATS

LAS VEGAS, Nev. 89106
1072 N. Rancho Drive
Phone (702) 647-3114
No In-State WATS
Outside Nevada 1-800-634-6227

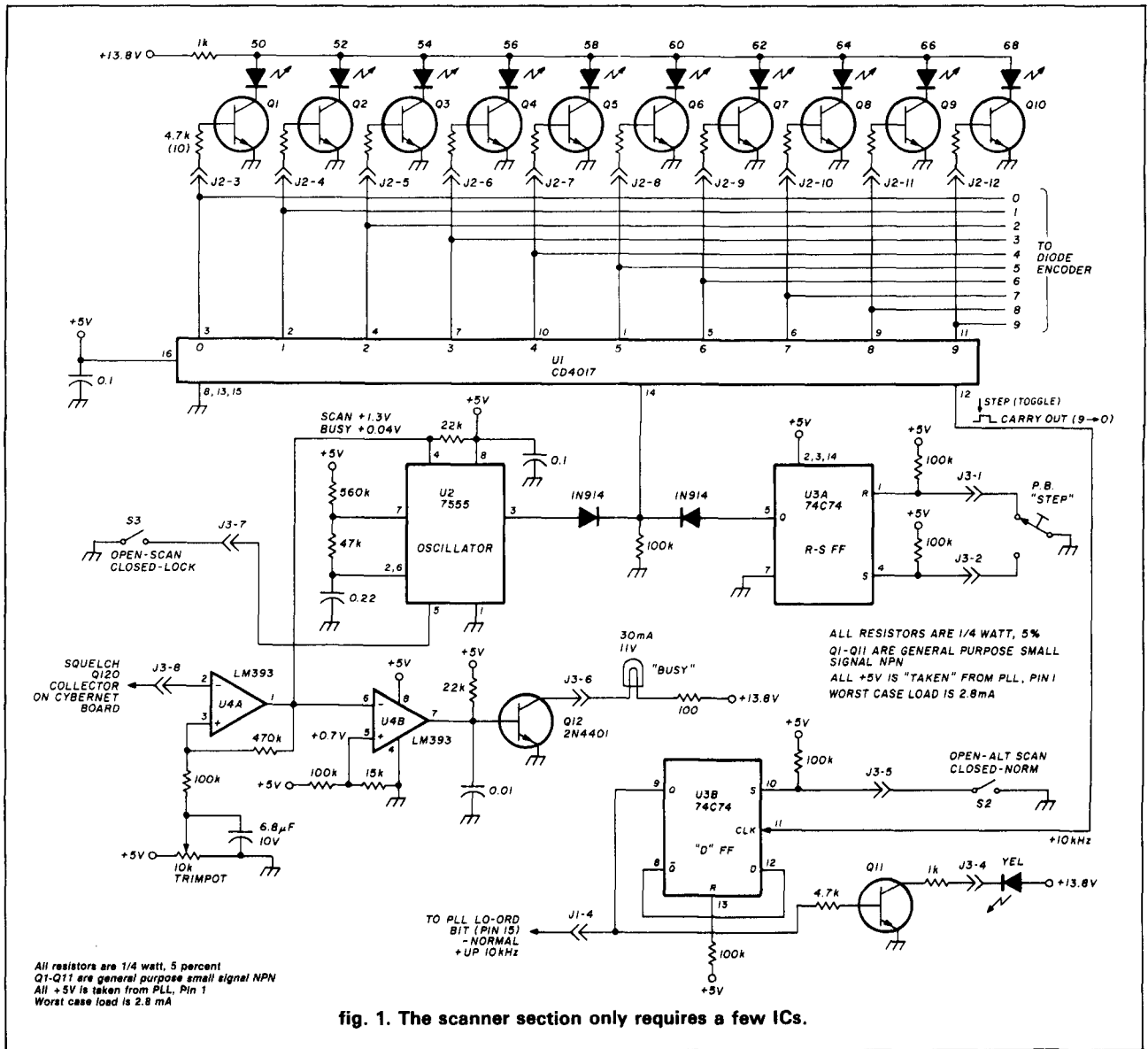CHICAGO, Illinois 60630
ERICKSON COMMUNICATIONS
5456 N. Milwaukee Avenue
Phone (312) 631-5181
Outside Illinois 1-800-621-5802



the CB). The difference frequency is filtered and applied to the PLL. This frequency must fall in the range of 2.24 to 2.68 MHz.

When we started this project, we had about a dozen crystals left over from an earlier 10-meter club project. These crystals were marked 12.61333 MHz and had been ordered for a PLL using a reference frequency of 5 kHz rather than 10 kHz. The scheme we used required the crystal to operate up or down one third of a 5 kHz step or 1.67 kHz. We found the oscillator (Q105) more agreeable to being "rubbered" up than down, and had no trouble reaching 12.615 MHz. This frequency would have resulted in having to shift down to 10 kHz from 29.7 to reach 29.69 and not being able to use 29.50, which was clearly not desirable. By reducing C118 to 15 pF we were able to move the fre-

quency up to 12.61833 MHz. Two units were built with crystals of 12.61833 MHz and they worked fine with the original value of C118.

The crystal's third harmonic of 37.855 MHz, when subtracted from the VCO frequency of 40.295 MHz, yields a difference of 2.44 MHz. To match at the 10 kHz PLL reference frequency, the PLL divider must divide by 244. The divide number is controlled by applying logic levels to the P0-P8 inputs of the PLL. Note that the PLL chip has internal pull-down resistors on these inputs. An open circuit is a logic zero, and a logic 1 is obtained by pulling an input up toward +5 volts.

We can develop a truth table based upon our choice of crystal. The P inputs of the PLL have binary "weights" with P0 having a value of 1, P1 having a

table 1. Truth table.

desired frequency (MHz)	VCO F (MHz)	mixer F* (MHz)	divider**	PLL program pin values								
				P8	P7	P6	P5	P4	P3	P2	P1	P0
29.50	40.195	2.3400	234	0	1	1	1	0	1	0	1	0
29.51	40.205	2.3500	235	0	1	1	1	0	1	0	1	1
29.52	40.215	2.3600	236	0	1	1	1	0	1	1	0	0
29.53	40.225	2.3700	237	0	1	1	1	0	1	1	0	1
29.54	40.235	2.3800	238	0	1	1	1	0	1	1	1	0
29.55	40.245	2.3900	239	0	1	1	1	0	1	1	1	1
29.56	40.255	2.4000	240	0	1	1	1	1	0	0	0	0
29.57	40.265	2.4100	241	0	1	1	1	1	0	0	0	1
29.58	40.275	2.4200	242	0	1	1	1	1	0	0	1	0
29.59	40.285	2.4300	243	0	1	1	1	1	0	0	1	1
29.60	40.295	2.4400	244	0	1	1	1	1	0	1	0	0
29.61	40.305	2.4500	245	0	1	1	1	1	0	1	0	1
29.62	40.315	2.4600	246	0	1	1	1	1	0	1	1	0
29.63	40.325	2.4700	247	0	1	1	1	1	0	1	1	1
29.64	40.335	2.4800	248	0	1	1	1	1	1	0	0	0
29.65	40.345	2.4900	249	0	1	1	1	1	1	0	0	1
29.66	40.355	2.5000	250	0	1	1	1	1	1	0	1	0
29.67	40.365	2.5100	251	0	1	1	1	1	1	0	1	1
29.68	40.375	2.5200	252	0	1	1	1	1	1	1	0	0
29.69	40.385	2.5300	253	0	1	1	1	1	1	1	0	1

1 = logic one (+5)
0 = logic zero (ground)

Note 1: Q105 oscillator 12.61833 MHz new crystal.

Note 2: Oscillator × 3 = 37.85499 MHz.

*2.680 maximum, 2.240 minimum.

$$**divisor = \frac{(F_{OUT} + 10.695) - (3 \text{ oscillator}) \text{ MHz}}{10 \text{ MHz}}$$

value of 2 and so on up to P8 with a value of 256. The frequency choice of 29.50 to 29.68 MHz works out so that P8 is always zero (floating), and the P5, P6, and P7 inputs are always logic 1, which we tied up to +5. To cover the desired frequencies, we need control only four inputs, P1 through P4. Since we have shown that the "divide by" number for 29.60 MHz is 244 and we are spacing our steps 20 kHz, it follows that 29.62 MHz would require two 10 kHz counts higher on 246. From the information that we now have, the truth table shown in table 1 has been developed.

Examination of the table reveals that the P0 input is a logic zero for all of the "standard" 10-meter FM channels, which happen to be represented by even numbers. Switching the P0 input to 1 (+) shifts the PLL up 10 kHz to ten "in between" frequencies which are odd numbers — 29.51, 29.53, 29.55, etc.

Table 1 also shows the frequencies at the VCO output and the mixer output. Note that the mixer frequency must fall in the range of 2.24 to 2.68 MHz for the PLL to operate correctly. Table 1 was derived from a spreadsheet program that does the mathematics involved with the crystal selection and frequency generation.† To check on the usability of a crystal, the user enters the crystal frequency and the highest output frequency desired; the program calculates the VCO

output frequency, the mixer output frequency, the divider necessary to match the 10 kHz input to the PLL, and the PLL program pin values. The spread sheet is useful for demonstrating what is happening in the circuit as well as for crystal and frequency selection.

To build the encoder, replace each + in the truth table with a diode. No diodes are needed for the — points on the table because of the pull-down resistors in the PLL.

construction

The first step in building this radio should be to get the CB working as a CB. (The referenced articles cover this subject in detail.^{2,3,4}) We took the additional step of inserting pins in the CB at the points where connections are to be made such as the speaker output, microphone input, and the volume and squelch potentiometers.

In addition to making the board easy to remove, we can interchange boards when problems arise. We found that the extra work was beneficial.

†A copy of the spread sheet, written in Lotus 123 and VisiCalc for an IBM PC and compatibles, or in VisiCalc for Apples, is available from the authors. Send an SASE for information.

The board used for the modification was made by Cybernet when the CB craze was in full swing. Cybernet manufactured these boards for several manufacturers such as Hy-Gain, Kraco, and others.

We found some CB boards with wrong value components. If the phase locked loop can not be made to lock by adjusting the VCO coil slug, check the value of R103 in the VCO circuit. The correct value is 1.5K, not 3.3K. Also, C101, which is buried in wax, should be 18 pF. (Some had a purple mark and measured 22 pF. If C101 is black, it's OK. This is apparently a production change that works on 27 MHz but doesn't work on the high end of 10 meters.)

We had a severe birdie problem on all 20 channels during tune-up of one of the first conversions that we built. The birdie was apparently caused by the 10.695 offset oscillator's being off in frequency. To prevent problems when the radio is being tuned up, all three oscillators must operate at the correct frequency. Radio Shack carries 3-10 pF trimmers (catalog No. 272-1338) that fit directly in the board; they are useful for adjusting the oscillators. Start with the 10.24 MHz reference oscillator. Loosely couple a frequency counter to the collector of transistor Q104. If the frequency is off, install a trimmer in location CT103 and try to move the frequency. C178 may have to be changed from 56 pF to a 39 or 43 pF capacitor. Set the frequency to exactly 10.24 MHz. To adjust the 10.695 MHz offset oscillator, connect the frequency counter to the emitter of Q109. Since the oscillator is not buffered, any appreciable capacitive loading will pull the oscillator frequency. We used a 10 to 1, low capacity oscilloscope probe to connect the counter. Install a trimmer in location CT102, and change C127 to a lower value. Adjust the CT102 for 10.695 MHz out with the transmitter keyed. Next connect the frequency counter to the dummy load at the output. Set up the P0-P8 PLL inputs to a known value such as 29.60 MHz and tune CT101 for the correct output, again with the

transmitter keyed. If C118 must be changed, use the largest value that will permit CT101 to bring the oscillator to the desired frequency. This will make CT101 much less critical to adjust.

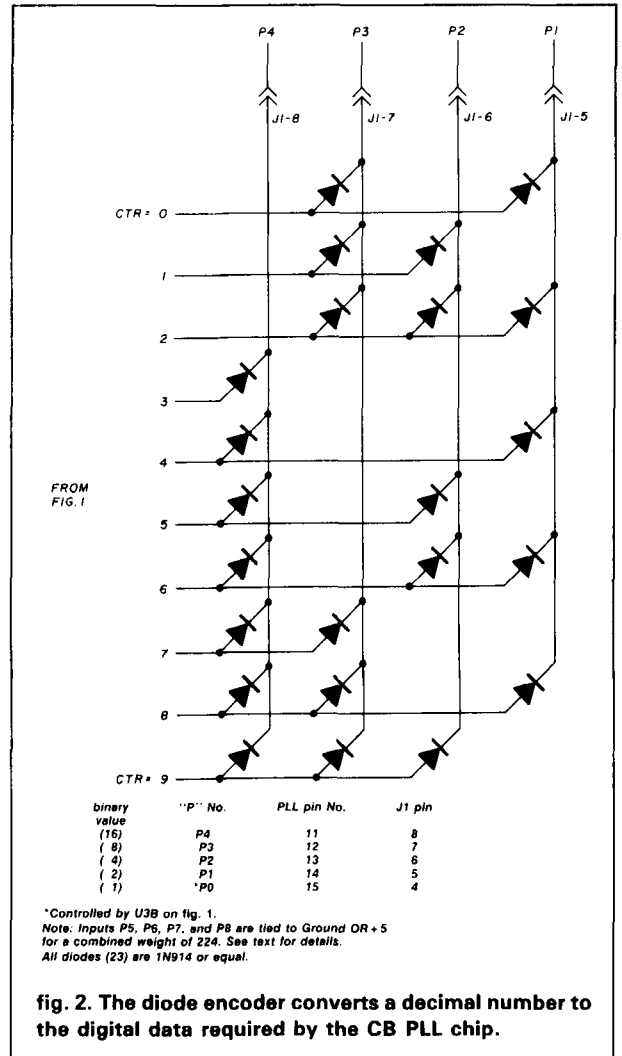


fig. 2. The diode encoder converts a decimal number to the digital data required by the CB PLL chip.

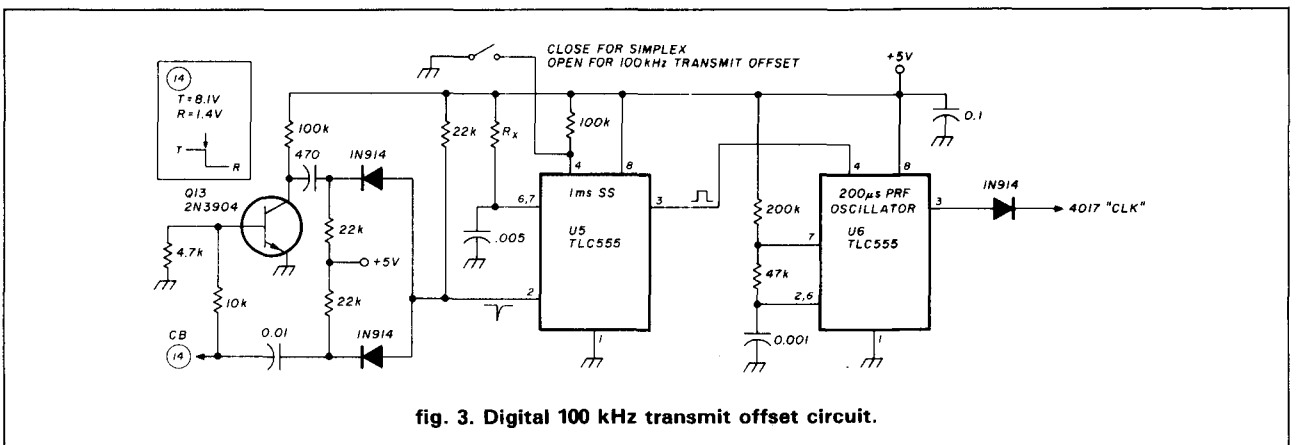


fig. 3. Digital 100 kHz transmit offset circuit.



The monthly magazine with a natural blending of two popular hobbies — Ham Radio and Computers

- ★ Articles on Ham Radio & Most Personal Computers
- ★ Hardware & Software Reviews
- ★ Various Computer Languages
- ★ Construction Articles
- ★ Much Much More...

"...received my moneys worth with just one issue..."

—J. Trenbick

"...always stop to read CTM, even though most other magazines I receive (and write for) only get cursory examination..."

—Fred Blechman, K6UGT

U.S.A.....\$15.00 for 1 year
 Mexico, Canada\$25.00
 Foreign\$35.00(land) - \$55.00(air)
 (U.S. funds only)
 Permanent (U.S. Subscription)\$100.00
 Sample Copy\$3.50



Circulation Manager
 1704 Sam Drive
 Birmingham, Alabama 35235
 Phone 205/854-0271

Name _____
 Call Sign _____
 Address _____
 City _____ State _____
 Zip _____ Phone _____
 Date _____
 Signature _____

154

conclusion

The scanner approach described above adds a new dimension to the CB-10 meter conversion by providing a simple yet versatile circuit. The digit offset control also has the capability of shifting up 100 kHz as well as down, in case you want to use the rig as a repeater — one local Amateur (Bob, W2XL) answered a call in the repeat mode and managed to work a station in Mexico.

In addition to the communication possibilities of a low power 10-meter FM rig, many local Amateurs use the radio to monitor 10 meters for isolated band openings. A dedicated rig eliminates the need to change frequency to check conditions; the radio is set up to monitor several repeaters. With the sunspot cycle on the decline, 10 meter openings are more sporadic, and when they occur, it's nice to know about them.

The circuits covered in this article can be used as shown or they can be used as a starting point for other innovative designs. There are other ways of obtaining the correct frequencies using a scanner approach such as using a decade counter and an adder to go directly into the PLL, which would make it easy to add the repeater offset. That may be a subject for a future article.

references

1. Ian MacFarquhar, VE3AQN, and Ken Grant, VE3FIT, "CB to 10 FM — One Group's Approach," *ham radio*, February, 1983, page 16.
2. Bob Heil, K9EID, "Experience 10-Meter FM Operation," *QST*, August, 1981.
3. J. Robert Witmer, W3RW, "Modifying a CB-Board Synthesizer for Amateur Use," *QST*, March, 1983.
4. Penn Clower, W1BG, "CB to CW? — Converting the HY-Gain Board," *ham radio*, July, 1982.

ham radio

AVAILABLE NOW



THE 1986 ARRL HANDBOOK FOR THE RADIO AMATEUR

Great gift idea for a ham friend or for yourself!

The new 1986 ARRL HANDBOOK is chockfull of projects, ideas, hints and kinks, theory and thousands of other handy things for your hamshack. New items include: switching power supplies, data and telemetry transmission, a section on conjugate matching by Walt Maxwell, data interface and Packet Radio, and remote control aircraft to name just a few examples. New projects include: 30 amp power supply, ATV monitoring instruments, digital frequency synthesizer, 1500 watt output 160 meter amplifier, state-of-the-art preamps for all Amateur VHF/UHF frequencies and much, much more. A grand total of 244 new pages! This is the reference book to have. Order your's today. ©1985. Over 1100 pages.

- AR-HB86
- AR-BB86

Softbound \$17.95
 Hardbound \$26.95



Please enclose \$3.50 to cover shipping and handling



ham radio magazine **BOOKSTORE**
 GREENVILLE, NH 03048

Unadilla Amateur Antenna Baluns

For 20 years, preferred by Amateur, Commercial and Military Operators
First with built-in lightning arrester-minimizes TVI, maximizes power handling



W2AU 1:1 & 4:1
Only **\$17.95**, UPS
shipping & tax included



W2DU-HF
Only **\$19.95**, UPS
shipping & tax included



W2DU-VHF
Only **\$19.95**, UPS
shipping & tax included

W2AU Broadband Ferrite Core Baluns

For medium power (1000 watts RF min.) and broadband operation 3-40 MHz.

W2AU 1:1

- * 50 to 50 or 75 to 75 ohms
- * For dipoles, V's, beams, quads

W2AU 4:1

- * 200 to 50 or 300 to 75 ohms
- * For high impedance antennas such as folded dipoles

W2DU Non-Ferrite Very High Power Baluns

W2DU-HF (High Power)

- * 1.8-30 MHz
- * 3000-9000 watts with 1:1 antenna SWR
- * 1500-5000 watts with 2:1 antenna SWR

W2DU-VHF (High Power and Extended Range)

- * 30-300 MHz
- * 2000-4000 watts with 1:1 antenna SWR
- * 1200-2400 watts with 2:1 antenna SWR

BONUS!

Free
With
Your
Order



The Dandy Dipole

Quickly design and construct any of over 180 multi-band dipole variations, using traps. Wiring tables are included to take away the guesswork. Also includes dozens of practical details.

Purchase from any of over
300 dealers nationwide,
or order direct

- Send free catalog PC/84
 W2AU 1:1 & W2AU 4:1 \$17.95 ea.
 W2DU-HF & W2DU-VHF \$19.95 ea.
 Total Order \$ _____
 Tax & UPS Shipping Included

Name _____
 Address _____
 City _____ State _____ Zip _____
 Phone () _____

- AmEx VISA Mastercard
 Card # _____
 Valid (AmEx only) _____
 Expires _____

COD Check Money Order
**To ORDER or request free full line catalog of
 baluns, antenna relays and antenna traps, call
 1-800-523-0027**

24 HOURS—7 DAYS A WEEK!

**NY/HI/AK/CAN residents please use coupon
 or call collect 315-437-3953, 8-5 EST**

1 week delivery for credit card & C.O.D.,
 2 weeks for personal check.

60 DAY MONEY BACK GUARANTEE

Unadilla/Reyco/Inline

Division of Microwave Filter Company, Inc.

6743 Kinne Street, E. Syracuse, N.Y. 13057 **HR11**

✓ 155

WARNING SAVE YOUR LIFE OR AN INJURY

Base plates, flat roof mounts, hinged bases, hinged sections, etc., are not intended to support the weight of a single man. Accidents have occurred because individuals assume situations are safe when they are not.

Installation and dismantling of towers is dangerous and temporary guys of sufficient strength and size should be used at all times when individuals are climbing towers during all types of installations or dismantlings. Temporary guys should be used on the first 10' or tower during erection or dismantling. Dismantling can even be more dangerous since the condition of the tower, guys, anchors, and/or roof in many cases is unknown.

The dismantling of some towers should be done with the use of a crane in order to minimize the possibility of member, guy wire, anchor, or base failures. Used towers in many cases are not as inexpensive as you may think if you are injured or killed.

Get professional, experienced help and read your Rohn catalog or other tower manufacturers' catalogs before erecting or dismantling any tower. A consultation with your local, professional tower erector would be very inexpensive insurance.

Paid for
By the
Following:

ROHN®
 P.O. Box 2000
 Peoria, IL 61656

HOT ROD ANTENNA

Achieve 1 or 2 db gain over ANY 1/2 wave two meter telescopic antenna. The AEA model HR-1 Hot Rod™ antenna was designed by Dr. D.K. Reynolds (designer of the IsoPole) to deliver maximum performance for any hand-held transceiver with a BNC fitting.

The factory-tuned HR-1 is 20% shorter, lighter and places far less stress on your hand-held connector and case. It will easily handle over 25 watts of power, making it an excellent emergency base or mobile antenna. In the collapsed position, the Hot Rod antenna will perform like a helical quarter wave.

The Hot Rod antennas can be expected to make the same improvement to hand-held communications that the IsoPole brand antennas have made to base station operations. Why pay more when the best costs less?

Prices and Specifications subject to change without notice or obligation.

**ADVANCED ELECTRONIC
APPLICATIONS, INC.**

P.O. Box C-2160,
 Lynnwood, WA 98036
 (206) 775-7373
 Telex: 152571 AEA INTL

AEA Brings you the
Breakthrough!

✓ 156



the HAM STATION

P.O. Box 4405
220 N. Fulton Ave.
Evansville, IN 47710

Stores Hours
MON-FRI 9AM - 6PM
• SAT 9AM - 3PM

WARRANTY SERVICE CENTER FOR:
ICOM, YAESU, TEN-TEC

Terms:
Prices Do Not Include Shipping.
Price and Availability Subject to
Change Without Notice
UPS COD \$2.50 Per Package

AEA	
ATU-1000 Superb Interface	\$1100.00
CP-100 Deluxe interface	CALL
CP-1 interface	189.95
MP-1 Micropatch	129.95
MBA-TOR Software	85.00
DR-DXDR QSO	85.00/75.00
PKT-1 Packet Controller	459.95
PK-64	CALL

ALINCO	
2 Mtr & 440 Mhz Amplifiers in Stock	CALL

ANTENNA SPECIALISTS (AVANTI)	
AP153 3G 2M on Glass	\$34.00
AP200 3G 220 MHz on Glass	38.00
AP450 3G 450 MHz	34.00
AP450 5G 450 MHz	38.00

ASTRON	
R57A 5-7 Amp	\$ 49.00
RS10A 7.5-10 Amp	59.00
RS12A 9-12 Amp	69.00
RS20A 16-20 Amp	89.00
RS20M 16-20 Amp w/meter	109.00
RS35A 25-35 Amp	135.00
RS35M 25-35 Amp w/meter	149.00
RS50A 37-50 Amp	199.00
RS50M 37-50 Amp	225.00

BENCHER	
BY-1 Black/By-2 Chrome	\$39/49.00
ZA-1A Balun	19.00

BUTTERNUT	
HF4B 20, 15, 12, 10 Mtr	\$195.00
HF3B Butterfly Beam	179.95
12 Mtr Kit	20.00
HF5V 80-10M Vertical	119.95
TBR-160S 160M Resonator	49.00
RMK-II Roof Mount Kit	49.00
STR-II Radial Kit	29.00
HF-2V 80 40M Vertical	115.00
2M CV5 5-1/2 WAVE 2M Vertical	55.00
SC-3000 30-512MHz Scanner Ant	55.00

B&W	
370-15 80-10M Folded Dipole	\$145.00
AT-110 5 Band Trap Dipole	76.00
AT-55 4 Band Trap Dipole	58.00
Coax Switches and Accessories in Stock	CALL

CONNECT SYSTEMS	
Private Patch III	\$479.95
Private Patch II	329.95
Separate Control Link Required Below 220.5 MHz	



CUSHCRAFT	
MULTI-BAND	
A3	\$215.00
A4	279.00
A743-A744	75.00
R3 Motor Tuned Vert.	279.00
A5 80-10M Vertical	99.00
VHF-UHF	
215WB 2M Wide Band	79.00
230WB Stacked 215's	219.00
32-19 Boomer 19ELE 2M	95.00
A147-4	32.95
A449-6	34.00
A449-11	44.00
Rango Ranger 2M 6M 220 450	39.95
OSCAR TWIST	
A144-10T	54.00
A144-20T	75.00
A147-20T	75.00
416TB	64.00
AOP-1 Package	149.00

DAIWA	
CN410M 3.5-150MHz	\$65.00
CN520 1.8-60MHz	63.00
CN540 50-148MHz	72.00
CN550 144-250 MHz	81.00
CN620B 1.8-150MHz	110.00
CN630 140-450MHz	130.00
CN720B Same As CN620B w/large Meter	CALL
CS401 4 Pos. Switch	62.00
CS201 2 Pos. Switch	23.00



HAL	
Computer Interfaces & Dedicated Terminals	

HEIL	
Products in Stock	CALL

HUSTLER	
All Amateur Antennas in Stock	CALL

HY-GAIN	
TH7DXS 7EL Tribander	\$479.00
Explorer 14 3EL Tribander	329.00
OK710 30/40 Mtr. Kit - Mono Banders in Stock	85.00
18HTS 80-10M Vertical	439.00
18AVT/WBS 80-10M Vertical	109.00
14AVQ/WBS 40-10M Vertical	75.00
2 Mtr. Beams in Stock	CALL
V2S, V3S, V4S Verticals in Stock	CALL
Rotors and Headphones in Stock	CALL



751 Top of the Line	\$1179.00
745 Gen. Cov	769.00
735 Fantastic New Xcvr	CALL
R71A World Class Receiver	629.95
R7000 Super Scanner	CALL
1271A New 1.2GHz Base Rig	CALL
471A/471H 430-450MHz All Mode	699.95/949.95
271A/271H 2M Allmode	569.95/749.95
47A 440MHz Mobile	399.95
37A 220MHz Mobile	CALL

ICOM	
27A/27H 2M 25W & 45W Mobile	CALL
3AT/4AT 220/440 H.T.'s	ea. 229.95
2AT 2M H.T.	199.95
02AT 2 Mtr. H.T.	CALL
04AT 440 MHz H.T.	319.95
3200 Dualband Mobile	CALL
Dual Band Antennas in Stock	CALL
Super Huge Inventory of Accessories & Radios	

KANTRONICS



Pack/rv Communicator in Stock	
UTU Universal Terminal Unit	\$179.95
CALL Ux Do-It-All Terminal Unit	CALL
Interface II Deluxe Interface	229.95
Large Inventory of Software & Pac-Term Programs in Stock	CALL

KLM

2M-14C 2M Circular Ant	\$ 85.00
2M-22C 2M Circular Ant	120.00
2M-16L BX 2M Ant	105.00
435-18C w/CS-2	120.00
435-40CX Circular Ant	149.95
Many More Antennas in Stock	CALL

LARSEN

NLA 150/220/450 MAG Mnt	ea. \$ 42.95
NLA 270 Dual Band MAG Mnt Ant	59.95

MFJ

1229 Interface/free Software	\$159.95
1224 Interface/free Software	85.00
1228 Interface/free Software	59.95
989 3KW Roller Inductor tuner	289.95
949C 300W W/Tuner w/D Load	135.00
941D 300 W/Full feature tuner	89.95
204 Antenna Bridge	71.95
422 Keyer Bencher Combo	99.95

MIRAGE

B1016 10/160W-Preamp	\$249.95
B3016 30/160W-Preamp	204.95
B23A 2/30W-Preamp	89.95
D1010N 10/100W 430-450 MHz	289.95

NYE

MB-V-A The Ultimate Tuner	\$499.95
---------------------------	----------

SANTEC

ST-20T New Superior Function H.T.	CALL
-----------------------------------	------

SHURE

444D Hi-Lo Z Desk Mic	\$ 55.00
-----------------------	----------



New 561 Corsair II	CALL
Titan-Your Last Amplifier	CALL
Century 22 CW Xcvr	\$349.95
525D Argosy	525.00
2510 Satellite Station	409.95
2591 2M H.T.	269.95
229 2KW Tuner	249.95
4229 2KW Tuner Kit	189.00
Large Stock of Ten Tec Products	CALL

TOKYO HY-POWER

HL30V 3 30 Amp	\$ 62.95
HL35V 3 30 Amp w/GasJet	75.00
HL160V 3 10-160W Amp	295.95
HL160V25 25-160W Amp	259.95
HL-20U 430-449 MHz 3-20W Amp	105.95
HL 120U 430-449 MHz	
10-100W Amp	319.95
HC-2000 2KW Tuner	295.95
HC 400L Tuner w/Dual Needle Mtr	175.95
HRA-2 2 Mtr. GasJet Preamp	119.95
HRA-7 70 CM GasJet Preamp	119.95

WELZ

SP-220 1.8-220 MHz Peak Mtr	\$49.95
SP-230 1.8-150 MHz Watt Mtr	46.95
SP-420 140-525 MHz Peak Mtr	63.95
Dual Band Base Antenna	CALL
CT15A Dummy Load DC-500MHz	\$12.00
CT15N Same as above but w/N-Conn	21.00
DP72S Mobile Duplexer	29.95
DP-ED 770-E Dual Band Antenna	29.95
DP-SPM Mag. Mnt. for above Antenna	24.95
Large Stock of All SWR & Power Meters	CALL



FRG9600 60-30MHz Scanner	CALL
FRG8800 HF Communications Rcvr	CALL
FT980 Deluxe Xcvr	1425.00
FT757GX Gen. Cov. Xcvr	CALL
FP757HD Heavy Duty Power Supply	175.00
FC757AT Auto Ant. Tuner	235.00
MMB-20 Mounting Bracket for 757GX	.24.00
FT726R Tr. Band Xcvr	CALL
FT726R Modules in Stock	CALL
MD-188 Desk Mic	69.00
FT209RH 2M H.T. 5W	299.95
FT270R 45W 2M Mobile Free FTS-8	CALL
FT2700 RH Dual Band Mobile Free FTS-8	CALL

Very Large Stock of Radios and Accessories
Call for Discount

ROTATORS

Alliance U-110	\$ 49.95
Alliance HD-73	99.95
Dawa	Call for Price
HyGan CD-45	CALL
HyGan Ham 4	CALL
HyGan T2-X	CALL
HyGan HDR300	CALL
Ken-Pro KR500	155.00
Ken-Pro KR5400	255.00
Ken-Pro KR5600	319.00



Send SASE for our new & used equipment list.



AMEX, MC, VISA & C.O.D.s WELCOME - FREIGHT FOB EVANSVILLE

For Orders and Price Checks Call 800-523-7731

Indiana call 1-812-422-0231
Service Dept. 1-812-422-0252

external product detector improves receiver performance

Add this circuit to
your R390A or other
older receivers

This unit is a combination of an IF amplifier, high stability local oscillator, wide dynamic range mixer and a separate audio amplifier circuit for SSB and CW reception. A stable high-current power supply is included so that the user needs only a speaker, a length of RG 58/U coax and a 120 VAC source of power. There is no need to re-enter the receiver past the IF output stage. The unit itself (**fig. 1**) is housed in an aluminum shielded cabinet.

Assembly and testing are straightforward. The only special equipment needed is a digital counter to set the oscilloscope and a 1 MHz heterodyne oscillator to the required frequency.

The construction and testing of each circuit should be done in the following order, completing each element before proceeding to the next:

- power supply
- audio amplifier
- VFO unit
- mixer-audio preamp (combined on board 3)

The power supply is a typical textbook assembly, with a three-terminal regulator. The bleeder R14 is used so that a constant load is placed on the power output at all times. To set the voltage, *before* AC is applied to the transformer, set R13 to the mid-point of the trimmer. Attach a voltmeter to the output point (at R14), apply 120 VAC to the primary of the transformer, observe the voltage at R14 and adjust trim-

mer potentiometer R13 to 12 volts. This circuit will need no further adjustments.

The assembly of the audio section has several important considerations. The TDA 2002 or TDA 2003 must have a 5-square-inch (12.7-cm²) heat sink. A piece of aluminum 2 inches (5 cm) per side and 2-1/2 inches (6.35 cm) long was used to sink the device. The sink can be grounded to the B minus (and cabinet), providing a current return path for power and an adequate sink for device heat. Each module of the working model was assembled on a 3 × 4 inch (7.6 × 10.6 cm) vector board, with push-pin mounting for components and sockets for the transistors.


Keep all leads as short as possible. The 5 PC leads were soldered to push pins staggered in alternate rows. The assembled module was speaker tested with an audio oscillator and an oscilloscope with satisfactory results. The low-frequency cut-off was about 100 Hz and the upper range fell off after 6 kHz.

The local oscillator was assembled on a separate vector board using a standard Colpitts design. Note that the oscillator/mixer portions are FET devices, and consequently are high impedance circuits. To prevent loading down, the circuit testing was done with 10X scope (probe) leads.

frequency adjustments

To set the center frequency to 455 kHz, first set the C2 capacitor to its mid-point. Set C1, the compression trimmer, also to about its mid-point. Measure the oscillator frequency at the output end of C7 with the counter set to 1 MHz range. The coil, L1, should have a tuned resonance of 455 kHz ± 50 kHz. Adjust the slug in L1 to a point well before it extends beyond the wind-

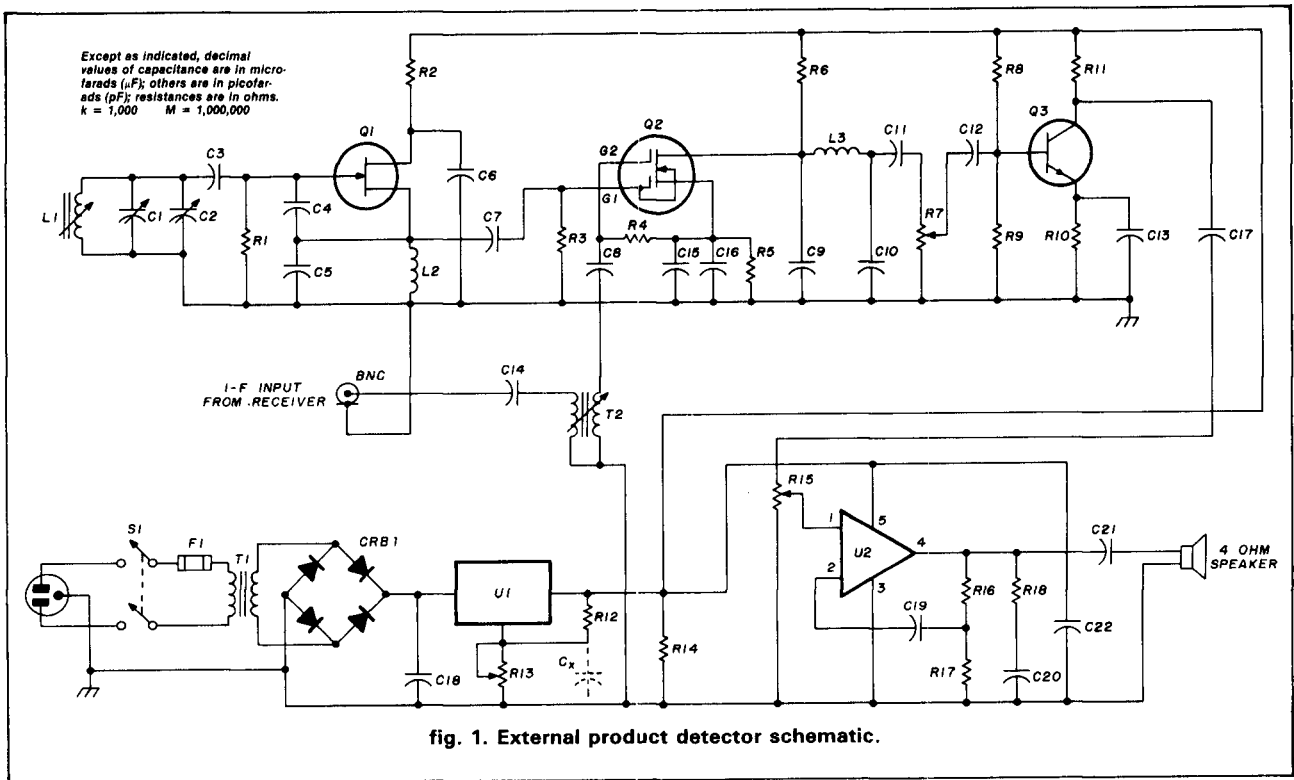By Alan Nusbaum, W6GB, 13222 Ballad Drive,
Sun City West, Arizona 85375



Parts list.

item	description	item	description
BNC	BNC male, chassis mounting	L1	J.W. Miller No. 23A474RPC
C1	20-100 pF trimmer	L2	1.2 mH, Miller No. 73F123AF
C2	5-20 pF SFL ("butterfly") variable USB-LSB offset tuning	L3	1.2 mH, Miller No. 73F123AF
C3	390 pF, mica, 500 volt	Q1	2N5486 Motorola
C4	300 pF, mica, 500 volt	Q2	3N201 Motorola
C5	500 pF, mica, 500 volt	Q3	2N2222 Motorola
C6	10 kilohm pF, ceramic, 50 volt	R1	100 kilohm, 1/2 watt
C7	100 pF, ceramic, 50 volt	R2	100 ohm, 1/2 watt
C8	0.01 μF , ceramic, 50 volt	R3	100 kilohm, 1/2 watt
C9	1000 pF, ceramic, 50 volt	R4	10 kilohm, 1/2 watt
C10	5000 pF, ceramic, 50 volt	R5	100 ohm, 1/2 watt
C11	1 μF , electrolytic, 50 volt	R6	1.5 kilohm, 1/2 watt
C12	1 μF , electrolytic, 50 volt	R7	100 kilohm trimmer, 1/2 watt
C13	50 μF , electrolytic, 10 volt	R8	91 kilohm, 1/2 watt
C14	0.01 μF , ceramic, 100 volt	R9	22 kilohm, 1/2 watt
C15	10 pF, 10 volt ceramic	R10	150 ohm, 1/2 watt
C16	10 kilohm pF, ceramic, 50 volt	R11	3.9 kilohm, 1/2 watt
C17	1 μF , electrolytic, 25 volt	R12	270 ohm, 1/2 watt
C18	4700 μF , electrolytic, 50 volt	R13	5 kilohm trimmer, 1/2 watt
C19	470 μF , electrolytic, 100 volt	R14	2 kilohm W.W., 5 watts
C20	0.1 μF , electrolytic, 50 volt	R15	100 kilohm potentiometer, 1/2 watt
C21	1000 μF , electrolytic, 50 volt	R16	220 ohm, 1/2 watt
C22	0.1 μF , electrolytic, 25 volt	R17	2.2 ohm, 1/2 watt
CRB1	MDA970-1 Motorola	R18	1 ohm, 1/2 watt
Cx	5 μF , 25 volt if the leads from regulator causes oscillation as seen on an oscilloscope	S1	DPST toggle switch
F1	buss fuse, 1 amp, 120 VAC	T1	115 volt primary, 17 volt, 2 ampere secondary
		T2	455 kHz Miller No. 8812
		U1	LM317K National

Note: All resistors 5 percent

NEW From AMERITRON

HERE IS THE EXCITING NEW AL-80A!



SETTING A NEW STANDARD OF EFFICIENCY IN MODERATELY PRICED KILOWATT AMPLIFIERS.

HEAVY DUTY TANK CIRCUIT ALLOWS PLATE EFFICIENCY OF 70% FROM 160 THROUGH 15 METERS.

The Ameritron AL-80A combines the time proven economical 3-500Z with a redesigned heavy duty tank circuit to achieve 70% efficiency from 160 to 15 meters. It has wide frequency coverage for MARS and other authorized services. Typical drive is 85 watts to give over 1000 watts PEP SSB and 850 watts CW RF output. A new Pi-L output circuit for 80 and 160 gives full band coverage and exceptionally smooth tuning.

The AL-80A will provide a signal output that is within 1/2 "S" unit of the signal output of the most expensive amplifier on the market—and at much lower cost. Size: 15 1/2"D. x 14"W. x 8"H. Weight: 52 lbs.

NEW AMERITRON RCS-4 REMOTE COAX SWITCH

Available at your dealer. Send for a catalog of the complete AMERITRON line.



The Ameritron RCS-4 is a remote controlled coax switch that selects one of four antennas by supplying all control voltages through the coax feed line. The elimination of a control cable results in a neat and inexpensive installation.

The indoor control console has bright LED antenna selection indicators.

The remote relay box is tower or mast mounted with a single clamp.

The RCS-4 operates from 120 VAC and covers frequencies from 1.8 through 30 MHz at full legal power.

AMERITRON, DIVISION OF PRIME INSTRUMENTS, INC.
9805 WALFORD AVENUE • CLEVELAND, OHIO 44102 • (216) 651-1740

157

ALL BAND TRAP "SLOPER" ANTENNAS!



FULL COVERAGE! ALL BANDS! AUTOMATIC SELECTION with PROVEN Weatherproof sealed Traps - 18 Ga. Copperweld Wire! GROUND MOUNT "SLOPERS" - No Radiate needed! Ground to rod, or house water faucet! Connect Top to Trees, Buildings, Poles, etc at ANY angle from Straightup to 60 degrees for excellent "SLOPER" DX Antenna Gain or bend it anywhere you need to! 2000 Watt PEP Input, max. Permanent or portable Use. Installs in 10 minutes. SMALL - NEAT - ALMOST INVISIBLE - No one will know you have a Hi-Power DX Antenna. Ideal For COND'Os APARTMENTS - RESTRICTED AREAS - Pre-tuned for 2-1 or less SWR over ALL bands (except 80-160-300Kc). No adjustments needed - EVER COMPLETELY ASSEMBLED, with 50 ft RG-58U Coax feedline and PL259 connector. Built in lightning arrester - ready to hookup! FULL INSTRUCTIONS!

No. 10805 - 80-40-20-15-10 - 1 trap 49 ft. - \$49.95
No. 10405 - 40-20-15-10 - 1 trap 26 ft. - \$46.95
No. 10205 - 20-15-10 - 1 trap 13 ft. - \$47.95
No. 1016 S-160-80-40-20-15-10 - 2 traps 83 ft. - \$79.95
SEND FULL PRICE FOR PP DEL IN USA (Canada is \$5.00 extra for postage, etc.) or order using VISA, MASTERCARD - AMER EXP. Give Number Ex Date. Ph 1-308-236-5333 weekdays. We ship in 2-3 days (Per Cks 14 days) Guaranteed 1 yr - 10 day money back! WESTERN ELECTRONICS
Dept. AH-11 Kearney, Nebraska 68847

158

MICROWAVE EQUIPMENT



RMLA - 2.3
Single Stage, Low Noise
Gas Fet Amplifier
\$60.00

Optimum Transistor Noise Figure less than 5 dB. Associated Gain Greater Than 15dB at 2.3 GHz. Source/Load must be 50 ± 10 ohm Non-Reactance. SMA Connectors. Requires ± 5VDC Power with -5VDC present when +5VDC applied. Power Supply and Sequencing is not supplied. Zener Protection. Unenclosed on 2" x 2" PC Board.

Write for Price/Delivery for any frequency from 1 to 6 GHz. Also VCO's, Signal Generators, Detectors, Attenuators, Filters, Mixers, and Converters.

Price includes Shipping and Insurance when paid by check or money order. Charge or C.O.D. orders, F.O.B., Brookfield, MO

ROENSCH MICROWAVE

R.R. 1, Box 156B,
BROOKFIELD, MISSOURI 64628

159

R-390A HF RECEIVER



Famous military receiver covers 0.5-32 Mhz AM-CW in 31 one Mhz bands using mechanical digital tuning. 455 KHz IF; has four Collins mechanical filters for selectable 2-4-8-16 KHz bandwidth. 100 KHz calibrator; BFO. No covers. 115/230 VAC 60 Hz; 10 1/2 x 19 x 16 1/4". 95 lbs. sh. (UPS in 2 pkgs.). Used-repairable \$215. Checked \$335. Manual, partial repro \$15.

PARTS FOR R-390A, used-checked;
PTO/VFO assembly \$40 If Collins Mfg. \$60
Mechanical filters 2 or 4 KHZ \$35
8 KHZ \$27 16KHZ \$20
Set of four mech-filters \$85

Power supply less 26Z5 tubes \$30 Most other parts available, except meters. Write for listing. Prices F.O.B. Lima, O. • VISA, MASTERCARD Accepted. Allow for Shipping • Send for NEW CATALOG '85 Address Dept. HR • Phone: 419/227-6573

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

160

The ISOTRON

NO TUNERS!
NO RADIALS!

ANTENNAS FROM 160-10 METERS NO COMPROMISE!

Just a few comments from our satisfied customers:

"... I have used your 80/40 meter Isotron while stationed in Guantanamo Bay Cuba and it worked great!... Dept. Of The Navy"

"On January 11 and 12 I got into the 74 magazine sabb contest. I didn't try for maximum number of contacts. Rather I tried for maximum number of states. In less than 3 hours total time I worked 32 states and Puerto Rico, that last one is about a 2800 mile haul from Aurora, Colorado.

Not too bad for what looks like a bird feeder... W4RZQ"

"I just got my Isotron 40 on the air and it has surpassed my wildest expectations. My first evening QSO was with KB6EUC and wait—my second was with HKRGUP in Columbia, South America. The antenna sits on a 30 foot mast and that is it. My RST reports have been great.

Congratulations on developing the Isotron. I am spreading the good word among my ham friends. I think it's a super, compact antenna whose time has finally come!... K2RQW"

"About two months ago I bought an Isotron 80 and just recently got it out of the shack and up on a 18-foot pole. I am really intrigued by it and have had a lot of fun trying to convince other stations that it is only 28 inches high. I worked California when it was hanging by a nylon cord from the ceiling of the shack and it works even better out on a pole... N2EDF"

WHY NOT ENJOY THEIR OPERATING PLEASURE & GIVE US A CALL.
WE WILL LOOK FORWARD TO TALKING WITH YOU.

*40-METER - \$52.95 PLUS \$3.75 SHIPPING 80-METER - \$63.95 Plus \$4.75 Shipping
80-40 Combination - \$110.00 plus \$8.50 Shipping

pictured—
Isotron 160

ASK FOR PRICES ON OTHER MODELS

* See review in October 73, 1984

BILAL COMPANY

S.R. 2, Box 62, Dept. 91

Eucha, OK. 74342 PH: 918-253-4094

VE Groups! Individual VEs! DeVERY Wants You!

Work with the VEC that was — and still is — one of the first (and best) in the VEC Program.

Upgrading? An SASE will bring you DeVERY exam dates and locations by return mail.

Call or write Jim Georgius,
W9JUG, Director

DeVERY ARS VEC Program

DeVERY Institute of Technology
3300 North Campbell
Chicago, Ill 60618
(312) 929-8500

✓ 162

DO YOU KNOW WHERE TO FIND REAL BARGAINS



on NEW and USED ELECTRONIC Equipment?

You'll Find Them
in the Nation's No. 1
Electronic Shopper Magazine

NUTS & VOLTS

Now in Our 5th Year

Nuts & Volts is published MONTHLY and features:
**NEW STATE-OF-THE-ART PRODUCTS •
SURPLUS EQUIPMENT • USED BARGAINS
• LOW COST AD RATES • PRIVATE AND
COMMERCIAL CLASSIFIEDS • NATIONAL
CIRCULATION • NEW PRODUCT NEWS
SECTION • AND A FREE CLASSIFIED AD
WITH YOUR SUBSCRIPTION**

SUBSCRIPTION RATES

- One Year - 3rd Class Mail \$10.00
 One Year - 1st Class Mail \$15.00
 One Year - Canada & Mexico (in U.S. Funds) .. \$18.00
 Lifetime - 3rd Class Mail (U.S. Only) \$35.00

ORDER NOW!

SEND: CHECK MONEY ORDER
 VISA MASTERCARD

TO: **NUTS & VOLTS MAGAZINE**
P.O. BOX 1111-H
PLACENTIA, CALIFORNIA 92670
(714) 632-7721

Name _____
Address _____
City _____
State _____ Zip _____
Card No. _____
Exp. Date _____

**IF YOU'RE INTO ELECTRONICS,
THIS MAGAZINE WILL SAVE YOU MONEY!**

Dealer Inquiries Invited

✓ 163

ings, then fine tune by adjusting C1, while keeping C2 at its mid-range value. If leads have been kept short, the 455 kHz point should be found without difficulty. The open-air maximum drift as measured on a counter was less than 100 Hz at the end of 1 hour.

The oscillator output voltage through C7 was about 1.5 volts peak-to-peak, which is the required amplitude. If the voltage is greater than 1.5 volts, reduce the value of C7. The loading of this output by Q2 has negligible effect on the amplitude of the voltage.

A test for upper and lower sideband heterodyning is the most important aspect of a product detector circuitry.

With C2 set at its center point, the counter should still register 455 kHz. Adjust C2 slowly to a lower value of capacitance and frequency should increase to about 458 kHz. Move C2 to a higher capacitance (at the same excursion as above) and the frequency should drop to 452 kHz. Return the tuning to mid-point, 455 kHz. Turn off the power.

Install Q2 (3N201) in the socket. Connect a stable signal generator set to 455 kHz to the signal input BNC connector. The amplitude of the signal should not exceed 100 mV peak-to-peak sine wave, unmodulated. Connect the scope to the output end of C11, which is the top of trimpot R7. Power up the circuit and sync the VFO with the signal generator so as to display a null on the scope. Swing C2 through its upper and lower excursions, verifying that the waveform remains linear through sum and difference mixing of the signals. The amplitude should be about 200 mV peak-to-peak (3-dB mixer gain). Move the scope probe to the output side of C17. Adjust R7 trimpot for an output of less than 500 mV peak-to-peak. There should be no distortion of the output signal. If all components have been wired correctly, the Pi-section filter C9, C10, and L3 will have removed all mixer by-products with just the product of the two oscillators displayed on the scope. Increasing the signal generator output to 250 mV peak-to-peak should not cause distortion of the output signal. Be aware that the voice products of a product detector vary over the speech range and signal strengths. High signal amplitudes should not distort. A reduction of the R7 gain potentiometer will reduce large signal distortion.

The MOSFET, Q2, can tolerate high signal levels without distortion, however Q3 can be overdriven. A distorted signal is not pleasant to listen to.

After these tests have been completed, you're ready to assemble the power audio IC and hook up the R390A IF output connector.

The input and interconnect cabling was done with RG 217/U coax. The low frequencies of the system could have tolerated audio cords with equal success.

The builder can use edge card connect boards with matching sockets. This writer drilled holes in the vector board corners and fastened the boards with 4-40 screws and 1/2-inch (1.27 cm) aluminum spacers. It all works happily together and that's what it's all about.

modifying the R390A

Several changes can be made to improve sensitivity, and noise figure of the R390A receiver. The modifications are made to the IF module only.

Disconnect AC power to the R390A. The rear terminal board TB102 has a jumper between terminals 3 and 4. Disconnect this jumper and ground terminal 4 to the receiver frame. Connect a voltmeter between terminal 3 and ground. Carefully remove the aluminum shields covering T501, T502, T503, and Z503.

Drill 3/16 (0.476 cm) holes in the top center of these shield cans. Be sure to de-burr afterward since the aluminum is soft.

Inspect the IF transformer T501. Locate the resistors shunting the primary and secondary winding. *Caution:* The Litz wire connecting the inductors is very fragile and easily broken. The resistor values in my receiver were 47 kilohms but could be as low as 15 kilohms in other models. Clip out these resistors, and replace the shields and observe the AGC voltage. Switch the receiver on and set the function switch to AGC, note that the voltage measures approximately 28 volts in the 2 kHz selectivity position. When peaking T501, T502, T503, and Z503, the voltage should increase to 34 volts (minimum) if all tubes are working properly. Replace the jumper on the TB102 AGC line, connect the Product Detector Module and you'll discover that you have a hot SSB receiver that rivals anything built today.

using it in other receivers

The application of the Product Detector-audio assembly is not limited to the type of receivers discussed in the text. If the IF frequency is other than 455 kHz, (such as the R-388), then the local oscillator coil can be chosen to work with the required matching IF. Miller coils cover most of the wanted ranges; the builder can also wind a coil to the frequency of interest. The old Hallicrafters receivers, as well as the Hammarlund, National, and RCA of WW2 vintage can regain their vigor, providing the first local oscillator is stabilized. Don't scrap the old boat anchors just because they won't copy SSB or CW like some of the newer radios. Add this stand-alone module and find out how good it was all along!

The author has several R390A receivers in restorable condition, with the manuals. They are laboratory units, not military surplus. A QSL card to W6GB will get details. — Ed

ham radio

DOCKING BOOSTER

Converts Your HT to a Powerful Mobile Unit



30 or 50 watts output
16 DB GaAs FET pre-amp
Fits on most car doors
Mic hang-up clip
Icom, Yaesu, Kenwood
2 Meters & 70 cm

\$149⁹⁵

CMC COMMUNICATIONS, INC.
5479 Jetport Industrial Blvd. • Tampa, FL 33614
Phone: 813-885-3996

✓ 164

Your Ham Tube Headquarters!

TUBES BOUGHT, SOLD AND TRADED
SAVE \$\$\$—HIGH \$\$\$ FOR YOUR TUBES

Call Toll Free 800-221-0860

Tubes

3-400Z	\$85.00	7360	\$10.00
3-500Z	85.00	7735A	27.50
4-400A	80.00	8122	110.00
4CX250B	50.00	8156	12.50
572B	55.00	8643	82.50
811A	12.00	8844	26.50
813	30.00	8873	175.00
6146B	6.50	8874	195.00
6360	4.25	8877	500.00
6883B	6.75	8908	12.50

MAJOR BRANDS ON RECEIVER TUBES
75% off list

Semiconductors

MRF 245/SD1416	\$30.00	SD1088	19.95
MRF 454	14.95	2N305575¢
MRF 455	10.95	2N6084	12.50

RF Connectors

PL259	10/\$4.95	M358	2.50 ea.
PL258	10/8.95	M359	1.75 ea.
UG 175/176	10/1.60	Type "N" Twist on	
UG255/u	2.50 ea.	(RG8/u)	\$4.75 ea.
UG273/u	2.25 ea.	Minimum Order \$25.00	

Allow \$3.00 min. for UPS charges ✓ 165

CeCo

COMMUNICATIONS, Inc.
2115 Avenue X Brooklyn, NY 11235

SERVING THE INDUSTRY SINCE 1922 Phone (212) 646-6300
Call CECo For Your CCTV Security And Color Production Requirements

Join AMSAT...Today

Amateur Radio Satellite OSCAR 10 provides:

- A New Worldwide DX Ham Band open 10 hours a day.
- Rag Chew With Rare DX Stations in an uncrowded, gentlemanly fashion.
- Popular Modes In Use: SSB, CW, RTTY, SSTV, Packet
- Full Operating Privileges open to Technician Class licensee or higher.

Other AMSAT Membership Benefits:

ORBIT Magazine Subscription:
Dependable technical articles, satellite news, orbital elements, product reviews, DX news, and more.

Satellite Tracking Software
Available for most popular PCs.

QSL Bureau, AMSAT Nets, Area Coordinator Support, Forum Talks

Construction of Future Satellites For Your Enjoyment!

AMSAT Membership is \$24 a year, \$26 outside North America. VISA and MC accepted.

AMSAT
P.O. Box 27
Washington, DC 20044

301 589-6062

✓ 166



NATIONAL SEMICONDUCTOR • PANASONIC
OK MACHINE • EWC, INC. • INTERSIL • AD
EAC, INC. • J. W. MILLER • AAVD ENGINEER
E. F. JOHNSON • ATLANTIC SEMICONDUCTOR

256K (262,144 x 1) DRAM 150NS \$5.70/1; \$39.95/9

DIODES • DIAMOND TOOL • UNGAR
ES • CW INDUSTRIES • AMDEX • G.E.
IGAR • YAGED • J. W. MILLER • LUXO
3C CHEMICALS • ARIES • PLESSEY



Factory Firsts

INTEGRATED CIRCUITS

7400 TTL

Part No.	Price	Part No.	Price
7400	1.00	7400	1.00
7401	1.00	7401	1.00
7402	1.00	7402	1.00
7500	1.00	7500	1.00

INTEGRATED CIRCUITS

4000 CMOS

Part No.	Price	Part No.	Price
4000	1.00	4000	1.00
4001	1.00	4001	1.00
4002	1.00	4002	1.00
4100	1.00	4100	1.00

INTEGRATED CIRCUITS

74HC00 CMOS

Part No.	Price	Part No.	Price
74HC00	1.00	74HC00	1.00
74HC01	1.00	74HC01	1.00
74HC02	1.00	74HC02	1.00
74HC03	1.00	74HC03	1.00
74HC04	1.00	74HC04	1.00
74HC05	1.00	74HC05	1.00
74HC06	1.00	74HC06	1.00
74HC07	1.00	74HC07	1.00
74HC08	1.00	74HC08	1.00
74HC09	1.00	74HC09	1.00
74HC10	1.00	74HC10	1.00
74HC11	1.00	74HC11	1.00
74HC12	1.00	74HC12	1.00
74HC13	1.00	74HC13	1.00
74HC14	1.00	74HC14	1.00
74HC15	1.00	74HC15	1.00
74HC16	1.00	74HC16	1.00
74HC17	1.00	74HC17	1.00
74HC18	1.00	74HC18	1.00
74HC19	1.00	74HC19	1.00
74HC20	1.00	74HC20	1.00
74HC21	1.00	74HC21	1.00
74HC22	1.00	74HC22	1.00
74HC23	1.00	74HC23	1.00
74HC24	1.00	74HC24	1.00
74HC25	1.00	74HC25	1.00
74HC26	1.00	74HC26	1.00
74HC27	1.00	74HC27	1.00
74HC28	1.00	74HC28	1.00
74HC29	1.00	74HC29	1.00
74HC30	1.00	74HC30	1.00
74HC31	1.00	74HC31	1.00
74HC32	1.00	74HC32	1.00
74HC33	1.00	74HC33	1.00
74HC34	1.00	74HC34	1.00
74HC35	1.00	74HC35	1.00
74HC36	1.00	74HC36	1.00
74HC37	1.00	74HC37	1.00
74HC38	1.00	74HC38	1.00
74HC39	1.00	74HC39	1.00
74HC40	1.00	74HC40	1.00
74HC41	1.00	74HC41	1.00
74HC42	1.00	74HC42	1.00
74HC43	1.00	74HC43	1.00
74HC44	1.00	74HC44	1.00
74HC45	1.00	74HC45	1.00
74HC46	1.00	74HC46	1.00
74HC47	1.00	74HC47	1.00
74HC48	1.00	74HC48	1.00
74HC49	1.00	74HC49	1.00
74HC50	1.00	74HC50	1.00
74HC51	1.00	74HC51	1.00
74HC52	1.00	74HC52	1.00
74HC53	1.00	74HC53	1.00
74HC54	1.00	74HC54	1.00
74HC55	1.00	74HC55	1.00
74HC56	1.00	74HC56	1.00
74HC57	1.00	74HC57	1.00
74HC58	1.00	74HC58	1.00
74HC59	1.00	74HC59	1.00
74HC60	1.00	74HC60	1.00
74HC61	1.00	74HC61	1.00
74HC62	1.00	74HC62	1.00
74HC63	1.00	74HC63	1.00
74HC64	1.00	74HC64	1.00
74HC65	1.00	74HC65	1.00
74HC66	1.00	74HC66	1.00
74HC67	1.00	74HC67	1.00

Don't buy from Hamtronics . . .

Unless you want the best possible equipment at the lowest possible price!!!

The "wheeler-dealer" is back and he's beating everyone else's "deals."

We all know there's no such thing as a free lunch . . . so How Can We Do This?

- **We don't** run alot of ads featuring sale items
- **We don't** spend alot of money on full page ads
- **We don't** have sales on just the fastest selling products
- **We don't** short cut you on service. We are a factory warranty repair facility for everything we sell!
- **We don't** mail out free catalogs
- **We don't** have a free WATS number.

You and every other Ham customer is paying for all these do-dads and sales gimicks.

Hamtronics puts the savings into your pocket.

Hamtronics guarantees to meet or beat any advertised price on every item we sell.

Hamtronics Has It All!

Let **Hamtronics** be your Ham Radio equipment dealer. We're celebrating our 35th year in the Ham business at the same location.

HAMTRONICS, INC.

A DIVISION OF TREVISE ELECTRONICS
4033 BROWNSVILLE RD., TREVISE, PA 19047
(215) 357-1400



✓ 169

HALF-PRICE SALE!

Super SSB Filters for ICOM
Models IC-730/740/745, R-70/71.
COMPARE!

ICOM FL-44A: 2.4kHz, 455kHz, 8-pole Reg \$159
FT-44A (Twin of FL-44A) **SALE \$79.50**

- Characteristics equal or exceed those of FL-44A.
 - Replaces inferior mechanical filter.
 - Easy drop-installation - complete instructions.
- Limited Quantities — Get 'em while they last!

GO FOX TANGO — TO BE SURE

SHIPPING: \$3, Air \$5 (US & Canada), \$10 Elsewhere
Order by mail or phone. VISA/MC or COD Accepted.

Ask About Our Fine Filters for Many Other Rigs

FOX TANGO CORPORATION

Box 15944 W. Palm Beach, FL 33416
(305) 683-9587



Quality Microwave TV Antennas

Multi-Channel 1.9 to 2.7 GHz
40dB Gain True Parabolic 20 Inch Dish
Complete System \$84.95 (Shipping Incl.)
Dealerships, Qty. Pricing, Replacement Parts
Phillips-Tech Electronics
P.O. Box 34772 • Phoenix, AZ 85067
(802) 947-7700 (\$3.00 Credit all phone orders!)

LIFETIME WARRANTY

MasterCard • Visa • COD's

✓ 170

NEW 20-PAGE CATALOG FREE

7 MILLION TUBES

Includes all current, obsolete, antique, hard-to-find receiving, transmitting, industrial, radio/TV types. **LOWEST PRICES.** Major brands in stock. Unity Electronics Dept.

P.O. Box 213, Elizabeth, N.J. 07206



✓ 171

RF Porta-Tenna

VHF/UHF Telescopic 1/4 & 5/8 Wavelength Antennas for Hand-Held Transceivers & Test Equipment

1/4 WAVELENGTH

Model No.	Freq. MHz	Description	Price
196-200	144-148	5/16-32 stud w/spring	\$5.95
196-204	"	BNC connector w/spring	7.95
196-214	"	BNC connector	6.95
196-224	144-UP	BNC conn. adj. angle	7.95
196-814	220-225	BNC connector	6.95

5/8 WAVELENGTH

191-210	"	5/16-32 for old TEMPO	22.95
191-214	"	BNC connector	19.95
191-219	"	PL-259 w/M-359 adpt.	22.95
191-810	220-225	5/16-32 for old TEMPO	22.95
191-814	"	BNC connector	19.95
191-940	440-450	5/16-32 for HT-220	22.95
191-941	"	1/4-32 stud	22.95
191-944	"	BNC connector	19.95

Largest Selection of Telescopic Antennas. Write for Info. Prices are postpaid via UPS to 48 States. For air delivery via UPS Blue add \$2.25. Florida add 5% sales tax. Payment by M.O. or Cashiers Check only. ✓ 172

RF PRODUCTS

P.O. Box 33, Rockledge, FL 32955, U.S.A.
(305) 631-0775



VOLUNTEER EXAMINATION BOOKS & TAPES



- Novice Class Q&A Test Guide Package \$ 9.95
- Technician Class Q&A Test Guide 19.95
- Advanced Class Q&A Test Guide 19.95
- Extra Class Q&A Test Guide 19.95
- 5 wpm Novice QSO Test Preparation Tape 9.95
- 5-7 wpm Speed Builder 9.95
- 7-10 wpm Speed Builder 9.95
- 10 wpm Plateau Breaker QSO's 9.95
- 10-12 wpm Speed Builder 9.95
- 12-15 wpm Calls & Numbers Speed Builder 9.95
- 13-15 wpm Random Code Practice 9.95
- 13 wpm General Class QSO Test Prep Tape 9.95
- 13-15 wpm Speed Builder 9.95
- 15-17 wpm Speed Builder 9.95
- 17-19 wpm Speed Builder 9.95
- 20-22 wpm Random Code Practice 9.95
- 20 wpm Extra Class QSO Test Prep Tape 9.95
- Test Guides Updated to New '85 Questions and Answers
- Slow Code Tapes Use 13 wpm Character Speed
- We Ship First Class Mail. Same Day
- Add \$3.00 postage & handling for Test Guides. 50¢ P&H for each tape
- 100% SATISFACTION OR MONEY BACK ✓ 173

GORDON WEST RADIO SCHOOL
2414 COLLEGE DR., COSTA MESA, CA 92626

Mon.-Fri. 10-4pm (714) 549-5000

build a handy RF probe

Build it simple
— or more complex,
for increased
sensitivity

An RF probe is a useful instrument to have around the shack — if you can find one that's sufficiently sensitive. This article will help you build your own, using solid-state Germanium or silicon diodes in simple circuits to provide the necessary sensitivity.

using diodes

Two principles must be understood in using diodes of all types: threshold of operation and detection sensitivity. Ideally, all diodes have a maximum sensitivity set by the diode equation:

$$I = I_s \{ \exp. (qV/kT) - 1 \} \quad (1)$$

where I_s is the saturation current, which sets the threshold, q is the electron charge, k is Boltzman's constant, and T is the absolute temperature (room temperature is about 290 degrees absolute), and V is the voltage. The expression (q/kT) is extremely important in solid-state electronics and has a nominal value of 39. Its reciprocal is 0.026 volt.

The smaller the value of I_s , the larger the threshold voltage required with any of these devices.* With the germanium diode, the threshold will occur at an anode-to-cathode voltage in the range of 0.1 to 0.25 volt, and with the silicon diode, 0.5 to 0.75 volt.

In practice, an operating current level between 0.1 and 1 mA is selected to compare various devices. In normal operation, the anode-to-cathode voltage at

*The value of I_s is a function of the numbers of the charge carriers in undoped or intrinsic material. In undoped germanium, there are 1131 times as many carriers than in silicon. This leads to at least 0.180 volt more bias for the silicon diode than for the germanium.

which the chosen level of current flows controls the minimum sensitivity of a diode probe.

Measuring current as a function of voltage in solid-state diodes, one finds a two-to-one change in device current with approximately 0.018 volt change in applied voltage. This is the sensitivity needed (see appendix).

Using a diode having a low threshold and full incremental sensitivity, as it can be called can improve the minimum sensitivity of an RF probe to allow the measurement of voltages in the 100 to 500 millivolt range. (This is why hot-carrier diodes are important.) The simplest circuit for using a high-threshold-sensitivity diode is shown in fig. 1. The input capacitor is selected so that its reactance $(1/\omega C)$ is small compared to the diode's apparent resistance, and not more than the source impedance of the signal source. The resistance value in the output circuit should be large compared to the diode resistance, which is approximately $0.026/I$ where I is in amperes. Such an RF probe can be used in some receiver alignment applications as well as many routine tuning problems, and it can be used with a sensitive analog meter or a digital voltmeter.

building a better probe

Reducing dependence on the threshold limitation results in better RF probes because of high inherent sensitivity of solid-state devices. To take advantage of this sensitivity, a fixed level of operating current must be introduced to overcome the threshold and then apply a signal voltage from a low-impedance source to achieve the current sensitivity solid-state devices are theoretically capable of delivering.

Possibly the easiest way to avoid the threshold problem is to use a transistor so that we can sense the current changes more easily. A circuit using the LM 334 controlled-current source is shown in fig. 2. An isolation resistance that reduces the voltage drop across the LM 334 to perhaps a volt and a half will separate the DC and RF circuits.

By Keats A. Pullen, Jr., W3QOM, 2807 Jerusalem Road, Kingsville, Maryland 21087


John J. Meshna Jr., Inc.

P. O. Box 62 19 Allerton St. E. Lynn, Ma. 01904 Tel: (617) 595-2275

COMPUTER TERMINAL BUILDING BLOCK \$50.00

This is a great beginning for a computer terminal. It is a brand new, Panasonic, 9" TTL input monitor complete with its own self-contained, switching power supply, and a removable (four screws) triple output power supply. The whole assembly runs on 115/230 V, 50/60 Hz. Now for some specifics: 9" green phosphor, TTL input monitor, attached regulated 12 VDC, 1.5 A power supply used exclusively to run the monitor and an attached triple output switching power supply with outputs of 5 VDC @ 3.5 A, +12 VDC @ 500 ma, and -12 VDC @ 500 ma. The assembly has mounting feet and should be a snap to make a case for. Comes with hook up data. New, factory boxed. We are offering this to you 4 ways:

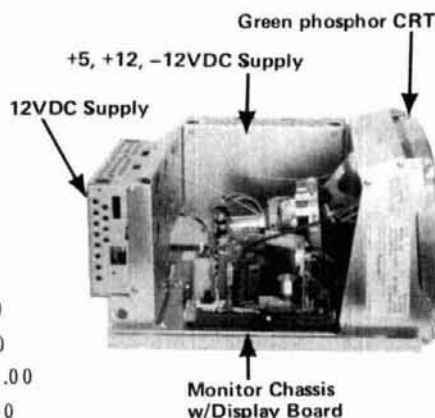- COMPLETE SET-UP AS SHOWN, including monitor, low voltage supply and triple output supply. SPL-116-38, 14 Lbs., \$50.00, 5/\$225.00
- TRIPLE OUTPUT SUPPLY ONLY, SPL-117-38, 3 Lbs. \$15.00
- 9" MONITOR ONLY, (you supply low voltage input) SPL-114-38, 10 Lbs. \$25.00
- 9" MONITOR W/LOW VOLTAGE SUPPLY ONLY, SPL-115-38, 12 Lbs. \$40.00



We are now selling guaranteed working, starlight scopes which allow sight in almost total darkness. They are so named because they incorporate a light amplification tube which uses the available star or moon light to allow you to see - without being seen. The scope has a spectral response of 4,500 to 8,000 angstroms, resolution of 50 lines/mm, viewing area of 25mm, standard 50mm F1.4 lens, optional telephoto 135mm F2.8 lens, cross hair reticle and optional carrying case. A great tool for security and naturalist applications. Runs on 9VDC transistor radio battery. Due to the nature of this device and people only having a one time use for it, we cannot accept returns for refund, credit or exchange on this item. To our knowledge, this is the least expensive starlight scope on the market. Includes 90 day warranty.

STARLIGHT SCOPE	SPL-130A-39	\$1,200.00
Optional Telephoto Lens, 135mm F2.8	SPL-131A-39	\$85.00
Optional Fitted Carrying Case	SPL-132A-39	\$65.00

ATTENTION:

**SECURITY PERSONNEL
NATURALISTS
HOBBYISTS**

NEW SEE-IN-THE-DARK EQUIPMENT!




1/2 Height 1 MEGabyte Disc Drives

Here we go with another blockbuster buy on disc drives which should make the competition's head spin! We are offering brand new, Mitsubishi no. 4853, 1/2 height, 1 megabyte, mini floppy disc drives. These drives are beautiful. They are fully Slugart 34 pin compatible. All are double side, double density, 80 tracks per side units. Each runs on +5vdc, .5 A and +12vdc, .7 A. Just the drives to use with your IBM, Sanyo or other computer. Each order will come with schematics and pin out data.

SPL-85C-35 \$175.00 each \$175.00 each, 2/\$325.00, 5/\$725.00


New, 75 watt power supply. +5vdc 5.5amps, +12vdc 4amps, -12vdc .3amps
115/230 input. Made by GI, fully enclosed, with schematic.
Shpg. wt. 4 lb. PS-10 \$50.00

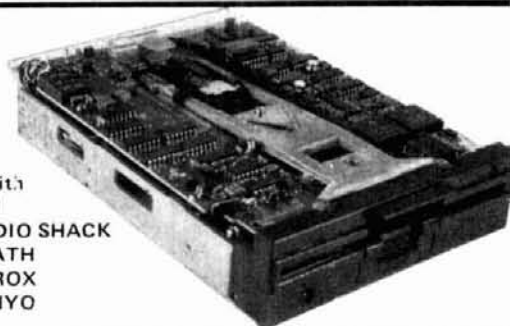- Use with
- IBM
 - RADIO SHACK
 - HEATH
 - XEROX
 - SANYO



HIGH POWER SURVEILLANCE IR SCOPE

This Infra-Red scope was designed specifically for long range surveillance use. The built-in, totally invisible, 50 watt halogen lamp IR source is coupled with a premium grade type 6032 image converter tube, 265 mm f4.2 lens, and 16 power military spec., color corrected eyepiece make this an ideal unit for viewing of clandestine activities or animals. The scope is capable of detection at more than 300 feet, recognition at 300 feet and positive facial identification at 150 feet. It runs on 12 VDC which makes it ideal for mobile use. It comes with a removable hand grip which allows for tripod mounting, 2 power cords for cigarette lighter or battery terminals, instructions and a 90 day warranty. Listed below are accessories which make this a very versatile instrument. The scope and accessories are new and guaranteed functional. Net wt. 5-1/4 Lbs.

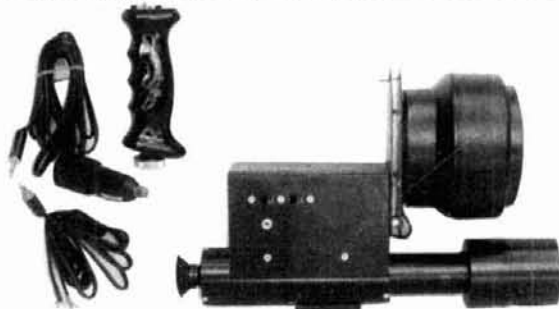

IR Scope part no. ELD Shpg. Wt. 7 Lbs. \$735.00 ea.

ACCESSORIES:

12 VDC GELL BATTERY for above, Shpg. Wt. 6 Lbs. \$35.00

BIOCULAR EYEPIECE which can be used in place of the standard eyepiece. This allows the scene being produced by the IR viewer to be seen by the operator up to 4 ft. away. 2 Lbs. \$89.95

MALE "T" f1.6 CAMERA DAPTER for SLR cameras

Shpg. Wt. 1 Lb. \$129.00

MALE "C" to FEMALE "T" ADAPTER for CCTV, requires use of above male "T" f1.6 adapter. Shpg. Wt. 1 Lb. \$29.95

Free 72 page catalogue available or send \$1.00 for 1st class service to P. O. Box 62 E. Lynn, Ma. 01904.

Phone (617) 595-2275 to place your order by phone. MC, VISA, or American Express charge cards accepted.



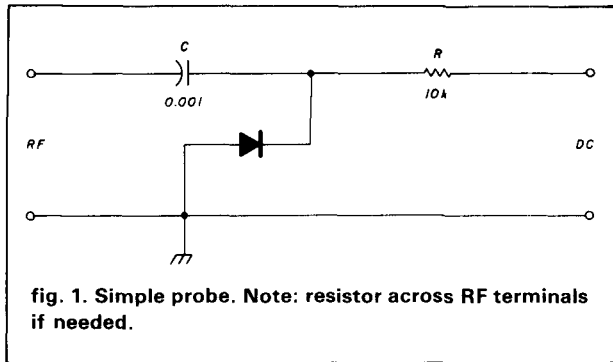


fig. 1. Simple probe. Note: resistor across RF terminals if needed.

A simple review of the principles underlying detection is included in the appendix.

The circuit shown in fig. 2 works as predicted, but it still is not optimum because very small current changes must be observed if sensitivity is to be optimized. For this, a reference voltage follower can be used, (fig. 3), resulting in a voltage-sensitive bridge. Full-scale indication on the output meter with output changes of 100 millivolts (the full-scale reading of the meter) can be achieved easily. This may correspond to as little as 30 mV of RF signal. The scale will not be linear, but will approach a square-law function.

Using the meter directly between the collector circuit of the detecting transistor and the voltage reference will also reduce the sensitivity of the detector. Two circuits that can do this, both reducing the current load on the detector output, are shown in fig. 4.

The basic problems are now solved. To minimize the loading the detector places on the source, a situation that is particularly important if the RF source has high-impedance characteristics, VMOS transistors such as the VN10KM can be used as an amplifier. These transistors are better used as wideband amplifiers, with the output taken in the drain circuit. A small amount of degeneration through the use of a source resistance is acceptable, although it does reduce the amplification. In no case should the amplification exceed ten, and it may be as small as 1.0 to 1.5. A possible circuit is in fig. 5.

If greater sensitivity is required, a pair of high-frequency bipolar transistors can be used in a cascode arrangement after the VMOS transistor and before the input of the detection transistor to get an additional X10 voltage gain. A useful circuit for this is shown in fig. 6. This circuit should also be broadband. The output load resistance required will be approximately $260/i_c$, with collector current, i_c , measured in milliamperes. The resulting unit will have a voltage gain of roughly 10, and can be built quite easily. It will extend the minimum sensitivity down to about the millivolt level. These amplifiers limit with input signals over about 10 millivolts, and will also rectify, distorting the input signal.

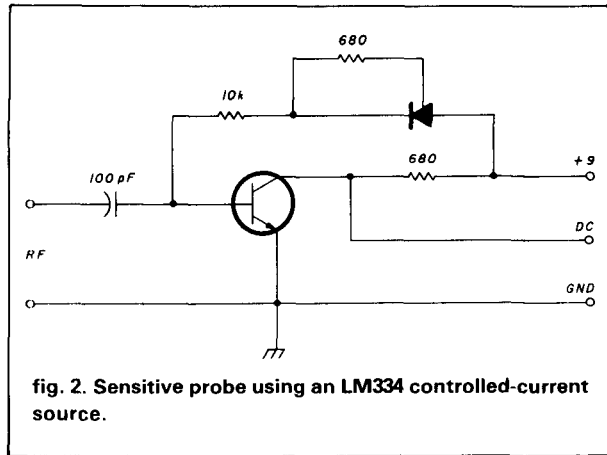


fig. 2. Sensitive probe using an LM334 controlled-current source.

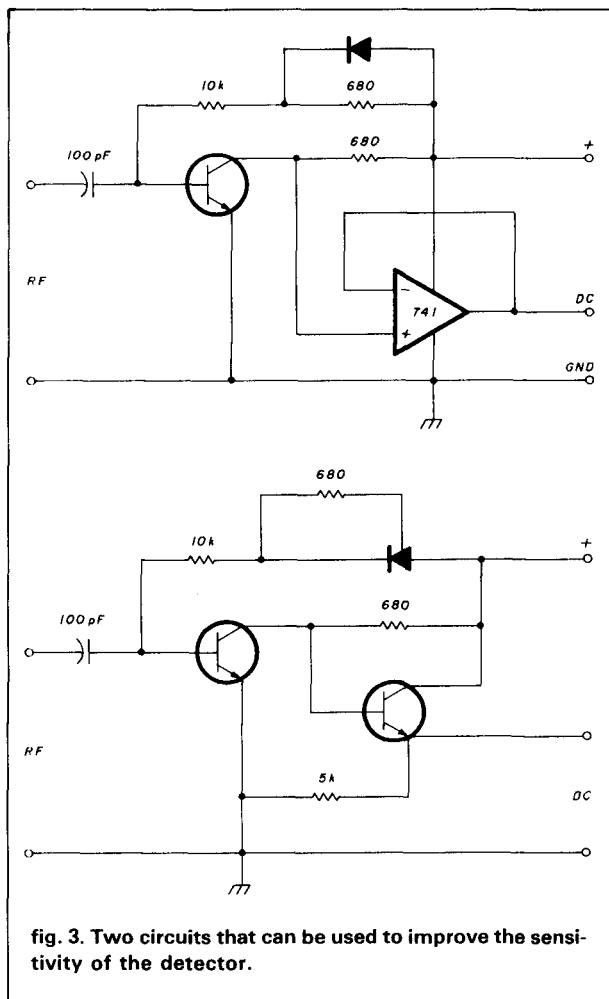


fig. 3. Two circuits that can be used to improve the sensitivity of the detector.

other applications

The buffered RF probe has a variety of applications of interest to Amateurs beyond its use in circuit testing. I have built one into a homebrewed Q meter, for example, and also into a low-frequency dip meter.

ASTRON — SALE!

RS-7A	45.00	RS-35A	123.75
RS-12A	62.75	RS-35M	138.95
RS-12M	78.95	VS-35M	156.95
RS-20A	79.95	RS-50A	179.95
RS-20M	96.45	RS-50M	203.25
VS-20M	114.95	VS-50M	223.95

KLM

2M16LBX.220-22LBX.432-30LBX-90.50	
2M-14C-85.50	2M-22C-108.50
435-18C-110.50	435-40CX-144.50

KENPRO ROTORS

KR4000/KR500	125.95/154.95
KR-5400/KR-5600	247.50/309.95

HENRY AMPS

2 KD CLASSIC	965.00
2002A/2004A Less Relay	1250./1350.
3002A/3004A Less Relay	2100./2100.

AMP SUPPLY

LK-500ZB	1,097.95
----------	----------

MIRAGE-FREE UPS BROWN ON ALL MIRAGE

A1015 - 235.50	C-22A - 85.95
B23A - 83.95	C-106 - 169.95
B215 - 245.50	C-1012 - 246.95
B108 - 149.95	D-24N - 177.50
B1016 - 235.50	D-1010N - 279.50
B3016 - 199.50	D-3010N - 251.00
MP-1 - 99.95	MP-2 - 99.95

TONNA 9F8T ANTENNAS ARE BACK! WE ARE THE EXCLUSIVE U.S. DISTRIBUTOR INTRODUCTORY SPECIAL:
1269/1296 QUAD ARRAY COMPLETE WITH 4-23el YAGIS, 'H' FRAME, POWER DIVIDER, PHASING LINES, CONNECTORS, TERRESTRIAL APPLICATIONS. REGULARLY 339.95 SALE PRICE

5 EL 6 METER YAGI	69.95	13 EL 2MTR YAGI	59.95	TONNA(CALL FOR SPEC. SHEET!!)	
21 EL 70cm YAGI	56.95	23 EL 1296/69 YAGI	46.95	19 EL 70cm YAGI	44.95
(ATV MODELS IN STOCK)		17 EL 2MTR SUPER YAGI	88.00	2MTR OSCARTWIST	65.95
70cm OSCARTWIST	68.95	55 EL 1296 SUPER YAGI	68.95	2 x 9 EL (18el)	
2 x 19 EL (38el.)		9 ± 19 el OSCAR ANTENNA 2M & 70cm ON A COMMONBOOM-GREAT FOR STACKING	75.95		

WATCH OUR ADD FOR NEW LINES!!

FOR THE BEST DEAL IN TOWN CALL THE BEST NUMBER AROUND 1-800-HAM-7373

CUSHCRAFT AOP-1 OSCAR PAK-133.50 RINGO RANGER II (2-220-440)-33.50
KENWOOD TS-940S/AT - CALL US! YAESU FT - 757GX XCVR - 695.95
KENWOOD TR2600A H.T. - CALL US! YAESU FT - 270RH XCVR - 365.95

KENWOOD

FACTORY AUTHORIZED DEALER
CALL US FOR AMERICA'S LOWEST PRICE ON ALL YOUR KENWOOD NEEDS (FREE UPS BROWN ON KENWOOD GEAR)

CUSHCRAFT

215WB - 73.00	A-3	200.45
4218XL - 91.00	A-4	267.45
R-3 - 250.95	40-2CD	267.45

OTHER MODELS IN STOCK — CALL

CUE DEE THE SWEDISH BOOMER
USED BY MANY TOP '10' CONTESTERS
144-15AN 2MTR15EL 75.95

PARABOLIC

1296-28 IW TRANSVERTER	339.95
1269-144 3W UP CONV	319.95
1296 DUAL TUBE AMP CAVITY	439.95
2PORT POWER DIVIDERS (2-220-432)	50.95
4PORT POWER DIVIDERS (2-220-432)	55.95
1296 2PORT DIVIDER	57.95
1296 4PORT DIVIDER	62.95
1269/96 DISH FEEDS	89.95
2304 DISH FEEDS	89.95
1296 SLUG TUNERS	65.95

YAESU — FACTORY AUTHORIZED DEALER CALL FOR THE BEST DEAL AROUND ON 'THE RADIO' FULL LINE (FREE UPS BROWN ON YAESU GEAR)

MUTEK LTD.

DO YOU OWN AN ICOM VHF XCVR? DO YOU WANT TO IMPROVE THE RECEIVER - TRY OUR MUTEK FRONT END BOARD - YOU'LL BE GLAD YOU DID!
RPCB211/251 RD FRONT END 143.95
FOR ICOM 211 OR 251
RPCB271 FRONT END FOR ICOM 271A OR 271H
RPCB225 FRONT END FOR YAESU 221/225
SLNA 505 6MTR PREAMP 84.95
SLNA-144S 2MTR PREAMP 84.95
100WRF SWITCHED, N.F. < 1db GAIN 15db
SBLA144E 2MTR MAST MOUNT R.F. SWITCHED PREAMP.250W THRU POWER, N.F. < 1db 15dbG 169.95
GLNA 433E 70CM MAST MOUNT R.F. SWITCHED PREAMP.50W THRU N.F. < 1db G=15db 172.95
GFBA-144E 2MTR MAST MT. PREAMP, 1KW THRU POWER G=15db N.F. < 8db WITH AMP SEQUENCER 289.95
GLNA-432E 70cm MAST MT PREAMP, 500W THRU, G=15db N.F. < 1db WITH AMP SEQUENCER 299.95
HIGH D.R. DBM XVRTRS FOR± 2MTRS COMING SOON!

SSB ELECTRONIC

K6001 6 To 10 DBM RCV CONV.	115.95
K2001 2 To 10 DBM RCV CONV.	115.95
K7001 70cm To 10 DBM RCV CONV	115.95
K2301G 23cm To 10 or 2 RCV CONV.G.F FRONT END AND DBM	159.95
TV-144-28-10 10W 2MTX XVRTR	209.95
TV-432-28-10 10W 70cm XVRTR	299.95
TV-220-28-10 10W 1 1/4M XVRTR Coming Soon	
DX-144 PREAMP N.F. < 4db	130.95
DX-220 PREAMP N.F. < 5db Coming Soon	
DX-432 PREAMP N.F. < 5db	130.95
(WON DAYTON 1985 N.F. CONTEST)	
DX-1296S PREAMP N.F. 5db	156.95
DX-2320 PREAMP N.F. < 8db	166.95
PA-2310 1269/1296 10W LINEAR AMP	275.95
LT-235 1296 10W LINEAR TRANSVERTER	610.95
2MIF	610.95
LSM-24 1269-2 OSCAR MODE L XMIT CONV. 1W	
OUTPUT, 2M.I.F.	299.95
MICROLINE 13 1/2W 2.3GHZ XVRTR SYSTEM	410.95
2M.I.F.	410.95
MICROLINE 13 3W 2.3GHZ XVRTR SYSTEM, 2M.I.F.	675.95
SLA-13 2304 3W AMP	285.95

MAST MOUNTED PREAMPS:

MV144V 250W R.F SWITCH WITH 12V SUPPLY INTERFACE	175.95
MV432V 150W R.F SWITCH WITH INTERFACE	185.95
MV-144S-01 1KW THRU PWR WITH SEQUENCER	309.95
MV-432S-01 500W THRU PWR WITH SEQUENCER	319.95
MV-1296S 100WTHRU PWR WITH SEQUENCER	349.95

OTHER HIGH QUALITY PRODUCTS IN STOCK-CALL FOR CATALOGUE

GREAT FOR OSCAR MODE 'L' OR 215.95

TERMS: Prices do not include shipping except where indicated and are subject to change without notice. At our discretion some COD's may require a deposit. Returns are subject to a 15% restocking charge *Continental USA only

16 S Mountain Blvd — Rt 309 Mountaintop, Pa 18707

HOURS: Monday thru Friday 10 a.m. - 4 p.m. Saturdays 10 a.m. - 12 p.m.

"24 HOUR PHONE SERVICE FOR YOUR CONVENIENCE!"

MC/VISA/C.O.D

THEY'RE ALL NEW FOR 1986!

Significant changes for 1986 mandate that all hams get both the North American and International Callbooks. **DX'ers and Contester's note** — Having both books is the only way you'll have all Foreign Amateur listings.

Order NOW.

NORTH AMERICAN CALLBOOK

The old US Callbook has been expanded and now contains the listings of all hams in North America plus Hawaii and US Possessions. This improved operating aid has all the latest calls and QTH information available at press time and will be an invaluable reference guide. With calls from Panama to Greenland, every ham should have a copy of this new book in their shack.

©1985.

CB-US86 Softbound \$21.95

INTERNATIONAL CALLBOOK

The Foreign Callbook is no more! In its place, the new International Callbook includes all Amateurs outside of the North American continent. All the latest callsigns and QTH's are listed to help ensure you get that prized QSL card. Universally recognized as the source of information. Order your's today. ©1985.

CB-F86 Softbound \$20.95



Order Both and SAVE. Reg. Price \$42.90

SPECIAL PRICE SAVE \$2.95

\$39.95



CB-USF

Books will be shipped in late November. Please enclose \$3.50 to cover postage and handling.



BOOKSTORE
GREENVILLE, NH 03048



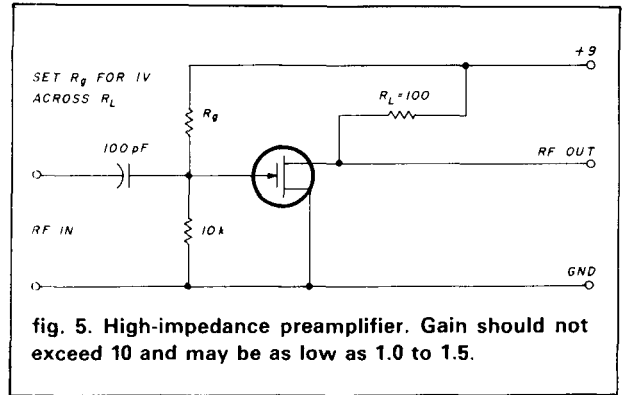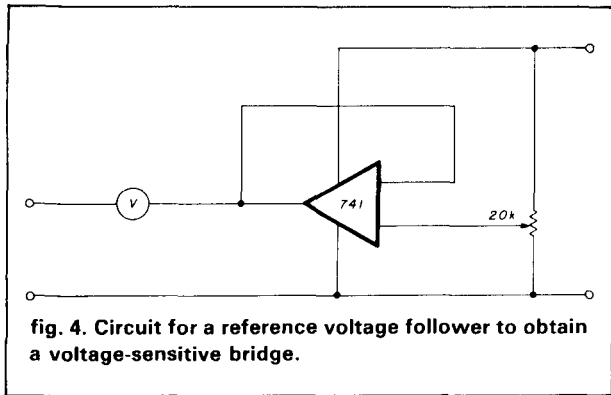


The buffer FET can be the VN10KM mentioned above. (I have described an instrument for testing FETs in *Design of Transistor Circuits, with Experiments*.¹)

The field-intensity meter uses the cascode amplifier operating into the transistor metering circuit. I did not use the FET here because I assumed that the dipole antenna, consisting of two collapsible TV antennas, would have essentially a low-impedance output. (A suitable loop may be used instead, however.) The unit seems to work quite well.

The low-frequency dip meter must use variable-inductance tuning because a variable capacitor of appropriate size for this application would be much too large, and smaller ones would have too high reactance. The basic oscillator circuit I used is based on an emitter-coupled amplifier with a variable LM 334 current source for the base drive on both transistors, **fig. 7**. The oscillation level is set with a potentiometer across the LM 334 control points, and magnetic coupling is used to test a circuit. I have arranged the assembly so that I can plug in a variety of slug-tuned coils; the coils have slugs on threaded rods with a short piece of piano wire soldered in the screw slot. The drive consists of a piece of quarter-inch brass rod drilled and slotted to engage the wire. The frequency change is slow and smooth.

I can also tap off RF output from the FET buffer for frequency counting or use as a signal source. This unit easily fills the gap between audio and 2 MHz, the lower limit on most dip meters. The actual circuit is a combination of **figs. 3, 4, and 7**.




The Q meter used the same metering circuit as the dip meter for measuring RF. The RF source I use is a conventional inexpensive signal generator, except that I have tapped in on it prior to its normal output stage. These deliberately generate distorted waveforms to create harmonics in the output. You may wish to put an FET buffer between the oscillator and the special output to ensure better frequency stability. A suitable circuit for this is shown in **fig. 8**. About 10 millivolts of RF are needed by the Q meter input circuit.

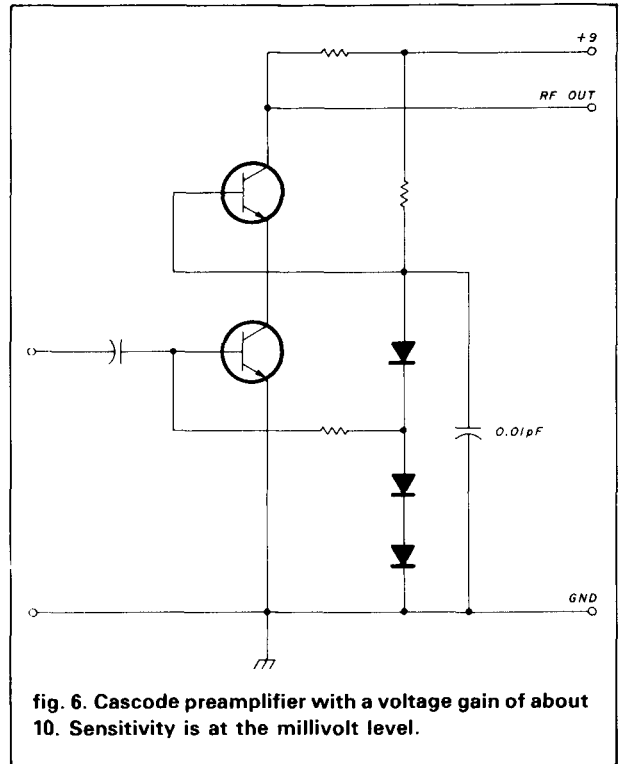

The RF drive transistor that provides the RF signal to the measurement circuit should be a high-frequency bipolar transistor, and should provide a voltage gain of approximately 10 overall. (Only a hundredth of this is actually applied to the tuned circuit, 100 microvolts.) The full output is used to calibrate the circuit, and the part to control the tuned circuit. One is then matched against the other, based on oscilloscope calibration. A possible circuit is shown in **fig. 9**. Minimum Q sensitivity will be about 20. About 25 mA of collector current will be needed by the 2N2222 or 2N2369 to provide the required signal voltage. A Q test circuit is shown in **fig. 10**.

calibration

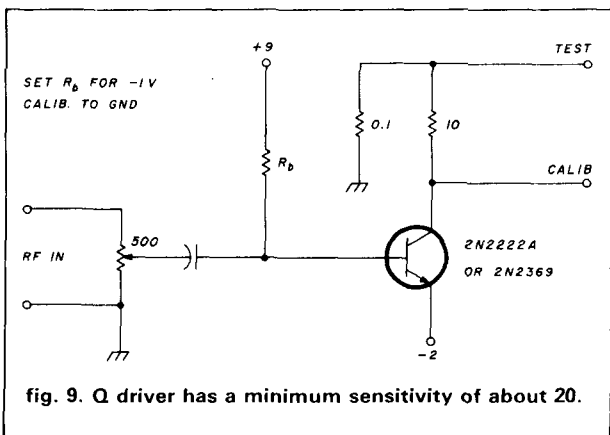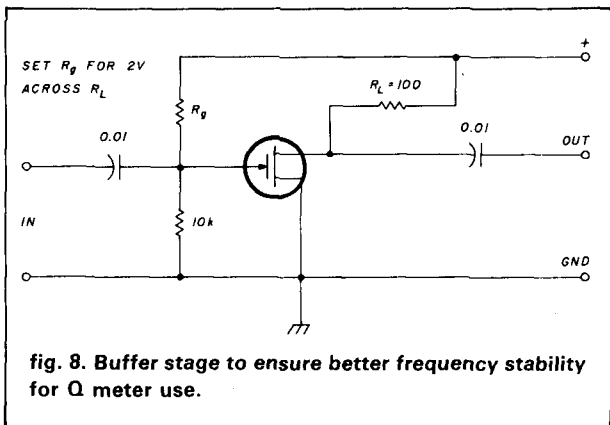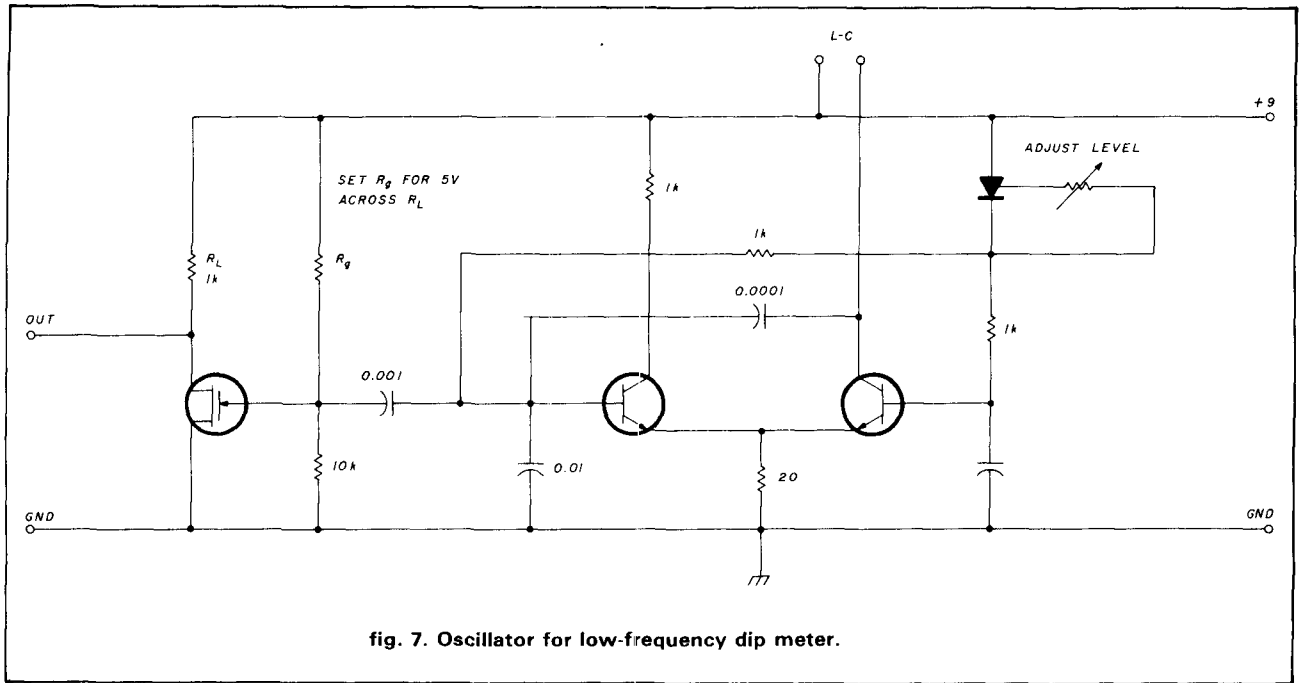This calibration technique, done with an oscilloscope, can be used wherever minimum or maximum



and an AC signal. RMS calibration should be used. The low-frequency calibration is used, with the help of the oscilloscope, to calibrate sinusoidal signal well within the upper limit of the oscilloscope (1/2 to 1 MHz for a 5 MHz unit). This calibration then is transferred to the Q meter measuring circuit. The source calibration voltage for setting the Q meter reference input may be adjusted for 20, 50, and 100 millivolts for the reference excitation. This will make possible measurements of Q to 100, 200, and 500. In addition, the meter is calibrated for a series of input signals ranging from about 10 mV to 100 mV, at least every 10 mV, to provide the actual Q measurement. A special scale may be made for the meter if desired. Since the Q is proportional to the RF voltage generated, calibration is important.

concluding remarks

These simple probe circuits can easily be built into transmitters, and receivers in which critical tuning is required as well as into other useful test instruments. In all cases, it is important to minimize probe loading on the circuit being tested without simultaneously degrading sensitivity. The VMOS circuits are ideal for this purpose, and they do not limit as readily as bipolar transistors. Where either germanium or silicon diodes can provide adequate sensitivity, they, of course, are the component of choice, but they do have the excessive threshold voltage requirement that the current-stabilized transistor circuits can help overcome.

RF measurements have always been a stumbling block in the typical Amateur station, including mine. I can remember building a nice wavemeter that I was

deflection is insufficient to assure proper circuit operation, but an actual voltage value is required. The oscilloscope can be calibrated with a reference voltmeter

WOW! AT LAST!! A VERY AFFORDABLE COMPUTER AT A VERY AFFORDABLE PRICE

POWERFUL FULLY PROGRAMMABLE WITH 2K OF MEMORY—PORTABLE—6.78" x 1.38" INCH MODULE SINGLE KEY ENTRY COMMANDS—DURABLE 40 KEY MEMBRANE TYPE KEYBOARD—2804 BASED FOUR CHIP DESIGN—EDUCATIONAL—UNIQUE SYNTAX-CHECK REPORT CODES FOR ERROR IDENTITY—GRAPH DRAWING AND ANIMATED DISPLAY—ACCURATE TO 9.12 DECIMAL PLACES FOR FULL RANGE MATH AND SCIENTIFIC FUNCTIONS—AT AN AFFORDABLE PRICE

WE CANNOT TELL YOU THE MAKE OF THE COMPUTER BUT IT WAS MADE BY A FAMOUS WATCH COMPANY. THEY USED TO SELL FOR \$99.95.

WE BOUGHT OUT WHAT THE FACTORY HAD LEFT IN STOCK AND HAD TO REMOVE THE LABELS. THESE UNITS ARE UNPACKAGED. LESS THE 9V WALL ADAPTER AND MANUAL. BECAUSE THIS IS A DISCONTINUED ITEM THERE IS NO WARRANTY.

GET THEM WHILE THEY LAST LIMITED SUPPLY

BUY 1st UNIT FOR \$19.95 BUY 2nd FOR \$16.95 9V DC WALL ADAPTOR \$4.95
BUY THE 3rd UNIT (NON OPERATING FOR PARTS) \$10.95 MANUAL (OVER 150 PAGES) \$2.95

See September 1984 issue of 73 for TIMEX/RTTY article

CHIP BONANZA (AT THESE PRICES THEY ARE A STEAL)

2708		\$1.00 EA OR 10 FOR \$ 9.00
2716		\$2.25 EA OR 10 FOR \$20.00
2732		\$3.25 EA OR 10 FOR \$30.00
2754		\$4.00 EA OR 10 FOR \$35.00
27138		\$7.00 EA OR 10 FOR \$60.00
6602		\$4.95 EA OR 10 FOR \$45.00
6610	(REG \$3.95)	\$1.95 EA OR 10 FOR \$18.00
66A06	(REG \$19.95)	\$5.95 EA OR 10 FOR \$50.00
66A21	(REG \$9.95)	\$2.95 EA OR 10 FOR \$25.00
4116	(or equivalent)	8 FOR \$ 5.99
4134		9 FOR \$12.95
XR-2211	(SPECIAL)	\$ 2.95
TMS 9900N1	MICRO-P 54 PIN 8 BIT DB + 16 BIT CPU	\$ 4.95
TMS 9901N1	MICRO-P PSI	\$ 2.95
TMS 9904N1	MICRO-P CLOCK GEN AND DRIVER	\$ 5.95
TMS 9918AN1	MICRO-P COLOR GRAPHICS AND DISPLAY	\$ 9.95
KEYBOARD (964)	48 KEYS MEASURE 4 x 10 (H1-TEK)	\$ 9.95

HAL'S COMPUTER GOODIES

Timex printer (reg \$99.95 now \$59.95)
Colec cassette player (battery op.) \$29.95
9V @ 850 Ma adapter (needed for 16K RAM packs) \$7.95
16K RAM pack module, new \$29.95
16K RAM pack module, refurbished \$19.95
RCA TV interface cable \$1.25
Dual jack cassette interface \$2.50
TV/Computer game switch \$3.95

Cassette Software:

I have cassette software and for list (reg \$9.95-\$14.95)
Hal's Special Price: 1 for \$3.95, 3 for \$10.95, 6 for \$19.50, 10 for \$29.50, 20 for \$50.00
or let Hal select 25 different cassettes (my choice at 25 for \$50.00!!)


APPLE II and APPLE II+ COMPUTER MAINFRAMES fully populated \$150
Power supply, case and keyboard, separately available Call or Write
Unit as described above, fully assembled & tested \$350 plus shipping
APPLE POWER SUPPLIES \$29.95

SHIPPING INFORMATION: ORDERS OVER \$25 WILL BE SHIPPED POST-PAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED OR ORDERS LESS THAN \$25 PLEASE INCLUDE ADDITIONAL \$2.50 FOR HANDLING AND MAILING CHARGES. MICHIGAN RESIDENTS ADD 4% SALES TAX. SEND 20¢ STAMP OR BASE FOR FREE FLYER. CANADIAN ORDERS ADD \$5.00 POSTAGE IN U.S. FUNDS.

HAL-TRONIX, INC.
P.O. BOX 1101 - DEPT. HR
SOUTHGATE, MICH. 48195
PHONE (313) 285-1782



"HAL" HAROLD C. NOWLAND W8ZXH

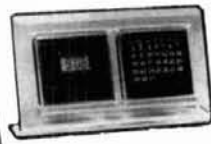

RECEIVE THIS LCD CALENDAR/CLOCK FREE WITH YOUR SUBSCRIPTION

WHAT'S REALLY HAPPENING IN HOME SATELLITE TV?

STV THE HOME SATELLITE TELEVISION MAGAZINE

A monthly of 100-plus pages—has everything you need to know about where to find equipment, how to install it, system performance, legal viewpoints, and industry insights! With your subscription to STV you will receive a FREE LCD Calendar/Clock.

- Only \$19.95 per year (12 monthly issues)
- \$1.00 for sample copy

ORR BOOKS



BEAM ANTENNA HANDBOOK
by Bill Orr, W6SAI and Stu Cowan, W2LX

The Beam Antenna Handbook, first published in 1955, has been completely revised and updated with the latest information on Beam Antenna design. Computer designed Yagis give maximum gain in minimum space. New info on Yagi HF and VHF beams and dimensions on beams for 10, 18 and 24 MHz WARC bands. Everything you need to know about beam design, construction and operation. 204 illustrations. 268 pages. 1st edition. ©1985.

RP-BA Softbound \$9.95

SIMPLE-LOW-COST WIRE ANTENNAS
by Bill Orr, W6SAI

Learn how to build simple, economical wire antennas. Apartment dwellers take note! Fool your landlord and your neighbors with some of the "invisible" antennas found here. Well diagrammed. 192 pages. ©1972. 2nd edition.

RP-WA Softbound \$7.95

THE RADIO AMATEUR ANTENNA HANDBOOK
by William I. Orr, W6SAI and Stuart Cowan, W2LX

Contains lots of well illustrated construction projects for vertical, long wire, and HF/VHF beam antennas. There is an honest judgment of antenna gain figures, information on the best and worst antenna locations and heights, a long look at the quad vs. the yagi antenna, information on baluns and how to use them, and new information on the popular Sloper and Delta Loop antennas. The text is based on proven data plus practical, on-the-air experience. 190 pages. ©1978. 1st edition.

RP-AH Softbound \$7.95

ALL ABOUT CUBICAL QUAD ANTENNAS
by Bill Orr, W6SAI — New 3rd Edition

Includes NEW data for WARC bands
The cubical quad antenna is considered by many to be the best DX antenna because of its simple, lightweight design and high performance. You'll find quad designs for everything from the single element to the multi-element monster quad. There's a wealth of data on construction, feeding, tuning, and mounting quad antennas. 112 pages. ©1982. 3rd edition.

RP-CQ Softbound \$6.95

Please add \$1.50 for one book, \$2.50 for two or more books to cover shipping and handling

Ham Radio's Bookstore Greenville, NH 03048

IF YOU HAVE A SATELLITE SYSTEM, THEN YOU REALLY NEED ...



OnSat

The best in satellite programming! Featuring: ★All Scheduled Channels ★Weekly Updated Listings ★Magazine Format ★Complete Movie Listing ★All Sports Specials ★Prime Time Highlights ★Specials Listing and ★Programming Updates!

- Only \$45.00 per year (52 weekly issues)
- 2 Years \$79.00 (104 weekly issues)
- \$1.00 for sample copy

Visa® and MasterCard® accepted (subscription orders only). All prices in US funds. Write for foreign rates.

Send this ad along with your order to:

STV®/OnSat®


P.O. Box 2384—Dept. HR • Shelby, NC 28151-2384
SUBSCRIPTION CALLS ONLY
TOLL FREE 1-800-438-2020



Rob, WA3QLS



Katherine, KA31YO

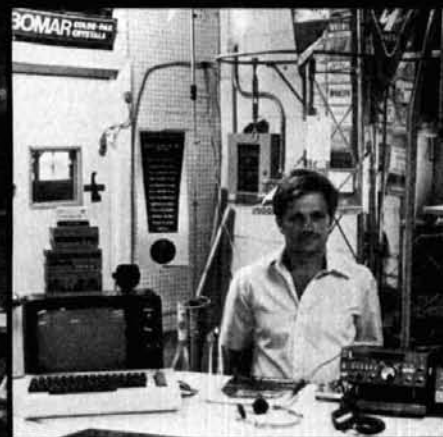

Paul, WA3QPX

Delaware Amateur Supply

71 Meadow Road, New Castle, Del. 19720 302-328-7728

Factory Authorized Dealer! 9-5 Daily, 9-8 Friday, 9-3 Saturday

**KENWOOD YAESU ICOM TENTECH
MICROLOG KDK SANTEC KANTRONICS**

800-441-7008

*Order & Pricing
New Equipment*

Large Inventory



Daily UPS Service



**All Other Calls
302-328-7728**

**No Sales Tax
in Delaware!
One mile off I-95**

Ham Radio's Bookstore

ARRL Q&A LICENSE MANUALS ALL LICENSE CLASSES NOW AVAILABLE!

ARRL Q&A License Manuals are keyed to the latest FCC Exam syllabi now in use by the Volunteer Examiners. These books are written in an easy-to-read conversational style that enhances understanding without scaring the student away. All technical subject areas are explained in clear terminology and with plenty of illustrations, diagrams and schematics. Rules are also fully covered. Each book has the official ARRL multiple choice question Pool with answers and a key to the FCC Exam syllabus for reference to other study publications. These are *the* study guides to have. All books ©1985 1st Editions.

- AR-TG General **Softbound \$5.00**
- AR-AG Advanced **Softbound \$5.00**
- AR-EG Extra **Softbound \$5.00**

HR CODE TAPES

Formerly Kantronics Tapes

These code tapes have been designed by experts to help you learn code. Several different methods are available for all classes of license. Transcripts enclosed for checking copy.

Gradient Tapes. (Slowly increasing in speed)

- KT-NG Novice 4-9 WPM **\$6.95**
- KT-GG General 7-15 WPM **\$6.95**
- KT-EG Extra 13-23 WPM **\$6.95**

QSO Simulation Tapes

- KT-QS01 7.5, 10, 13 & 15 WPM 1 hour **\$5.95**
- KT-QS02 7.5, 10, 13 & 15 WPM 1 hour **\$5.95**
- KT-QS03 13 WPM 1 hour **\$5.95**

ANTENNA COMPENDIUM edited by ARRL Staff

This book has more than 20 antenna articles that have never been published before. Subjects covered include: Quads, Yagis, Phased Arrays, Log Periodics, Subsurface Antennas, "The Old Spruce Antenna", as well as discussions on Smith Charts, antenna design, the G5RV multi-band antenna and antenna polarization. Great summer reading and full of ideas for Fall '85 antenna projects. ©1985, 1st Edition.

- AR-AC **Softbound \$9.95**

AMECO STUDY GUIDES

Designed for VEC Exams

AMECOA Study Guides are taken from the FCC Amateur Exam syllabus, PR-1035 and have answers keyed to ARRL's recently released study material. These study guides are compatible with ARRL and all other VEC Exams. While nothing can guarantee that you will pass, AMECO Study Guides will make sure that you are fully prepared and ready to go when you sit down for the exam. Written in clear, concise, easy-to-read format, each question fully explained. Novice and General books cross referenced to AMECO's 102-01 for a more thorough explanation.

- 27-01 Novice Class **Softbound \$2.95**
- 12-01 General Class **Softbound \$4.95**
- 26-01 Advanced Class **Softbound \$4.95**
- 17-01 Extra Class **Softbound \$4.95**

THE AMATEUR RADIO VERTICAL HANDBOOK

by Cpt. Paul H. Lee, USN (Ret.), N6PL

This is the **only** book dedicated to the vertical antenna and will be of interest to all those using or looking to use the vertical design. Based upon the author's years of work with a number of different vertical antenna designs, you'll get plenty of theory and design information along with a number of practical construction ideas. Included are designs for simple 1/4 and 5/8-wave antennas as well as broadband and multi-element directional antennas. Paul Lee is an engineer and avid ham and is Amateur Radio's resident expert on the vertical antenna. ©1984, 2nd edition.

- CQ-VAH **Softbound \$9.95**

COMPUTER WIMP

By John Bean

"166 things I wish I had known before I bought my first computer." Based upon ten years of often frustrating experience, this light-hearted, text is designed to help you learn about computers and to make intelligent decisions about their purchase. Author Bean first examines common pitfalls about purchasing a computer. He then examines warranties, how to deal rationally with malfunctions, how to buy by mail, how to talk "technobabble" or computerese, how to avoid computer phobia, games, software piracy and much more. 1st Edition 285 pages • 1983

- TP-CW **Softbound \$9.95**

COMMUNICATIONS SATELLITES

by Larry Van Horn

Here's the most exhaustive text ever written about communications satellites! Easy-to-read text along with plenty of pictures and illustrations make this new book a veritable gold mine of information. Nine chapters include: OSCAR, weather, domestic and international communications satellites, DBS, space shuttle, U.S. Military and space surveillance systems and Soviet Space program. Also included are four appendices on satellite frequency cross references, satellite compendium, current geostationary satellites and a bibliography. Must reading for all satellite users. ©1985 1st edition 216 pages.

- GE-CS **Softbound \$12.1**

THE COMPLETE DX'ER

by Bob Locher, W9KNI

DX'ing can be as simple as turning the radio on and searching across a band, or it can be hours spent studying propagation reports, sunspot figures and the DX newsletters looking for tidbits of information. The first part of the book is designed to teach the reader DX'ing fundamentals: Part two is for the "over 200 countries worked" operator and has plenty of handy tips, aids and ideas. Part three is full of more esoteric hints for the "over 300 countries worked" operator. This book tells **all** and should be required reading before anyone starts their quest for DXCC. Even if you don't care about DXCC, Bob's easy-to-read style of writing is most enjoyable reading. ©1984, 1st edition.

- ID-DX **Softbound \$10.**

UNDERSTANDING DATA COMMUNICATIONS

(Includes Packet Information)

By G. Friend, J.L. Flke, H.C. Baker and J.C. Bellamy

Covers basic concepts of data transmission and reception: asynchronous and synchronous protocols, error control & networking data communications systems. Data terminals are fully discussed as are message and transmission terminals, modems and interfaces, fiber optics and satellite communications systems. Packet Networks and standard are covered with information on X.25 switching architecture. ©1984 1st edition 272 pages.

- TI-UUC **Softbound \$14**

COMPUTER

COMPUTER PROGRAMS FOR THE RADIO AMATEUR

by Wayne Overbeck, N6NB, and Jim Steffen, KC6A

Here's the best source book of computer programs for 1 Radio Amateur. Besides covering computer basics, this book gives you programs that will help you log, determine sunrise/sunset times, track the Moon's path across the sky, use Greyline propagation and set up record systems for WAS, DXCC and VUCC, or any other award. You can either buy the book alone or you can buy the book with the programs already on disk. Take full advantage of your computer with this well written source book. ©1984, 1st edition, 327 pages.

Program Listing

- Data Base Mgmt.**
- Logs, Awards Data Base, Gridlocator
- Latitude/Longitude Programs**
- Data File, Beamheadings, DX Display, Sunrise Chart, Greyline, DX Checker
- Contest and Duping**
- Dupechecker, General Contest Logger, Field Day Logger, Sweepstakes Logger, Log Print
- Antenna Programs**
- Antenna Scaler, Matching Evaluator, Vertical Pattern Plot
- EME**
- EME System Calculator, Sky Locator, Moontracker

- HA-0657 **Softbound \$17**
- HA-0657 book with program disk **\$29**
- specify computer (see list below)
- Program disk alone **\$19**
- specify computer (see list below)

Programs available for: Apple II (DOS 3.3), IBM PC-DOS TRS-80 Model I and Model III and Commodore C-64. Please mark your order with the program disk you want



By
Chip Lohman
NN4U

AMATEUR RADIO COMPUTER SOFTWARE

ANTENNA DESIGN

This self-prompting program covers dipoles, Yagis, long wires, rhombics, quads, loops, verticals and other antennas. You simply enter the frequency you are designing an antenna for, the antenna you want to make, and the computer will give you all the initial design specifications you need. The results can be stored on disk for permanent retention.

- HD-AD (For C-64) **\$9.95**

PROPAGATION CHART

Invaluable addition to any Hamshack. The Propagation Chart allows you to determine the maximum usable frequency (MUF) and the optimum frequency (FOT) between your QTH and any spot on the globe. You can get either a screen display, a printed tabular list over several days, or a printed graph of MUF and FOT. You also get automatic beam headings and distance to the DX station. Covers 160-10 meters and the new WARC bands.

- HD-PC (For C-64) **\$16.95**

SUPER LOG

Super log gives you all the advantages of a computerized data base without significantly changing the traditional log format. For contesters, Super Log can be configured to either manually or automatically enter contact number as well as time of contact. Make an error and you can easily

go back and edit the entry. Super Log also allows you to print out either selected contents or the whole log. Will print QSLs.

- HD-SL (For C-64) **\$19.95**

CONTEST LOG

This disk contains four different contest programs; ARRL Sweepstakes, Field Day, Universal WW Contest log, plus a dupe checking routine. Each program is designed for real time use. It automatically enters date, time, band and serial number for each contact. A 24-hour clock is displayed at the top of the VDT screen. When the contest is over, the program will print your results listing all duped and scored contacts in serial sequence with all the necessary information as well as completed score at the bottom of the page.

- HD-CL (For C-64) **\$24.95**

MASTER LOG

Over three years of development went into this program. It creates a file of 2100 individual records with up to 13 different entries per record. Master Log can do a search and select based upon time, frequency, mode or any of the other variable parameters. It keeps track of DXCC and WAS status, prints QSL labels and can search its whole file in less than 5 seconds! Complete documentation is included to help you learn and use this truly state-of-the-art logging program.

- HD-ML **\$28.95**

Ham Radio has many other books in stock not shown here.

Call or write today for your free catalog or to place an order. (603) 878-1441 8-4 EST

Please enclose \$3.50 with your order to cover postage and handling.



Holiday Special

Stocking Stuffers and Other Gift Ideas

BEAM ANTENNA HANDBOOK

by W6SAI and W2LX

Completely revised and updated the **Beam Antenna Handbook** includes the very latest state-of-the-art antenna design. Computer generated beam dimensions for the 40, 30, 20, 17, 15, 12, 10 and VHF bands are included eliminating the need for time consuming math calculations. Also covered are: Beam height and optimum apex of radiation, how element types and hardware effect performance, effect of nearby objects on radiation patterns, feedlines, baluns and matching systems and much more. Ham Radio VHF columnist W1JR, and noted European VHF'er DL6WO's VHF antenna designs are covered extensively as well as NBS VHF long Yagis. 268 clearly written pages — 204 easy-to-understand illustrations, make this the book to buy for beam construction. ©1985. 1st edition.

RP-BA Softbound \$9.95

1985-86 ARRL REPEATER DIRECTORY

You could call this book the "repeater bible". Close to 8,000 listings include stations organized first by frequency then by state and region. All of the important details such as access tones, auto patch, etc. are also included. If you do any traveling and take a two-meter rig with you, this is the book to have! ©1984.

AR-RD Softbound \$3.00

ARRL OPERATING MANUAL

Brand New 2nd edition. Just released and fully revised! This book tells you all about how to operate your station. Message handling, emergency traffic, tips for successful contesting and DX'ing are fully covered as well as new sections on digital communications and satellite operation. The reference section has been greatly expanded to include many new entries. ©1985 2nd Edition.

AR-OG Softbound \$5.00

SOFTWARE

RTTY MAILBOX MSO

for Vic 20 and C-64 Computers

Turns your Commodore home computer into a powerful, easy-to-use message handling system. Messages can be stored, read or deleted by either incoming RTTY signals or by using the computer's keyboard. Each message is listed in a directory by file name, along with date and time of message initiation. The Basic/Assembly language software combines high speed with user friendly features and fully controls your transmitter and receiver with automatic identification, an optional special message and automatic transmission of date and time during MSO use. You can also use this program to operate direct RTTY and 60, 67, 75 or 100 wpm Baudot or 110 baud ASCII. Vic 20 needs 24k of memory to use this program.

VC-CP Use with AEA CP1 interface & equiv. **\$79.95**

VC-MF Use with MFJ interface & equiv. **\$79.95**

VC-KT Use with Kantronics interface & equiv. **\$89.95**

RF NOTES by John Simmons, W6MDI

Here's an easy way to get answers for often asked electronics questions. **RF NOTES** contains programs written by RF consulting engineers that answer: *dB conversion*, to convert voltage, current or power levels to dB; *dBm conversions*, converts voltages or power levels to dBm and dBm to voltage or power; *VSWR calculations*, calculates VSWR and return loss when both reflected and incident powers are known; *Filter design*, 14 different filter configurations including schematics (6 low pass, 4 high pass, 2 band pass and 2 band elimination circuits); *Basic Micro-strip and basic strip line design*; and *resonant circuits*, design parallel and series resonant circuits, Pi, capacitive impedance divider and inductive impedance divider. This disk is an invaluable reference for all Radio Amateurs. Graphics cards required.

E-RF (IBM PC only) Monochrome Monitor **\$59.95**

E-RFC (IBM PC only) Color Monitor **\$59.95**

CONTENDER II LOGGING DATABASE

(Commodore C-64)

This Commodore C-64 program will meet just about every logging need you can imagine. It can be used as a contest log, general log or dupe checker and can be used for all band WAS, WAZ or DXCC. The storage disk holds up to 2,000 exchanges and can be edited and updated simply and easily. Each entry contains callsign, signal reports, automatic or manually entered time and date, band and mode as well as name and QTH. Contender will also print QSL's, mail labels and contest dupe sheets. The Contender USA-CA (three disks) is a Worked All County data base that saves time and hassle and a tremendous amount of paperwork.

CT-C Basic Contender (C-64) 1 disk **\$34.95**

CT-CUSA Contender Plus USA-CA (C-64) 3 disks **\$49.95**

PACKET RADIO THRU SOFTWARE

AX.25 Protocol

You can get on Packet Radio two ways. One is with a sophisticated "black box." The other is by making your computer act like a "black box" by programming it in a high level machine language code. W4UCH has written a machine language program for the Radio Shack TRS-80 Models 1, 3 and 4 computer (Model 4 works with Model 3 disk while in Model 3 mode). This book has twelve chapters plus seven appendices that take you step by step through the process of setting your computer to first convert the digital information into a useable format and then to decode the information. ©1984, 3rd edition.

RE-AX Softbound **\$21.95**

RE-MI Model 1 Disk **\$29.00**

No Documentation included
 RE-MIII Model III & 4 Disk **\$29.00**

No Documentation included
 RE-BD special book and disk **\$49.95**

(Specify disk; Mod. I or Mod. III)

COMPUTERIZED DX EDGE

Generate your own Greyline display.

Xantek has adapted their best selling DX Edge to the computer world and it comes at a very reasonable price. This computerized operating aid brings into your ham shack the ability to know and predict when and where DX is going to appear. When you are using the program, the computer will automatically update the information as the sun progresses across the face of the Earth. To make the computerized DX Edge even easier to use, the display is keyed to the DXCC list and the 40 CQ zones. Disk and documentation are just \$34.95. This is something you've Got to have! ©1985.

XN-C64 (For Commodore C-64)

\$4.95

AEA MORSE UNIVERSITY


Contains • C-64 code training cartridge software package (no disk or cassette necessary).

• ARRL's *Tune In The World With Ham Radio*
Great NEW way to study for your Novice License!

This brand new package contains all one needs to learn the code and theory for the Novice class Radio Amateur exam. Basic code is taught using a character by character teaching routine. Practice can be either with individual letters or in groups of up to nine characters. Proficiency is developed through practice sessions that can be: progressively speeded up during the session, either random characters or five letter groups, Farnsworth (high speed characters, slow spacing) or slow speed sending. AEA has incorporated a video game to make the code learning process even more fun. You can also enter text from the keyboard for "customized" practice sessions or as an example of how code should sound. An analysis routine is included so that the computer can check one's progress in learning the code. ARRL *Tune In The World* booklet will give you all you need to know to pass the Novice theory and regulations Exam. Great state-of-the-art teaching device. Sure to be a hit this fall. Get one now. It's a great holiday season gift!

AEA-MU (For C-64)

\$39.95

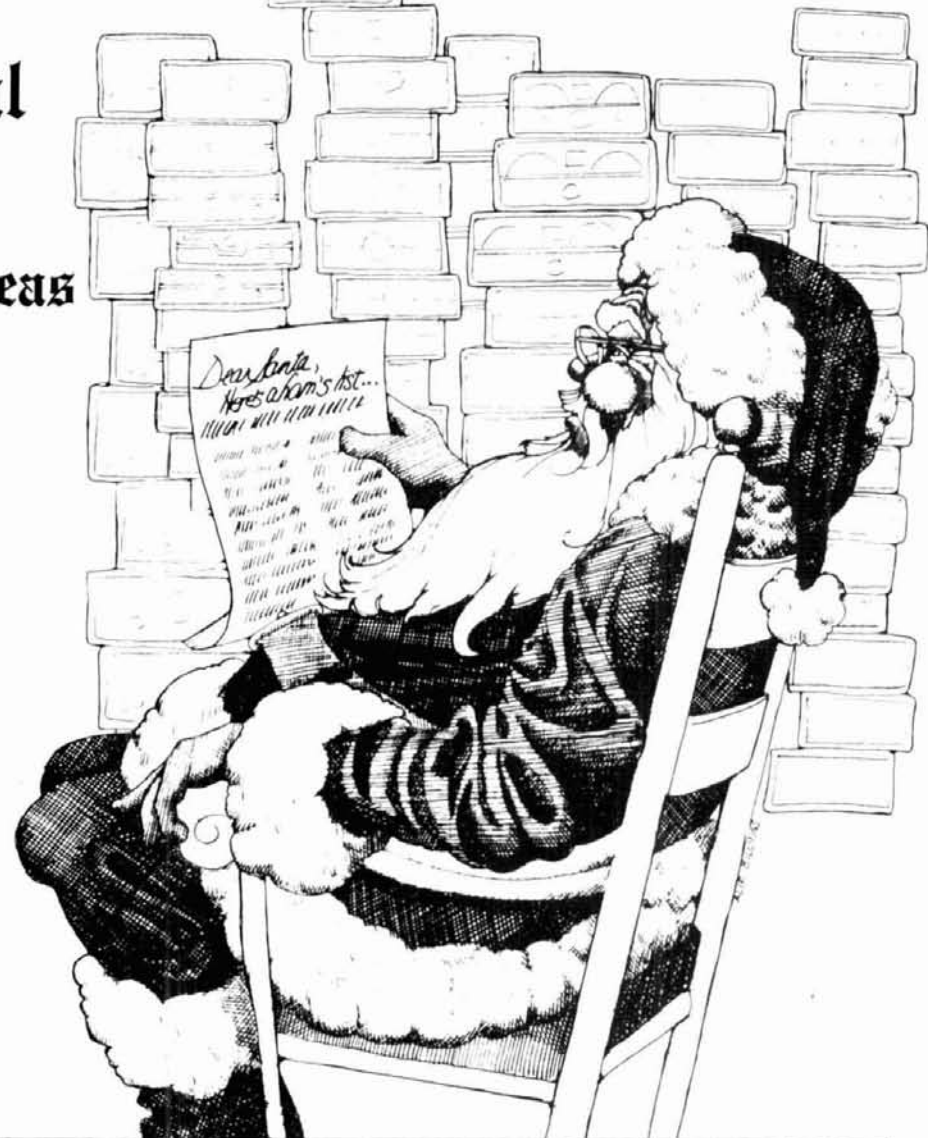

NEW

Alpha Delta Model DX-A 160-80-40 METER QUARTER WAVE

TWIN SLOPER ANTENNA

The Model DX-A combines the tremendous firepower of the quarter wave sloper with the wide bandwidth of a half wave dipole. Simple to install, quick to tune. Proven longhaul DX performance.

- Installs like an inverted-V dipole. One leg for 80 meters (67') and the other leg for 160/40 meters (55'). Fed with a single 50 ohm coax. SO-239 connector provided on mounting bracket.
- Configuration provides wide bandwidth on all three bands. Typically 70 kHz on 160 meters, 200 kHz on 80 meters and full band on 40 meters. Much wider than most other loaded slopers, dipoles or verticals. Tuner usually not required.
- Model DX-A also operates on 30-17-12 meters. VSWR of less than 2.5:1. Easily matched with a tuner.
- High-power operation. Rated at 1500 watts P.E.P. output. No traps to break

down. A single "ISO-RES" isolator-resonator is used in the 160/40 meter leg.

- Current lobe up high for maximum radiation and excellent DX performance. Can be installed from 25 to 40' high.
- The Model DX-A Antenna is fully assembled, uses all stainless steel hardware, a UV-protected "ISO-RES" coil, #12 copper wire and is rated for severe environments. Specially coated wire disappears from your neighbors' view.

\$49⁹⁵ Available from your local Alpha Delta Dealer or add \$4.00 shipping and handling (USA only).

ALPHA DELTA COMMUNICATIONS, INC.

P.O. Box 571 Centerville, OH 45459
(513) 435-4772 Orders • (513) 376-4180 Antenna Tech Info



current solutions to current problems

✓ 180



"TUNE IN" THE WORLD OF SPECIALIZED COMMUNICATIONS!

Thousands of "Ham Radio" operators across the country are enjoying "Specialized Communications" modes. Whether it's FSTV, SSTV, FAX, OSCAR, EME, RTTY, PACKET or COMPUTERS, today's Radio Amateur is a highly skilled Communications Specialist!

Providing full, in-depth coverage of these modes is our business and we've been doing it now for over 19 years! And now we're expanding!

Iowa Residents Must Add 4% Sales Tax.
4% Added To All Charge Card Orders.



Now published "monthly" 10 times per year, SPEC-COM™ readers are kept up-to-date in a world of fast moving modern technology.

Why not give us a try? Back issue samples are available for just \$2.00 ppd. (Master Article Indexes add \$1.00).

Special Six Month Trial Subscription -\$10.00. U.S./Canada/Mexico Annual Subscription \$20.00. (Foreign Subscriptions slightly higher).

SPEC-COM™
Amateur Radio Specialized
Communication Journal
P.O. Box H
Lowden, Iowa 52255
(319) 944-7669 (Membership Services)

✓ 181

AZOTIC INDUSTRIES

2026 W. BELMONT
CHICAGO, IL 60618
312-975-1290

ELECTRONIC COMPONENTS & SUPPLIES

- RF CONNECTORS
- UG CONNECTORS
- AUDIO CONNECTORS
- LINEAR IC'S
- DIGITAL IC'S
- TRANSFORMERS
- METERS
- COMPUTER CABLES
- DISKETTES
- IDC CONNECTORS
- D-SUBMINIATURE
- TEST EQUIP
- TRANSISTORS
- DIODES
- TRIM CAPS
- RELAYS
- SWITCHES
- TOOLS

VISIT OUR RETAIL STORE
HRS. MON-FRI 10-5 SAT 10-2
PHONE ORDERS WELCOMED
312-975-1290 ✓ 182

STATION MANAGER/ADVANCED

A General Purpose Logging Program

Designed for the IBM® PC,® XT,® enhanced PC jr.® Menu driven; prompts for easy use; full color displays; multiple logs (each up to 1,000 entries with user editing), several reporting methods including one by partial call sign.

FALL SPECIAL

\$59.00 includes: 90 pg. User's Guide & Diskette (source code included)

\$20.00 — User's Guide only (may be applied to full purchase price)

Ohio residents include sales tax.

OMEGA CONCEPTS

Professional software for the Radio Amateur™

P.O. Box 615
Troy, OH 45373



T.L. Jones (KB80A)
Author ✓ 183

IBM is a registered trademark of International Business Machine Corp.

Electronic Repair Center Servicing

Amateur Commercial Radio

The most complete repair facility on the East Coast.

Large parts inventory and factory authorized warranty service for Kenwood, Icom and Yaesu.

SEND US YOUR PROBLEMS

Servicing "Hams" for 30 years, no rig too old or new for us.

HAMTRONICS, INC.

4033 Brownsville Road

Treose, Pa. 19047

215-357-1400



**"HAM HOTLINE"
THE PROVEN MONEYMAKER**

The "Ham Hotline" is a complete mailing list of novice amateur radio operators and current hams who have renewed, upgraded or modified their FCC licenses. These ham enthusiasts have proven to be excellent prospects for radio equipment, accessories and publications.

The Hotline is **UPDATED EVERY TWO WEEKS** with an average of 8,000 names and addresses each month. And, because we know the Hotline is the most up-to-date amateur radio listing available, we'll guarantee 98% deliverability.

Target your sales efforts to your most likely buyers. Call DCC Data Service today and begin your subscription to the "Ham Hotline" . . . the proven moneymaker.

DCC Data Service ✓ 184

1990 M Street, N.W. Suite 610
Washington, D.C. 20036

Toll-free 1-800-431-2577

In DC & AK 202-452-1419

FREE CATALOG!

Features Hard-to-Find Tools
and Test Equipment



Jensen's new catalog features hard-to-find precision tools, tool kits, tool cases and test equipment used by ham radio operators, hobbyists, scientists, engineers, laboratories and government agencies. Call or write for your free copy today.

✓ 185

**JENSEN
TOOLS INC.**

7815 S. 46th Street
Phoenix, AZ 85040
(602) 968-6231

**SPS
DIST.**

**'TI'
FINDER +**



Complete Line of
Satellite Receiving Systems

**SPS
San Pierre, IN**

(219) 828-7255 — 828-3091

✓ 186

ROHN

brings the top to you

ROHN brings the top to you with its patented design. For the ultimate "on the ground" service and antenna installation, a ROHN "Fold-Over" Tower is your best buy. Your safety comes first with "Fold-Over." For complete details write:

ROHN

**"FOLD-OVER"
TOWERS**

P.O. BOX 2000, PEORIA, IL 61656 U.S.A.
TWX: 910-652-0646 FAX: 309-697-5612

**Now You Can Receive
The Weak Signals With The**

ALL NEW AMECO PREAMPLIFIER



Model PT-2 is a continuous tuning 6-160 meter Pre-Amp and master power station control. It is specifically designed for use with a transceiver. The PT-2 contains new sophisticated control circuitry that permits it to be added to virtually any transceiver with No modification. No serious ham can be without one. Other features include: *Improves sensitivity and signal-to-noise ratio. *Boosts signal up to 26 db. *For AM or SSB. *Bypasses itself automatically when the transceiver is transmitting. *FET amplifier gives superior cross modulation protection. *Advanced solidstate circuitry. *Simple to install. *Improves immunity to transceiver front-end overload by use of its built-in-attenuator. *Provides master power control for station equipment.

Model PT-2 . . . 117 V. 60 Hz. ✓ 187
Model PT-2E . . . 220-240 V., 50-60 Hz.

AMECO EQUIPMENT CO.
275 Hillside Ave. Williston Park, N.Y. 11596

NEMAL ELECTRONICS INTERNATIONAL

**INTRODUCING
NEMAL**

ASTRO™ SERVICE

GUARANTEED SAME DAY SHIPMENT OR WE PAY THE FREIGHT ON ORDERS OF \$100 OR MORE FOR STOCK ITEMS RECEIVED PRIOR TO 12 NOON EASTERN TIME.

Factory Authorized Distributor for

COLUMBIA ELECTRONIC CABLES

DIVISION CAROL CABLE COMPANY

COAXIAL CABLES

Over 75 types in stock, available in full roll or cut to order. Nemal offers cable made to both military as well as commercial specifications including Teflon cables, Silver plated cables and high power RF cables.



MULTI CONDUCTOR CABLES


Large inventory of both shielded and non-shielded types from 2 to 120 conductor and from 10 to 24 Gauge. Jacket types available for specific applications including PVC, Polyethylene, and neoprene. Complete Columbia line.



Exclusive

AVAILABLE IN
250-500-1000
FT. ROLLS
OR BY
THE FOOT

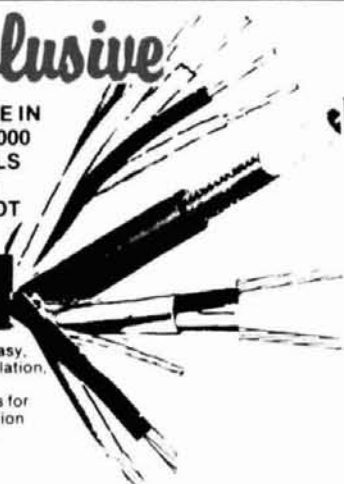Designed for easy, one-step installation, providing the required cables for most earth station equipment... all in a direct burial jacket.



SATELLITE CONTROL CABLE

IMPROVED!

NEW!!! Lowest Loss

ACTUATOR CABLES

ST-1 2 @ 16 gauge + 2 @ 22 gauge with foilshield and drain wire **24¢/FT**

ST-2 2 @ 12 gauge + 3 @ 22 gauge with foilshield and drain wire **36¢/FT**

Direct Burial Black Polyethylene Jacket

TYPE 4

1 - RG6/U 18-Gauge, 96% Copper Shield
2 @ 12-Gauge
3 @ 18-Gauge
3 @ 20-Gauge Shielded plus Tinned Copper Drain Wire
3 @ 22-Gauge Shielded plus Tinned Copper Drain Wire

**79¢
FT**

TYPE 5

2 - RG6/U 18 Gauge, 96% Copper Shield
2 @ 12 Gauge
3 @ 18 Gauge Shielded plus Tinned Copper Drain Wire
3 @ 22-Gauge Shielded plus Tinned Copper Drain Wire

**89¢
FT**

Call for 1000 FT pricing

COAXIAL CABLE SPECIALS

RG8/U mil spec 96% copper shield polyethylene	\$29/100'
RG8/U (EQ Belden 8214) 96% copper shield foam	\$31/100'
RG58/U mil spec 96% copper shield polyethylene	\$10/100'
RG62A/U mil spec 96% copper shield 93 ohm	\$14/100'
RG213/U mil spec 96% copper shield noncontam	\$36/100'
RG214/U tinned copper-double shield	\$65/100'

NEMAL ELECTRONICS INTL., INC.

12240 N.E. 14th Ave., No. Miami, FL 33161

Telephone: (305) 893-3924

TELEX 532362

• COMPLETE MULTICONDUCTOR LINE
• PRICING AVAILABLE FOR ALL QUANTITIES

*Also available Complete line of top quality connectors and SMATV equipment
FRANCHISED DISTRIBUTOR — KINGS CONNECTORS
Authorized Distributor: Amphenol, Blonder-Tongue, Cable Wave Systems, Tyton, B&K
*Call or write for complete pricing

• WE'LL BE GLAD TO CUT ANY OF OUR CABLES TO MEET YOUR EXACT LENGTH REQUIREMENTS



REVIEWS

Butternut HF-2V vertical antenna

About seven years ago, Butternut burst on the scene with one of the first "new" antenna ideas for the Amateur market. Their HF-5V was a five-band, no-trap antenna that covered 80-10 meters. I was one of the first to get one for review and was very much impressed with its performance. In head-to-head competition with comparable antennas, the Butternut always was at least one S-unit stronger during on-the-air tests. Owners of Butternut's current model, the HF-6V, have told me that it does equally well.

Recognizing that the six-band HF-6V was a little short for 80 and 40 meters and the fact that the high bands are going to be at best marginal for the next few years, Butternut modified their basic antenna design to optimize performance on 80 and 40 meters. The net result is the HF-2V antenna. The HF-2V incorporates all of the design features of the HF-6V — stainless steel hardware, T-6061 aluminium tubing, for strength and a double-walled base section for even more structural integrity and no traps.

the antenna

As with any antenna project, the first task was to read the instruction manual from cover to cover and take a full inventory of all the parts and hardware. All you need to assemble the antenna is a blade screwdriver, pliers, and a knife. A set of nut drivers would also be handy.

Assembly is straightforward and should only take an hour or so to accomplish. Identification of parts and hardware is easy if you use the schematic diagram that comes with the unit. The antenna is constructed of telescoping aluminum with sections held together with stainless nuts and bolts.

The antenna is loaded four feet from the base with an L/C combination made of very heavy duty aluminum wire and high voltage transmitting mica caps. Since the antenna is almost a full quarter wave on 40, very little of the 40-meter coil is used to tune the antenna. Should there be too much inductance for 40, a shorting strap is provided. The antenna is impedance matched at the base with an adjustable coil.

about radials

A lot of fuss is made about radials for vertical antennas and rightfully so. Many of those who install verticals constantly complain that the performance is less than was expected. In a major-

ity of the cases, the prime reason is that there were either no radials or an insignificant number of radials under the antenna. In Butternut's opinion, it's best to assume that the earth you're working over is poor and that you'll need to engineer an artificial ground of your own. Radials can be either buried or laid atop the ground, whichever is easier. In general, it's better to install more short radials above ground than to lay just a few long ones. 16 50-foot radials will work rather well in most installations. The ideal radial system would include 120 resonant radials, 1/4 wave on each band. Needless to say, that is beyond the capabilities of most of us.

checkout and adjustment

Tune-up is simply a matter of adjusting the two loading coils for minimum SWR and adjusting the base impedance matching coil to correctly match the coax. As mentioned before, because the antenna is almost a full 1/4 wave on 40, very little inductance is needed to tune the antenna. To set up and tune it, you need to first short out a full seven turns of the 40 meter coil.

Now it's simply a matter of tuning the antenna for the lowest SWR on first 80 and then 40 meters. The next procedure is to attach the base step-up transformer and match the feedline to the antenna. This is a little trickier than it sounds, and took me more than a few minutes to accomplish. In order to get a proper match, you either expand or compress the coil to increase or decrease the inductance needed to get a proper match. I found that no matter how much I changed the coil, I couldn't get a proper match. Sometimes drastic measures are necessary; I used one here, reasoning that no matter how much I expanded the coil, I still had too much inductance to match the antenna. So I cut the coil in half, reattached it, and again applied power. The result was that the antenna was nearly matched and required only one minor change to complete tune up.

optional accessories and top loading

Butternut offers a number of accessories you can use to tailor the HF-2V to your own personal needs. As most low band operators will know, top loading antennas is a very practical way to make short antennas perform better. The top loading kit gives you four 25-foot stranded "umbrella" wires and insulators. The "umbrella" is designed to improve the overall antenna performance on 80 meters (and 160 with optional TBR-160 160-meter base loading kit). It will also improve the bandwidth of the antenna to over 100 kHz on 80 and approximately 35 kHz on 160 meters. Butternut also has a 30 and 20-meter resonator kit that can be added to the antenna. Unfortunately, you can only add one or the other, but not both.

operation

I've had this antenna up now for several months and have used it on both 80 and 75 as

RF TRANSISTORS

FRESH STOCK - NOT SURPLUS
TESTED — FULLY GUARANTEED

P/N	Rating	Each	Match Pr.
MRF406	20W	\$14.50	\$32.00
MRF412/A	80W	18.00	45.00
MRF421	100W	25.00	56.00
MRF421C	110W	—	60.00
MRF422*	150W	38.00	82.00
MRF426/A*	25W	18.00	42.00
MRF428**	150W	55.00	125.00
MRF433	12.5W	12.00	30.00
MRF435*	150W	42.00	90.00
MRF448/A	30W	12.50	30.00
MRF450/A	50W	14.00	31.00
MRF453/A	60W	15.00	35.00
MRF454/A	80W	16.00	36.00
MRF455/A	60W	12.00	28.00
MRF458	80W	20.00	46.00
MRF460	60W	18.00	42.00
MRF464*	80W	25.00	60.00
MRF466*	40W	18.75	48.00
MRF475	12W	3.00	9.00
MRF476	3W	2.75	8.00
MRF477	40W	11.00	25.00
MRF479	15W	10.00	23.00
MRF485*	15W	6.00	15.00
MRF492	90W	18.00	40.00
SRF2072	75W	15.00	33.00
SRF3662	110W	28.00	60.00
SRF3775	75W	15.50	34.00
SRF3795	85W	18.50	37.00
CD2545	50W	23.00	52.00
SD1076	70W	17.00	40.00
SD1451	50W	15.00	36.00

Selected High Gain Matched Quads Available

VHF/UHF TRANSISTORS

Rating	MHz	Net Ea.	Match Pr.
MRF212	10W	136-174	\$16.00 —
MRF221	15W	136-174	10.00 —
MRF222	25W	136-174	14.00 —
MRF224	40W	136-174	13.50 32.00
MRF231	3.5W	66-88	10.00 —
MRF234	25W	66-88	15.00 39.00
MRF237	4W	136-174	3.00 —
MRF238	30W	136-174	12.00 —
MRF239	30W	136-174	15.00 —
MRF240	40W	136-174	18.00 —
MRF245	80W	136-174	28.00 65.00
MRF247	75W	136-174	27.00 63.00
MRF250	50W	27-174	20.00 46.00
MRF260	5W	136-174	7.00 —
MRF261	10W	136-174	9.00 —
MRF262	15W	136-174	9.00 —
MRF264	30W	136-174	13.00 —
MRF607	1.75W	136-174	3.00 —
MRF641	15W	407-512	22.00 —
MRF644	25W	407-512	24.00 54.00
MRF646	40W	407-512	26.50 59.00
MRF648	60W	407-512	33.00 69.00
2N3866*	1W	30-200	1.25 —
2N4427	1W	136-174	1.25 —
2N5591	25W	136-174	13.50 34.00
2N5642*	20W	30-200	13.75 34.50
2N5945	4W	407-512	10.00 —
2N5948	10W	407-512	12.00 —
2N6080	4W	136-174	6.25 —
2N6081	15W	136-174	7.50 —
2N6082	25W	136-174	8.90 —
2N6083	30W	136-174	9.30 24.00
2N6084	40W	136-174	11.75 28.50

TMOS FET

MRF134*	5W	2-200	\$10.50 —
MRF137*	30W	2-200	22.50 —
MRF138**	30W	1.5-150	35.00 —
MRF150**	150W	1.5-150	80.00 —
MRF172*	80	2-200	65.00 —

Selected, matched finals for Kenwood, Yaesu, Icom, Atlas, etc. Technical assistance and cross-reference information on CD, PT, RF, SRF, SD P/Ns.

QUANTITY DISCOUNTS AVAILABLE
WE SHIP SAME DAY C.O.D./VISA/MC
INFORMATION AND CALIF. ORDERS: (619) 744-0728
OUTSIDE CALIF. ORDER DESK: 800-854-1927



RF PARTS

1320-16 Grand Ave., San Marcos
California 92069 (619) 744-0728

MISSOURI RADIO CENTER

ANTENNA SALE

HYGAIN TOWERS

HG37SS	C
HG52SS	A
HG54HD	L
HG70HD	L

CUSHCRAFT

A3	205 00
A4	275 00
R3	255 00
40-CD2	275 00
AV5	96 00
32-19	89 00
215WB	75 00
ARX2B	35 00
A144-11	46 00
A144-20T	69 00
424B	75 00
AOP-1	137 00

KLM

KT34A	329 00
KT34XA	475 00
432-20LBX	64 00
432-30LBX	90 00
435-18C	109 00
435-40C	149 00
2M-13LBA	77 00
2M-14C	85 00
2M-16LBX	89 00
2M-22C	115 00

HYGAIN

TH3JR	C
TH7	A
EX 14	L
14AVQ	L
18AVT	L
V2	
V3	
V4	

HUSTLER

25% OFF ALL MOBILE	
6BTV	125 00

AEA

144SR	42 00
-------------	-------

BUTTERNUT

HF6V	110 00
HF2V	110 00
RG213U	\$ 26/foot

ROTATORS

CD45	139 00
HAM IV	228 00
T2X	275 00

AVANTI 2M	29 95
HI-Q BALUN	9 95

KENPRO

KR400	119 00
KR500	149 00
KR600	199 00
KR5400	249 00

102 NW BUSINESS PARK LANE
KANSAS CITY, MISSOURI 64150
816-741-8118

CALL TOLL FREE
1-800-821-7323

MASTERCARD VISA & C.O.D. WELCOME

well as on 40 meters and have been quite impressed with its performance. On 80 the antenna has performed as well as my 1/4-wave sloper, and actually outperformed it in certain directions and conditions. When Ron Wright was on Tonga, A35EA, I was able to work him through a fair-sized pileup without too much difficulty. Not being a fan of 40 meters, my operating experience there is admittedly spotty. But this antenna has performed very well and I've been able to work just about everyone I called.

The Butternut HF-2V is the perfect antenna for those who want good low band performance without investing a lot of time and money installing a larger antenna. Its performance is comparable with a number of other antennas, and HF-2V owners will get years of excellent results with this antenna.

It's interesting to note that the recent DX'pedition by the Texas DX Society took a Butternut HF-2V to the island of Desescheo. Used with the optional TBR-160, it accounted for thousands of contacts on 80 and 160. The expedition members have reported that the antenna was a breeze to set up and performed flawlessly. I remember that during that operation, night after night, they came pounding through with perfectly Q-5 signals on 160.

specifications

weight	131 pounds/5.9kg
height	32 feet/9.75 meters
feedpoint impedance	50 ohms
VSWR at resonance	1.5/1 over a suitable ground
VSWR < 2/1	65 kHz on 80, full band on 40
power rating	2 kW PEP/1 kW CW (less with TBR-160)
wind no ice	80 MPH/125 kph when properly guyed

— de N1ACH

MFJ-204 antenna bridge

The MFJ-204 Antenna Bridge is designed to do three basic tasks: measure antenna impedance, measure resonant frequency, and to tune antenna tuners "off the air." It's a handy piece of test equipment that every ham should have. There are several reasons that an antenna bridge is a much more versatile tool than its cousin the noise bridge. The noise bridge is basically a wide-band oscillator that can be used to roughly determine resonant frequency or impedance of an antenna. I say "roughly" because the wideband oscillator is difficult to use, is imprecise and can sometimes give misleading results. The antenna bridge, on the other hand, has a tunable oscillator that can be set to the precise frequency you want to work on. The MFJ 204 covers 1.6-2.5, 3-4, 7-11, and 13-30 MHz so you get full coverage of all HF Amateur Radio bands.

To measure antenna impedance, the first thing you do is set the oscillator to the frequency you want to work on. This is done by loosely coup-

ling the antenna bridge to your receiver and listening for the beat note. You then connect the antenna bridge to the antenna to be measured and adjust the resistance control for a dip on the antenna bridge's meter. Once you get this dip, you flip the bridge over and read the resistance from the factory-calibrated chart on the back of the unit. On my 160 vertical antenna, I measured an impedance of 35 ohms, just about where it should be.

Using the antenna bridge to both measure resonant frequency and tune an antenna tuner is pretty much the same process. When used with an antenna tuner, the antenna bridge eliminates one of the most annoying aspects of the hobby — the ubiquitous and infamous "tuner-upper."

The MFJ 204 measures 2-1/2 x 2 x 7 inches and weighs just about a pound. It will run off a 9-volt battery or an optional 110-volt AC power supply. It's covered by the standard MFJ 12-month warranty and should give many years of good, reliable service.

I've since used the antenna bridge on several antenna projects and have enjoyed its utility. As long as I can keep the review unit, I think I'll let the noise bridge gather dust.

N1ACH



computer interface

The Computer Patch Model CP-100 Interface is a complete terminal unit for Morse, Baudot, ASCII, and AMTOR. It will interface a computer running communications software via TTL levels (RS-232 optional) to your radio. With the optional current loop provisions, the CP-100 can be used with a mechanical teleprinter also. The tuning indicator is a ten-segment bargraph featuring discriminator-type operation which graphically shows selective-fading and is ideal for AMTOR use (tuning 'scope outputs are also




available). The CP-100 also features a front panel squelch control which inhibits data to the computer when no signal is present (thus preventing print when receiving noise). Front panel selec-

RAMSEY

THE FIRST NAME IN ELECTRONIC TEST GEAR


PRICE CUT

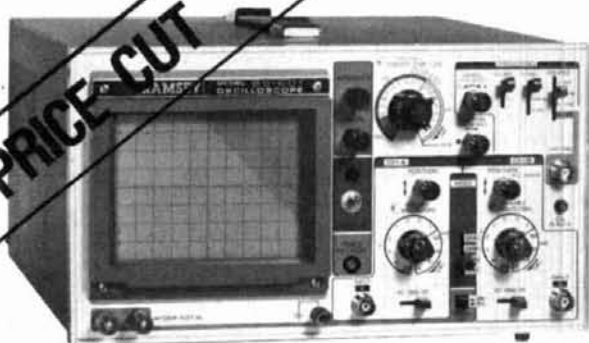

20 MHz DUAL TRACE OSCILLOSCOPE

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a component testing circuit for resistor, capacitor, digital circuit and diode testing • TV video sync filter • wide bandwidth & high sensitivity • internal graticule • front panel trace rotator • Z axis • high sensitivity x-y mode • regulated power supply • built-in calibrator • rock solid triggering. *USA — add \$10.00 per unit for postage, overseas orders add 15% of total order for insured surface mail

~~\$399.95*~~
\$369.95*

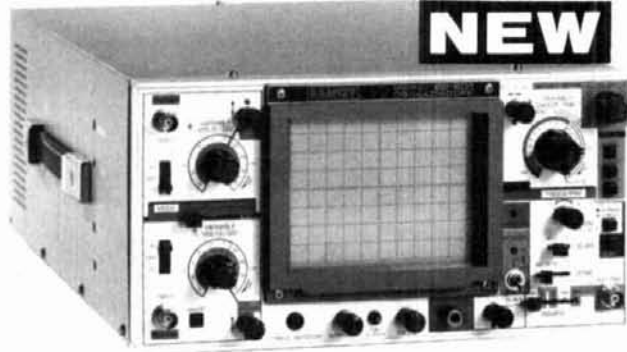

NEW

45 MHz DUAL SWEEP OSCILLOSCOPE

The Ramsey 825 is a dual time base, delayed sweep unit that includes a built-in signal delay line to permit clear viewing during very short rise times of high frequency waveforms. Other features include: variable trigger holdoff • 20 calibrated sweep time ranges from 0.5 μ s/div. to 0.2 μ s/div. • fully adjustable sweep time • X5 sweep magnification • five trigger sources, CH1, CH2, LINE, EXTERNAL and INTERNAL (V model) • front panel x-y operation, Z axis input • sum difference of CH1 and CH2 waveforms displayed as single trace • sweep gate and sweep output • auto focus • single sweep. *USA — add \$10.00 per unit for postage, overseas orders add 15% of total order for insured surface mail

~~\$799.95*~~
\$669.95*



RAMSEY D-1100 VOM MULTITESTER

Compact and reliable, designed to service a wide variety of equipment. Features include • mirror back scale • double-jeweled precision moving coil • double overload protection • an ideal low cost unit for the beginner or as a spare back-up unit.


\$19.95 test leads and battery included
12.95



NEW RAMSEY 1200 VOM MULTITESTER

Check transistors, diodes and LEDs with this professional quality meter. Other features include: decibel scale • 20K volt metering system • 3 1/2" mirrored scale • polarity switch • 20 measuring ranges • safety probes • high impact plastic case.

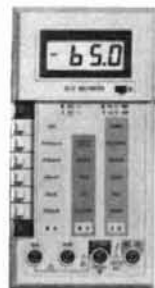\$24.95 test leads and battery included
19.95



RAMSEY D-3100 DIGITAL MULTIMETER

Reliable, accurate digital measurements at an amazingly low cost • in-line color coded push buttons, speeds range selection • abs plastic tilt stand • recessed input jacks • overload protection on all ranges • 3 1/2 digit LCD display with auto zero, auto polarity & low BAT. indicator

\$49.95 test leads and battery included



CT-70 7 DIGIT 525 MHz COUNTER

Lab quality at a breakthrough price. Features • 3 frequency ranges each with pre amp • dual selectable gate times • gate activity indicator • 50mV @ 150 MHz typical sensitivity • wide frequency range • 1 ppm accuracy

\$119.95 wired includes AC adapter

CT-70 kit \$99.95
BP-4 nicad pack 8.95



CT-90 9 DIGIT 600 MHz COUNTER

The most versatile for less than \$300. Features 3 selectable gate times • 9 digits • gate indicator • display hold • 25mV @ 150 MHz typical sensitivity • 10 MHz timebase for WWV calibration • 1 ppm accuracy

\$149.95 wired includes AC adapter

CT-90 kit \$129.95
OV-1 0.1 PPM oven timebase 59.95
BP-4 nicad pack 8.95



CT-125 9 DIGIT 1.2 GHz COUNTER

A 9 digit counter that will outperform units costing hundreds more • gate indicator • 24mV @ 150 MHz typical sensitivity • 9 digit display • 1 ppm accuracy • display hold • dual inputs with preamps

\$169.95 wired includes AC adapter

BP-4 nicad pack 8.95



CT-50 8 DIGIT 600 MHz COUNTER

A versatile lab bench counter with optional receive frequency adapter, which turns the CT-50 into a digital readout for most any receiver • 25 mV @ 150 MHz typical sensitivity • 8 digit display • 1 ppm accuracy

\$169.95 wired

CT-50 kit \$139.95
RA-1 receiver adapter kit 14.95



DM-700 DIGITAL MULTIMETER

Professional quality at a hobbyist price. Features include 26 different ranges and 5 functions • 3 1/2 digit, 1/2 inch LED display • automatic decimal placement • automatic polarity

\$119.95 wired includes AC adapter

DM-700 kit \$99.95
MP-1 probe set 4.95



PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies UP in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01 Hz resolution & built-in signal preamp/conditioner

\$49.95 wired

PS-2 kit \$39.95



PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for shifting RF • ideal receiver/TV preamp

\$44.95 wired includes AC adapter

PR-2 kit \$34.95



PS-1B 600 MHz PRESCALER

Extends the range of your present counter to 600 MHz • 2 stage preamp • divide by 10 circuitry • sensitivity 25mV @ 150 MHz • BNC connectors • drives any counter

\$59.95 wired includes AC adapter

PS-1B kit \$49.95

ACCESSORIES FOR RAMSEY COUNTERS

- Telescopic whip antenna—BNC plug .. \$ 8.95
- High impedance probe, light loading .. 16.95
- Low pass probe, audio use .. 16.95
- Direct probe, general purpose use .. 13.95
- Tilt ball, for CT-70, 90, 125 .. 3.95



PHONE ORDERS CALL
716-586-3950

TELEX 466735 RAMSEY CI

TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for refund • add 6% for shipping and insurance to a maximum of \$10.00 • overseas add 15% for surface mail • COD add \$2.50 (COD in USA only) • orders under \$15.00 add \$1.50 • NY residents add 7% sales tax • 90 day parts warranty on all kits • 1 year parts & labor warranty on all wired units.



RAMSEY ELECTRONICS, INC.
2575 Baird Rd.
Penfield, N.Y. 14626

WE SHIP WORLDWIDE

Barry Electronics Corp.

WORLD WIDE AMATEUR RADIO SINCE 1950
Your one source for all Radio Equipment!

For the best buys in town call:
212-925-7000
Los Precios Mas Bajos en
Nueva York

KITTY SAYS: WE ARE NOW OPEN 7 DAYS A WEEK.
Saturday & Sunday 10 to 5 P.M.
Monday-Friday 9 to 6:30 P.M. Thurs. to 8 P.M.
Come to Barry's for the best buys in town.


ONV Safety
belts-in stock



IC—R71A, 751, 745, 27A/H, 37A, 47A, R-7000,
127A, 271A/H, 3200A, 471A/H, 735



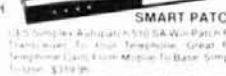FT-ONE, FT-980, FT-757GX, FRG-8800
FT-726R, FRG-9600, FT-270RH, FT-2700RH
YAESU ICOM Land Mobile Hi/T
FT-12/703R IC2AT Midland Standard
FT-2709RH IC20AT Wilson Maxon
FTC-1903 IC-04AT Yaesu FTC 2203, FT 4703
Icom IC M12 Marine M700
Tempo M-1



CELLULAR PHONES STOCKED

WELZ
FLUKE 77 Multimeter



Nye MBV-A 3 Kilowatt Tuner



SANTEC ST-222/UP
ST-20T
ST-442/UP
HT-7



MURCH Model 2000 A, A.L.S. B in stock



HEIL EQUIPMENT IN STOCK



New TEN TEC 2591HT, Corsair II, Argosy II, Century 22



AMERITRON AMPLIFIER AUTHORIZED DEALER

Yaesu FTR-2410, Wilson
ICOM IC-RP 3010 (440 MHz)
ICOM IC-RP 1210 (1.2 GHz)



ALPHA AMPLIFIERS


Complete Butternut Antenna Inventory in Stock!

DIGITAL FREQUENCY COUNTERS
Morse University
Morse 101000 0-10GHz 1209MHz
0-600 MHz 0-1.3GHz 1209MHz

Long range Wireless Telephone for export in stock

BENCHER PADDLES, BALUNS, AUDIO FILTERS, IN STOCK

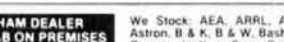MIRAGE AMPLIFIERS
ASTRON POWER SUPPLIES
Ailco/Falcon Amps



Commercial Equipment Stocked ICOM, MAXON, Midland, Standard, Wilson, Yaesu. We serve municipalities, businesses, Civil Defense, etc. Portables, mobiles, base, repeaters.

Local Ham Club Speeches Given

WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS

COMMERCIAL RADIOS stocked & serviced on premises.

Amateur Radio Courses Given On Our Premises, Call

Export Orders Shipped Immediately. TELEX 12-7670

Gobble Up Our Thanksgiving Savings
See You at SCARA, CT—Nov. 10th

ICOM Day at Barry's—November 23rd

KENWOOD



R-600, R-1000, R-2000, TS-940S/AT
TS-430S, TR-3600A, TR-7950,
TW-4000A, Kenwood Service/Repair
TH2131/41AT, TM-211A/
411A & TS-711A/811A.

COMPU-FIRE EXTINGUISHERS
EXL-5000E RTTY/AMTOR TERMINAL

VoCom/Mirage/Daiwa
Tokyo Hy-Power
Amplifiers &
5/8 HT Gain
Antennas IN STOCK

Large inventory of
Saxton Wire & Cable

Soldering Station,
48 Watts, \$68

Computer Interfaces
stocked: MFJ-1224
AEA CP-1, PKT-1, DR-DX
CP-100, PK-64, Dr. QSO,
Morse University

MICROLOG AIR I, Air Disk,
SWL, Morse Coach

KANTRONICS
UTU, Interface II,
Challenger, Packet Comm

EIMAC
3-500Z
572B, 6JS6C
12BY7A &
4-400A

BIRD
Wattmeters &
Elements
In Stock

AEA 144 MHz
AEA 220 MHz
AEA 440 MHz
ANTENNAS

MAIL ALL ORDERS TO BARRY ELECTRONICS CORP., 512 BROADWAY, NEW YORK CITY, NY 10012.

New York City's LARGEST STOCKING HAM DEALER
COMPLETE REPAIR LAB ON PREMISES

"Aquí Se Habla Español!"

BARRY INTERNATIONAL TELEX 12-7670
MERCHANDISE TAKEN ON CONSIGNMENT
FOR TOP PRICES

Monday-Friday 9 A.M. to 6:30 P.M. Thursday to 8 P.M.
Saturday & Sunday 10 A.M. to 5 P.M. (Free Parking)

AUTHORIZED DIST. MCKAY DYMEK FOR
SHORTWAVE ANTENNAS & RECEIVERS

Subways: BMT—Prince St. Station
IND—F—Train Bwy. Station

Bus: Broadway #6 to Spring St.
Path—9th St. 4th Ave. Station

We Stock: AEA, ARRL, Alpha, Ameco, Antenna Specialists, Astac, Astron, B & K, B & W, Bash, Bencher, Bird, Butternut, CDE, CES, Collins, Communications Spec. Connectors, Covercraft, Cushcraft, Daiwa, Dentron, Digimax, Drake, ETO (Alpha), Eimac, Encomm, Heil-Sound, Henry Hustler (Newtronics), Hy-Gain, Icom, KLM, Kantronics, Larsen, MCM (Daiwa), MFJ, J.W. Miller, Mini Products, Mirage, Newtronics, Nye Viking, Palomar, RF Products, Radio Amateur Callbook, Robot, Rockwell Collins, Saxton, Shure, Telex, Tempo, Ten-Tec, Tokyo Hi Power, Trionyx TUBES, W2AU, Waber, Wilson, Yaesu Ham and Commercial Radios, Vocom, Vibroplex, Curtis, Tri-Ex, Wacom Duplexers, Repeater, Phelips Dodge, Fanon Intercoms, Scanners, Crystals, & Radio Publications.

WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS

DEALER INQUIRIES INVITED. PHONE IN YOUR ORDER & BE REIMBURSED

COMMERCIAL RADIOS stocked & serviced on premises.
Amateur Radio Courses Given On Our Premises, Call
Export Orders Shipped Immediately. TELEX 12-7670

tion of 110 and below or 300 baud operation is provided along with an internal monitor speaker. The CP-100 is housed in an attractive metal case, minimizing any potential RF interference efforts.

For further information, contact Advanced Electronic Applications Inc., P. O. Box 2160, Lynnwood, Washington 98036.

Circle #302 on Reader Service Card.

new division

Nemal Electronics International has opened a new value-added division specializing in cable assemblies for the aerospace, data processing, and commercial markets.


With state-of-the-art production and test equipment, the new Nemal facility is capable of producing more than 1000 assemblies daily. Nemal also maintains an extensive inventory of component parts and cables allowing for next-day delivery on a wide variety of RF and data cables, made and tested to exact customer requirements.

For additional information, contact Nemal Electronics International Inc., 12240 N.E. 14th Avenue, North Miami, Florida 33161.

Circle #303 on Reader Service Card.

smart patch plus™

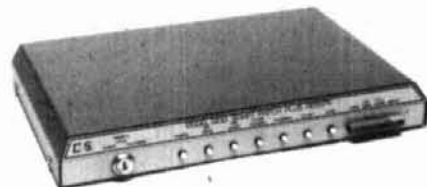The new Smart Patch Model 5100 from C.E.S. combines the features of the original Smart Patch with an exciting new communications tool called "automatic remote."



Installed in the home or office, model 5100 allows mobile or handheld radios the ability to make or receive telephone calls, as well as allow the operation of the base station in telephone fashion through the use of in-house telephones. The base station radio can be selectively called by mobiles using touchtone encoders.

Special emergency features provide safety to those who face crisis while mobile. These features include EMERGENCY 911 AUTODIAL, as well as an included beeper box installed in the home or office that responds loudly to a user programmed code. A keylock on the front panel protects the user from unauthorized use.

Autopatch features include USER PROGRAMMABLE access codes, sophisticated toll restrict, and simplex operation, allowing the unit to work from base directly; no repeater is required. Only five connections to base station radio are required.

For further information, contact CES, Inc., P.O. Box 2930, Winter Park, Florida 32790.

Circle #304 on Reader Service Card.

Iron Powder and Ferrite TOROIDAL CORES

Shielding Beads, Shielded Coil Forms
Ferrite Rods, Pot Cores, Baluns, Etc.

Small Orders Welcome
Free 'Tech-Data' Flyer

AMIDON
Associates


Since 1963

12033 Otsego Street, North Hollywood, Calif. 91607

In Germany: Elektronladen, Wilhelm — Melies Str. 88, 4930 Koldau 18, West Germany
In Japan: Toyomura Electronics Company, Ltd., 7-9, 2-Chome Sota-Kanda, Chiyoda-Ku, Tokyo, Japan



Introducing...

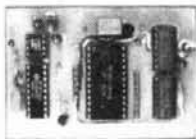

VAX
ON CALL
It's on duty when
you're not.

OC-1 ONLY \$59.95 Complete with
Shipping/Handling USA

ON CALL is a complete selective call system so you don't have to monitor the frequency, or it can be used as a decoder for controlling equipment at the repeater site and at home.

- Compare these features:
- 4 digit 16 tone sequential decoder programmable. 43,680 different codes. DTMF* Format with Auto reset
 - 1 AMP SPST relay output, momentary or latched for external paging device, such as Auto horn, tape recorder, speaker Audio etc.
 - Flashing LED call indicator (Energizes when your code has been accessed)
 - easy connection to any radio
 - 12-16 volt DC operation
 - size 3 1/2 x 2 1/2 x 5 in
 - can be used for clubs or emergency groups for help situations

To Order Send
Check or Money
Order To

CURRENT DEVELOPMENT CORPORATION

E. Carter Rd.
PO Box 384
Westmoreland, NY
13490
or Phone:
315-733-3719

✓ 122



EXMET your source for **Discounted Prime** 6061-T6/6061-T6511 aluminum Tubing and Rod that is stronger than steel and 1/3 the weight.

O.D. and wall	TUBING Length	Price per Length
1/2" x .058	12 ft	\$ 12.50
7/8" x .058	12 ft	19.50
1" x .058	12 ft	21.75
1-1/4" x .058	12 ft	27.35
1-1/2" x .049	12 ft	28.80
1-1/2" x .058	12 ft	33.00
1-1/2" x .065	12 ft	38.40
1-1/2" x .083	12 ft	48.00
1-1/2" x .125	24 ft	86.40
1-1/2" x .250	24 ft	105.15
2" x .058	12 ft	42.25
2" x .065	12 ft	45.50
2" x .125	24 ft	110.40
2" x .250	24 ft	187.20
3" x .065	12 ft	81.50

O.D.	ROD Length	Price per Length
1/8"	12 ft	\$ 2.00
3/16"	12 ft	4.50

Volume discounts on orders over \$500.00. Other sizes of tubing and rod quoted upon request. Minimum order \$50.00 tubing, \$50.00 rod.

Policies: All prices FOB Twinsburg, Ohio. Payment is COD, or save COD charges by enclosing a check or money order with your order. Ohio residents add 5-1/2% sales tax.

Exmet, Inc.

2170 E. Aurora Rd., P.O. Box 117, Twinsburg, Ohio 44087
216-425-8455

✓ 193



EVERY COMMODORE HAM NEEDS A COMPANION!

From **JIM GRUBBS, K9EI**

the author of **Command Post, Micro-Wave Radio and Gateway to the World**, QSKY Publishing announces **THE COMMODORE HAM'S COMPANION**.

INCLUDES:

- Over 80 sources for Commodore amateur radio software and hardware
- A bibliography of over 60 magazine articles and reviews about using Commodore machines in the ham shack
- How to use your Commodore computer to join the packet radio revolution
- Where to find specialized programs for such things as slow scan television, satellite tracking and more
- How to realize a dramatic increase in speed without learning machine language programming
- Why the Commodore machines are the easiest to interface

14 chapters / 160-page paperback


Price: \$15.95 + \$2.50 First Class shipping and handling. Mastercard and Visa accepted.



P.O. Box 3042 • Springfield, IL 62708

✓ 194

FALCON COMMUNICATIONS

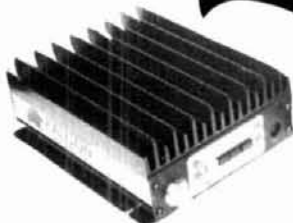

Falcon Communications, Well Known For MOSFET Repeater Power Amplifiers, Also Makes A Hard Working Line Of Bipolar Power Amplifiers For Mobile/Base Use. Our 2 Meter Amplifiers Include:

Model 5121	2 Watts in = 150 out 1 Watt in = 90 out	List \$285
Model 5122	10 Watts in = 150 out 2 Watts in = 50 out	List \$275
Model 5123	30 Watts in = 150 out 10 Watts in = 90 out	List \$235

A FEW FEATURES:

- 1) Made in the USA
- 2) All mode (FM, SSB, CW)
- 3) Optional plug-in receive preamp
- 4) Automatic COR or remote keying
- 5) Built in thermal protection
- 6) Full 1 Year warranty

For Information On Our Complete Line See Your Local Dealer Or Call Factory Direct

CIRCLE 155 ON READER SERVICE CARD

P.O. Box 8979 • Newport Beach, CA 92658
(714) 760-3622

Gunnplexers & accessories 10 & 24 GHz



A. Microwave Associates 10 GHz Gunnplexer. Two of these transceivers can form the heart of a 10 GHz communication system for voice, mcw, video or data transmission, not to mention mountaintop DXing! MA87141-1 (pair of 10 mW transceivers) \$251.95. Higher power units (up to 200 mW) available. **B.** Microwave Associates 24 GHz Gunnplexer. Similar characteristics to 10 GHz unit. MA87820-4 (pair of 20 mW transceivers) \$739.20. **C.** This support module is designed for use with the MA87141 and MA87820 and provides all of the circuitry for a full duplex audio transceiver system. The board contains a low-noise, 30-MHz fm receiver, modulators for voice and mcw operation, Gunn diode regulator and varactor supply. Meter outputs are provided for monitoring received signal levels, discriminator output and varactor tuning voltage. RXMR30VD assembled and tested \$119.95. **D.** Complete, ready to use communication system for voice or mcw operation. Ideal for repeater linking. A power supply capable of delivering 13 volts dc at 250 mA (for a 10 mW version), microphone, and headphone and/or loudspeaker are the only additional items needed for operation. The Gunnplexer can be removed for remote mounting to a tower or 2 or 4 foot parabolic antenna. TR10GA (10 GHz, 10 mW) \$399.95. Higher power units available. TR24GA (24 GHz, 20 mW) \$639.95. Also available: horn, 2 and 4 foot parabolic antennas, Gunn, varactor and detector diodes, search and lock systems, oscillator modules, waveguide, flanges, etc. Call or write for additional information. Let ARR take you higher with quality 10 and 24 GHz equipment!

Advanced Receiver Research

Box 1242 • Burlington CT 06013 • 203 582-9409



✓ 195

November 1985 133

Uncle Ben says...

**"I give you
much more than
just the lowest price..."**

When you get that exciting new piece of equipment *from me*, you know you are going to be completely happy... I see to it, personally! I also give you earliest delivery, greatest trade-in allowances, my friendly assistance in every possible way.

Just ask any of the many thousands of hams all over the world who have been enjoying my friendly good service for over a half a century.

73, Uncle Ben, W2SOH



"Uncle Ben" Snyder, W2SOH
the head man of

HARRISON
"HAM HEADQUARTERS,
USA®" ...Since 1925!

• **CALL ME...**

(516) 293-7995

• **WRITE ME...**

For my prompt,
personal reply.

• **SEE ME...**

At one of the world's largest
Ham Supply Centers!

HARRISON
HAS THEM ALL!
KENWOOD



Kenwood TH21AT, 31AT, 41AT



Kenwood TR-7950/7930



Kenwood TS-940S




Kenwood TS-430S



Kenwood TR-2600, TR-3600



Kenwood TS-711A (2m)
TS-811A (70 cm)

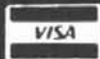

HARRISON RADIO

...Since 1925!

"HAM HEADQUARTERS, USA"
2263 Route 110 (at Smith St.)
E. Farmingdale, NY 11735
1-(516) 293-7995

CHARGE IT!

HAM MART

Ham Radio's guide to help you find your local

California

C & A ROBERTS, INC.
18511 HAWTHORN BLVD.
TORRANCE, CA 90504
213-370-7451
24 Hour: 800-421-2258
Not The Biggest, But The Best —
Since 1962.

FONTANA ELECTRONICS
8628 SIERRA AVENUE
FONTANA, CA 92335
714-822-7710
714-822-7725
The Largest Electronics Dealer in San
Bernardino County.

JUN'S ELECTRONICS
3919 SEPULVEDA BLVD.
CULVER CITY, CA 90230
213-390-8003
800-882-1343 Trades
Habla Espanol

Connecticut

HATRY ELECTRONICS
500 LEDYARD ST. (SOUTH)
HARTFORD, CT 06114
203-527-1881
Call today. Friendly one-stop shopping
at prices you can afford.

Delaware

**AMATEUR & ADVANCED
COMMUNICATIONS**
3208 CONCORD PIKE
WILMINGTON, DE 19803
(302) 478-2757
Delaware's Friendliest Ham Store.

DELAWARE AMATEUR SUPPLY
71 MEADOW ROAD
NEW CASTLE, DE 19720
302-328-7728
800-441-7008
Icom, Ten-Tec, Microlog, Yaesu,
Kenwood, Santec, KDK, and more.
One mile off I-95, no sales tax.

Florida

AMATEUR ELECTRONIC SUPPLY
1898 DREW STREET
CLEARWATER, FL 33575
813-461-4267
Clearwater Branch
West Coast's only full service
Amateur Radio Store.
Hours M-F 9-5:30, Sat. 9-3

AMATEUR ELECTRONIC SUPPLY
621 COMMONWEALTH AVE.
ORLANDO, FL 32803
305-894-3238
Fla. Wats: 1 (800) 432-9424
Outside Fla: 1 (800) 327-1917
Hours M-F 9-5:30, Sat. 9-3

Hawaii

HONOLULU ELECTRONICS
819 KEEAUMOKU STREET
HONOLULU, HI 96814
(808) 949-5564
Serving Hawaii & Pacific area for 53
years.

Illinois

ERICKSON COMMUNICATIONS, INC.
5456 N. MILWAUKEE AVE.
CHICAGO, IL 60630
312-631-5181
Hours: 9:30-5:30 Mon, Tu, Wed & Fri;
9:30-8:00 Thurs; 9:00-3:00 Sat.

Indiana

THE HAM STATION
808 NORTH MAIN STREET
EVANSVILLE, IN 47710
812-422-0231
Discount prices on Ten-Tec, Cubic,
Hy-Gain, MFJ, Azden, Kantronics,
Santec and others.

Massachusetts

James Millen Components by
ANTENNAS ETC.
16 HANSOM ROAD
ANDOVER, MA 01810
617-475-7831
Bezels, binding posts, capacitors, con-
densers, chokes, coils, ceramics, H.V.
connectors, plate caps, hardware
knobs, dials, scopes and grid dippers.
Inquire SASE or visit.

TEL-COM, INC.
675 GREAT ROAD, RTE. 119
LITTLETON, MA 01460
617-486-3400
617-486-3040
The Ham Store of New England
You Can Rely On.

Michigan

ENCON PHOTOVOLTAICS
Complete Photovoltaic Systems
27600 Schoolcraft Rd.
Livonia, Michigan 48150
313-523-1850
Amateur Radio, Repeaters, Satellite,
Computer applications.
Call Paul WD8AHO

Nevada

AMATEUR ELECTRONIC SUPPLY
1072 N. RANCHO DRIVE
LAS VEGAS, NV 89106
702-647-3114
Dale Porray "Squeak," AD7K
Outside Nev: 1 (800) 634-6227
Hours M-F 9-5:30, Sat. 9-3

New Jersey

KJI ELECTRONICS
66 SKYTOP ROAD
CEDAR GROVE, NJ 07009
(301) 239-4389
Gene K2KJI
Maryann K2RVH
Distributor of: KLM, Mirage, ICOM,
Larsen, Lunar, Astron. Wholesale -
retail.

NEW YORK

BARRY ELECTRONICS
512 BROADWAY
NEW YORK, NY 10012
212-925-7000
New York City's Largest Full Service
Ham and Commercial Radio Store.

VHF COMMUNICATIONS
915 NORTH MAIN STREET
JAMESTOWN, NY 14701
716-664-6345
Call after 7 PM and save! Supplying all
of your Amateur needs. Featuring ICOM
"The World System." Western New
York's finest Amateur dealer.

Dealers: *YOU SHOULD BE HERE TOO!*
Contact Ham Radio now for complete details.

flea market



RATES Noncommercial ads 10¢ per word; commercial ads 60¢ per word **both payable in advance.** No cash discounts or agency commissions allowed.

HAMFESTS Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing) on a space available basis only. Repeat insertions of hamfest ads pay the non-commercial rate.

COPY No special layout or arrangements available. Material should be typewritten or clearly printed (not all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

DEADLINE 15th of month preceding month.

SEND MATERIAL TO: Flea Market, Ham Radio, Greenville, N. H. 03048.

BACK ISSUES QST, 73, Ham Radio. Stamp for list. Koepke, 6 Katherine Rd., Albany, NY 12005.

DIGITAL AUTOMATIC DISPLAYS. All transceivers. Six 1/2" digits. 5" wide x 1-1/4" x 9" cabinet. Send \$1.00 for information. Be specific. Grand Systems, PO Box 2171, Blaine, Washington 98230.

ANTIQUE RADIOS Schematics, tubes and literature. Send SASE to VRS (HR), 376 Cilley Rd., Manchester, NH 03103 for large list.

PRINTED CIRCUIT BOARDS TORCCC. Electronics will print any schematic, 6" x 9" maximum, on a circuit board for \$1.50 (larger schematics - 0 add \$1.25 per additional 50 square inches). Send check and schematic to: TORCCC Electronics, 2161 North California, Chicago, Illinois 60647.

WANTED: Regency XL2000 Transceiver or newer 10 channel 148-162 MHz or Wilson WH2510, PO Box 929, Blacksburg, VA 24060-0929. (703) 382-4458.

NEW CODE SYSTEM. Curlycode, by W4BUP, lets beginners know code without "study", helps YOU boost your speed! Systems shows how sound patterns make unforgettable shapes in your minds-eye. Eight Curlycode shapes show most letters. Average of two different endings for each shape show all 61 characters. Booklet \$6.50. Complete set: Booklet, wall chart, pocket card, special chart, all for \$11.50. Discount 20 percent for 10 or more complete sets. Minds-eye Publications, Dept. H1, Box 1310, McLean, VA 22101.

THE GOOD SAM HAMS invite RV operators to check in the Good Sam Ham net 14.240 ± Sundays 1900Z also 3.880 ± Tuesdays at 2359Z. Net control N5BDN, Clarksville, IN.

SCHEMATIC: Radio receivers 1920's/60's. Send brand name, model No., SASE. Scaramella, PO Box 1, Woonsocket, RI 02895-0001.

CABLE TV CONVERTERS/DESCRAMBLERS. Jerrold, Hamlin, Zenith - many others. Factory units/lowest dealer prices. Complete illustrated catalog, \$2.00. Pacific Cable Co., Inc., 7325-1/2 Reseda Blvd., Dept. 1006, Reseda, CA 91335. 818/716-5914.

NEW VLF 2 kHz-500 kHz products by K1RGO. L-101B VLF converter, L-201 VLF broadband preamplifier, L-400 VLF active antenna and more. Write for free catalog. LF Engineering Co., 17 Jeffrey Road, East Haven, CT 06512.

ICOM AND KENWOOD SEPARATE NEWSLETTERS: 5 years of back issues! Now available TS930S & 430S users modifications supplement. Send 39¢ SASE for 12 page FREE Brochure to: International Radio, Inc., 1532 SE Village Green Dr., Suite L, Port St. Lucie, FL 33452.

HELP: Need schematic for Knight 2-meter transceiver Model TR-108. Will pay for copy, Ph. (209) 626-4219. KB6JDT, Donald M. Cox, 318 Park Blvd., Orange Cove, CA 93646.

SIGNAL GENERATORS, URM-25D, 10 kHz thru 50 MHz \$245.00. URM-26B, 4 MHz thru 405 MHz \$245.00. HP614A, 900 MHz thru 2100 MHz \$345.00. HP618B, 3.8 GHz thru 7.6 GHz \$375.00. HP608C 10 MHz thru 480 MHz \$345.00. TS-510/U 10 MHz to 420 MHz \$295.00. All lab calibrated. Have good stock so order today. We accept M/C, VISA, or check. FOB Otto. Immediate shipment. Phone Bill Slep 704-524-7519. Slep Electronics Company, Highway 441, Otto, NC 28763.

CABLE TV CONVERTERS & EQUIPMENT: Plans and parts. Build or buy. FREE information. C&D Electronics, 626 Flowerdale, Dept. HR, Ferndale, MI 48220.

TR-7 USERS: NB-7 Noise blander (new) \$65.00 ppd. HS-75 headset (padded) new \$14.00 ppd. SL-300, SL-500 CW filter \$55.00 ea. ppd. K3UKW, Tony Musero (215) 271-8898.

FOR SALE: Kenwood TR-7800 two meter transceiver \$200.00/offer; Regency & Hallicrafters 150-174 MHz receivers \$15.00 each; Realistic SSB/AM CB \$75.00. WB9YBM, Klaus Spies, 8502 Oketo, Niles, Illinois 60648.

ELECTRON TUBES - Radio & TV types 75% off list price - huge inventory! Also industrial types. Send for Free Catalog today or call Toll Free (800) 221-5802. Box HC, Transletronics, Inc., 1365 - 39th Street, Brooklyn, NY 11218. See our display ad this issue.

IMRA, International Mission Radio Association helps missionaries. Equipment loaned. Weekday net, 14.280 MHz, 2-3 PM Eastern. Eight hundred Amateurs in 40 countries. Brother Frey, 1 Pryer Manor Road, Larchmont, New York 10538.

ELECTRON TUBES: - Receiving, transmitting, microwave ... all types available. Large stock. Next day delivery, most cases. Daily Electronics, PO Box 5029, Compton, CA 09224 (213) 774-1255.

CHASSIS and cabinet kits. SASE K3IWK.

CUSTOM MADE embroidered patches. Any size, shape, colors. Five patch minimum. Free sample, prices and ordering information. Hein Specialties, Inc., Dept. 301, 4202 N. Drake, Chicago, IL 60618.

CX7 REPAIRS. 415-549-9210.

RTTY-EXCLUSIVELY for the Amateur Teleprinter. One year \$10.00. Beginners RTTY Handbook \$8.00. PO Box RY, Cardiff, CA 92007.

TRS-80 Model I/III/IV OWNERS. HF antenna design program calculates dimensions for dipole, yagi, and quad antennas. \$14.95 (cassette) + \$2.00 s&h to Cynwyn, Dept. H, 4791 Broadway, Suite 2F, New York, NY 10034.

OLD RADIO transcription discs wanted. Any size, speed, W7FIZ, Box 724 HR, Redmond, WA 98073-0724.

RUBBER STAMPS: 3 lines \$4.50 PPD. Send check or MO to G.L. Pierce, 5521 Birkdale Way, San Diego, CA 92117. SASE brings information.

RF DESIGN PROGRAM calculates stability, gain, noise figure circles, and more. For C-64 and IBM-PC, \$29.95. Jim Alllyn, N7JA, 7000 Litchford Road, #26, Raleigh, NC 27609.

AMATEUR RADIO CLASSES: Chelsea Civil Defense will sponsor evening classes at Chelsea High School starting October 16, 1985, for Novice (basic level ham license), and Tech/General licenses. Minimal cost for materials only. For information: Frank Masucci, 136 Grove Street, Chelsea, MA 02150.

NEW! CW WORD COPYING COURSE Complete. Easy-to-learn. QSO-Trainer™ code course. Includes two 60-minute audio cassettes and complete instructions. Send \$16.95 (Indiana add 85 cents). Money back, satisfaction guarantee (less \$2.00 shipping and handling). Business-size SASE gets free information. AVC Innovations, Inc., Dept. HC2, PO Box 20491, Indianapolis, IN 46220.

UHF PARTS. We stock GaAs Fets, trimmers, and many of those impossible to find parts for the UHF builder. For example: MCF 1202 at \$10.00, Finger Stock at \$7.50 per 16" strip. SASE brings list. Microwave Components, 11216 Cape Cod, Taylor, Mich. 48180

SELL: TS147A Test Set. 8.5-9.6 GHz CW-FM generator, frequency meter, power, manual. \$50.00 plus UPS. Huntley, W6RNC, PO Box 478, Nevada City, Calif. 95959.

COMPUTERIZE YOUR IC-720 or R-70 Keyboard frequency entry, 64 memories, scanning (frequency, memory, and mode). Many more features. Requires no interface, just cable - directions included. For Commodore 64. Cassette \$14.95, disk \$16.75, ppd. Cables also available. David Oliver, W9ODK, Rt. 2, Box 246, Shevlin, MN 56676.

WANTED: Operations manual schematic for Sierra 305 A-L frequency selective level meter. Weber, 2605 West 82nd Place, Chicago, IL 60652.

WANTED: Old tube HiFi equipment. Working or not, complete or parts. All makes and models. Jack Smith, 59 Millpond, N. Andover, MA 01845.

RECEIVERS: Good operating and appearance with manual. HA-350, \$50.00; NC-173; NC-300 \$100.00 each. All plus shipping. Lisains, 116 Orton, W. Caldwell, NJ 07006. (201) 226-7943.

FREE 3 month subscription. Send callsign to Westlink Report-H11, 28221 Stanley Court, Canyon Country, CA 91351. New only!

KTSB ANTENNA 160m-10m no traps. \$59.95. Weather Boot Kit \$8.95. Open-wire, roller-inductor, antenna accessories and much more. Kilo-Tec, PO Box 1001, Oak View CA, 93022. Tel: 805-646-9645.

WANTED: R-1490/GRR-17 receiver, parts and manual. Gene Mottern, 313 Royal Drive, Kingsport, Tenn 37663.

2 METER AMP KITS: 8877 legal limit kit \$395. 3CX800A7 900W kit \$325. Also HV power supplies, CX600N relays, parts and EME newsletter. SASE for catalog. 2 Meter EME Bulletin, 417 Staudaer St., Bozeman, MT 59715

COMING EVENTS

Activities - "Places to go . . ."

GEORGIA: Southnet II Packet Radio Conference hosted by Georgia Tech Amateur Radio Club and sponsored by the Georgia Radio Amateur Packet Enthusiast Society. November 23 and 24, Georgia Tech campus downtown Atlanta. Tech sessions 8:30 to 5:00 Saturday and 8:30 to 12 Noon Sunday. For further information: Bill Crews, WB2CPV, 1421 Hampton Ridge Road, Norcross, GA 30093. (404) 923-1978.

MASSACHUSETTS: The Honeywell 1200 Radio Club and the Waltham Amateur Radio Association will hold their annual Amateur Radio and electronics auction, Saturday, November 23 at the Honeywell Plant, 300 Concord Road, Billerica. Doors open 10 AM. Free admission and parking. For more information: Doug Purdy, N1BUB, 3 Visco Road, Burlington, MA 01803.

ILLINOIS: Waukegan Squadron Civil Air Patrol will hold its annual Fall Hamfest, Sunday, November 3, Lake County Fairgrounds, Rt. 120 and 45, Graylake. Doors open 7 AM. Admission \$3.00. Tables \$5.00. Large indoor area, cafeteria, free parking. For further information and reservations SASE to CAP, 637 Emerald St., Mundelein, IL 60060.

COLORADO: AMSAT will hold its third annual Space Symposium in Vail, November 9. AMSAT has issued a call for papers to be presented at the symposium. Topics may include those of interest to Amateur Radio Satellite enthusiasts. Abstracts may be sent to AMSAT, PO Box 8005, #281, Boulder, CO 80306. For further information: Molly Hardman, N3CHZ, Chairperson, (303) 939-9334 or AMSAT Headquarters (301) 589-6062.

MINNESOTA: The annual Handi-Ham Winter Hamfest, Saturday, December 7, Eagles Club, Faribault. Registrations 9 AM. Handi-Ham auction of equipment, dinner at noon followed by a program. Talk in on 19/79. For information: Don Franz, W0FIT, 1114 Frank Avenue, Albert Lea, MN 56007.

Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio Belgium
Sierenhout
Brusselsesteenweg 416
B-9218 Gent
Belgium

Ham Radio Holland
Postbus 413
NL-7800 Ar Emmen
Holland

Ham Radio Europe
Box 2084
S-194 02 Upplands Vashy
Sweden

Ham Radio France
SM Electronic
20 bis, Ave des Clairons
F-89000 Auxerre
France

Ham Radio Germany
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Canada
Send orders to
Ham Radio Magazine
Greenville, NH 03048 USA
Prices in Canadian funds
1 yr \$29.95, 2 yrs \$53.30
3 yrs \$75.40

Ham Radio Italy
Via Pordenone 17
I-20132 Milano
Italy

Ham Radio Switzerland
Karin Ueber
Postfach 2454
D-7850 Loerrach
West Germany

Ham Radio England
c/o R S G B
Alma House
Cranborne Road
Potters Bar
Herts EN6 3JW
England

GLITCHWITCH

- STOPS EQUIPMENT DAMAGING TRANSIENTS
- ADDS PROTECTION TO EXISTING AC STRIPS
- SIMPLY PLUGS IN TO OUTLET
- SUPERIOR TO CONVENTIONAL SINGLE VARISTOR TYPES
- HAS 3 HEAVY DUTY VARISTOR TRANSIENT SUPPRESSORS
- PROTECTS AGAINST BOTH LINE-LINE AND LINE-GROUND SPIKES

GlitchWitch is a robust, easily used transient suppression network. It occupies one socket in an AC outlet box or strip and prevents overvoltage spikes in that AC circuit. 4500 Amp. peak rating devices. Inexpensive protection for \$\$\$ equipment and data. Most other devices do not guard against line-ground spikes and do not provide the safety of GLITCHWITCH. Guard your gear.

check or money order \$17.95 ppd.

GLITCHWITCH

P.O. B. 643
SUDBURY, MA. 01776

Steve Stutman, Prop.



NEW JERSEY: The 4th annual Jersey Shore Ham/Computer/Electronics Flea Market, November 3, 9 AM to 3 PM, Neptune City Recreational Hall, Neptune City Shopping Center, Neptune. Admission \$3.00. Children under 12 and XYL's free. Refreshments available. Table \$6.00. Tailgating \$3.00. Send payment and SASE to Jersey Shore Hamfest, PO Box 192, West Long Branch, NJ 07764. Talk in on 147.045 and 146.52 simplex. (201) 222-3009.

LOUISIANA: The Twin City Hams are sponsoring a Hamfest, Saturday, November 9, West Monroe Convention Center, North 7th Street, West Monroe 9 AM to 4 PM. Free swap tables. Amateur Radio exams will be given. Talk in on 146.52 simplex and 146.25/146.85. For more information: Benson Scott, AESV, 107 Contempo Street, West Monroe, LA 71291.

MASSACHUSETTS: The MIT UHF Repeater Association and the MIT Radio Society offer monthly Ham Exams. Novice through Extra, Wednesday, November 20, 7 PM, MIT room 1-134, 77 Mass Ave., Cambridge, MA. Reservations requested 2 days in advance. Contact Ron Hoffmann at (617) 253-5820/646-1641. Exam fee \$4.00. Bring copy of current license, two forms of picture ID and completed form 610 available from FCC in Boston (223-6609).

WISCONSIN: The Milwaukee Repeater Club is proud to sponsor the "6.91 Friendly Fest" on Sunday, November 24, Serb Hall, 51st and Oklahoma. Bring your swapfest bargains and sample good food and beverages. Also bowling. Tickets \$3.00. 4' tables \$4.00. Save \$1.00—SASE with payment to Milwaukee Repeater Club, PO Box 2123, Milwaukee, WI 53201 before November 11. Talk in on 146.31/91 and 146.52.

ILLINOIS: The Chicago Amateur Club will hold its annual Ham Auction, November 6, 7 PM to 10 PM, Edgebrook Golf Course Field House, 6100 N. Central Ave., Chicago. For information: (312) 545-3622.

INDIANA: The Allen County Amateur Radio Technical Society's 13th annual Fort Wayne Hamfest, Sunday, November 10, 8 AM to 4 PM, Allen County Memorial Coliseum, Coliseum Blvd., US 30. Indoor tables available \$8.00. AC power extra. Premium tables with AC \$20.00 each. Admission \$3.50 advance. \$4.00/door. Children under 11 free. Ladies' activities, forums, banquet Saturday night. Nearby motels and restaurants. VE exams Saturday, November 9 advance registration only. Talk in on 146.28/88. For information or reservations: ACJ-ARTS Hamfest, PO Box 10342, Fort Wayne, IN 46851.

MICHIGAN: The Oak Park High School Electronics Club presents the 16th annual Swap N Shop, December 1, Oak Park High School, Oak Park, 8 AM to 4 PM. Admission \$2.50. After 12 Noon \$1.50. All 8' tables \$8.00. SASE to Herman Gardner, Oak Park High School, 13701 Oak Park Blvd., Oak Park, MI 48237 or call (313) 968-2675.

OHIO: The Massillon ARC will sponsor "Auctionfest 85", November 24, Massillon K of C Hall, off Rt. 21, 8 AM to 5 PM. Sellers setup 7 AM. Admission \$2.50 advance and \$3.50 at the door. Tables available at \$7.00 per 8' space. Refreshments and sit down dinner. Free parking. Auction 11 AM. Talk in on W8NP, 147.78/18. For advance registration and information: MARC, PO Box 73, Massillon, OH 44646. SASE please.


NEW YORK: 7th annual "Ham-Central", Sunday, December 1, Main Hall, Lutheran School, Moriches Road, St. James, Long Island, close to NYC. Doors open 7:30 AM for sellers/dealers. 9 AM general public. Table space \$10.00/8' includes two free admission tickets. General admission \$3.00. XYL and kids under 12 free. Seminars plus ARRL and AM-SAT. Food and refreshments available. Nearby shopping malls and historic sites. Talk in on 144.550/145.150 and 146.52 MHz. For reservations and information call after 6 PM Bob Yarnus, K2RGZ (516) 981-2709 or Andy Feldman, WB2FXN (516) 928-3868.

FIRST US YL WINS SWEDISH AWARD. Emily Maytan, AC2V, of Yonkers, NY, has become the first American YL to win the "100-SM" award for confirmed contacts with 100 Swedish hams. Only 659 other hams worldwide have previously won this award.

OPERATING EVENTS — "Things to do . . ."

The Armored Forces Amateur Radio Net (A.F.A.R.) will operate from 0002Z November 10 to 2400Z November 11 to commemorate Veterans' Day 1985. Phone 80, 40, 20, 15 meters. CW on 40 meters. Certificate available for contact with member station. Send #10 SASE to WB1DWR #90, 16 Berkeley Circle, Newington, CT 06111.

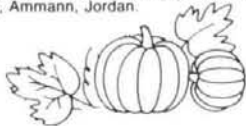The Royal Jordanian Radio Amateur Society has announced plans for JY50, a two week celebration marking the 50th birthday of His Majesty, King Hussein, JY-1 starting November 7 through November 21. For the special "Worked JY50 certificate" send copies of log and either 10 IRC's or \$5 (US) to the Royal Jordanian Radio Amateur Society, JY50 Celebration, PO Box 2353, Ammann, Jordan.



QUADS — TOWERS — QUADS — TOWERS — QUADS —

QUADS — TOWERS — QUADS — TOWERS — QUADS —

DO YOU WANT THE STRAIGHT INFO ON QUADS?

Info on verticals, dipoles, mini-quads, Yagis, including comparative performances? Without pulling any punches.

Our references are ANY AMATEUR WHO USES A SKYLANE QUAD.

Our prices are lower than any comparable Quad or tower

Info on quads **half a buck**, and info on BOTH towers and quads for **a buck**. Charge due to increased cost of postage and printing.

SKYLANE PRODUCTS

PO Box 2968
Satellite Beach, FL 32937
(305) 773-1342

✓ 206

MAKE CIRCUIT BOARDS THE NEW, EASY WAY



WITH TEC-200 FILM

JUST 3 EASY STEPS:

- Copy circuit on TEC-200 film using any plain paper copier
- Iron film on to copper clad board
- Peel off film and etch

SATISFACTION GUARANTEED
convenient 8 1/2 x 11 size

5-Sheet Starter Pack \$3.95

10 sheets only \$5.95

add 50¢ postage. NY res. add sales tax

The MEADOWLAKE Corp.

Dept. H, P.O. Box 497
Northport, New York 11768

✓ 207

TEST EQUIPMENT RE-CONDITIONED AND LAB CALIBRATED

URM-25 SIGNAL GENERATOR, 10 KHZ TO 50 MHZ AM/CW MODULATION, 400 & 1 KHZ RF OUTPUT 0-2V OR 0-1V PRECISION 50 OHM STOP ATTENUATOR, SMALL PORTABLE UNIT \$245.00

URM-26 SIGNAL GENERATOR 4 MHZ TO 405 MHZ CALIBRATED OUTPUT 0 TO 2V, MODULATION 400/1000 HZ, CALIBRATED OUTPUT ATTENUATOR, SMALL PORTABLE UNIT 245.00

HP606A SIGNAL GENERATOR, 50 KHZ TO 65 MHZ, RF OUTPUT 0.1 TO 3V IN 50 OHMS, CRYSTAL CALIBRATOR, 400/1000 HZ MODULATION 375.00

HP608C SIGNAL GENERATOR, 10 MHZ TO 480 MHZ, 0.1 MV TO 1V RF OUTPUT INTO 50 OHMS, AM/CW OR PULSE MODULATION, CALIBRATED ATTENUATOR 345.00

TS-510/U SIGNAL GENERATOR, 10 MHZ TO 420 MHZ, AM/CW OR PULSE EMISSION OUTPUT VOLTAGE 0 TO 5V, CALIBRATED ATTENUATOR, 400/1000 HZ MODULATION 295.00

HP614A SIGNAL GENERATOR 900 TO 2100 MHZ 0.5 MV TO 1V INTO 50 OHMS, INTERNAL OR EXTERNAL PULSE OR FM MODULATION CALIBRATED OUTPUT 345.00

HP616A SIGNAL GENERATOR 1.8 GHZ TO 4.2 GHZ CALIBRATED OUTPUT 0.1 MW TO 1V INTO 50 OHMS INTERNAL, EXTERNAL PULSE OR FM MODULATION 375.00

HP618B SIGNAL GENERATOR 3.8 GHZ TO 7.6 GHZ 0.1 MV TO 1V INTO 50 OHMS, CALIBRATED OUTPUT, INTERNAL, EXTERNAL, PULSE FM AND SQUARE WAVE MODULATION 375.00

HP620A SIGNAL GENERATOR 7 GHZ TO 11 GHZ CALIBRATED OUTPUT 0.1 MV TO 1V INTO 50 OHM INTERNAL, EXTERNAL, PULSE AND FM MODULATION 450.00

SG-557/URM-52 SIGNAL GENERATOR 3.8 GHZ TO 7.6 GHZ, 0.1 MV TO 1V INTO 50 OHM CALIBRATED OUTPUT, INTERNAL, EXTERNAL PULSE FM AND SQUARE WAVE MODULATION MILITARY VERSION OF HP-618B 325.00

SG-13/U AIRCRAFT VOR/ILS SIGNAL GENERATOR RANGE 108 MHZ THRU 135.9 MHZ AND 329.9 TO 335 MHZ, OUTPUT SIGNAL INCLUDE VOR, LOC AND GLIDESLOPE AND 1000 CPS SAME AS COLINS 4791.2. OPERATES FROM 28 VDC AT 3 1/2 AMPS BENCH POWER SUPPLY OR AIRCRAFT BATTERY IDEAL FOR AIRCRAFT RADIO REPAIR 285.00

JERROLD 900A SWEEP GENERATOR, RANGE 0.5 TO 1200 MHZ, 0.5 TO 400 MHZ SWEEP WIDTH, OUTPUT IS FLAT 5DB TO 800 MHZ, 1.5 DB TO 1200 MHZ BUILT-IN RF DETECTOR 325.00

HP851B/851B SPECTRUM ANALYZER AND DISPLAY SECTION, FREQ RANGE 10.1 MHZ TO 12 GHZ, TYPE N COAXIAL INPUT, WITH EXTRA WAVEGUIDE MIXERS RANGE CAN GO TO 40 GHZ, TEN CALIBRATED SPECTRUM WIDTHS 100 KHZ TO 2 GHZ SENSITIVITY UP TO -100 DBM 1,650.00

WE ACCEPT VISA, M/C, OR CHECK. ADD SHIPPING. WE SHIP BEST WAY. SATISFACTION GUARANTEED, IMMEDIATE SHIPMENT. PHONE BILL SLEP 704-524-7519.

SLEP ELECTRONICS  CO

HIGHWAY 441
OTTO, NORTH CAROLINA 28763

✓ 208

CHARGE YOUR CLASSIFIED ADS

to your
MC or VISA
write or call

HAM RADIO MAGAZINE

Greenville, NH 03048

(603) 878-1441

THE GUERRI REPORT

Ernie Gueri
W6 MGI

new components and techniques for RF designers

When manufacturers offer new equipment, the resulting design is a complex function of expected market, engineering hours, and the availability of necessary technology and components. Fortunately for designers of RF equipment, new components are rapidly being developed to keep pace with the boom in telecommunications.

Among the more exciting developments in the semiconductor industry is the emergence of commercial Gallium Arsenide (GaAs) ICs. Both analog and digital functions are being implemented. The digital functions — prescalers, counters, memories, and shift registers — are capable of operation at 2 to 3 GHz, allowing the design of phase locked loops and frequency synthesizers at low microwave frequencies using only a few chips. The required interstage amplifiers are now also available as off-the-shelf GaAs IC amplifier blocks (Microwave Monolithic Integrated Circuits, or MMICs) covering octave (2:1) bandwidths with 10 to 30 dB of gain. These gain blocks are available from 50 MHz to over 18 GHz. Prices are high right now but we can expect dramatic reductions as sales volume increases.

In the realm of discrete devices, the High Electron Mobility Transistor (HEMT) is just now ready to emerge commercially. This improved class of GaAs FET can provide noise figures of about 1 dB at almost 10 GHz, with 8 to 10 dB of gain! Several companies have developed low-cost ICs based on HEMT concepts which would integrate large portions of complex microwave receivers into a single chip.

One of the most fundamental concepts in modern telecommunications

is frequency translation, or mixing. Most receivers and transceivers have several conversions from one frequency or band to another. An important characteristic of the translation device is its ability to minimize the generation of unwanted products. Mixer development has now advanced to the point where we have image rejection mixers (the image is automatically suppressed by about 20 dB) well into the microwave region. There is a similar class called "termination insensitive mixers" that perform well even with highly reactive loads. The development of complex GaAs MMICs will soon permit the implementation of active frequency converters with high dynamic range, selectable image characteristics, and conversion "gain" instead of an insertion loss. We should see these devices — up to 4-5 GHz — readily available in the not-too-distant future.

Plain old resistors and capacitors are taking on a new look. Chip- and surface-mounted components with superb characteristics well into the microwave region are now available. The fact that most modern circuits operate at low voltage and power levels means that spacings and insulation can be very small. This in turn reduces the overall size of the component, and hence its parasitic inductance and capacitance. This trend will continue to provide more components with nearly perfect RF characteristics in the VHF/UHF and low microwave ranges.

Even coaxial cables continue to undergo substantial improvement. Semi-rigid coax with foil shielding, foam dielectric, and non-contaminating jacket is available at very affordable prices. This type of cable is usable to 500 MHz with losses of less than 0.1 dB/meter. Small diameter hardline is

now available to the UHF/Microwave enthusiast on the surplus market, thanks to the huge quantities used by military and cable TV applications. These cables are nearly the ultimate in transmission lines; they boast very low losses well into the microwave region, 100 percent shielding, and closed-cell foam insulations with permanent water intrusion barriers. Properly installed, these cables can have a useful life of more than 20 years.

Some of the least heralded advances in component design have taken place in the realm of interstage filters. Multipole ceramic and crystal filters with flat passbands, steep skirts, and low spurious responses have become available at remarkably low prices. Made for virtually all of the standard IF frequencies (455 kHz, 10.7, 21.4, 30, and 45 MHz), these marvelous filters, buried deep in our equipment, give us selectivity and freedom from unwanted responses that would have been a dream just a few years ago.

The advances continue. Monolithic crystal filters with narrow bandwidths (5-15 kHz) have been fabricated at over 250 MHz. Surface Acoustic Wave (SAW) filters with good characteristics up to 1.5 GHz are now available commercially. The availability of these higher frequency filters means that next-generation equipment can use up-conversion (IF higher than the incoming signal) to give us image-free, single conversion (large dynamic range) performance.

As the spectrum becomes more intensely populated, we are fortunate that component designers and manufacturers are investing in the technology to assure that there will be room for all of us.

ham radio

New

New

THE STANDARD OF EXCELLENCE

Definitely Superior!

AZDEN PCS-5000

COMMERCIAL — GRADE



UNPRECEDENTED WIDE FREQUENCY RANGE: Covers 140,000-153,000 MHz in steps that can be set to any multiple of 5 kHz up to 50 kHz.

CAP/MARS/NAVY MARS, BUILT IN: The wide frequency range facilitates use of CAP and ALL MARS FREQUENCIES including NAVY MARS. **COMPARE!**

TINY SIZE: Only 2 inches high, 5½ inches wide and 7¼ inches deep!

MICROCOMPUTER CONTROL: Gives you the most advanced operating features available.

UP TO 11 NONSTANDARD SPLITS: **COMPARE** this with other units!

20 CHANNELS OF MEMORY IN TWO SEPARATE BANKS: Retains frequency, offset information, PL tone frequency.

DUAL MEMORY SCAN: Scan memory banks separately or together. **ALL** memory channels are tunable independently. **COMPARE!**

MEMORY SCAN LOCKOUT: Allows you to skip over channels you don't want to scan.

TWO RANGES OF PROGRAMMABLE BAND SCANNING: Limits are quickly reset. Scan ranges separately or together with independently selective steps in each range. **COMPARE!**

BUSY SCAN AND DELAY SCAN: Busy scan stops on an occupied channel. Delay scan provides automatic auto-resume.

DISCRIMINATOR CENTERING (AZDEN EXCLUSIVE PATENT): Always stops on frequency desired when scanning.

PRIORITY MEMORY AND ALERT: Unit constantly monitors one memory channel for signals, alerting you when channel is occupied.

LITHIUM BATTERY BACKUP: Memory information can be stored for up to 5 years even if power is removed.

FREQUENCY REVERSE: Allows you to listen to repeater input frequency.

ILLUMINATED KEYBOARD WITH ACQUISITION TONE: Keys are easily seen in the dark, and actuation is positively verified audibly.

CRISP, BACKLIGHTED LCD DISPLAY: Easily read no matter what the lighting conditions!

DIGITAL S/R/F METER: Shows incoming signal strength and relative transmitter power.

MULTI-FUNCTION INDICATOR: Shows a variety of operating parameters on the display.

FULL 16-KEY TOUCHTONE PAD: Keyboard functions as auto-patch when transmitting.

MICROPHONE CONTROLS: Up/down frequency control and priority channel recall.

PL TONE GENERATOR BUILT IN: Instantly program any of the standard PL frequencies into the microcomputer. **COMPARE!**

TRUE FM, NOT PHASE MODULATION: Unsurpassed intelligibility and audio fidelity. **COMPARE!**

HIGH/LOW POWER: Select 25 watts or 5 watts output — fully adjustable.

SUPERIOR RECEIVER: Sensitivity is better than 0.15 microvolt for 20-dB quieting. Commercial-grade design assures optimum dynamic range and noise suppression. **COMPARE!**

DIRECT FREQUENCY ENTRY: Streamlines channel selection and programming.

OTHER FEATURES: Rugged dynamic microphone, built-in speaker, mobile mounting bracket, remote speaker jack, and all cords, plugs, fuses and hardware are included.

EXCLUSIVE DISTRIBUTOR. DEALER INQUIRIES INVITED. FOR YOUR NEAREST DEALER OR TO ORDER

AMATEUR-WHOLESALE ELECTRONICS TOLL FREE...800-327-3102

8817 S.W. 129th Terrace, Miami, Florida 33178 Telephone (305) 233-3631 Telex: 80-3356

MANUFACTURER:

JAPAN PIEZO CO., LTD.

1-12-17 Kamirenjaku, Mitaka, Tokyo, 181 Japan

Telex: 781-2822452






Eureka!

We just struck gold with a miniature, high quality and very reliable DTMF decoder at a rock bottom price of \$59.95. Our DTD-1 will decode 5040, 4 digit codes with the security of wrong digit reset. It contains a crystal controlled, single chip DTMF decoder that works great in bad signal to noise environments and provides latched and momentary outputs. Why carry that heavy gear when its size is only 1.25 x 2.0 x .4 inches and it comes with our etched in stone, legendary, one year warranty.

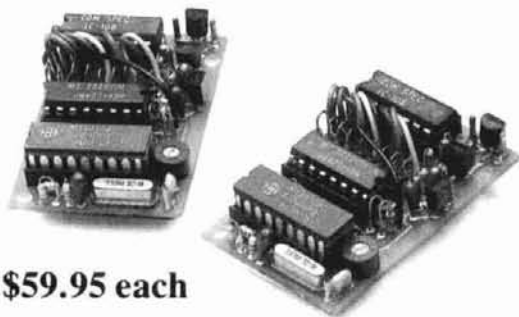Instead of sifting through the field... searching, use our super quick one day delivery and cash in on a rare find.



\$59.95 each

**COMMUNICATIONS
SPECIALISTS**

426 W. Taft Ave., Orange, CA 92665-4296
Local (714) 998-3021 • FAX (714) 974-3420
Entire U.S.A. 1-800-854-0547



THINGS TO LOOK FOR (AND LOOK OUT FOR) IN A PHONE PATCH

- A patch should work with any radio. AM, FM, ACSB, relay switched or synthesized.
- Patch performance should not be dependent on the T/R speed of your radio.
- Your patch should sound just like your home phone.
- There should not be any sampling noises to distract you and rob important syllables. The best phone patches do not use the cheap sampling method. (Did you know that the competition uses VOX rather than sampling in their \$1000 commercial model?)
- A patch should disconnect automatically if the number dialed is busy.
- A patch should be flexible. You should be able to use it simplex, repeater aided simplex, or semi-duplex.
- A patch should allow you to manually connect any mobile or HT on your local repeater to the phone system for a fully automatic conversation. Someone may need to report an emergency!
- A patch should not become erratic when the mobile is noisy.
- You should be able to use a power amplifier on your base to extend range.
- You should be able to connect a patch to the MIC and EXT. speaker jack of your radio for a quick and effortless interface.
- You should be able to connect a patch to three points inside your radio (VOL high side, PTT, MIC) so that the patch does not interfere with the use of the radio and the VOL. and SQ. settings do not affect the patch.
- A patch should have MOV lightning protectors.
- Your patch should be made in the USA where consultation and factory service are immediately available.


**ONLY
PRIVATE PATCH III
GIVES YOU ALL
OF THE ABOVE
BEWARE OF INFERIOR
IMITATIONS**

**N
E
W**

PRIVATE PATCH III

SIMPLEX SEMI-DUPLEX INTERCONNECT

**N
E
W**

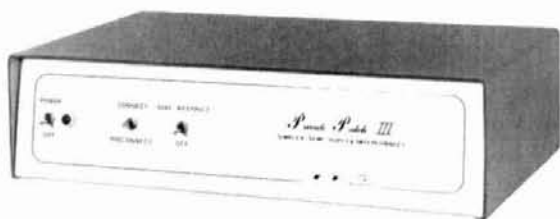

With an amazingly low price, the all new PRIVATE PATCH III is the most powerful personal phone patch system available. You can use it simplex, repeater aided simplex (from your base) or semi-duplex (at the repeater). That's right, you will never have to buy another patch PRIVATE PATCH III does it all! There are many new and important features which were formerly only available in our top commercial models.

With a flick of the new connect switch you can patch your friends on the repeater into the phone system. One of them may need to report an emergency!

No hassles with busy signals! If you call a number that is busy, just put your MIC down and relax. PRIVATE PATCH III will disconnect automatically.

The new CW ID keeps you completely informed as to patch status. ID occurs when you access and again when you disconnect. ID is also sent after toll call attempts, all automatic disconnects, manual disconnect and when timeout is imminent. And of course your CW ID chip is free.

PRIVATE PATCH III does not interfere with the normal use of your base radio. A new audio pre-amp permits audio take off before the VOL. control. As a result, the VOL. and squelch settings do not affect patch operation. Of course you can also connect PRIVATE PATCH III to the MIC and EXT speaker jacks as before.

A new digit counting system makes the toll restrict positive even in areas where you do not have to dial "1" first. A secret five digit code disables the toll restrict for one toll call. Re-arm is automatic.

Additional new features: MOV lightning protection — Three digit access code (eg. *93 — Spare relay position on board — Plus former features: 3/6 minute timeout timer — Digital fast VOX (pat. pend.) — 115 VAC supply — Modular Jack and cord plus much more!


Please write or call for our four page brochure to get the complete story.

Options:
FCC approved coupler
12 VDC or 230 VAC power

Warranty? Yes, one full year!

DEALERS

- | | |
|---|---|
| AMATEUR ELECTRONIC SUPPLY
Milwaukee WI, Wickliffe Oh,
Orlando FL, Clearwater FL,
Las Vegas NV | JUNS ELECTRONICS
Culver City CA, Reno NV |
| COLES COMMUNICATIONS
San Antonio TX | MIAMI RADIO CENTER CORP.
Miami FL |
| ERICKSON COMMUNICATIONS
Chicago IL | MIKES ELECTRONICS
Ft. Lauderdale, Miami FL |
| HAM RADIO OUTLET
Anaheim CA, Burlingame CA,
Oakland CA, Phoenix AZ,
San Diego CA, Van Nuys CA | N&G DISTRIBUTING CORP.
Miami FL |
| HENRY RADIO
Los Angeles CA, Anaheim CA,
Butler MO | PACE ENGINEERING
Tucson AZ |
| | THE HAM STATION
Evansville IN |
| | CANADA:
DOLLARD ELECTRONICS
Vancouver, BC |

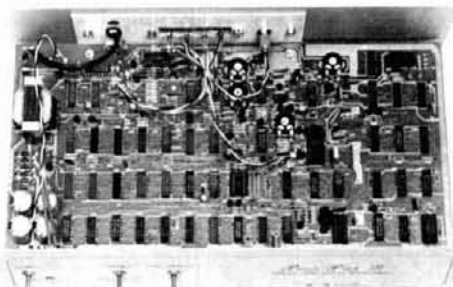

CONNECT SYSTEMS INCORPORATED (213) 373-6803 212
23731 Madison St., Torrance, CA 90505



Celebrate your buying decision with the money you've saved.

When it comes to getting maximum HF performance for your dollar, the choice is clear. Yaesu's FT-757GX.

Nowhere else will you find so many HF features packed into one compact, mobile-ready package. At a price that's got the competition baffled.

For starters, each 757 includes an electronic keyer. 600-Hz CW filter. AM and FM modes. AF speech processor. And a 25-kHz marker generator. All at no extra charge.

And working the DX has never been easier with dual VFOs, single-button VFO/memory swap for split-frequency operation, eight

memories, and push-button quick memory and band scan.

The 757 also lets you listen from 500 kHz to 30 MHz with its high-performance general coverage receiver. The transmitter covers 160 through 10 meters, including the new WARC bands, with 100 watts output on sideband, FM and CW.

CW buffs will enjoy the delights of full QSK operation. Plus the massive heatsink and duct-flow cooling system allow continuous RTTY operation for up to 30 minutes. Use the FP-757HD heavy-duty power supply option for continuous-duty applications.

And of course, there's the 757's highly attractive price. It's the

perfect way to get all the HF performance you desire, with money left over to apply toward other ham gear. Perhaps a power supply for base station use. An antenna or antenna tuner. Or whatever else makes your operation complete.

So ask your dealer today about Yaesu's FT-757GX. The most celebrated HF price/performer on the air.

YAESU

*Yaesu Electronics Corporation
6851 Wallball Way, Paramount
CA 90723 (213) 633-4007*

*Yaesu Cincinnati Service Center
9070 Gold Park Drive, Hamilton
OH 45011 (513) 874-3100*

KENWOOD

...pacesetter in Amateur radio

“Digital DX-terity!”



TS-430S

Digital DX-terity—that outstanding attribute built into every Kenwood TS-430S lets you QSY from band to band, frequency to frequency and mode to mode with the speed and ease that will help you earn that dominant DX position from the shack or from the mobile!



- Covers all Amateur bands 160 through 10 meters, as well as the new 30, 17, and 12 meter WARC bands. High dynamic range, general coverage receiver tunes from 150 kHz to 30 MHz. Easily modified for HF MARS operation.
- Superb interference reduction. Eliminate QRM with the IF shift and tuneable notch filter. A noise blanker suppresses ignition noise. Squelch, RF attenuator, and RIT are also provided. Optional IF filters may be added for optimum interference reduction.

- **Reliable, all solid state design.** Solid state design permits input power of 250 watts PEP on SSB, 200 watts DC on CW, 120 watts on FM (optional), or 60 watts on AM. Final amplifier protection circuits and a cooling fan are built-in.
- **Memory channels.** Eight memory channels store frequency, mode and band data. Channel 8 may be programmed for split-frequency operation. A front panel switch allows each memory channel to operate as an independent VFO or as a fixed frequency. A lithium battery backs up stored information.
- **Programmable, multi-function scan.**
- **Speech processor built-in.**
- **Dual digital VFOs.**
- **VOX circuit, plus semi break-in with sidetone.**

Optional accessories:

- PS-430 compact AC power supply
- SP-430 external speaker
- MB-430 mobile mounting bracket
- AT-130 compact antenna tuner covers 80-10 meters, incl. WARC bands
- AT-250 automatic antenna tuner covers 160-10 meters, incl. WARC bands
- TL-922A 2 kW PEP linear amplifier
- FM-430 FM unit
- YK-88C (500 Hz) or YK-88CN (270 Hz) CW filters
- YK-88SN (1.8 kHz) narrow SSB filter
- YK-88A (6 kHz) AM filter
- MC-42S UP/DOWN hand mic.
- MC-60A/80/85 deluxe desk mics.
- SW-2000/200A SWR/power meters
- SW-100A SWR/power/volt meter
- PC-1A phone patch
- HS-4, HS-5, HS-6, HS-7 headphones



KENWOOD

TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut Street
Compton, California 90220

Complete service manuals are available for all Trio-Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.